
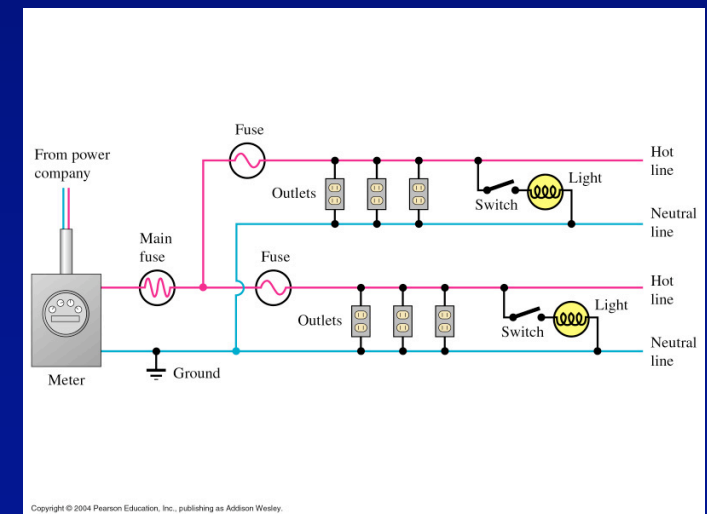
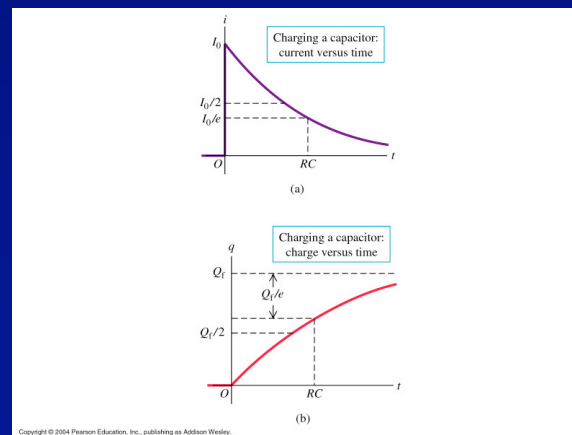


Chapter 26: Direct-Current Circuits

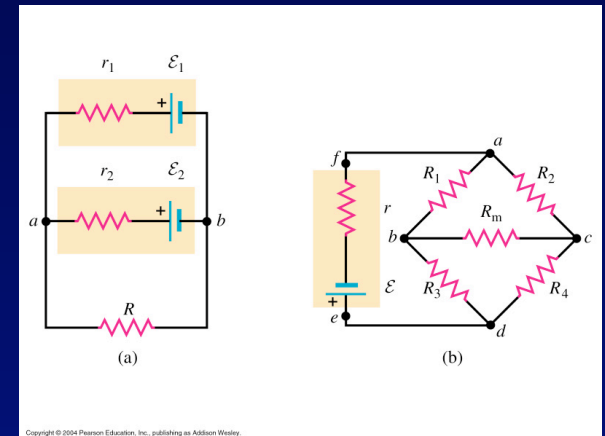
- Batteries in series and parallel
- Resistors in series and parallel
- Kirchhoff's Rules
- Electrical measuring instruments



Batteries in series


- Batteries in **series**:

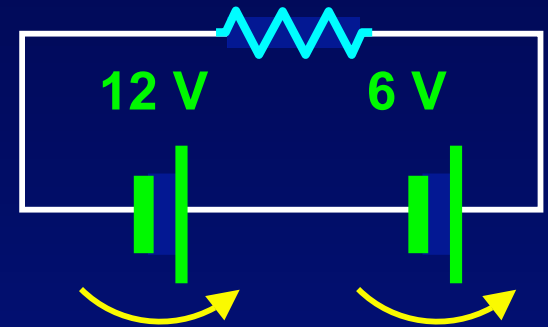- ⚡ first battery does work on charge
- ⚡ second battery does more work
 - » voltages add (**18 V across R**)



- Batteries in **series**:

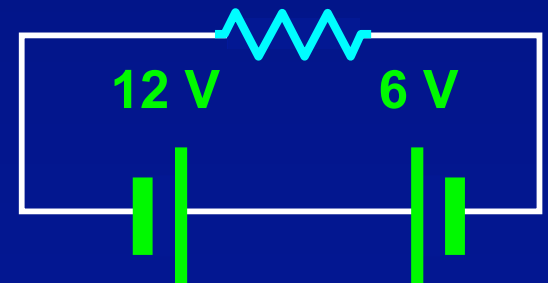
- ⚡ first battery does work on charge
- ⚡ charge does work on second battery
 - » voltages subtract (**6 V across R**)
 - » **second battery is being charged by the first one**



Batteries in parallel

- Batteries in **parallel**:

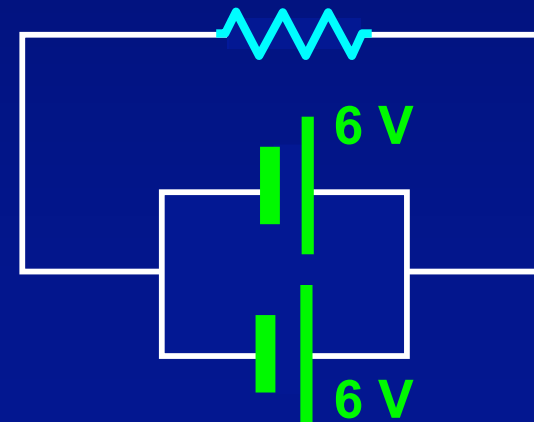- ⚡ each charge only goes through one of the batteries
 - » voltage is the same (**6 V across R**)
- ⚡ but each battery does less work (since only some of the charge goes through it)
 - » batteries last longer
 - » Can be used to recharge (see Examples 26.4 and 26.5).



Resistors in series

- Same charge has to flow through all the resistors

same current: $I_1 = I_2 = I_3 = I$


- Total work done by battery must equal sum of energy lost as charge moves through resistors

⚡ voltages add: $V = V_1 + V_2 + V_3$

- Ohm's Law, $V = I R$, gives:

$$IR_{eq} = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

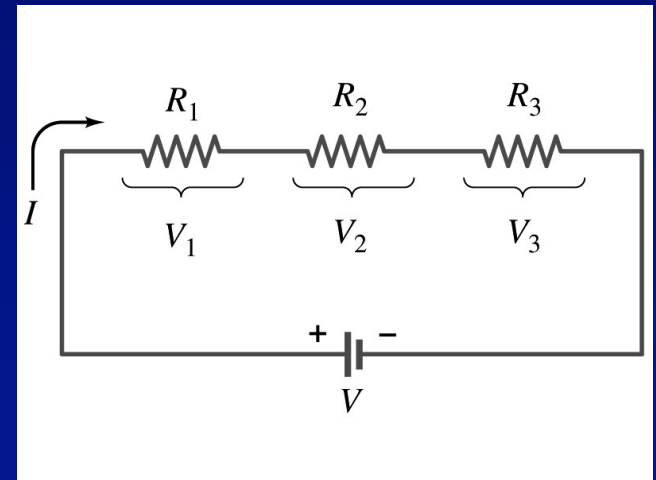

Resistors in parallel


- Current splits up into several branches. However, total current must be conserved!
- But the **voltage is the same** across each resistor

⚡ currents add: $I = I_1 + I_2 + I_3$

⚡ $V = V_1 = V_2 = V_3$


- From Ohm's Law, $V = I R$, we find:
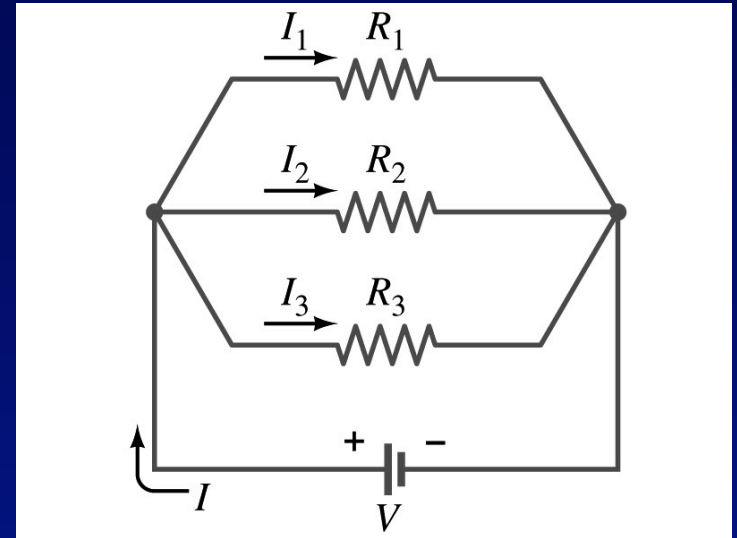
$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$



$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

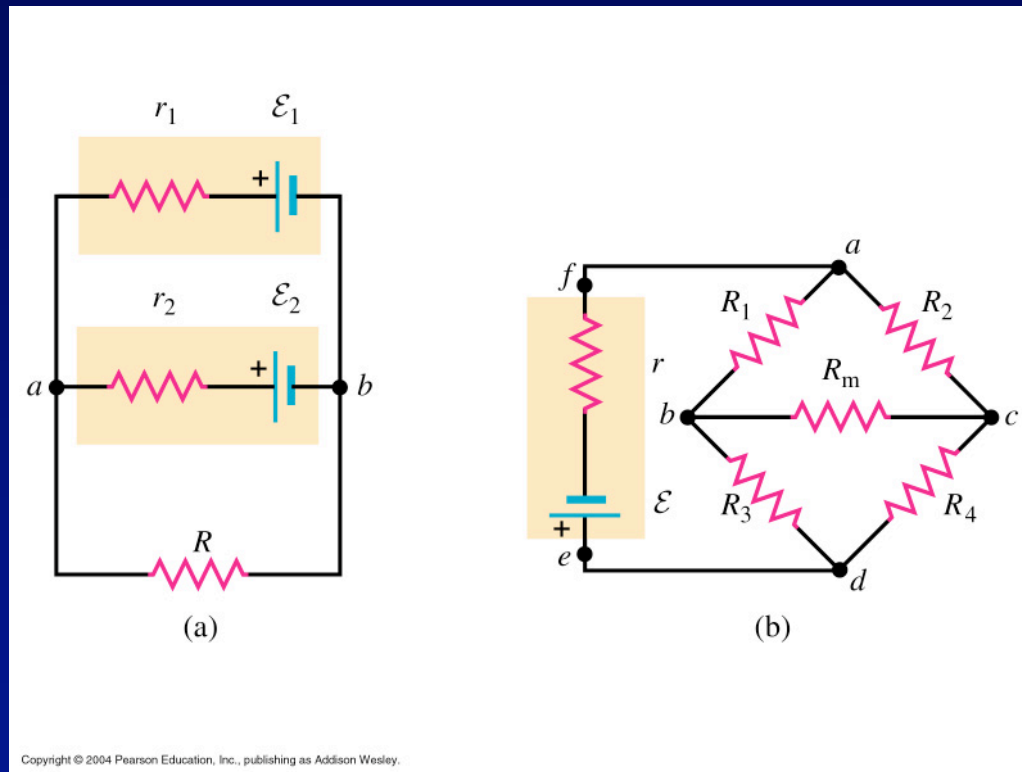- What do we do with more complicated circuits?
 - ⚡ Parallel and series rules are not enough!



➡ use **Kirchhoff's rules!**

ConcepTest 26.1


- The resistor is the same in both circuits. How does the current through the resistor in the upper circuit (I_1) compare with that in the lower one (I_2) ?

batteries

(1) $I_1 > I_2$

(2) $I_1 < I_2$

(3) $I_1 = I_2$

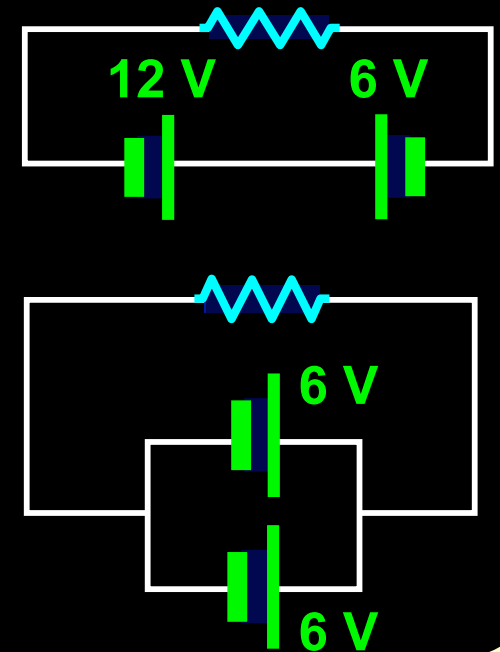

Kirchhoff's Rules

New Topic


Kirchhoff's Junction Rule

- At any junction point, the sum of all currents entering the junction must equal the sum of all currents leaving.

(or: what goes in has to come out!)

$$I_3 = I_1 + I_2$$

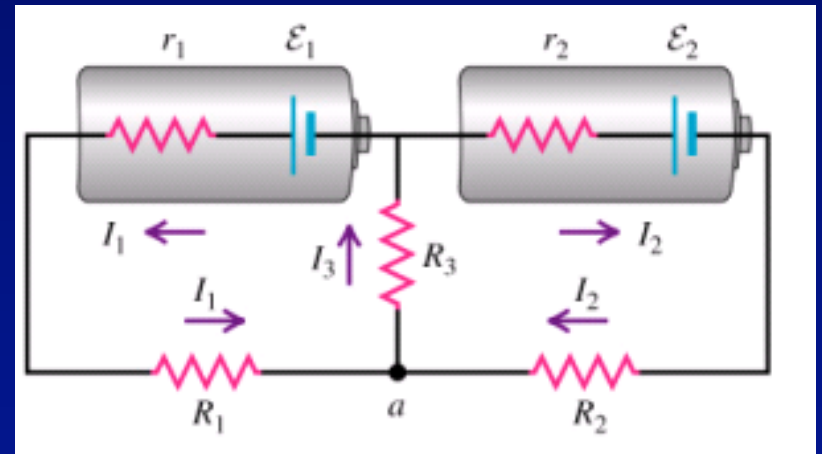This rule follows from
conservation of charge !



Kirchhoff's Loop Rule

- “The sum of voltage drops and gains around any closed circuit loop must be zero”

$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 + \dots = 0$$


- This rule follows from *conservation of energy*

Sign convention:

- sign for voltage drop and
- + sign voltage gain.


It depends on several factors:

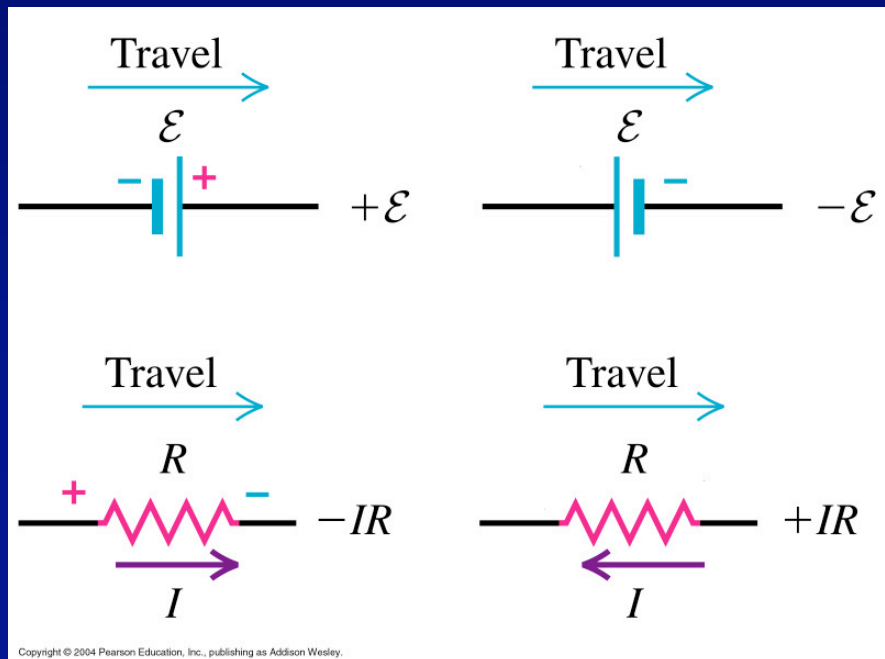1. emf or resistor
2. direction of current
3. direction of loop travel



Loop Rule Example

(with numbers)

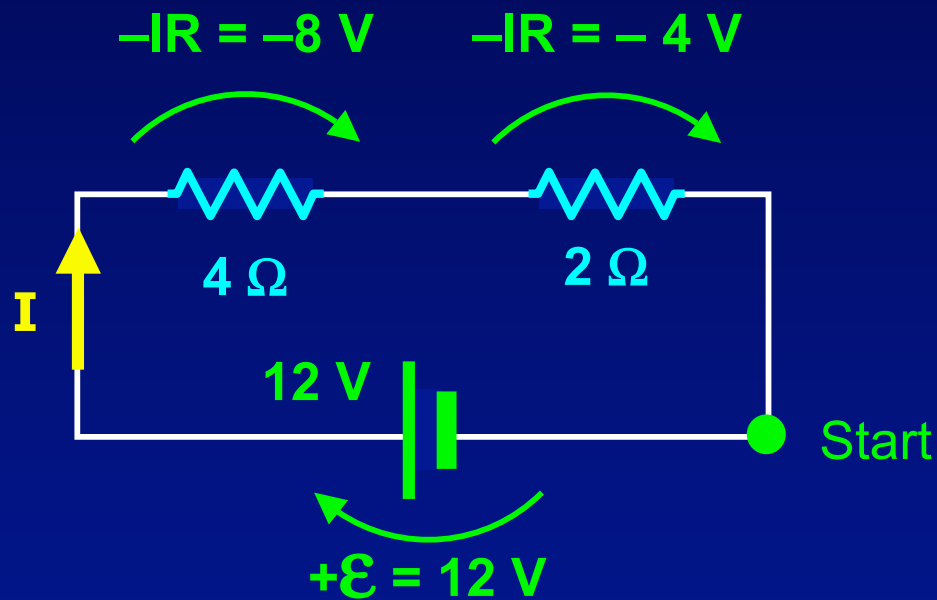

Current in each resistor?

Total resistance = $6\ \Omega$

Ohm's Law: $I = V / R$
 $= 12\text{ V} / 6\ \Omega$
 $= 2\text{ A}$

Voltage drop across resistor?

$$V = IR$$

$$\Delta V = +12\text{ V} - 8\text{ V} - 4\text{ V} = 0\ \checkmark$$


Loop Rule Example

(without numbers)

The first thing we have to do is?
Define currents!

Next: Define travel direction:
top loop (CW)
bottom loop (CW)

Now apply Loop rule to each loop

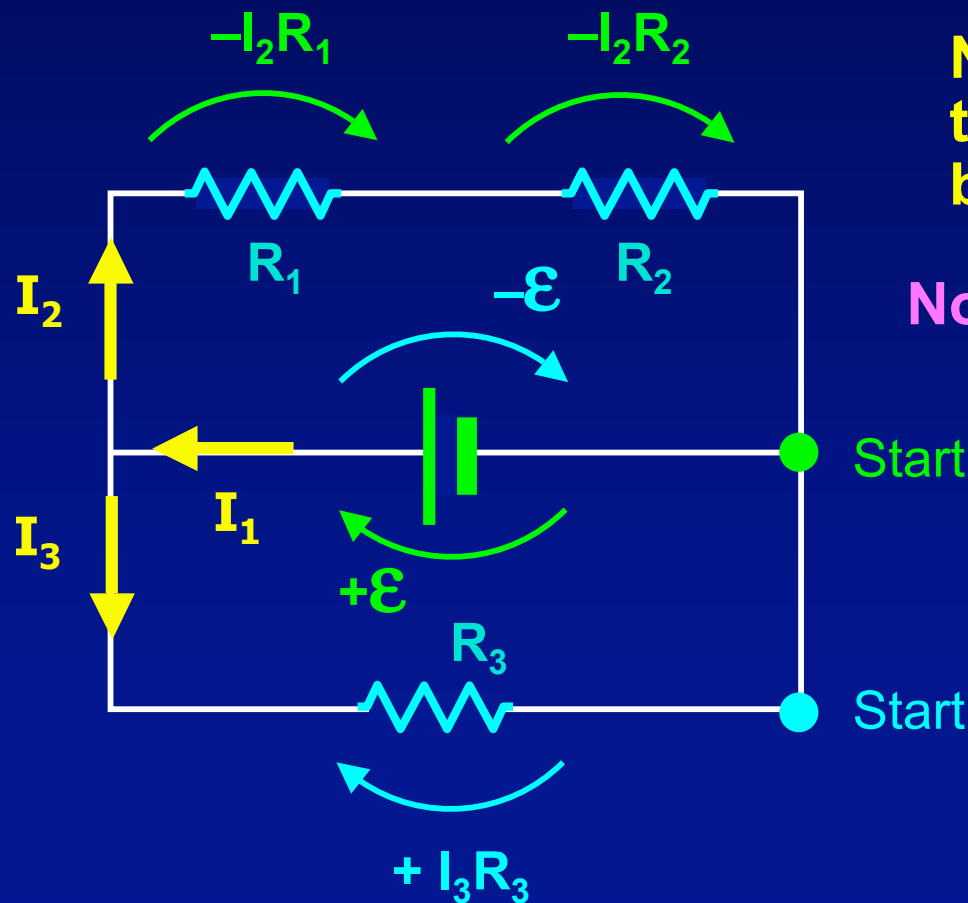

$$\Delta V = +\mathcal{E} - I_2 R_1 - I_2 R_2 = 0$$

$$\Delta V = +I_3 R_3 - \mathcal{E} = 0$$

Example: Wheatstone bridge


- A device to measure resistance. When the bridge is balanced by adjusting R_3 , no current flows through the ammeter. Determine R_x .

Label each current with a symbol and a direction.

$$V_{AB} \text{ is same as } V_{AD} : \\ I_3 R_3 = I_1 R_1 \quad (1)$$

$$V_{BC} \text{ is same as } V_{DC} : \\ I_3 R_x = I_1 R_2 \quad (2)$$
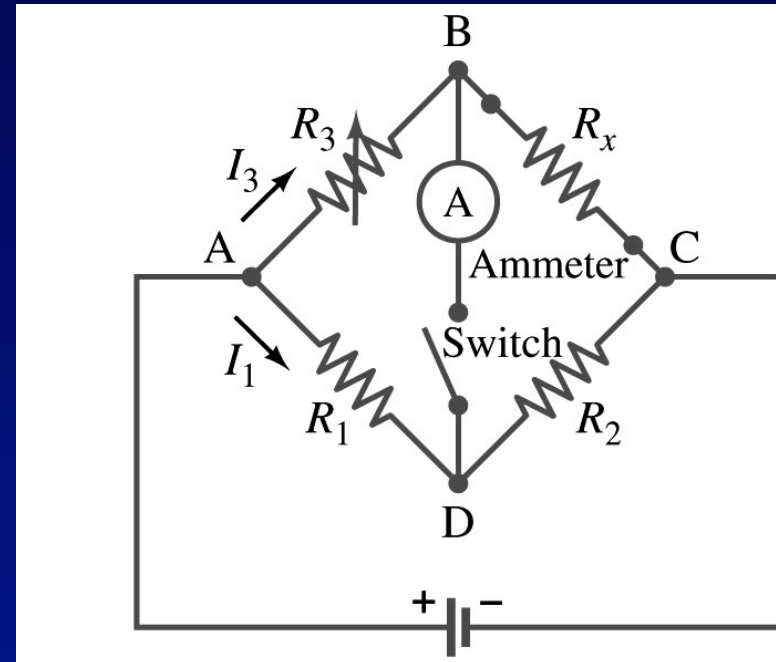
$$\text{Solve for } R_x : \\ R_x = R_2 R_3 / R_1$$



$$\begin{aligned} \text{If } R_1 &= 630 \, \Omega \\ R_2 &= 972 \, \Omega \\ R_3 &= 65.7 \, \Omega, \\ \text{then } R_x &= 65.7 \, \Omega \end{aligned}$$

Example: using Kirchhoff's Rules

- Determine the currents flowing through each resistor in the circuit shown.


Label each current with a symbol and a direction.

Junction rule at point a:
 $I_3 = I_1 + I_2 \quad (1)$

Upper loop (ahdcba):
 $-30I_1 + 45 - I_3 - 40I_3 = 0 \quad (2)$

Outer loop (ahdefga):
 $-30I_1 + 20I_2 + I_2 - 80 = 0 \quad (3)$

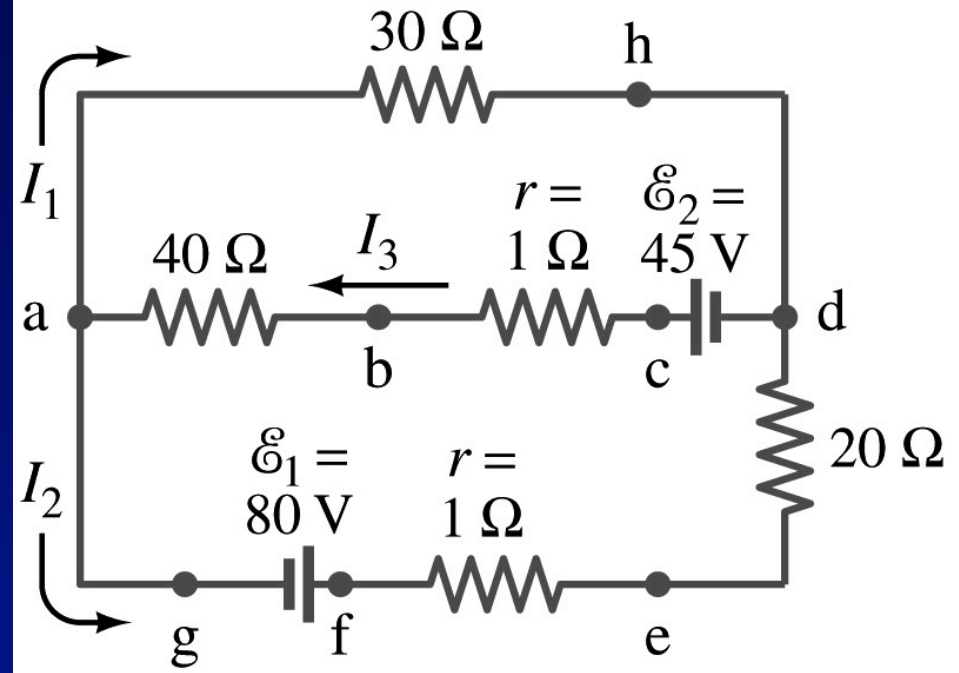Lower loop (agfedcba):
 $+80 - I_2 - 20I_2 + 45 - I_3 - 40I_3 = 0 \quad (4)$



Solve from (1), (2), (3):
 $I_1 = -0.87 \text{ A}$ (opposite to assumed)
 $I_2 = 2.6 \text{ A}$
 $I_3 = 1.7 \text{ A}$

Example: a complex network

- The picture shows a bridge-type circuit with 5 equal resistors connected to a battery.
 - Find the current in each resistor
 - What's the equivalent resistance of the five resistors?

There are 5 different currents.
Junction rule can reduce the number to 3. Choose currents and 3 loops as shown:



$$\text{loop 1 (ccw): } +13 - I_1 \times 1 - (I_1 - I_3) \times 1 = 0$$

$$\text{loop 2 (cw): } -I_2 \times 1 - (I_1 + I_3) \times 2 + 13 = 0$$

$$\text{loop 3 (ccw): } -I_1 \times 1 - I_3 \times 1 + I_2 \times 1 = 0$$

$$I_1 = 6 \text{ A}, I_2 = 5 \text{ A}, I_3 = -1 \text{ A}$$

$$R_{eq} = 13 / (5 + 6) = 1.2 \Omega$$

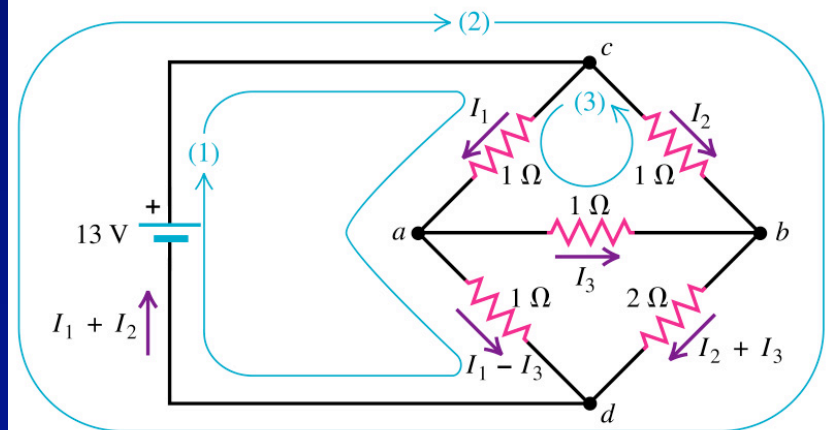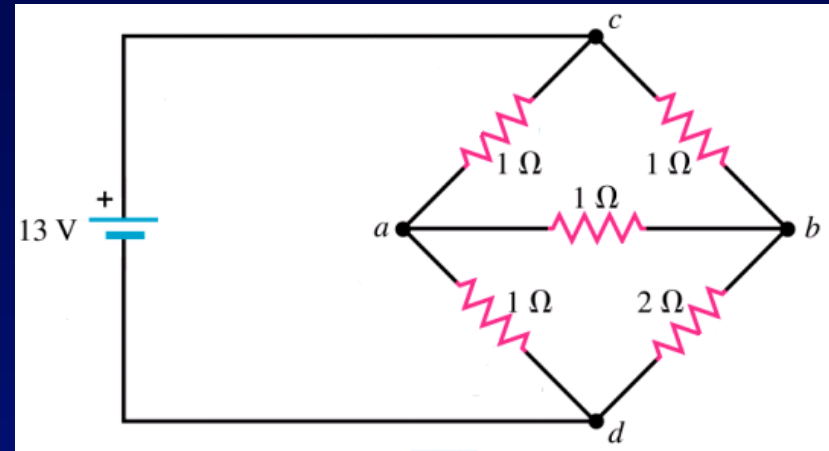


Copyright © 2004 Pearson Education, Inc., publishing as Addison Wesley.

ConcepTest 26.2

Kirchhoff's Rules

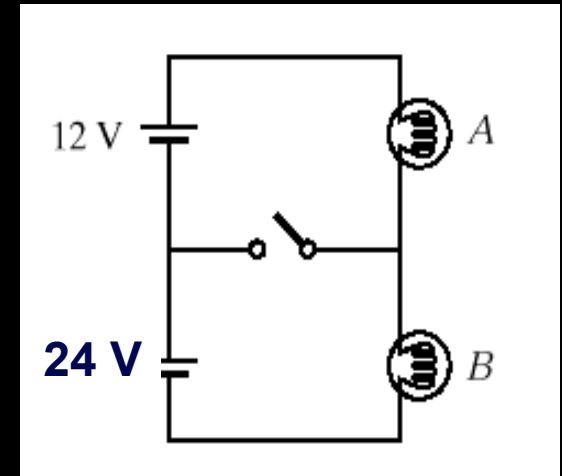- The light bulbs in the circuit are identical. When the switch is closed, what happens?
 - (1) both bulbs go out
 - (2) intensity of both bulbs increases
 - (3) intensity of both bulbs decreases
 - (4) A gets brighter and B gets dimmer
 - (5) A gets dimmer and B gets brighter
 - (6) nothing changes




Electrical Measuring Instruments

New Topic

d'Arsonval Galvanometer


- No current, no movement.
- If there's a current passing through the coil, then the permanent magnet will cause it to deflect.
- A spring brings it back.
- The amount of deflection is directly proportional to the current
- Full-scale deflection I_{fs} : the maximum current it can measure
- Resistance in coil R_c (as small as possible)
- So the voltage across the coil at full deflection is $V = I_{fs} R_c$

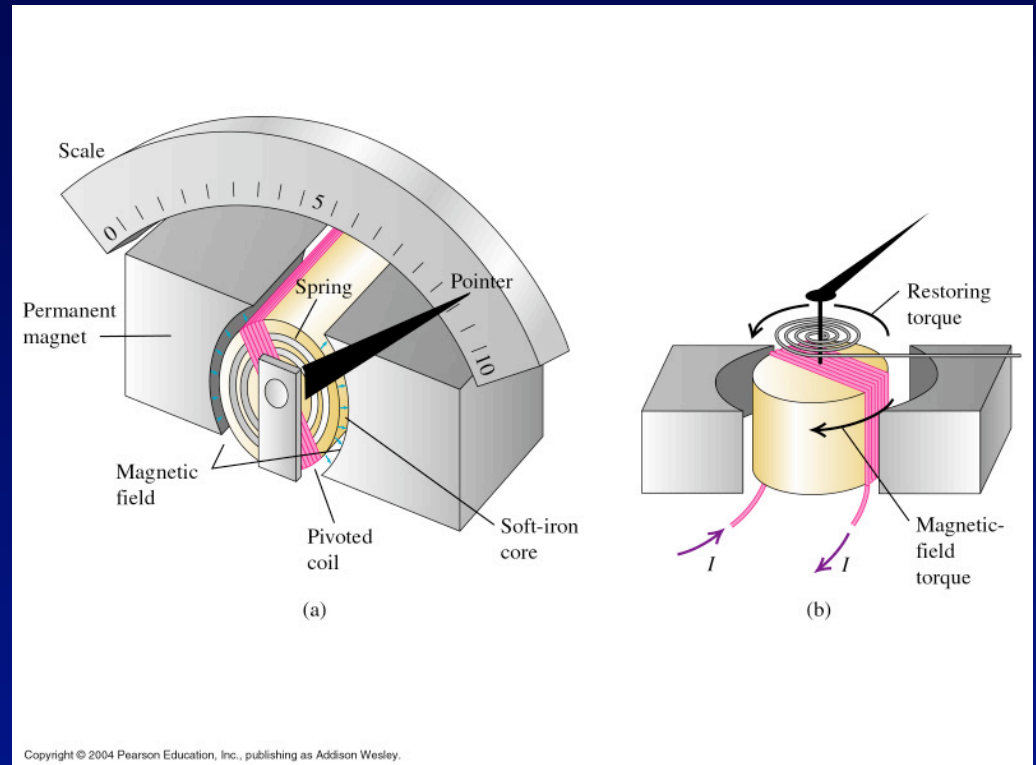

Ammeter

- Ammeter can be adapted to measure larger currents by connecting a shunt resistor in parallel as shown

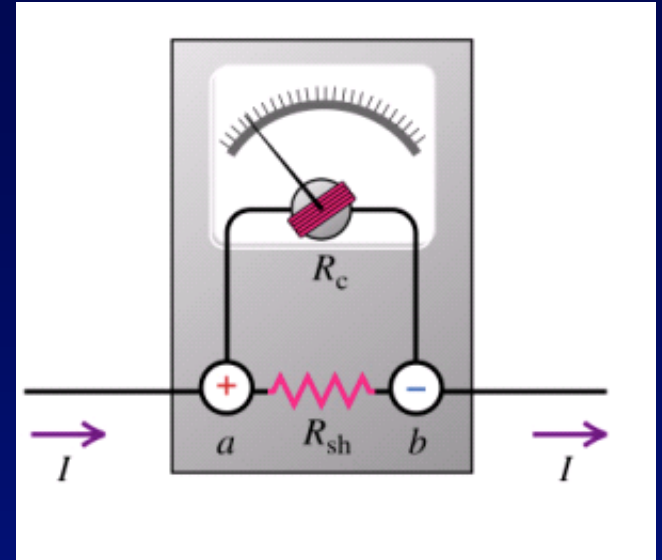Example: What shunt resistance is required to make the 1.00-mA, 20- Ω meter into an ammeter with a range of 0 A to 50.0 mA ? (Example 26.8)



$$I_{fs} R_c = (I_a - I_{fs}) R_{sh}$$

$$R_{sh} = \frac{I_{fs} R_c}{I_a - I_{fs}} = \frac{1 \times 20}{50 - 1} = 0.408 \, \Omega$$

$$R_{eq} = 0.400 \, \Omega$$

Question: how much current is in each resistor?

Answer: 1 mA in the coil and 49 mA in the shunt resistor.

Voltmeter

Question: How can we make a 1.00-mA, 20- Ω galvanometer into a voltmeter with a maximum range of 10.0 V ? (Example 26.9)

- Answer: by connecting a large resistor in series as shown.


$$V_{ab} = I_{fs} (R_c + R_s)$$

$$R_s = \frac{V_{ab}}{I_{fs}} - R_c = \frac{10}{0.001} - 20 = 9980 \, \Omega$$

$$R_{eq} = 10000 \, \Omega$$

The voltage across the coil is $I_{fs} R_c = 0.02 \, \text{V}$.

The voltage across the added resistor is 9.98 V.

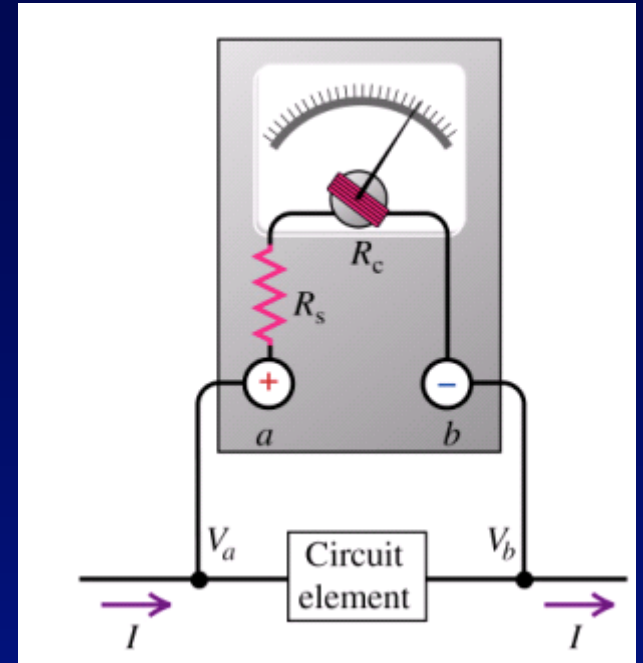

ConcepTest 26.3

- The circuit in which the ammeter and the voltmeter are correctly arranged to measure the unknown resistance R is

- (a) 1
- (b) 2
- (c) 3
- (d) 4
- (e) 5

Ammeter and Voltmeter

