
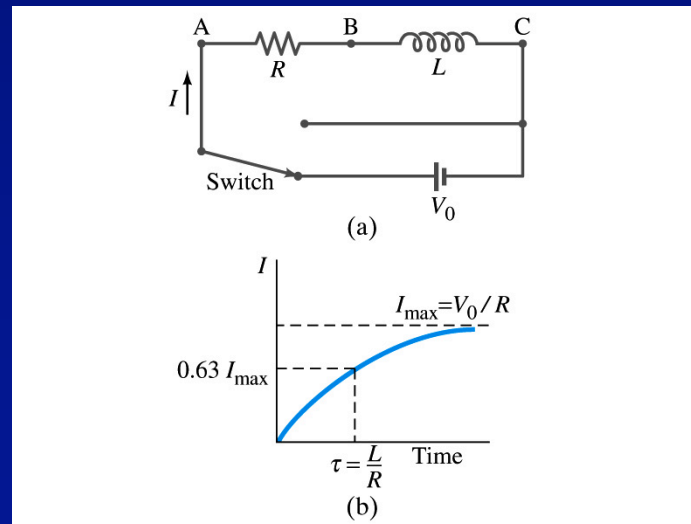


chapter 30

Inductance

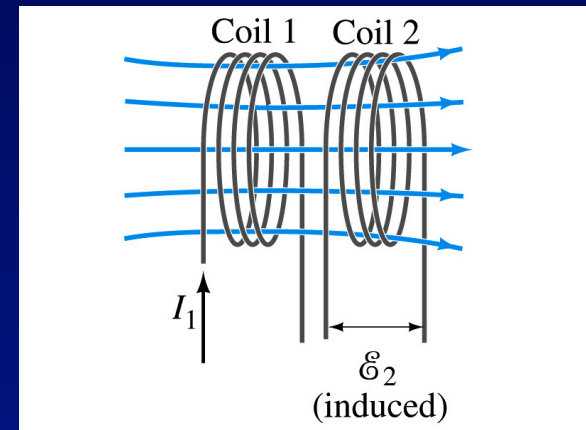- Mutual Inductance
- Self-Inductance
- Energy stored in a magnetic field
- LR Circuits
- LC Circuits
- LRC Circuits




Mutual Inductance

New Topic

Mutual Inductance

The magnetic flux in coil 2 created by coil 1 is proportional to I_1 . Define

$$M_{21} = \frac{N_2 \Phi_{21}}{I_1}$$

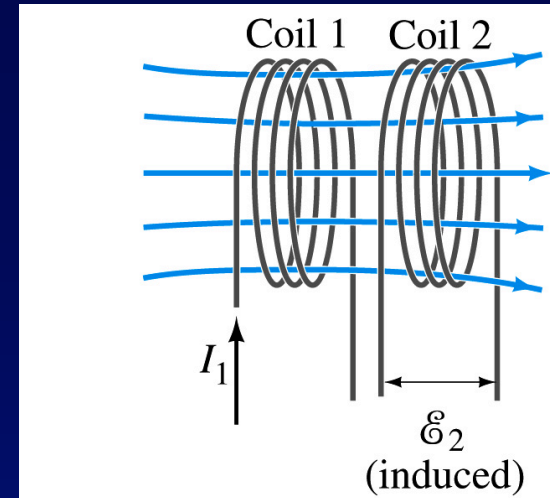

M_{21} is called the mutual inductance. It depends only on the geometric factors, NOT on the currents.

Faraday's law:

$$\mathcal{E}_2 = -N_2 \frac{d\Phi_{21}}{dt}$$

$$\mathcal{E}_2 = -M_{21} \frac{dI_1}{dt}$$

The reverse situation is

$$\mathcal{E}_1 = -M_{12} \frac{dI_2}{dt}$$

$$M_{12} = M_{21} = M$$

The SI unit for M is **henry** (H). $1 \text{ H} = 1 \text{ V.s/A} = 1 \text{ } \Omega.\text{s}$

Example: Solenoid and coil

The magnetic field inside the solenoid is


$$B = \mu_0 \frac{N_1}{l} I_1$$

The magnetic flux through the coil is

$$\Phi_{21} = BA = \mu_0 \frac{N_1}{l} I_1 A$$

Hence the mutual inductance is

$$M = \frac{N_2 \Phi_{21}}{I_1}$$

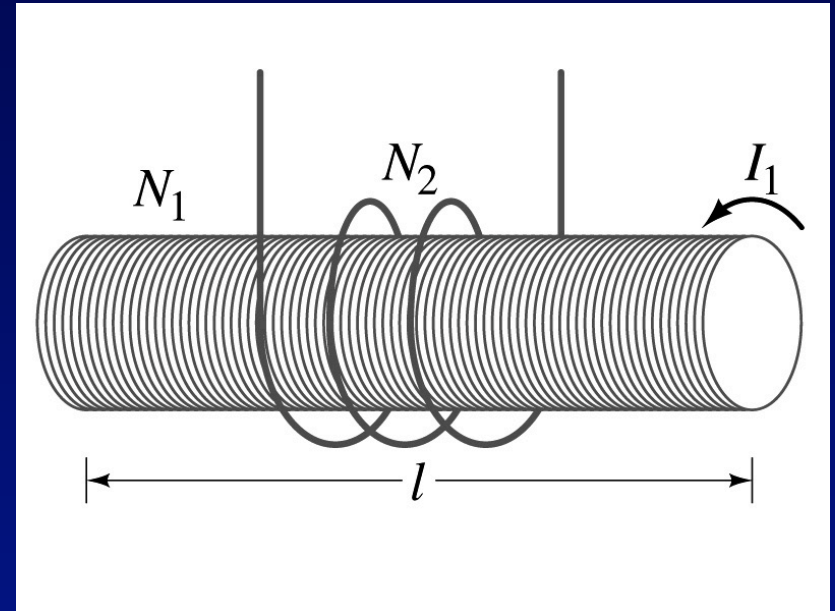

$$M = \mu_0 \frac{N_1 N_2 A}{l}$$

Examples of Mutual Inductance


- Transformer
- Heart pacemaker
 - ⚡ Power in an external coil is transmitted via mutual inductance to a 2nd coil inside the body.
 - ⚡ No surgery is needed to replace a battery like in battery-operated pacemakers.
- It can be a problem: **interference**
 - ⚡ Any changing current can induce an emf in another part of the same circuit or in a different circuit

Self Inductance

New Topic

The concept of self-induction

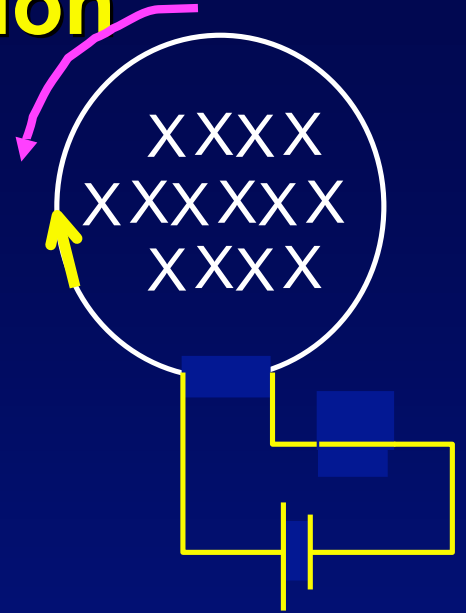
- Consider the loop at the right.
 - switch closed \Rightarrow current starts to flow in the loop.
 - magnetic field is produced in the area enclosed by the loop.
 - flux through loop changes
 - emf induced in loop opposing initial emf
- **Self-Induction:** the act of a changing current through a loop inducing an opposing current in that same loop.



Self-Inductance

The total magnetic flux in the coil is proportional to the current I . Define

$$L = \frac{N\Phi_B}{I}$$

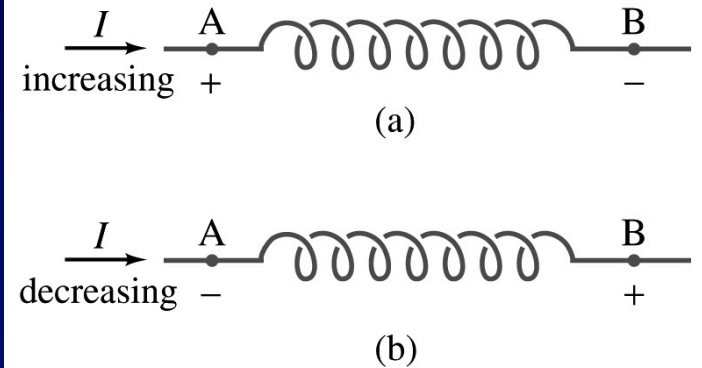

L is called self-inductance. It depends only on the geometric factors, NOT on the current. Such coil is called an inductor.

Use Faraday's law:

$$\mathcal{E} = -N \frac{d\Phi_B}{dt}$$

$$\mathcal{E} = -L \frac{dI}{dt}$$

The SI unit for L is also **henry** (H). **1 H = 1 $\Omega \cdot s$.**

Example: Solenoid inductance

The magnetic field inside the solenoid is

$$B = \mu_0 \frac{N}{l} I$$


The total magnetic flux through the coil is

$$\Phi_B = BA = \mu_0 \frac{N}{l} IA$$

Hence the self-inductance is

$$L = \frac{N\Phi_B}{I} \text{ or}$$

$$L = \mu_0 \frac{N^2 A}{l}$$

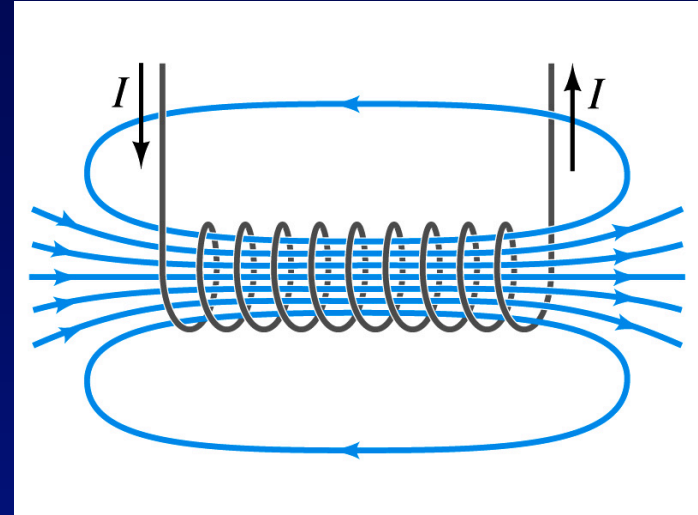

For $N=100$, $l=5$ cm, $A=0.3$ cm², $L=4\pi$
 $\times 10^{-7} \times 100^2 \times 0.3 \times 10^{-4} / 0.05 = 7.5$ μ H.

If filled with an iron core ($\mu=4000 \mu_0$), $L= 30$ mH.

Voltage across an inductor

- Inductor does not oppose current that flows through it. It opposes the **change** in the current.
 - ⚡ It's a current stabilizer in the circuit.



$$V_{ab} = iR$$

(a) Resistor with current i flowing from a to b :
potential drops from a to b



$$V_{ab} = L \frac{di}{dt}$$

(b) Inductor with current i flowing from a to b :


- If $di/dt > 0$: potential drops from a to b
- If $di/dt < 0$: potential increases from a to b
- If i is constant ($di/dt = 0$): no potential difference

ConcepTest 30.1

Inductance

- Consider the two inductors shown:
 - Inductor 1 has length l , N total turns and has inductance L_1 .
 - Inductor 2 has length $2l$, $2N$ total turns and has inductance L_2 .
- What is the relation between L_1 and L_2 ?

(1) $L_2 < L_1$ (2) $L_2 = L_1$ (3) $L_2 > L_1$

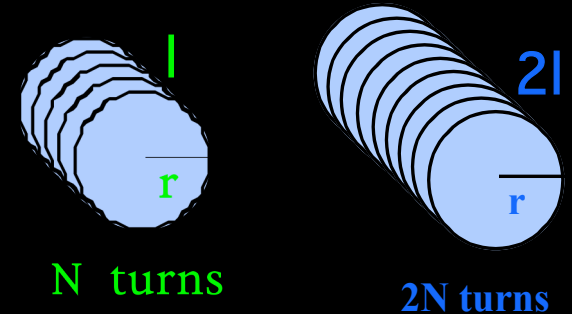


ConcepTest 30.2

Inductance

- A small, circular ring of wire is inside a larger loop that is connected to a battery and a switch S. The small ring and the larger loop both lie in the same plane. When the switch S is closed,

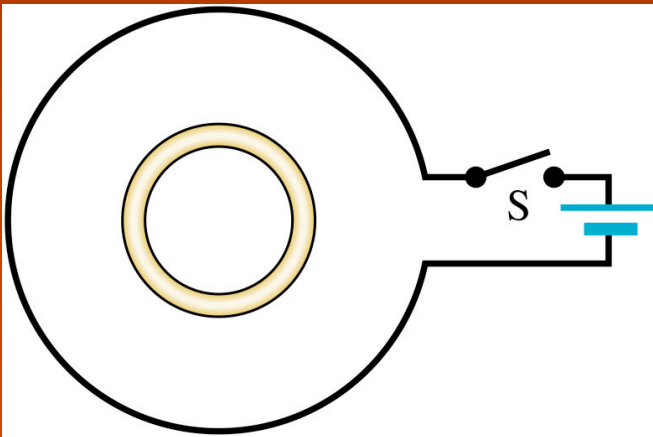- 1) a clockwise current flows in the ring, caused by self-inductance
- 2) a counterclockwise current flows in the ring, caused by self-inductance
- 3) a clockwise current flows in the ring, caused by mutual inductance
- 4) a counterclockwise current flows in the ring, caused by mutual inductance
- 5) nothing happens



Energy Stored in a Magnetic Field

New Topic

Energy Stored in a Magnetic Field

When an inductor is carrying a current which is changing at a rate dI/dt , the energy is being supplied to the inductor at a rate


$$P = I\varepsilon = LI \frac{dI}{dt}$$

The work needed to increase the current from 0 to I is

$$W = \int P dt = \int_0^I LI dI = \frac{1}{2} LI^2$$

By energy conservation, the energy stored in the inductor is

$$U = \frac{1}{2} LI^2$$

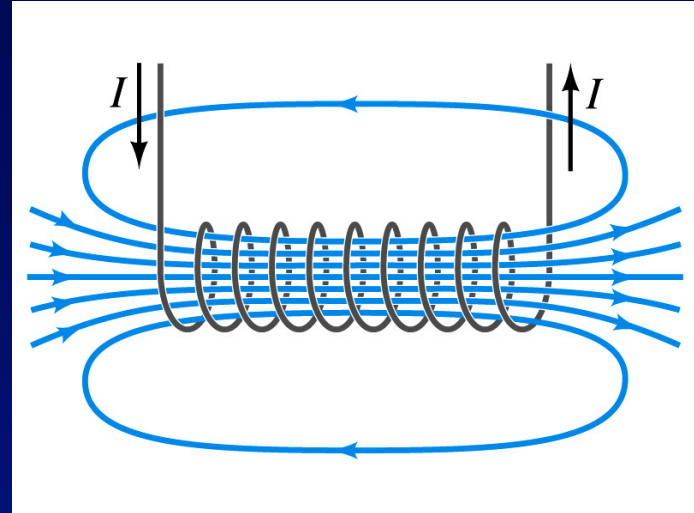

Energy Stored in a Magnetic Field

Question: Where exactly does the energy reside?

$$U = \frac{1}{2} LI^2$$

Answer: It resides in the magnetic field.

$$\text{Using } L = \mu_0 \frac{N^2 A}{l}$$

$$\text{and } B = \mu_0 \frac{N}{l} I$$


$$U = \frac{1}{2} \left(\mu_0 \frac{N^2 A}{l} \right) \left(\frac{Bl}{\mu_0 N} \right)^2 = \frac{1}{2} \frac{B^2}{\mu_0} Al$$

The conclusion is valid for any region of space where a magnetic field exists.

Compare with the electric case:

$$U = \frac{1}{2} CV^2$$

$$u = \frac{1}{2} \epsilon_0 E^2$$

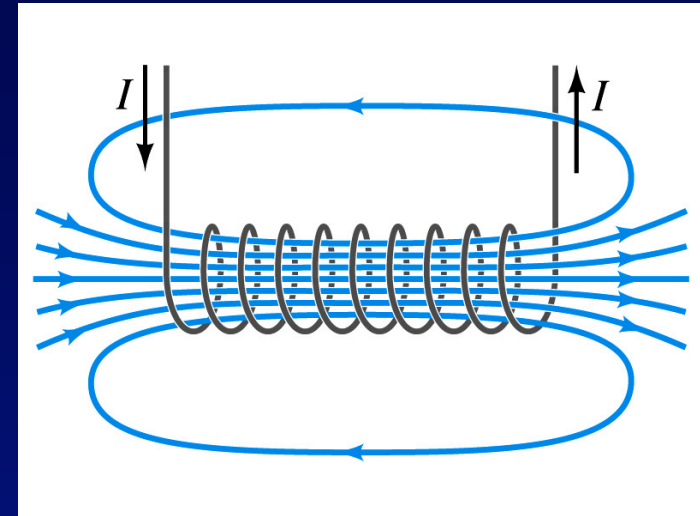

Or energy density

$$u = \frac{1}{2} \frac{B^2}{\mu_0}$$

ConceptTest 30.3

Inductors

If you want to double the energy stored in an inductor, the current in the inductor must

- (1) stay the same
- (2) double
- (3) triple
- (4) quadruple
- (5) increase by a factor of 1.4

LR Circuit

New Topic

LR Circuits

Question: What happens when the switch is thrown to connect with the battery?



Answer: Current starts to flow, eventually reaching the steady value of V_0/R .

$$\text{loop rule: } V_0 - IR - L \frac{dI}{dt} = 0$$

Solve differential equation

$$I(t) = \frac{V_0}{R} \left(1 - e^{-t/\tau} \right)$$

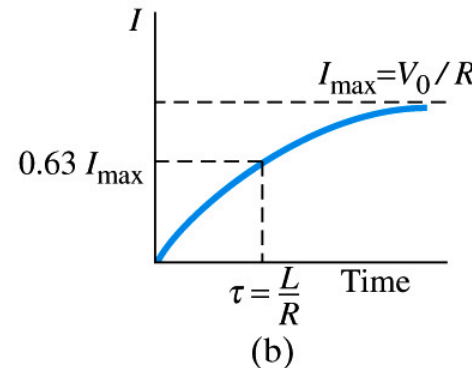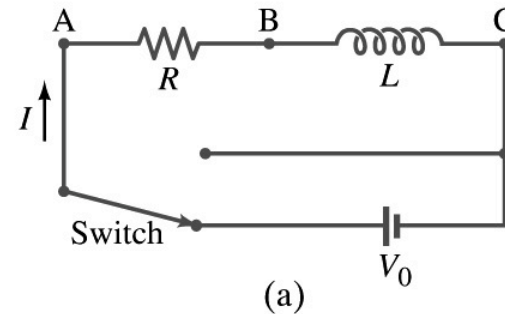Where $\tau = L/R$ is called the time constant.



LR Circuits



Question: What if the switch is thrown to disconnect with the battery?

$$\text{loop rule : } -IR - L \frac{dI}{dt} = 0$$

Solve differential equation

$$I(t) = \frac{V_0}{R} e^{-t/\tau} \quad \text{time constant } \tau = L/R$$

Summary: there is always some reaction time when a LR circuit is turned on or off. The situation is similar to RC circuits, except here the time constant is proportional to $1/R$, not R .

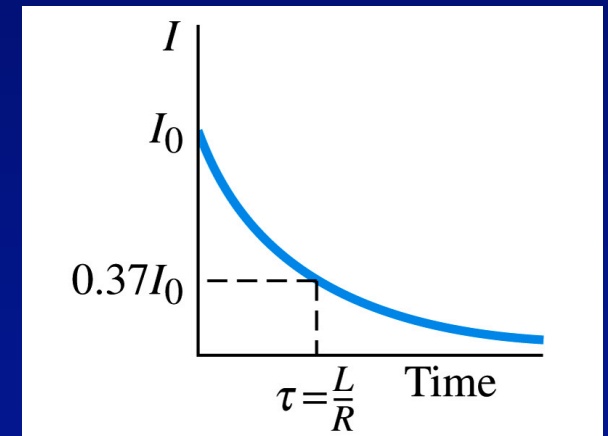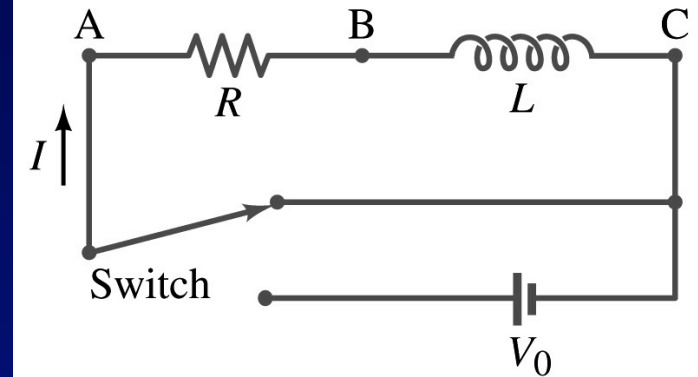


ConcepTest 30.4

LR Circuits

Which circuit has the longer time constant after the switch is thrown to position a?
(assume $R=1\ \Omega$ and $L=1\ \text{H}$)

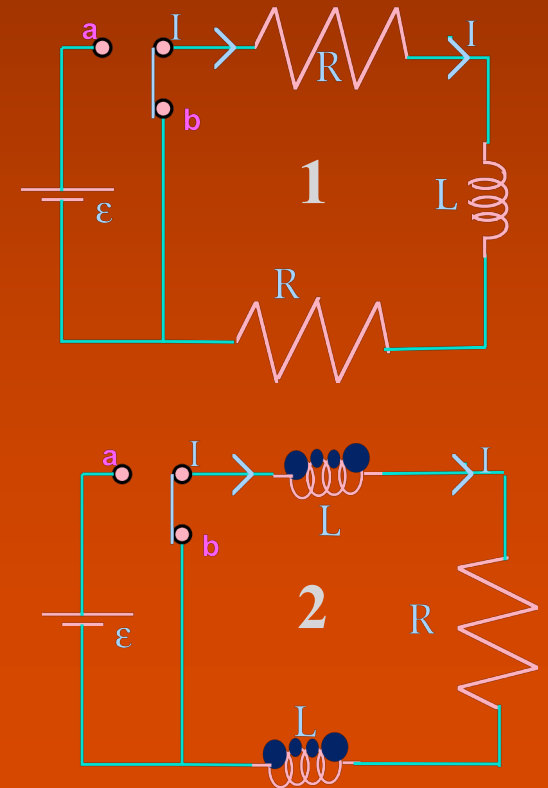- (1) Circuit 1
- (2) Circuit 2
- (3) They are the same
- (4) Not enough info



LC Circuit

New Topic

LC Circuits

The capacitor is charged to Q_0 .
At $t=0$, the circuit is closed.
What will happen?

$$\text{loop rule: } \frac{Q}{C} - L \frac{dI}{dt} = 0$$

Using $I = -dQ/dt$, one gets


$$\frac{d^2 Q}{dt^2} + \frac{Q}{LC} = 0$$

Solve differential equation

$$Q(t) = Q_0 \cos(\omega t + \phi)$$


where

$$\omega = 1 / \sqrt{LC}$$

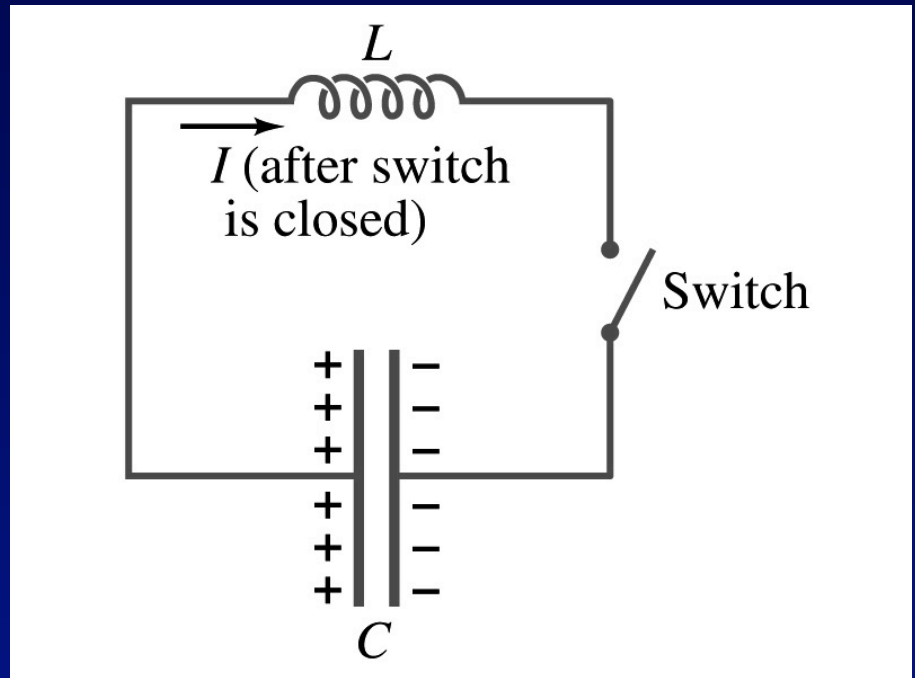

LC Circuits


$$Q(t) = Q_0 \cos(\omega t + \phi)$$

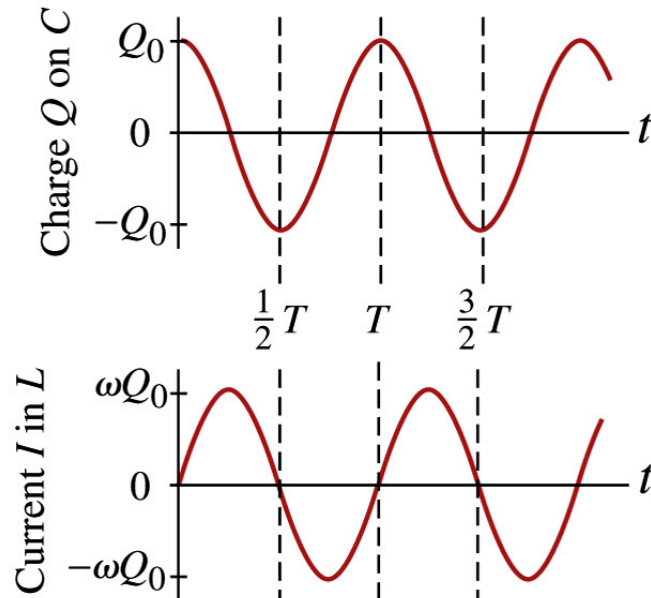

$$I(t) = \frac{dQ}{dt} = -Q_0 \omega \sin(\omega t + \phi)$$


Charge oscillates! So does the current and voltage.

What about energy?

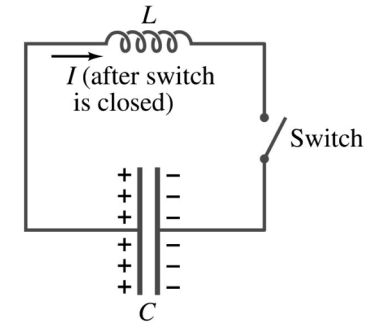

$$U_E = \frac{1}{2} \frac{Q^2}{C} = \frac{Q_0^2}{2C} \cos^2(\omega t + \phi)$$
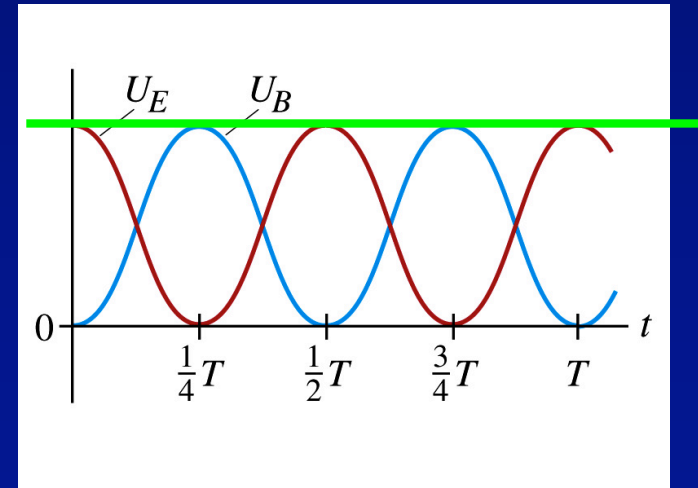
$$U_B = \frac{1}{2} L I^2 = \frac{Q_0^2}{2C} \sin^2(\omega t + \phi)$$



The total energy is conserved.

A natural oscillator in the circuit

Inductor-Capacitor Circuit

$$\text{Magnetic energy} = \frac{1}{2}Li^2$$

$$\text{Electric energy} = q^2/2C$$

$$\frac{1}{2}Li^2 + q^2/2C = Q^2/2C$$

$$i = \pm \sqrt{1/LC} \sqrt{Q^2 - q^2}$$

$$i = dq/dt$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$q = Q \cos(\omega t + \phi)$$

Mass-Spring System

$$\text{Kinetic energy} = \frac{1}{2}mv_x^2$$

$$\text{Potential energy} = \frac{1}{2}kx^2$$

$$\frac{1}{2}mv_x^2 + \frac{1}{2}kx^2 = \frac{1}{2}kA^2$$

$$v_x = \pm \sqrt{k/m} \sqrt{A^2 - x^2}$$

$$v_x = dx/dt$$


$$\omega = \sqrt{\frac{k}{m}}$$

$$x = A \cos(\omega t + \phi)$$

ConceptTest 30.5

Inductance

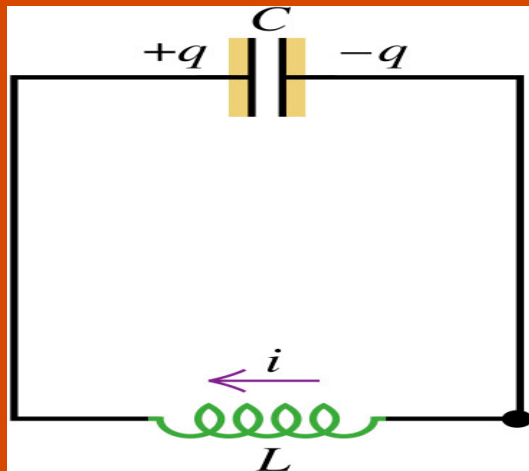- An inductor (inductance L) and a capacitor (capacitance C) are connected as shown.
 - If the values of both L and C are doubled, what happens to the time required for the capacitor charge to oscillate through a complete cycle?
- 1) it becomes 4 times longer
 - 2) it becomes twice as long
 - 3) it is unchanged
 - 4) it becomes $1/2$ as long
 - 5) it becomes $1/4$ as long





LRC Circuit


New Topic

LC Oscillations with Resistance

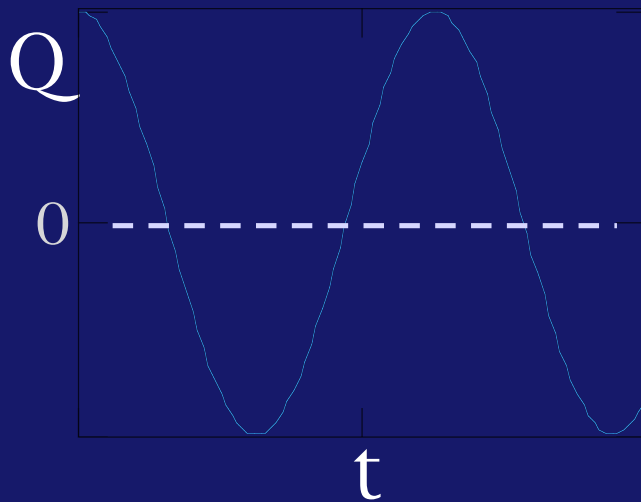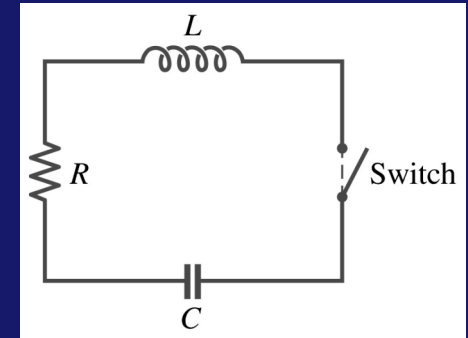- If L has finite Resistance, then
 - energy will be dissipated in R and
 - the oscillations will become damped.



$$R = 0$$

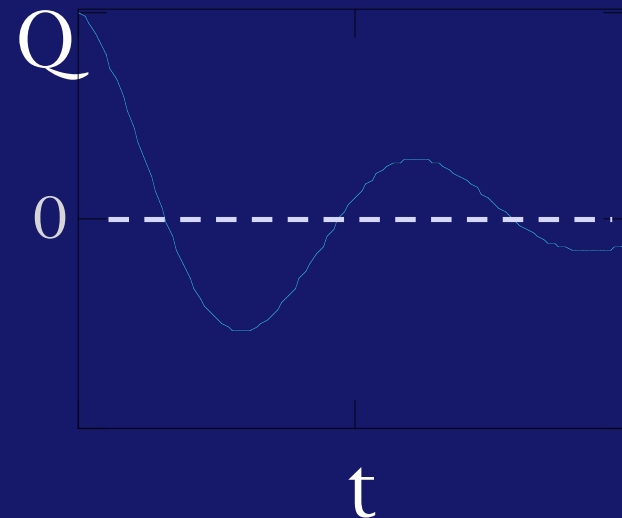

$$R \neq 0$$

Real circuits always have resistance R .

LRC Circuits

Damped oscillations! 3 scenarios.

A) Under-damped if $R^2 < 4L/C$.



B) Critical damping if $R^2 = 4L/C$.

C) Over-damped if $R^2 > 4L/C$.

For under-damping:

$$Q(t) = Q_0 e^{-\frac{R}{2L}t} \cos(\omega' t + \phi)$$
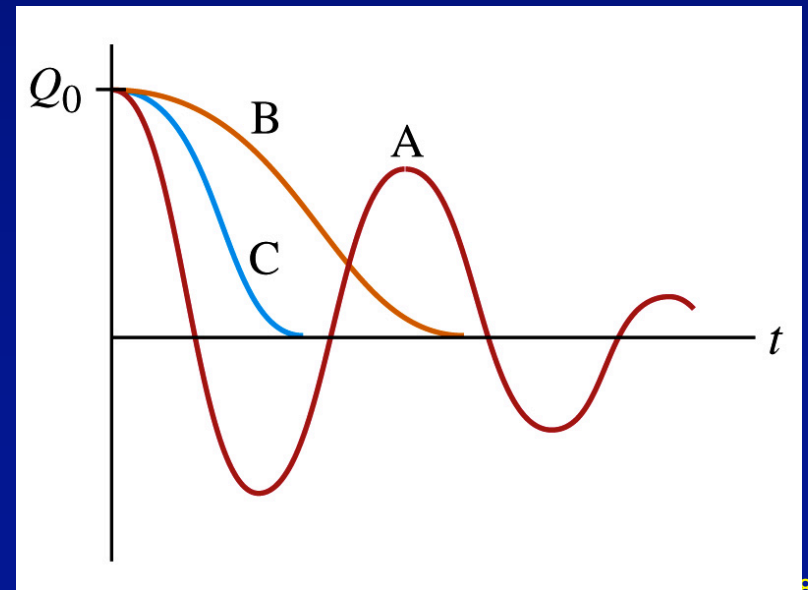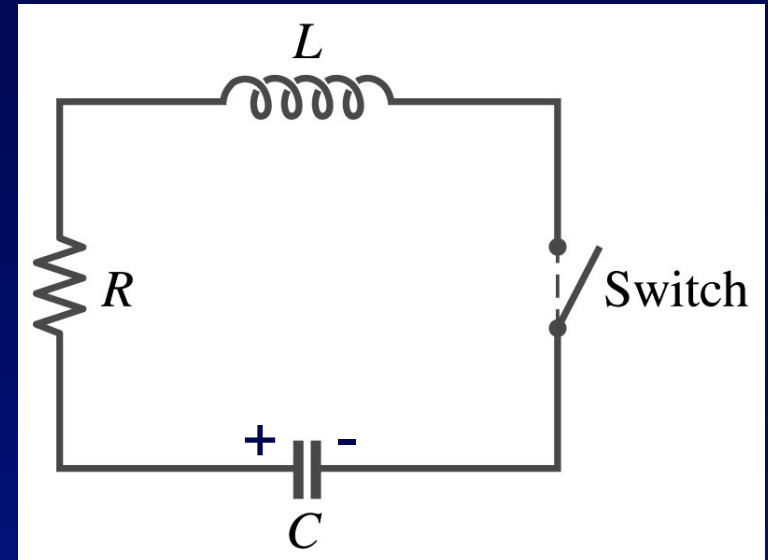
$$T = \frac{2\pi}{\omega'} = \frac{2\pi\sqrt{LC}}{\sqrt{1 - \frac{R^2 C}{4L}}}$$



Summary of Various Direct Current Circuits

RC circuit, time constant $\tau = RC$ (transient)

LR circuit, time constant $\tau = L/R$ (transient)

LC circuit, oscillation period $T = 2\pi\sqrt{LC}$ (oscillator)

LRC circuit, damped oscillation period

$$T = 2\pi\sqrt{LC} / \sqrt{1 - \frac{R^2C}{4L}}$$


(damped oscillator)

We will discuss what happens if we use a **AC-source** to replace the DC-source (Chapter 31) in these circuits.

Example: LR circuit

At $t=0$, the circuit is closed.

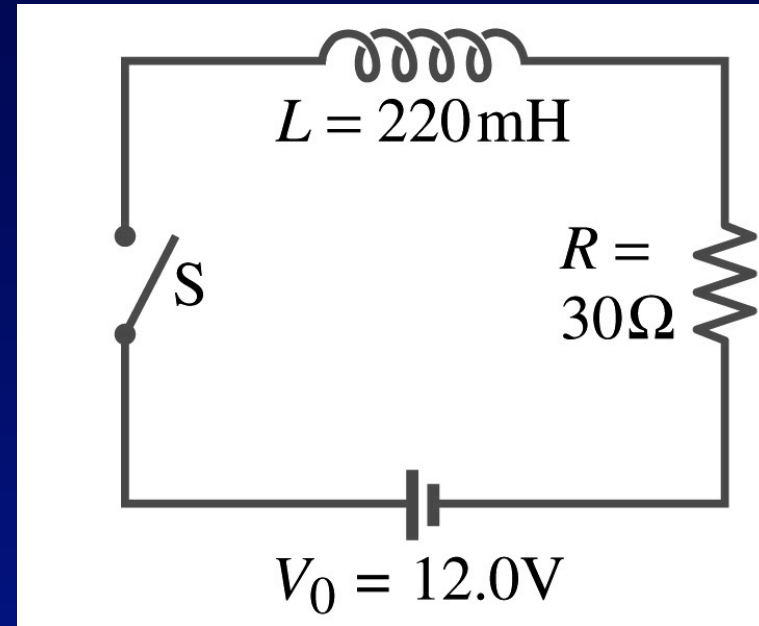- a) What is the current at $t=0$?
- b) What is the time constant?
- c) What is the maximum current?
- d) How long will it take the current to reach half of its maximum value?
- e) At this instant in d), at what rate the energy is being delivered by the battery?
- f) At what rate is energy is being stored in the inductor?



Example: LC circuit

A **1200-pF** capacitor is fully charged by a **500-V** dc power supply. It is disconnected from the power supply and is connected, at $t=0$, to a **75-mH** inductor. Determine

- a) the initial charge on the capacitor
- b) the frequency of oscillation
- c) the maximum current
- d) the total energy oscillating in the circuit

