Alternating Current (AC) Circuits



AC Circuits

- AC Circuit with only R
 AC circuit with only L
 AC circuit with only C
 AC circuit with LRC
 phasors
- Resonance
- Transformers







Physics Motivation

- Last time we discovered that a LC circuit was a natural oscillator.
- However, any real attempt to construct a LC circuit must account for the resistance of the inductor. This resistance will cause oscillations to damp out.



- Question: Is there any way to modify the circuit above to sustain the oscillations without damping?
- Answer: Yes, if we can supply energy at the rate the resistor dissipates it! How? A sinusoidally varying emf (AC generator) will sustain sinusoidal current oscillations! i(t)=lcos(ωt) or v(t)=Vcos(ωt)

• But first, let us look at R, L, C separately before putting them together.

Phasor Diagram

How to graphically represent an AC source?

$$i = I \cos \omega t$$

A phasor is a vector in the x-y plane, rotating counter-clockwise with angular velocity
 0.

Magnitude is the peak value
 Projection on the x-axis is the value at a given time

Same for emf:

ωt

 $i = I \cos \omega t$

0

right © 2004 Pearson Education. Inc. publishing as Addison We

 $v = V \cos \omega t$

ω

RMS current and voltage

$$i = I \cos \omega t$$

root-mean-square:

$$I_{rms} = \sqrt{i^2}$$

$$\overline{i^2} = \frac{1}{T} \int_0^T i^2 dt = \frac{I^2}{2T} \int_0^T (1 + \cos 2\omega t) dt = \frac{I^2}{2}$$

 $I_{rms} = \frac{I}{\sqrt{2}}$

$$V_{rms} = \frac{V}{\sqrt{2}}$$



In the US, the 120-V AC voltage supplied to household refers to the rms value. What is the peak voltage? 170 V

AC Circuit Containing only Resistance



The AC source is given as

$$i = I \cos \omega t$$

So the voltage across the resistor is

$$v_R = iR = IR\cos\omega t = V_R\cos\omega t$$

The resistor voltage is in phase with the current.

The power dissipated in the resistor is p=iv, or at an average rate

$$\overline{P} = I_{rms}^2 R = \frac{V_{rms}^2}{R}$$

AC Circuit Containing only Inductor



The AC source is given $i = I \cos \omega t$

So the voltage across the inductor is

$$v_L = L\frac{di}{dt} = -IL\omega\sin\omega t = V_L\cos(\omega t + 90^\circ)$$

The inductor voltage leads the current by 90 degrees.

Define reactance of inductor $X_L = \omega L$, then $V_L = I X_L$. Its unit is Ohm. For example, a 0.3-H inductor connected to a 60-Hz ac-source has a reactance of $X_L = 2\pi x 60 \times 0.3 = 113 \Omega$.

AC Circuit Containing only Capacitor



$$q = \int_{0}^{t} i dt = \frac{I}{\omega} \sin \omega t = \frac{I}{\omega} \cos(\omega t - 90^{\circ}) \qquad v_{C} = \frac{I}{\omega C} \cos(\omega t - 90^{\circ})$$

The capacitor voltage lags the current by 90 degrees.

Define reactance of capacitor $X_c = 1/\omega C$, then $V_c = I X_c$. Its unit is Ohm. For example, a 1-µF capacitor connected to a 60-Hz ac-source has a reactance of $X_c = 1/(2\pi x 60 \times 10^{-6}) = 2.7 \text{ k}\Omega$.

Summary: AC source $i = I \cos \omega t$

Define V = IX

 $v_R = IR \cos \omega t$ resistance $X_R = R$.



$$v_L = IL\omega \cos(\omega t + 90^{\circ})$$

inductive reactance
 $X_L = L\omega$.



$$v_C = \frac{I}{\omega C} \cos(\omega t - 90^\circ)$$

capacitive reactance $X_c=1/(\omega C)$.



Frequency Dependence

resistance $X_R = R$.

inductive reactance $X_L = \omega L$.

capacitive reactance $X_c = 1/(\omega C)$.



AC-driven LRC Circuit in Series



Given ac-source i=lcos(ωt)

Let v_R , v_L , v_C represent the voltages at a given time.

- Physics questions:
 - What is the impedance Z of the entire circuit as defined by the peak values V=IZ?
 - Does the source voltage lead or lag the current? By how much?
- In other words: If one can write v= v_R+v_L+v_C = Vcos(ωt+φ), then what is V and φ ?
- Or: How to add the voltages v= v_R+v_L+v_C, noting that they are varying with time and in general out of phase with each other?



AC-driven LRC Circuit in Series
(Trigonometry Method)Given:
$$i = I \cos \omega t$$
 andFind the sum: $v_R = iR = IR \cos \omega t$ $v_L = IX_L \cos(\omega t + \pi/2)$ with $X_L = L\omega$ $v = v_R + v_L + v_C$
 $= IR \cos(\omega t) - I(X_L - X_C) \sin(\omega t)$
 $= V \cos(\omega t + \varphi)$ (desired form)
 $= V \cos(\omega t) - V \sin \varphi \sin(\omega t)$ $v_c = IX_c \cos(\omega t - \pi/2)$ with $X_c = \frac{1}{\omega C}$ Used: $\cos(A + B) = \cos A \cos B - \sin A \sin B$

Solution:

$$V\cos\varphi = IR$$
$$V\sin\varphi = I(X_L - X_C)$$

$$V = IZ \text{ with } Z = \sqrt{R^2 + (X_L - X_C)^2}$$
$$\tan \varphi = \frac{X_L - X_C}{R} \text{ or } \cos \varphi = \frac{R}{Z}$$

The sign of the phase difference ϕ

The total voltage at time t is

 $v = V \cos(\omega t + \phi)$

$$i = I \cos \omega t$$



where ϕ is the phase angle by which voltage leads the current.

The figure shows the case $X_L > X_C$ which means ϕ is positive. Or the voltage leads the current.

If $X_L < X_C$, then ϕ is negative. Or the voltage lags the current. The figure is

It can be seen more easily from $tan\phi$.

$$\tan\phi = \frac{X_L - X_C}{R}$$





The Impedance Triangle

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
$$X_L = \omega L$$
$$X_C = \frac{1}{\omega C}$$
$$\tan \phi = \frac{X_L - X_C}{R} \text{ or } \cos \phi = \frac{R}{Z}$$



General results, valid for any combination of L, R, C in series. For example, if LR circuit, set $X_c=0$.

Check special cases:

R only:
$$X_{L} = 0, X_{C} = 0$$
, so $Z = R, \phi = 0$

L only:
$$R = 0, X_C = 0$$
, so $Z = X_L, \phi = +90^\circ$

C only:
$$R = 0, X_L = 0$$
, so $Z = X_C, \phi = -90^\circ$

Who is driving?

We derived the results with a driving current

$$i = I \cos \omega t$$

 $v = V \cos(\omega t + \phi)$

\$\overline{\phi}\$ is the angle by whichvoltage leads the current.

The same results for Z and ϕ apply if we have a driving emf

 $v = V \cos \omega t$

$$i = I\cos(\omega t - \phi)$$

 ϕ is the same angle by which current lags the voltage.

It's all relative: the physics is the same.



The Power Factor

The power is only dissipated in the resistor, so

the average power is $\overline{P} = I_{rms}^2 R$

But
$$R = Z \cos \phi$$



$$\overline{P} = I_{rms}^2 Z \cos \phi = I_{rms} V_{rms} \cos \phi = \frac{1}{2} IV \cos \phi$$

The factor $\cos\phi$ is called the power factor.

For example: For a pure resistor (ϕ =0), cos ϕ =1. For a pure inductor (ϕ =90⁰) or capacitor (ϕ =-90⁰), cos ϕ =0.

ConcepTest 31.1 Phasor Diagram

Consider this phasor diagram. Let us assume that it describes a series circuit containing a resistor, a capacitor, and an inductor. The current in the circuit has amplitude I, as indicated in the figure. Which of the following choices gives the correct respective labels of the voltages across the resistor, the capacitor, and the inductor ?

 $V_1; V_2; V_3$ $V_1; V_2; V_4$ $V_{2}; V_{2}; V_{4}$ 5) 6) $V_3; V_4; V_2$



ConcepTest 31.2 AC Circuit

An AC-current source (purple line) is connected in series to a resistor, an inductor, and a capacitor. The voltage across each element (blue line) is given separately in the pictures shown below. Give the order in which the pictures correspond to the inductor, resistor, and capacitor, respectively. ABC
BCA
CAB
ACB
BAC
CBA



ConcepTest 31.3 LRC Circuit

In an *L-R-C* series circuit as shown, the current has a very small amplitude if the emf oscillates at a very high frequency. Which circuit element causes this behavior?

- 1) the resistor *R*
- 2) the inductor *L*
- 3) the capacitor *C*
- 4) misleading question the current actually has a very *large* amplitude if the frequency is very high



Resonance in AC-circuit



Resonance in AC Circuit

Recall:

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

• For fixed R,C,L the current I will be a maximum at the resonant frequency ω_0 which makes the impedance Z purely resistive.

Z is minimum when:

$$X_L = X_C$$

So the frequency at which this condition is satisfied is given from:

$$\omega_{0}L = \frac{1}{\omega_{0}C} \implies \omega_{0} = \frac{1}{\sqrt{LC}}$$

- Note that this resonant frequency is identical to the natural frequency of the LC circuit by itself!
- At this frequency, the current and the driving voltage are in phase!

$$\cos\phi = \frac{R}{Z} = 1, \ \sin\phi = 0$$

Resonance in AC Circuit



At resonance, I and V are in phase. V, I and P are at their maximum.



Applications of AC Circuits

Capacitor as filters

(a)

Signal

Signal

(b)

 X_{C}

Circuit

A

A

Tweeter and woofer



 $X_L = 2\pi f L$



 $2\pi fC$

Circuit

B

B



More about AC circuits

Impedance matching: when

$$R_1 = R_2 \text{ (or } Z_1 = Z_2)$$

maximum power is delivered from circuit 1 to circuit 2.



Three-phase AC (4-wire transmission lines)

 $V_1 = V_0 \sin\omega t$ $V_2 = V_0 \sin(\omega t + 2\pi/3)$ $V_3 = V_0 \sin(\omega t + 4\pi/3)$

More power delivered (3 times)
 Smoother flow.





Transformers

Transformers change alternating (AC) voltage to a bigger or smaller value

Input AC voltage V_p in the primary produces a flux





Changing flux in secondary induces emf V_s

$$\boldsymbol{V}_{s} = \boldsymbol{N}_{s} \frac{\Delta \boldsymbol{\Phi}_{B}}{\Delta \boldsymbol{t}}$$

Same $\Delta \Phi / \Delta t !!$



Transformers

Nothing comes for free, however!

- voltage increase comes at the cost of current
- output power cannot exceed input power
- power in = power out (assume no heat loss)



If voltage increases, then current decreases If voltage decreases, then current increases

Example: Transmission Lines

An average of 120 kW of electric power is sent to a small town from a power plant 10 km away. The transmission lines have a total resistance of 0.4 Ω. Calculate how much power is saved if the voltage is stepped up from 240 V to 24,000 V and then down to 240 V again, rather than simply transmitting at 240 V.



ConcepTest 31.4

What is the voltage across the light bulb?

Transformers

- (1) 30 V
- (2) 60 V
- (3) 120 V
- (4) 240 V
- (5) 480 V

