

ECE4740: Digital VLSI Design

Lecture 5: Dynamic behavior of inverter


161

RC circuits ahead!

Dynamic behavior

162

Dynamic behavior: intuition


 


- $V_{out}(t)$ depends on $\tau = R_{on}C_{load}$



163

C_{load} depends on fan-in and fan-out

  
- Fan-out: number of load gates connected to output of driving gate
 - All wiring and total input capacitance determine C_{load}
- Fan-in: number of inputs to gate



164

  


Contamination delay or min-delay

 


Electronic glitch

 - Undesired **transition** that occurs before the signal settles to intended value
- Glitches can go from rail to rail
- Caused by logic (can be prevented)



RC model for dynamic behavior*

 - First-order RC model
- Step function $V_{SS} \rightarrow V_{DD}$



Rise time
(10% to 90%) is
 $t_r \approx 2.2RC$

$$V_{out}(t) = V_{dd}(1 - e^{-t/\tau}) \quad \tau = RC$$

*simple RC model is unable to model electronic glitches

169

Reality is more complicated

- Parasitic capacitances that affect transient behavior of cascaded inverter pair:


 


Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

170


Idea: lump everything into C_{load}

 

171

Lump everything into C_{load}

 
- Use the so-called **Miller effect** for $C_{gd1,2}$
- Linearize all non-linear capacitances



172

Miller capacitance*

 
- Miller effect
 - Capacitor experiencing identical but opposite voltage swings at both its terminals
 - Replace with cap to GND of **twice the C**



*Miller effect depends on gain: $C_M = (1-g) \cdot C_{in}$ (we assume $g = -1$)

173

Lumped load capacitance

 

$$C_{load} = 2C_{gd1} + 2C_{gd2} + C_{db1} + C_{db2} + C_{g3} + C_{g4} + C_w$$

- Only consider capacitances that switch!

174


Will determine maximum clock frequency

Propagation delay

175

First-order analysis

 - Exact computation difficult as $C_L(v)$ and $i(v)$ are non-linear in voltage $v(t)$



176

Computing the average on resistance

- Integrate over time:

$$R_{eq} = \frac{1}{t_2 - t_1} \int_{t_1}^{t_2} R_{on}(t) dt$$

average between
 t_1 and t_2

- Resistance is equal to: $R_{on}(t) = \frac{V_{DS}(t)}{I_{DS}(t)}$
- But we are lazy and approximate it as:


$$R_{eq} \approx \frac{1}{2} (R_{on}(t_1) + R_{on}(t_2))$$

average at
endpoints t_1 and t_2

177

Simple approximation of R_{eq}

 - Discharge of capacitor from V_{DD} to GND
- Propagation delay: 50% discharge = $V_{DD}/2$
- Idea: **average resistance at endpoints**



178

Intuition on R_{eq}

$$R_{eq} \approx \frac{3}{4} \frac{V_{DD}}{I_{DSATn}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

$$I_{DSATn} = \mu_n C_{ox} \frac{W_n}{L_n} \left((V_{DD} - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right)$$

- Increasing width W reduces R_{eq}
- Increasing length L increases R_{eq}
- If $V_{DD} \rightarrow V_{Tn}$ then R_{eq} increases a lot!
- For $V_{DD} \gg V_{Tn} + V_{DSAT}/2$ resistance is almost independent of V_{DD}

179

Use RC circuit to model t_{pHL}/t_{pLH}

- Decay time from 100% to 50% is

$$t_{pHL} = \ln(2) R_{eqn} C_L \approx 0.69 R_{eqn} C_L$$

any ideas why?

- Same can be obtained for low-to-high time


$$t_{pLH} = \ln(2) R_{eqp} C_L \approx 0.69 R_{eqp} C_L$$

- Propagation delay:

$$t_p = \frac{t_{pHL} + t_{pLH}}{2} \approx 0.69 C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right)$$

180

Real inverter transient response

 

From simulation: $t_{pHL} = 39.9ps$ and $t_{pLH} = 31.7ps$ for 0.25 μm process

Image taken from: http://bwrcs.eecs.berkeley.edu/Classes/icdesign/ee141_f01/Notes/chapter5.pdf

181

Propagation delay t_p vs. V_{DD}

 


Image Taken From: http://bwrcs.eecs.berkeley.edu/Classes/icdesign/ee141_f01/Notes/chapter5.pdf

182

Example: Intel's speed step tech.

- Adjust voltage and clock frequency to operation conditions
- Used in virtually all processors nowadays

- Why would someone do that?

 


Image taken from: <http://news.softpedia.com/news/Intel-Geneseo-vs-AMD-Torrenza-36730.shtml>

183

Ways to reduce t_{pHL}

- Increase V_{DD} : trade energy vs. performance
- Assume

$$t_{pHL} \approx 0.52 \frac{C_L}{(W_n/L_n)\mu_n C_{ox} V_{DSATn}}$$

- Reduce C_L : fanout, interconnect, C_{DS}
- Increase W/L ratio: careful with self loading

184

Another way to reduce t_{pHL}

- Carrier mobility μ_n depends on temperature
- Again, assume $V_{DD} \gg V_{Tn} + V_{DSAT}/2$

$$t_{pHL} \approx 0.52 \frac{C_L}{(W_n/L_n)\mu_n C_{ox} V_{DSATn}}$$

- For electrons in Si, we have $\mu_n \propto T^{-2.4}$
- Increasing the temperature reduces carrier mobility*, which increases propagation delay

*due to increased scattering; for holes we have $\mu_p \propto T^{-2.2}$

185

Cooling makes CMOS faster

- Known to gaming enthusiasts who overclock their CPUs → liquid cooling

CPU Frequency World Record ranking on 3 February 2018

nominal clock is 4.3 GHz in turbo mode

RANK	SCORE	USER	PROCESSOR	COOLING
#1	8722.78 MHz	 The Stilt	AMD FX-8370 @ 8722.8MHz	Liquid Nitrogen
#2	8709 mhz	 AndreYang	AMD FX-8150 @ 8709MHz	Liquid Nitrogen
#3	8659.64 mhz	 Smoke	AMD FX-8370 @ 8659.6MHz	Liquid Nitrogen
#4	8615.39 mhz	 slammms	AMD FX-8350 @ 8615.4MHz	Liquid Nitrogen
#5	8543.71 mhz	 wytiwx	Intel Celeron D 352 @ 8543.7MHz	Liquid Nitrogen

http://hwbot.org/benchmark/cpu_frequency/halloffame

186

We can make gates faster

Minimizing the propagation delay

187

PMOS/NMOS ratio


- One approach: Size PMOS and NMOS so that R_{eq} 's match (ratio of about 2-to-3)
 - leads to symmetric VTC
 - optimizes noise margins
 - leads to equal t_{pHL} and t_{pLH}
- How about minimizing t_p ?

188

Minimizing t_p

- Widening PMOS
 - reduces R_{eqp} , which reduces t_{pLH}
 - also increases parasitic C_L , which increases t_{pHL}
- There is an **optimal** PMOS width!
 
$$C_L = (C_{dp1} + C_{dn1}) + C_W + (C_{gp2} + C_{gn2})$$



189

Minimizing t_p (cont'd)

$$C_L = (C_{dp1} + C_{dn1}) + C_W + (C_{gp2} + C_{gn2})$$

- Assume PMOS β times larger than NMOS

$$C_{dp1} \approx \beta C_{dn1} \quad C_{gp2} \approx \beta C_{gn2} \quad \beta = \frac{(W/L)_p}{(W/L)_n}$$

- Propagation delay becomes

$$t_p \approx \frac{0.69}{2} \left((1 + \beta)(C_{dn1} + C_{gn2}) + C_W \right) \left(R_{eqn} + \frac{R_{eqp}}{\beta} \right)$$

190

After some math...

- Optimal value of β is

$$\beta_{opt} = \sqrt{\frac{R_{eqp}}{R_{eqn}} \left(1 + \frac{C_W}{C_{dn1} + C_{gn2}} \right)}$$


ratio r of symmetric VTC-sized resistors

- if C_W small, then you can ignore this
- If C_W large, then larger PMOS needed

- Interesting: **smaller PMOS reduces t_p** (at the cost of VTC symmetry and noise margin)

191

Example

 

minimum propagation delay t_p

symmetric t_{pHL} , t_{pLH} , and VTC

Image taken from: http://bwrcs.eecs.berkeley.edu/Classes/icdesign/ee141_f01/Notes/chapter5.pdf

192