

ECE4740: Digital VLSI Design

Lecture 7: Power consumption


224

Practice helps a lot

Sizing examples

225

Your turn: compute the p-delay

 


$$t_{p,i} = t_{p0} \left(1 + \frac{C_{ext,i+1}}{\gamma C_{g,i}} \right) \quad \gamma = 1 \quad t_{p0} = 3ps$$

226

Solution

$$t_{p1} = t_{p0} \left(1 + \frac{2C_g}{C_g} \right) = t_{p0}3$$
 
$$t_{p3} = t_{p0} \left(1 + \frac{100fF}{5C_g} \right) = t_{p0}21$$



$$t_{p2} = t_{p0} \left(1 + \frac{C_g + 5C_g + 10fF}{2C_g} \right) = t_{p0}9$$

$$\gamma = 1$$

$$t_{p0} = 3ps$$

$$t_p = t_{p0}(3 + 9 + 21) = t_{p0}33 = 99ps$$


227

Very important

Energy and power consumption

228

Trends in power consumption

 

229

Main sources of power consumption

- **Dynamic power consumption** dominating in most applications
 - Charging and discharging capacitors
 - Short circuit currents (short between supply rails during switching)
- **Static power consumption** increasing with shrinking transistors!
 - Leakage (leaking diodes and transistors) already a concern for ultra low-power applications (e.g., watches, hearing aid devices, sensors)


230

Still dominating in most designs

Dynamic power consumption

231

Energy consumption 1→0

 

$$E = V \cdot I \cdot t$$


- Energy stored in capacitor:

$$E_C = \int_0^\infty i_{VDD}(t) v_{out} dt = \int_0^\infty C_L \frac{dv_{out}}{dt} v_{out} dt = \int_0^\infty C_L v_{out} dv_{out} = \frac{1}{2} C_L V_{DD}^2$$

- Energy taken by supply: $E_{VDD} = C_L V_{DD}^2$

232

Charging and discharging

 

- Energy stored in C_L : $E_C = \frac{1}{2} C_L V_{DD}^2$
- Energy taken from supply: $E_{VDD} = C_L V_{DD}^2$
- Only half* of the energy stored in C_L !

*other half is "wasted" in PMOS transistor (resistance)


233

Charging and discharging (cont'd)

- Each switching cycle $L \rightarrow H \rightarrow L$ takes a fixed amount of energy: $E_{cyc} = C_L V_{DD}^2$
- Energy dissipation is independent of
 - (size of NMOS/PMOS) but depends on load
 - discharging circuitry (except the capacitance)
 - time of switching cycle
- Reducing energy: Reduce C_L and V_{DD}

234

Example: compute energy* (0-1-0)

 

- Miller effect $2C_g$, E_4 and E_6 remain same

$$E = V_{DD}^2 (2C_g + 2C_g + 8C_g + C_W + 32C_g + C_L)$$

*Remember: this is the energy of a 0-1-0 switching cycle

235

Dynamic power consumption

- Power = energy / time
- Power consumption: $P_{dyn} = C_L V_{DD}^2 f_{0 \rightarrow 1 \rightarrow 0}$
- Gate switched on and off $f_{0 \rightarrow 1 \rightarrow 0}$ times per second (switching frequency)
- Example: 0.25 μ m design with 1M gates
 - $V_{DD}=2.5V$, 500MHz, $C_L=15fF/gate$ (fan-out 4)
 - 46.875 μ W per gate \rightarrow 46.875W (!!!)

236

Dynamic power consumption

$$P_{total} = V_{DD}^2 f_{clk} \sum_k \frac{\alpha_k}{2} C_k$$


clock frequency f_{clk}

node/gate index k

switching activity (per clock cycle) α_k

load capacitance for node k C_k

 - Switching activity: α_k # of switches per cycle



237

How to reduce dynamic power?

$$P_{total} = V_{DD}^2 f_{clk} \sum_k^K \frac{\alpha_k}{2} C_k$$

reduce supply voltage (points to V_{DD}^2)
 reduce clock frequency (points to f_{clk})
 reduce number of gates (points to \sum_k^K)
 reduce node activities (points to α_k)
 reduce fan out (points to C_k)
 reduce wire loads (points to C_k)

238


Example revisited

- 0.25 μ m CMOS design with 1M gates
 - $V_{DD}=2.5V$,
 - 500MHz with 0-1-0 per cycle
 - $C_L=15fF/gate$ (fan-out 4)
 - Average activity 10%
- 4.6875 μ W per gate \rightarrow 4.6875W
- Reduce V_{DD} to 1.8V \rightarrow 2.43W

239

Compute dynamic power consumption
 
$$P_{total} = V_{DD}^2 f_{clk} \sum_k^K \frac{\alpha_k}{2} C_k$$




- Circuit switches once per clock cycle at every node (only for this simple example):

$$V_{DD} = 2V \quad f_{clk} = 1\text{GHz}$$

240

Solution
 
$$E = V_{DD}^2 (2C_g + 4C_g + 10\text{fF} + 2C_g + 10C_g + 100\text{fF})$$




- Circuit switches **once per clock** cycle: $\alpha_k = 1$

$$P_{total} = 2^2 \cdot 1\text{GHz} \cdot \frac{1}{2} \cdot 128\text{fF} = 256\mu\text{W}$$

241

Oh wait, sizing?!

 

- Sizing can reduce propagation delay
- But this is **not free in terms of power!**

$$C_{tot} = 2(C_g + fC_g + f^2C_g + \dots + f^N C_g)$$

- **Not easy to size inverters for min. power**

Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

242


Another source of dynamic power consumption

Crossover/direct-path currents

243

Crossover or direct-path currents

 - Finite slope of input signal causes direct path between V_{DD} and GND for short time




244

Direct path/crossover energy

- Energy consumed per switching 0-1-0:
 
$$E_{dp} = V_{DD} \frac{I_{peak} t_{sc}}{2} + V_{DD} \frac{I_{peak} t_{sc}}{2} = V_{DD} I_{peak} t_{sc}$$



245

Direct path/crossover power

- Average power consumption:

$$P_{dp} = V_{DD} I_{peak} t_{sc} f$$

- Peak current is determined by
 - saturation current:
 - depends on transistor size
 - technology
 - temperature
 - ratio between input and output slopes (C_L)

246

Reduce direct-path currents

$$P_{dp} = V_{DD} I_{peak} t_{sc} f$$

$$t_{sc} \approx \frac{(V_{DD} - 2V_T)}{V_{DD}} \frac{t_r}{0.8}$$


 rise or fall time

- Reduce W/L
- Reduce V_{DD}
- Make circuit switch fast: reduce t_r and t_f

247

Approximation for 0-1-0 cycle


$$E_{dp} \approx \frac{\beta}{12} (V_{DD} - 2V_T)^2 t_r$$

- Under a lot of assumptions $\beta = \mu \epsilon_{ox} / t_{ox} * W/L$
 - symmetry of β_n and β_p , and threshold voltages
 - no output load... $C_L = 0$
 - Input and output voltage rise linearly with ramp time t_{ra}
- Energy increases in V_{DD} squared!


From the book H. J. M. Veendrick, Deep-Submicron CMOS ICs, from *Basics to ASICs*. Kluwer Academic Publishers, Deventer, 2000

248

Impact of input/output slopes

 

 - Large load C_L
 - Output fall time larger than input rise time
 - Transistors off before output changed



- Small load C_L
 - Output fall time smaller than input rise time
 - Both transistors conducting for long time

249

I_{peak} as function of C_L

 


Image adapted from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

250