

ECE4740: Digital VLSI Design

Lecture 14: Pass transistors and
transmission gates

500

Ratio'ed logic

Other CMOS logic styles


501

Why do we even care?

- Advantages of static CMOS
 - Low static power
 - Robust
 - Supported by most synthesis & back-end tools
- “Disadvantages” of static CMOS
 - For N inputs, requires (at least) $2N$ transistors
 - PUN can be area consuming
 - Same function is computed twice

502

Ratio'ed logic

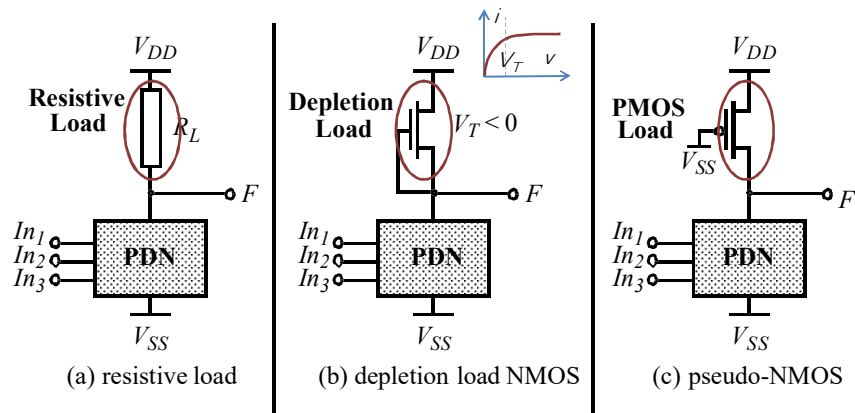


- Goal: Reduce # of transistors over CMOS
- **Ratio'ed = functionality depends on ratios!**

503

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris


Ratio'ed logic with resistive load

 

- N transistors + load R_L
- $V_{OH} = V_{DD}$ remember 2015 practice prelim 1?
- $V_{OL} = R_{PDN} / (R_{PDN} + R_L)$ ✓
- Asymmetric VTC
- Reduced noise margin
- Static power consumption
- $t_{pLH} = 0.69 R_L C_L$ remember 2015 practice prelim 1?
- What is t_{pHL} ? ✓

504

Pseudo-NMOS w/ active load

 

- $V_{OH} = V_{DD}$
- For V_{OL} assume NMOS lin. & PMOS sat.

$$V_{OL} \approx \frac{\mu_p W_p}{\mu_n W_n} V_{DSATp}$$

to make V_{OL} small
make PMOS small

505

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

VTC of pseudo-NMOS

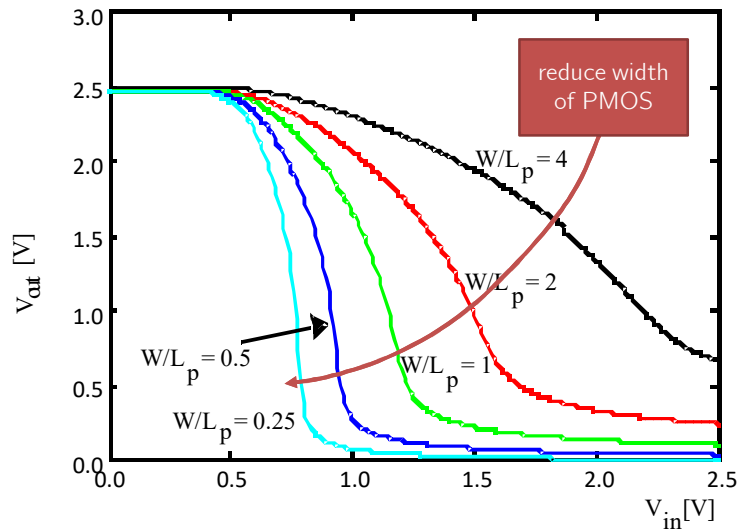


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

506

Disadvantage: Static power

- Static power consumption when output is low (direct current through PMOS)
- Assume PMOS is in saturation:

$$P_{low} = V_{DD} I_{low} \approx V_{DD} \left| k_p \left(-(V_{DD} - V_{Tp}) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right) \right|$$

- One would need better loads!


507

Ratio'ed logic

Other CMOS logic styles

508

Improving loads is critical

 


- Differential cascode voltage switch logic (DCVSL)

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

509

DCVSL details

 


- PDN1 and PDN2 are mutually exclusive
 - If PDN1 conducts PDN2 is off
 - And vice versa

- DCVSL has full rail-to-rail swing
- No static power consumption
- Provides complementary signal
- Gate is still ratio'ed!

510

DCVSL example: XOR/XNOR

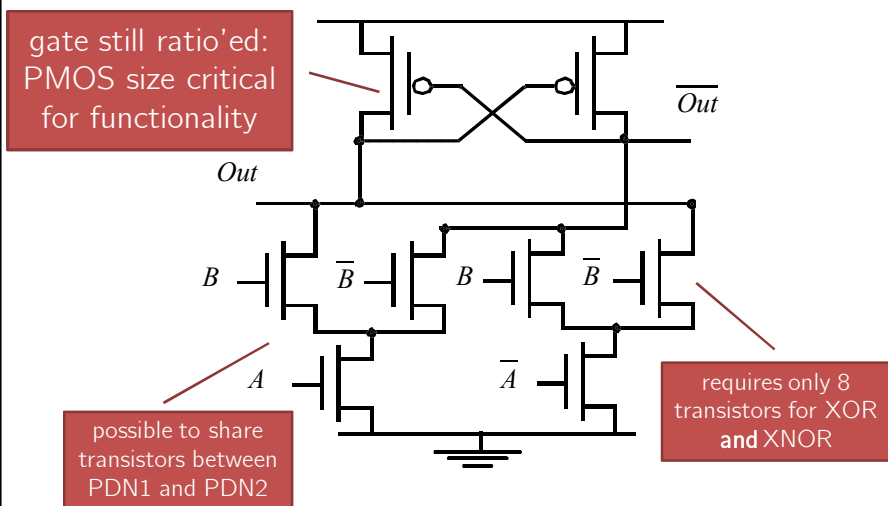

511

Image taken from: CMOS VLSI Design: A Circuits and Systems Perspective by Weste, Harris

Why aren't we always using DCVSL?

- Advantages of differential cascode voltage switch logic (DCVSL) over static CMOS
 - Complementary outputs immediately available
 - May reduce # of transistors up to 2x
 - Keeps values (similar to latches)
- Disadvantages
 - Doubles number of wires (affects density)
 - Often higher dynamic power dissipation
 - Design tools mostly handle only static CMOS

512


Useful for certain logic gates

Pass-transistor logic

513

Full adder in static CMOS

C_{in}	A	B	Σ	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

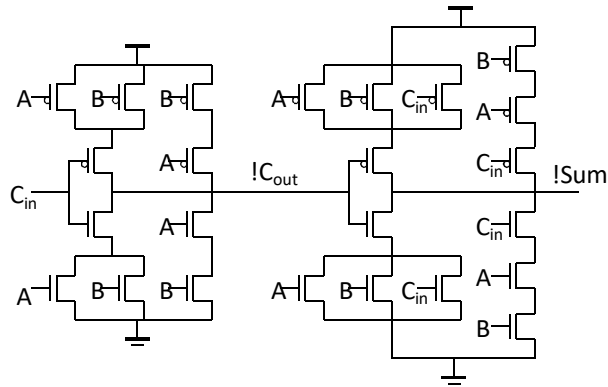


- Requires 24+4 (for C and Sum inv.) transistors

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

514

Is there a better way?

 - XOR/XNOR gates usually require a large number of transistors in static CMOS logic
- Remember: **pass transistors**
 - NMOS switch closes if gate input is high




- **But, NMOS pass strong 0 but weak 1**

515

Pass transistor (PT) logic


- What is this circuit doing?

 

- Find truth table
- Is it static (is there always a low impedance path to both rails)?
- How many transistors would you need with static CMOS?

516

AND gate with pass transistors

 

A	B	F=A*B
0	0	0
0	1	0
1	0	0
1	1	1

- Requires 4 logic gates (needs an inverter)
- CMOS logic would require 6 logic gates
- The gate can be static
- No rail-to-rail swing

517


Properties of PT logic

- Gate can be static (if designed properly)
- **N transistors instead of 2N**
- Usually no static power consumption
- **Ratioless**
- Gate has no signal directivity, i.e., is bidirectional (versus unidirectional)
- Non-inverting logic

518

Complementary PT logic (CPL)

 
- Also called differential PT logic (DPL)



- Similar to DCVSL
 - Input complementary inputs
 - Output complementary outputs

519


CPL/DPL efficient for XOR etc.

 

- Pros
 - No need for extra inverters (theoretically)
 - Static and modular (same topology)
 - Simple XOR (good for adders)

520


Disadvantages of CPL/DPL

 

- Cons
 - Additional routing overhead (2x)
 - Static power dissipation problems
 - Bidirectional

521



CPL/DPL-based full adder

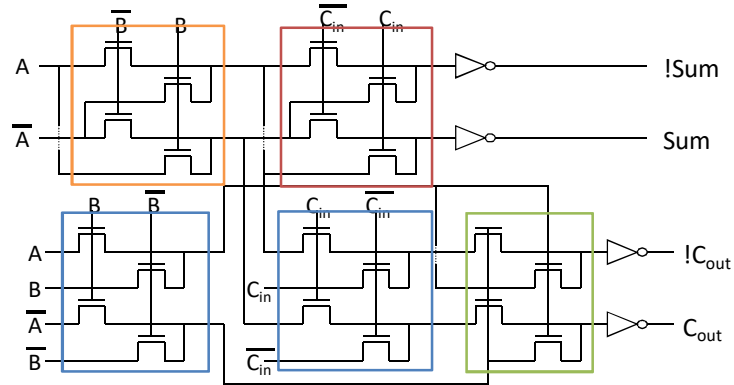

- $20 + 4 * 2 = 28$ transistors (=static CMOS)
- Why are we using inverters at the output?



522

Cascading pass transistors

  

523

VTC of PT AND gate

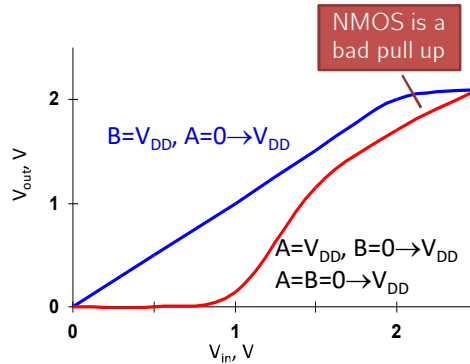 


- Pure PT logic is not regenerative
 - Signal gradually degenerates after passing through a number of PTs (use inverters to fix)


524

Buffered pass transistor logic

- Buffer needed to recover weak 1

 

 node x can only charge up to $V_{dd} - V_{Tn}$




- Body effect makes it even worse

525

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Body effect revisited

 


- Large V_{SB} when pulling high (B is tied to GND and S charged close to V_{DD})
- Voltage drop at node **x** is even worse

$$V_x = V_{DD} - \left(V_{Tn0} + \gamma \left(\sqrt{|2\phi_f| + V_x} - \sqrt{2\phi_f} \right) \right)$$

526


V_T drop causes static power

 

- Pass transistor suffers from body effect
- M_2 may be weakly conducting forming a path from V_{DD} to GND

527


Solution 1: level restorer

 

- Full swing on node $x \rightarrow$ no static power
- No static backwards current (restorer only high when A is high)
- For correct operation M_r must be sized properly \rightarrow results in ratio'ed logic!

528


Solution 1: level restorer (cont'd)

 

- Ratio'ed logic:
 - When node x going from 1 to 0, M_n must be stronger than pull up M_r
 - Otherwise x never goes below V_M of inverter
- Need to size M_n and M_r

529

Sizing the level restorer

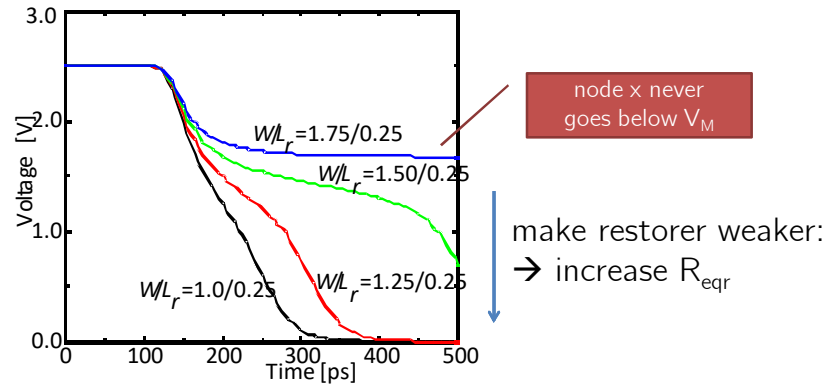

- Restorer also affects speed and power
 - Increases capacitance at node x

530


Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Proper way of using pass transistors

Transmission gates

531


Transmission gate

 

- Full swing bidirectional switch controlled by the gate signal C
- NMOS good pull-down; PMOS good pull-up
- Enables rail-to-rail swing



532

Resistance of transmission gate

 


- TG has only mild non-linearity

533

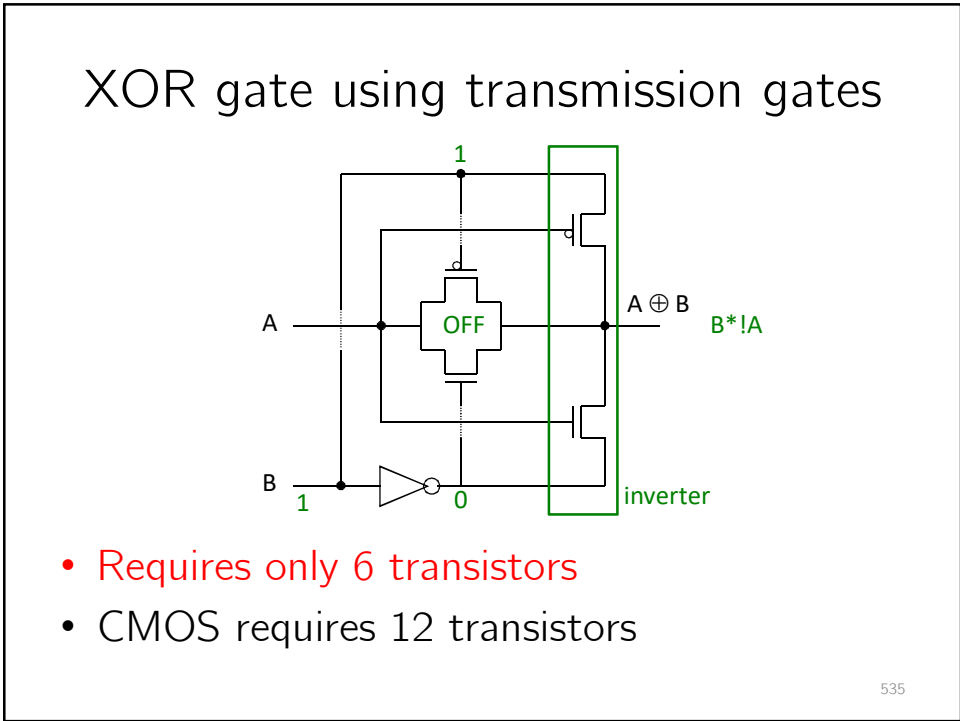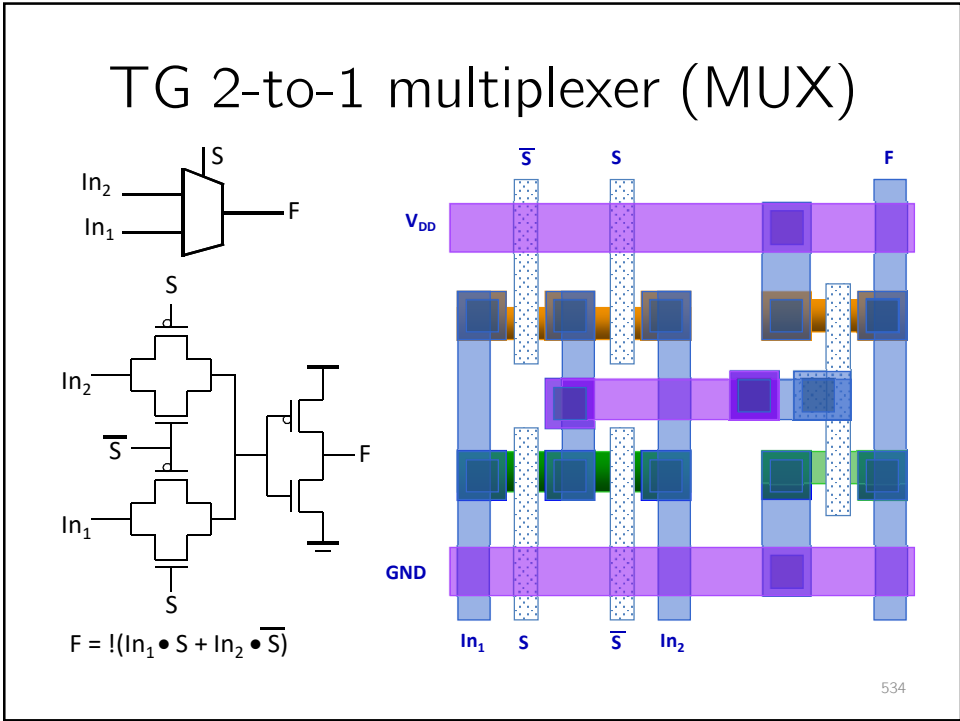


XOR gate using transmission gates

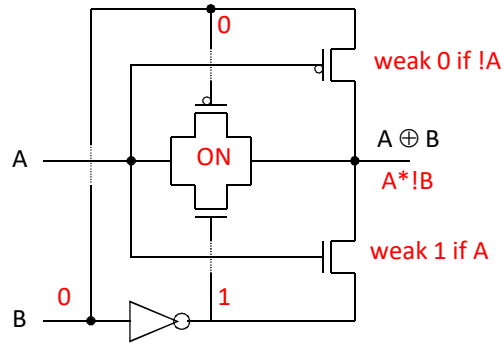

- Requires only 6 transistors
- Transmission gate ensures no voltage drop!

536

TG-based full adder

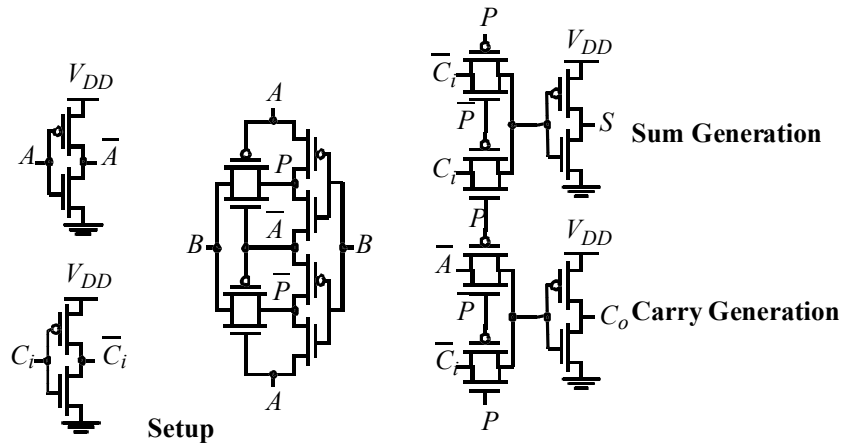


- Similar delays for sum and carry

537

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic


TG-based full adder (cont'd)

 

- 16 transistors (opposed to 28 for CMOS)
- Full rail-to-rail swing


538

(Differential TG logic)

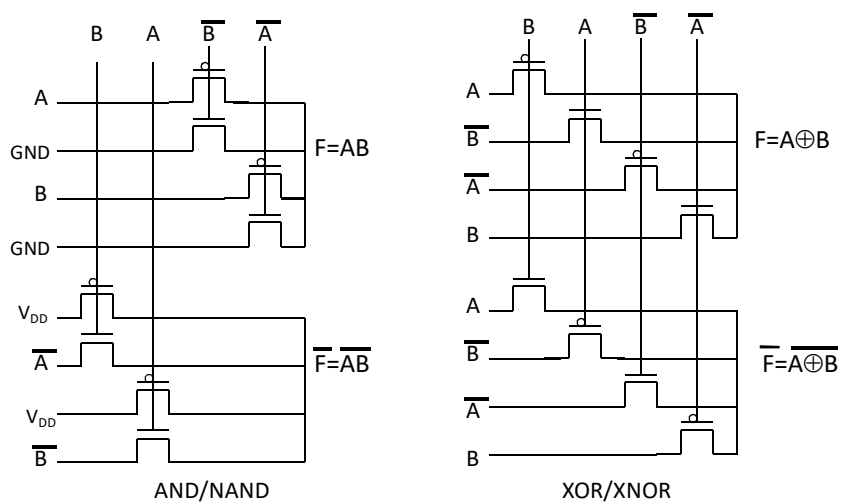

539

Caveat: delay in TG networks

 

- Elmore delay of RC chain:

quadratic delay increase in number of TGs


$$t_p = 0.69 \sum_{k=0}^n CR_{eq}k = 0.69CR_{eq} \frac{n(n+1)}{2}$$

540

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic

Delay optimization

- Insert buffers into TG network

 

$$t_p = 0.69CR_{eq} \frac{n(m+1)}{2} + \left(\frac{n}{m} - 1\right) t_{inv}$$

- Optimum number of buffers:

rule of thumb: no more than 2-3 TGs in series

$$m_{opt} = 1.7 \sqrt{\frac{t_{inv}}{CR_{eq}}} \approx 3.4$$

541

Image taken from: Digital Integrated Circuits (2nd Edition) by Rabaey, Chandrakasan, Nikolic