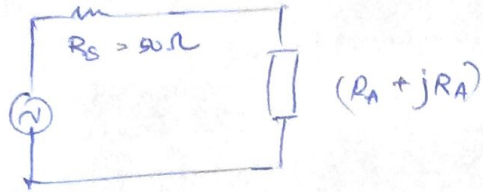


#1.



Out of 50 mW, 25 mW enters  $\Rightarrow \frac{P_T}{P_S} = \frac{1}{2}$

$$\frac{P_T}{P_S} = \frac{4R_S R_A}{|\tilde{Z}_S + \tilde{Z}_A|^2} \Rightarrow \frac{1}{2} = \frac{4 \times 50 \times R_A}{|50 + R_A + jR_A|^2}$$

$$\Rightarrow 400 R_A = (50 + R_A)^2 + R_A^2$$

$$\text{(OR)} \quad 2R_A^2 + 100R_A + 2500 = 400R_A$$


$$\Rightarrow R_A^2 - 150R_A + 1250 = 0$$

$$R_A = 75 + 25\sqrt{7} = 141.44$$


$$\text{or} \\ 75 - 25\sqrt{7} = 8.856$$

$\therefore$  Antenna load impedance is  $8.856 \pm j8.856 \Omega$   
(OR)

$$141.44 \pm j141.44 \Omega$$

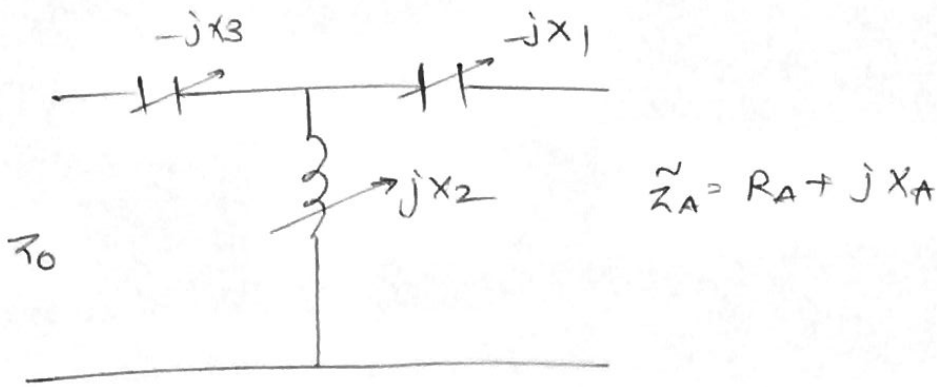

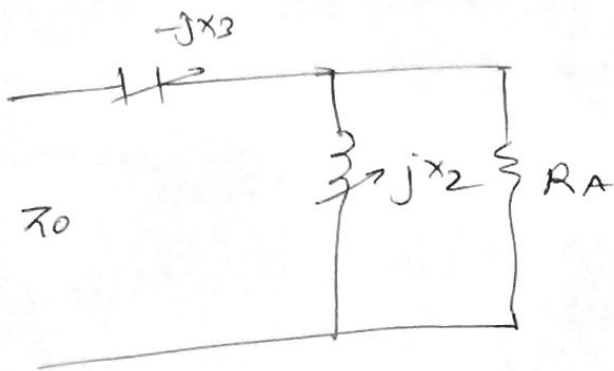choosing  $X_1 = X_A$ , the circuit simplifies as



$$Z_{in} = Z_0$$

$$Z_L = -jX_3 + (jX_2 \parallel R_A)$$

$Z_L = Z_0^*$  since  $Z_0$  is real  
imaginary part of  $Z_L = 0$

$$Z_L = -jX_3 + \frac{R_A jX_2}{R_A + jX_2} = -jX_3 + \frac{R_A X_2 j(R_A - jX_2)}{R_A^2 + X_2^2}$$

$$= \frac{R_A X_2^2}{R_A^2 + X_2^2} + j \left( \frac{R_A^2 X_2 - X_3}{R_A^2 + X_2^2} \right)$$

$$X_3 = \frac{R_A^2 X_2}{R_A^2 + X_2^2} \quad \text{and} \quad \frac{R_A X_2^2}{R_A^2 + X_2^2} = Z_0$$

$$X_3 = \sqrt{Z_0(R_A - Z_0)} \quad \downarrow \quad X_2 = \sqrt{\frac{Z_0 R_A^2}{R_A - Z_0}}$$