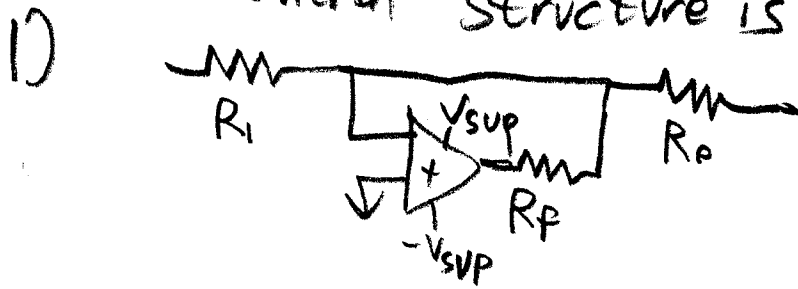


# ECE4803 HW #3 Solns

General structure is



Asides:

$$\#2: R_o = 49.9k \parallel 390k = 44.24k$$

$$\#4: R_o = 75k \parallel 1.5M = 72.34k$$

From lecture, plug in negative supply voltage for  $V_{in} > 0$  case

$$V_{out} = \frac{\frac{V_{in}}{R_i} + \frac{V_{sup}}{R_f}}{\frac{1}{R_i} + \frac{1}{R_f} + \frac{1}{R_o}}$$

for  $\frac{V_{in}}{R_i} + \frac{V_{sup}}{R_f} > 0$

$$V_{in} > -V_{sup} \frac{R_i}{R_f}$$

slope is  $\frac{\frac{1}{R_i}}{\frac{1}{R_i} + \frac{1}{R_f} + \frac{1}{R_o}}$

Defines dead band

#1: edge =  $(14V) \frac{10k\Omega}{150k\Omega} = 0.9333V$

slope =  $\frac{1}{\frac{1}{10} + \frac{1}{150} + \frac{1}{100}} = 0.8571$

#2: edge =  $(14V) \frac{49.9}{150} = 4.6573V$

slope =  $\frac{1}{\frac{1}{49.9} + \frac{1}{150} + \frac{1}{44.24}} = 0.4037$

#3: edge =  $(14V) \frac{91}{150} = 8.4933V$


slope =  $\frac{1}{\frac{1}{91} + \frac{1}{150} + \frac{1}{18}} = 0.1501$

#4 edge:  $(14V) \frac{30}{150} = 2.8V$


slope:  $\frac{1}{\frac{1}{30} + \frac{1}{150} + \frac{1}{72.34}} = 0.6193$
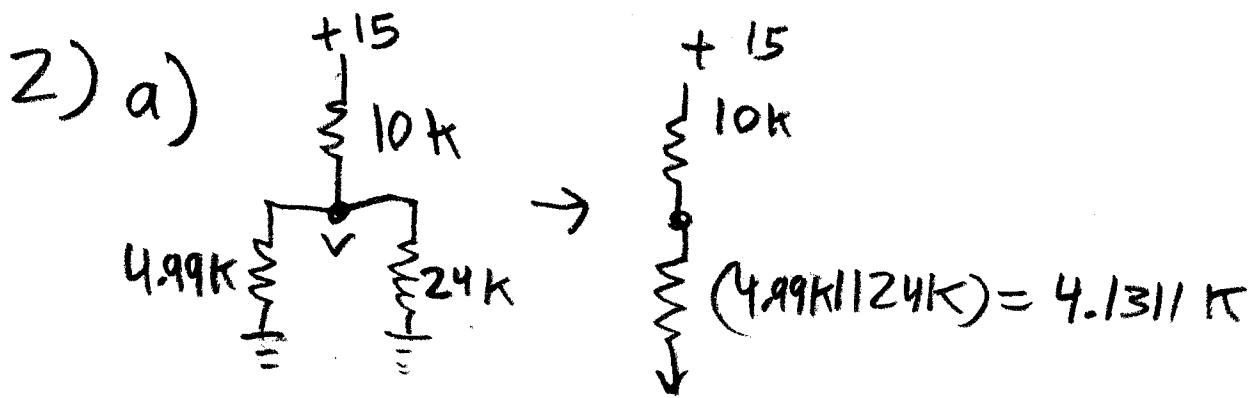
#5 edge:  $(14V) \frac{68}{150} = 6.3467V$

slope:  $\frac{1}{\frac{1}{68} + \frac{1}{150} + \frac{1}{33}} = 0.2846$



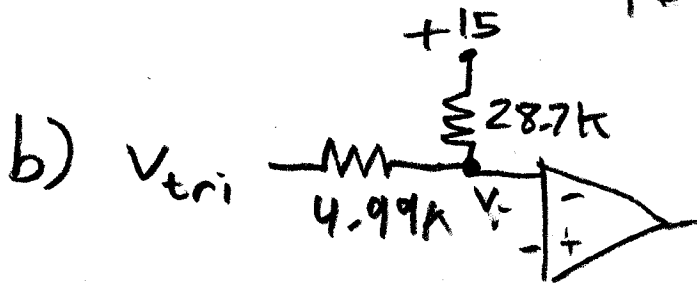voltage divider:  $15V \frac{4.131}{10 + 4.131} \approx \boxed{4.39V}$



$$V_- = \frac{V_{tri}(28.7) + 15 \times 4.99}{28.7 + 4.99}$$

$$33.69V = 28.7V_{tri} + 74.85$$

$$28.7V_{tri} = 33.69V - 74.85$$


$$V_{tri} = 1.1739V - 2.608V$$

For  $V_- = 4.39, V_{tri} = 2.5454V$

$V_+ = 0, V_{tri} = -2.608V$

Aside: For  $V_- = 4.29, V_{tri} = 2.4280V$

3) a) n-channel

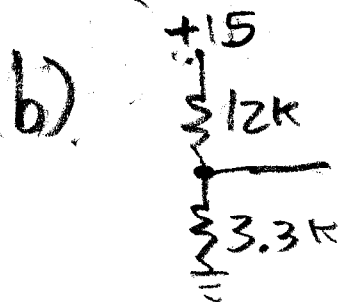

$$(5V) \times \frac{3.3k}{3.3k + 12k} = \boxed{1.078V}$$

c)  $\frac{I_{CON}}{C} T_0 = V_{th}$

$$I_{CON} = V_{th} f_0 C$$

$$= (1V)(4186 \text{ Hz})(10 \text{ nF})$$

$$= 4.186 \times 10^{-5} \text{ A} = \boxed{41.86 \mu\text{A}}$$

d)  $\boxed{0V}$

e)

$$\frac{V_g}{560\Omega} = \frac{6.4 - (V_g + 0.7)}{270\Omega}$$
$$V_g 270 = (6.4 - V_g - 0.7) 560$$
$$V_g (270 + 560) = (6.4 - 0.7) 560$$
$$\boxed{V_g = 3.846V}$$

If we used 5.6 instead of 6.4, we get

$$\boxed{V_g = 3.3V}$$


DC value

$$c) \frac{-2.608 + 2.5454}{2} = \boxed{-0.0313 \text{ V}}$$

$$pk - to\ pk = 2.608 + 2.5454 = 5.1534 \text{ V}$$

$$\frac{0.0313}{5.1534} = \boxed{0.61\%}$$

d)

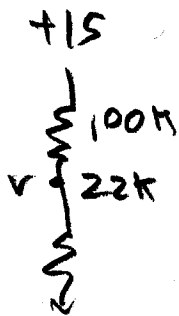

$$v = (15\text{V}) \frac{22\text{k}}{(22+100)\text{k}} = \boxed{2.7 \text{ V}}$$

e)

$$\frac{I_{con}}{C} T_0 = 2 V_{pk-pk}$$

$$\left( \frac{I_{con}}{4.7\text{nF}} \right) \left( \frac{1}{261.63\text{Hz}} \right) = 2 \times 5.1534 \text{ V}$$

$$I_{con} = (2 \times 5.1534 \text{ V}) (4.7\text{nF}) (261.63 \text{ Hz})$$

$$= 1.2674 \times 10^{-5} \text{ A}$$

$$= \boxed{12.674 \mu\text{A}}$$