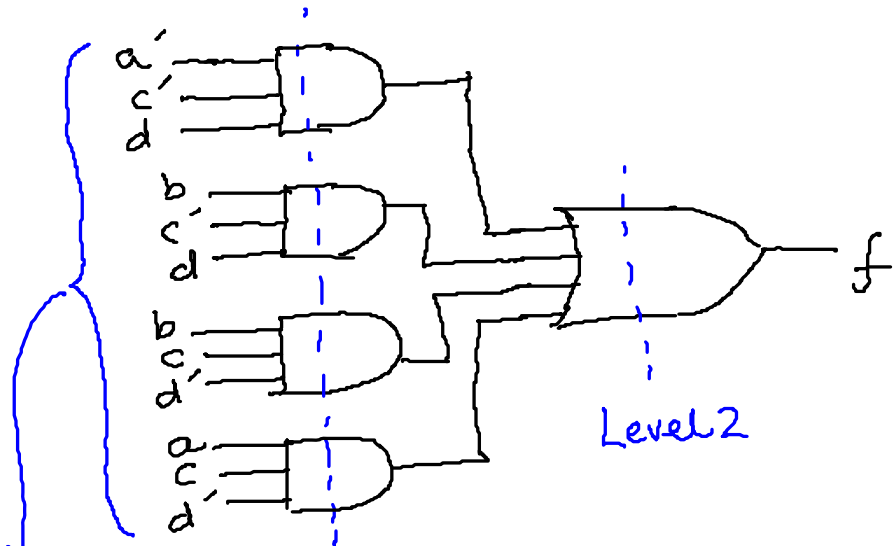


7.1 Multiple-Level Gate Circuits

Levels of gates : Maximum number of gates connected between a circuit input and the output

Two level: sum of products, product of sums
(SOP) (POS)

$$f = a'c'd + bc'd + bcd' + acd'$$



SOP

AND-OR


Two levels

Five gates

16 gate inputs

coming from Level 1
flipflops
where both
Q and Q' is
available

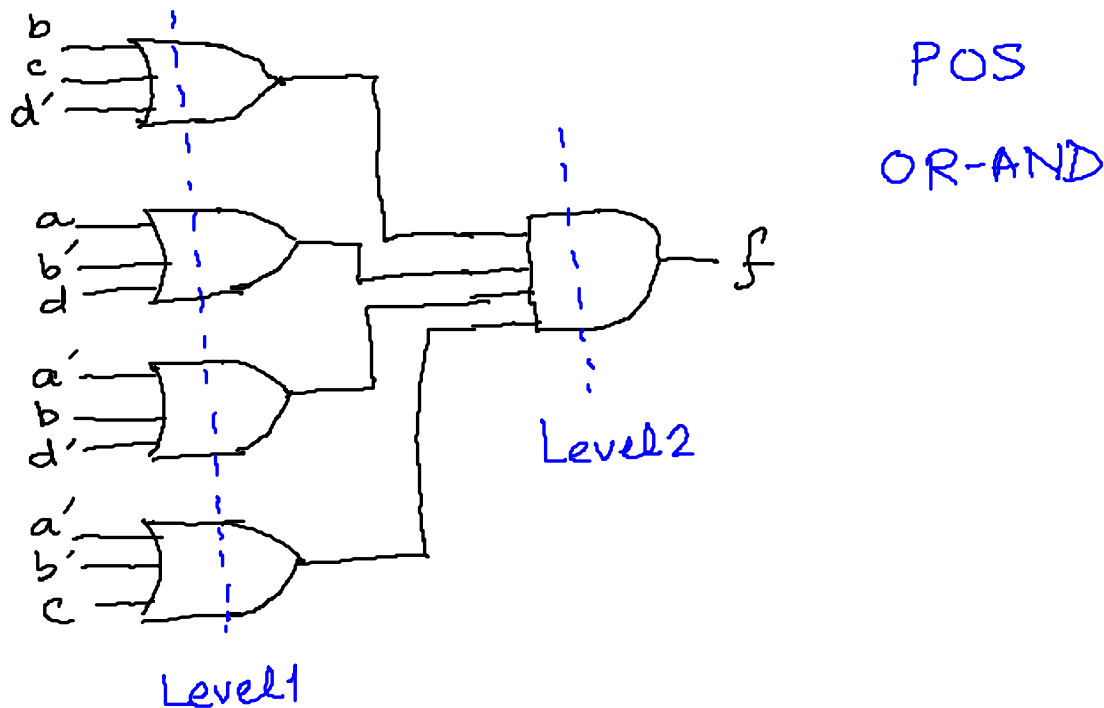
$$f = (b + c + d')(a + b' + d)(a' + b + d')(a' + b' + c)$$



The number of levels in an AND-OR circuit can usually be increased by *factoring* the SOP expression from which it was derived.

$$\begin{aligned}
 f &= a'c'd + bc'd + bcd' + acd' \\
 &\stackrel{\text{factor}}{=} c'd(a' + b) + cd'(a + b)
 \end{aligned}$$


$$c'd(a'+b) + cd'(a+b)$$

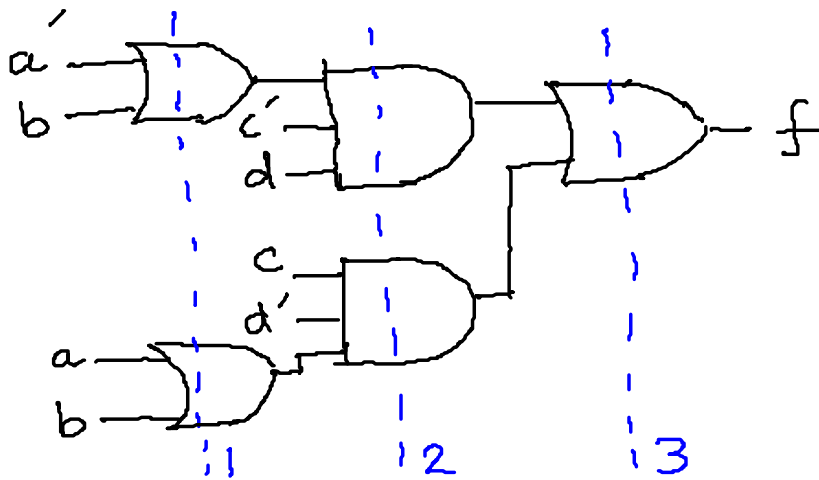

Three levels
 Five gates
 12 gate inputs
 Best three level solution

 Example:

$$f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$$




$$a'c'd + bc'd + bcd' + acd'$$

product of sums

$$f' = c'd' + ab'c + cd + a'b'c$$

$$f = (c+d)(a'+b+c)(c'+d')(a+b+c')$$

 

Two levels

Five gates

14 gate inputs


Best two level
solution

The number of levels in an OR-AND circuit can usually be increased by multiplying out some of the terms in the POS expression from which it was derived

$$f = \underbrace{(c+d)(a'+b+c)}_{(c+d(a'+b))} \underbrace{(c'+d')(a+b+c')}_{(c'+d'(a+b))}$$

using $(x+Y)(x+Z) = x+YZ$

 
$$\begin{aligned} f &= (c+d(a'+b))(c'+d'(a+b)) \\ &= (c+a'd+bd)(c'+ad'+bd') \end{aligned}$$



Three levels
Seven gates
16 gate inputs

 8.3 Gate Delays & Timing Diagrams


When the input to a logic gate is changed, the output will not change instantaneously.



propagation delay
 E_1 1 to 0 change
 E_2 0 to 1 change


typical $E \sim 10^{-9}$ s

Timing Diagrams




 


assume $\epsilon = 20\text{ns}$

held at constant values


 



8.4 Hazards in Combinational Circuits

   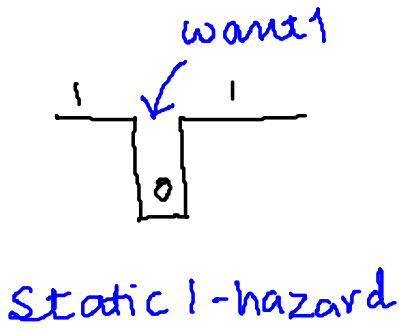

Static-1 Hazard

$$X + X' = 1$$

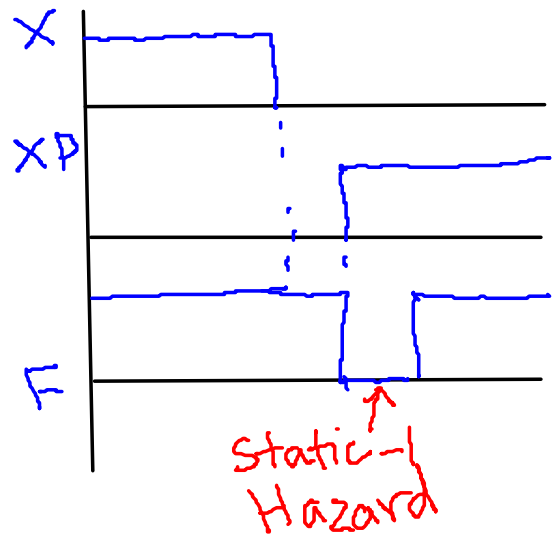
 


 

$$F = AB' + BC$$

Fix $A=1$ & $C=1$


$$F = B + B'$$

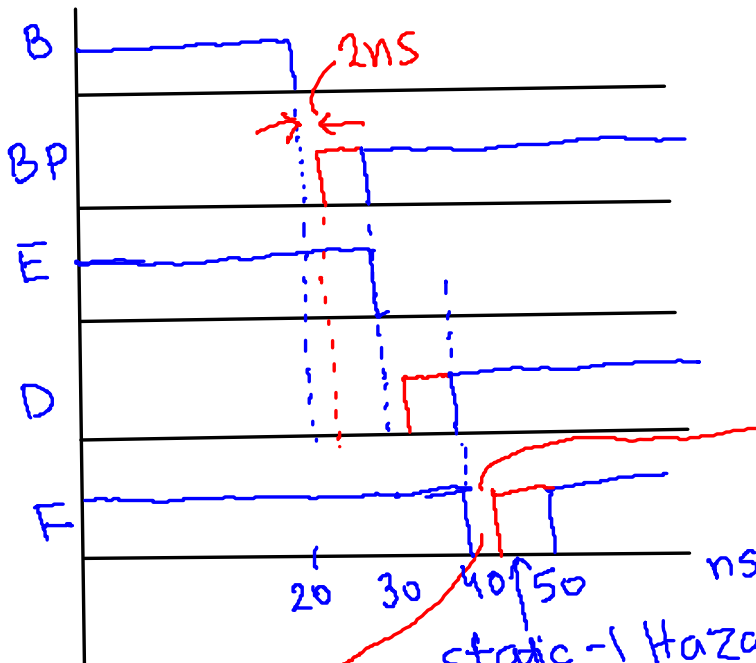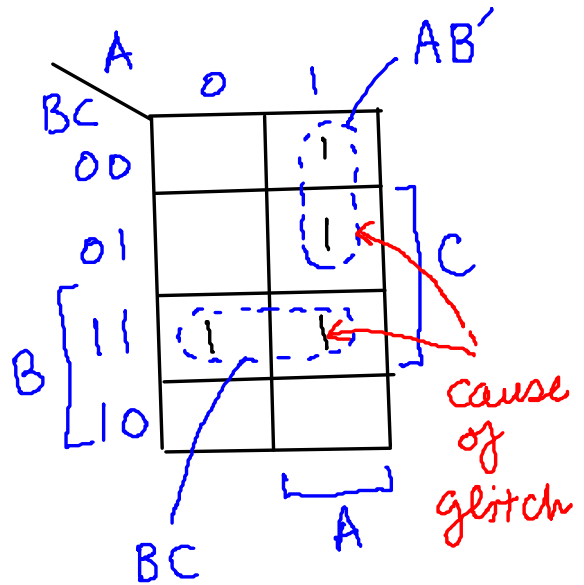


— gate delays 10ns
 — not gate delay 2ms
 others 10ns


this glitch might not show up if inertial delay $\geq 2ns$

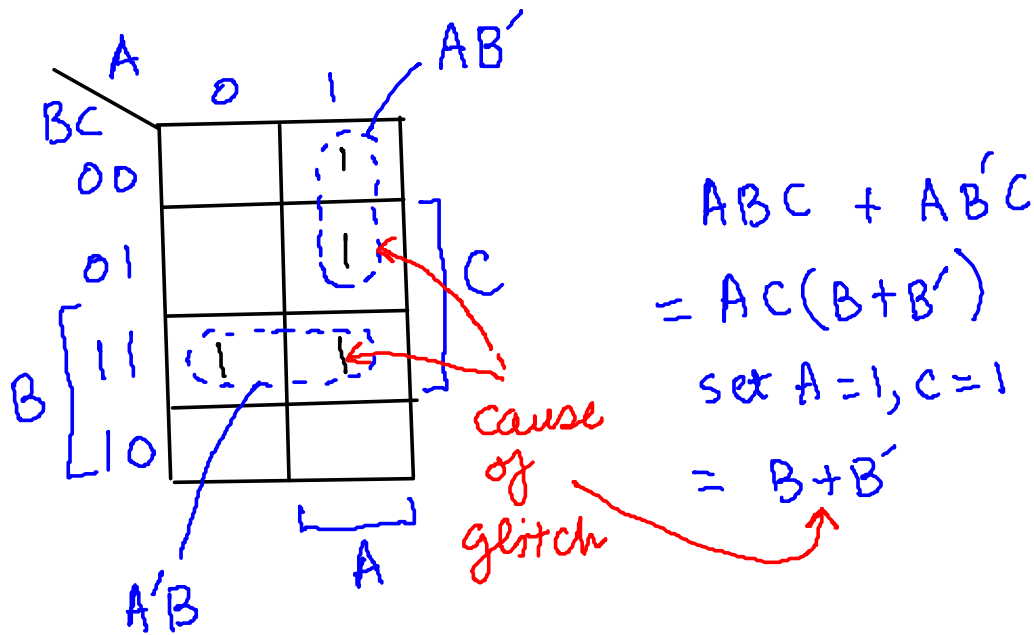if inertial delay = 0 then gate is said to have ideal or transport delay




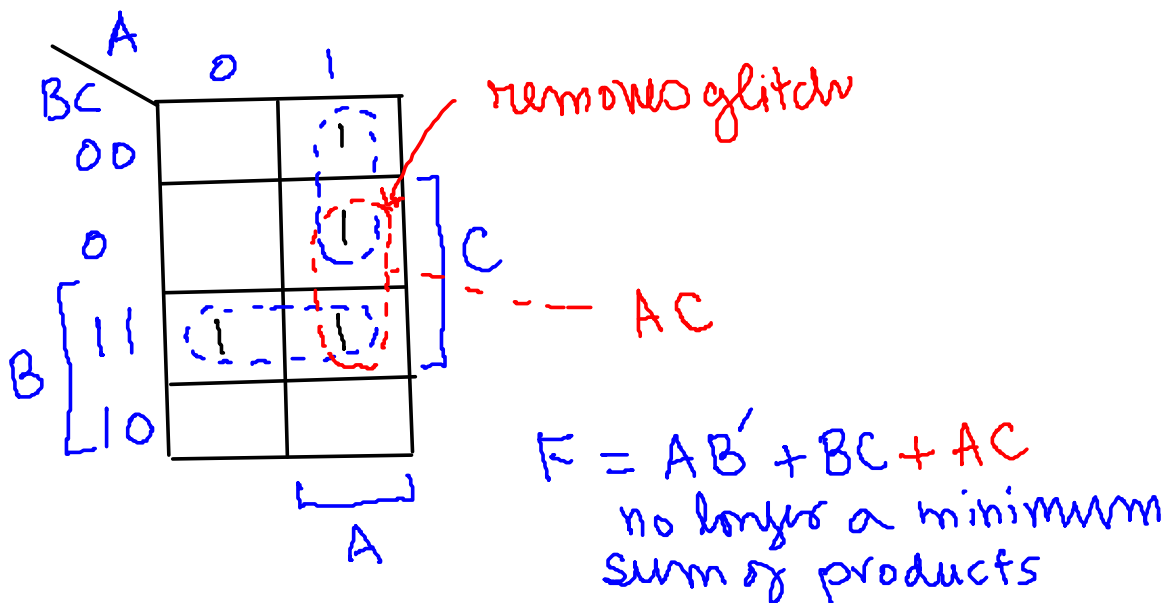
If any two adjacent 1s are not covered by the same rectangle, a 1-hazard exists



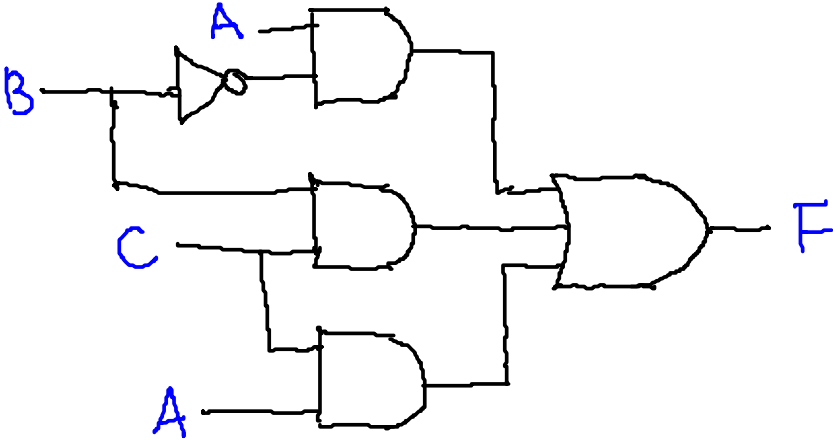



Zero hazards

$$X X' = 0$$

  

↑
0-hazard

$$F = (A + C)(A' + D')(B' + C' + D)$$

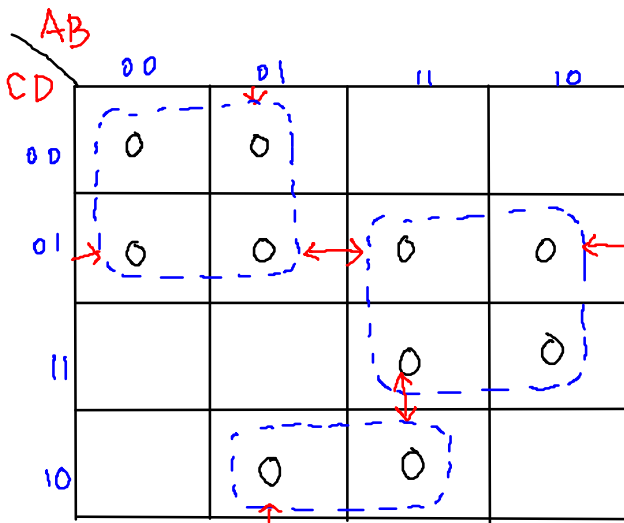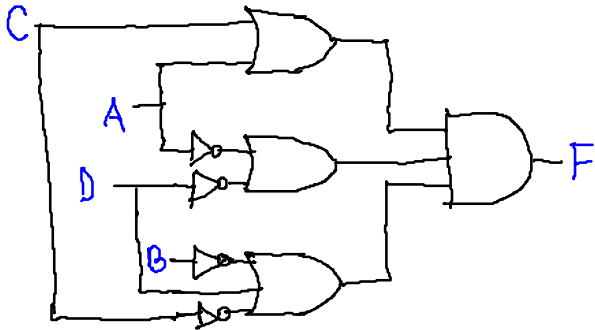


A = 0, B = 1, D = 0 & C changes from 0 to 1

$$F = (A + C)(A' + D')(B' + C' + D) = CC' \leftarrow \text{glitch}$$

See fig. (c) page 226

Eliminate glitch

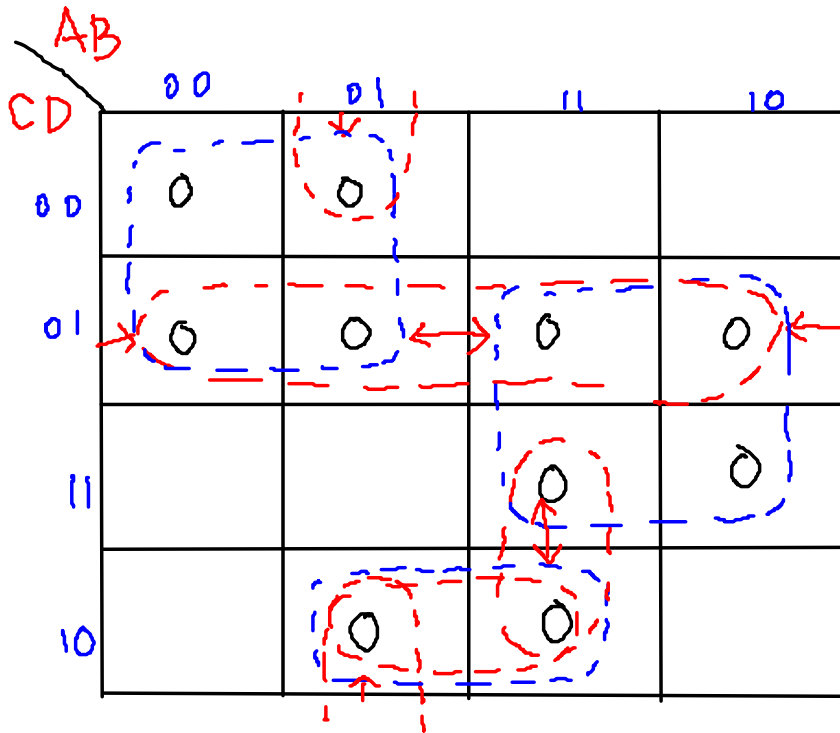

$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$