


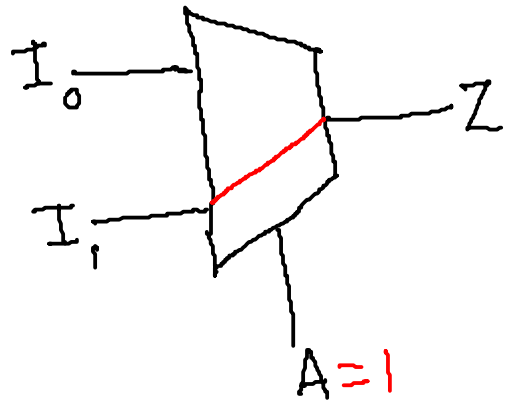
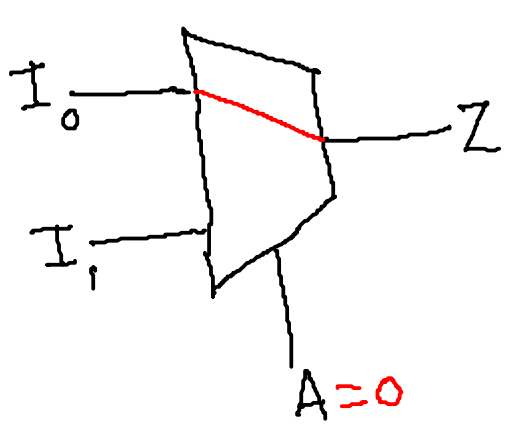
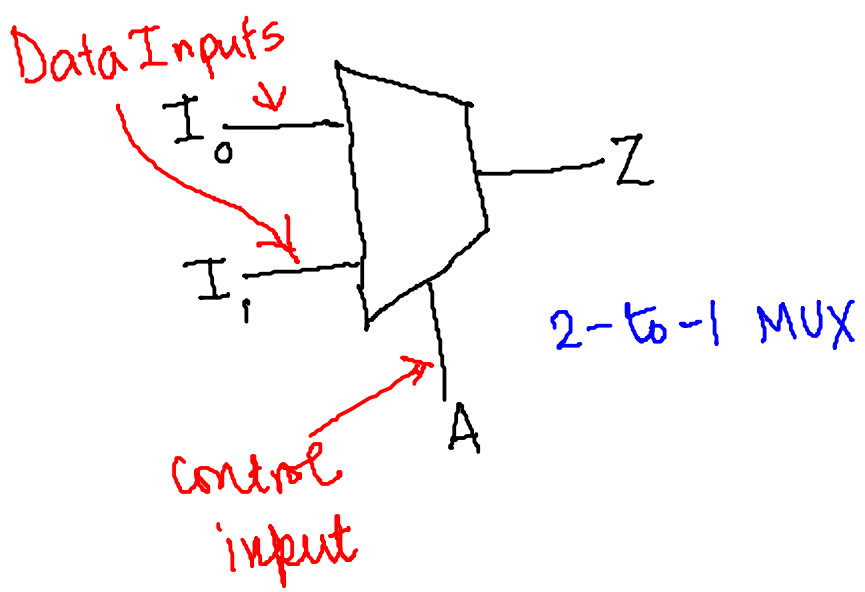


9.2 Multiplexers (MUX)

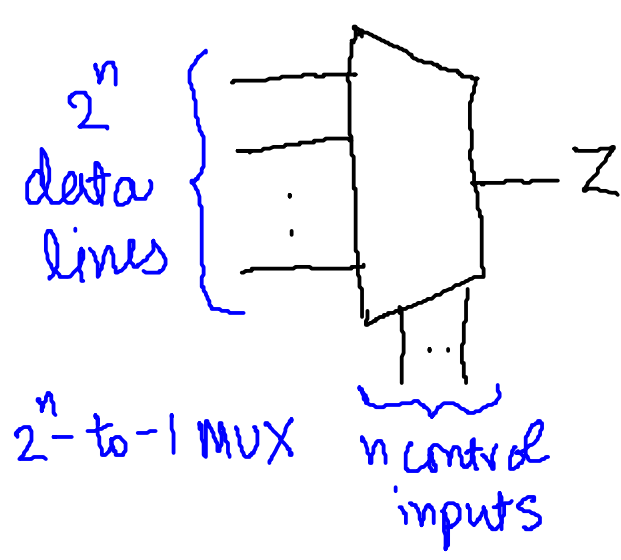

$$Z = A'I_0 + AI_1$$

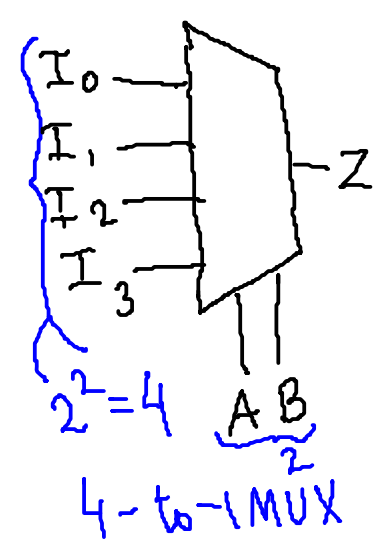




 




$$Z = \underbrace{A'B'}_{m_0} I_0 + \underbrace{A'B}_{m_1} I_1 + \underbrace{AB'}_{m_2} I_2 + \underbrace{AB}_{m_3} I_3$$

minterms
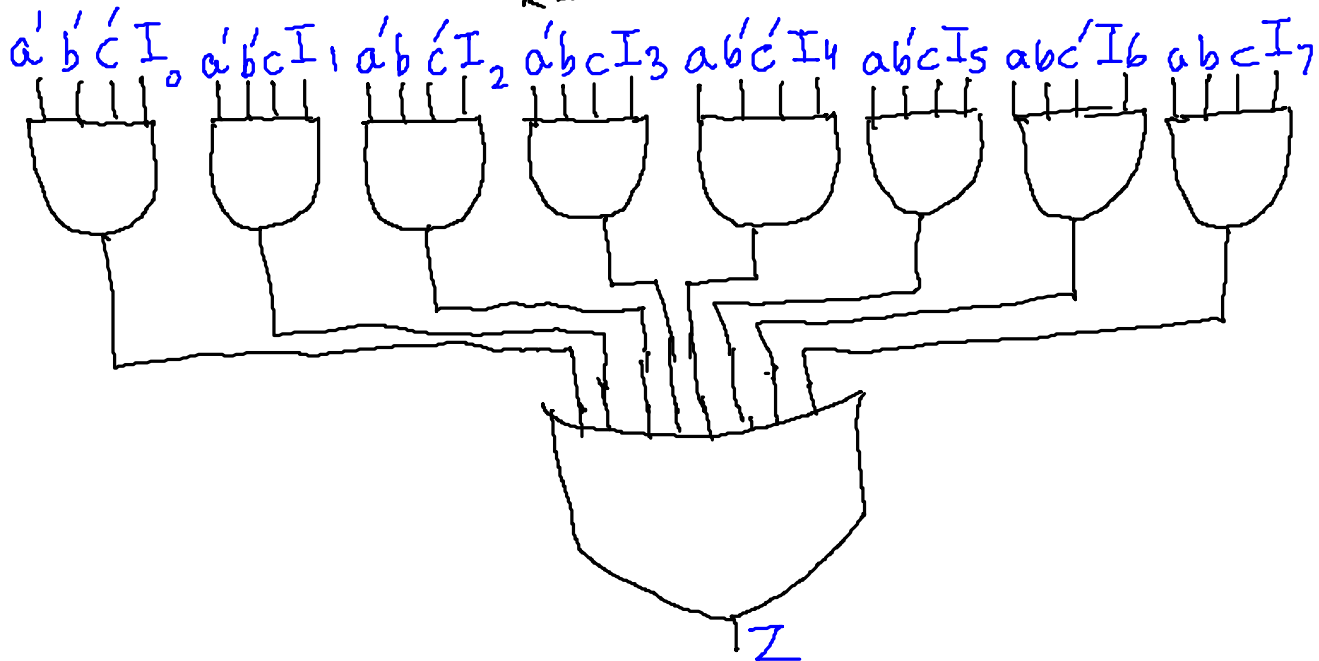
$$Z = \sum_{k=0}^{2^n-1} m_k I_k \quad 2^n\text{-to-1 MUX}$$



  
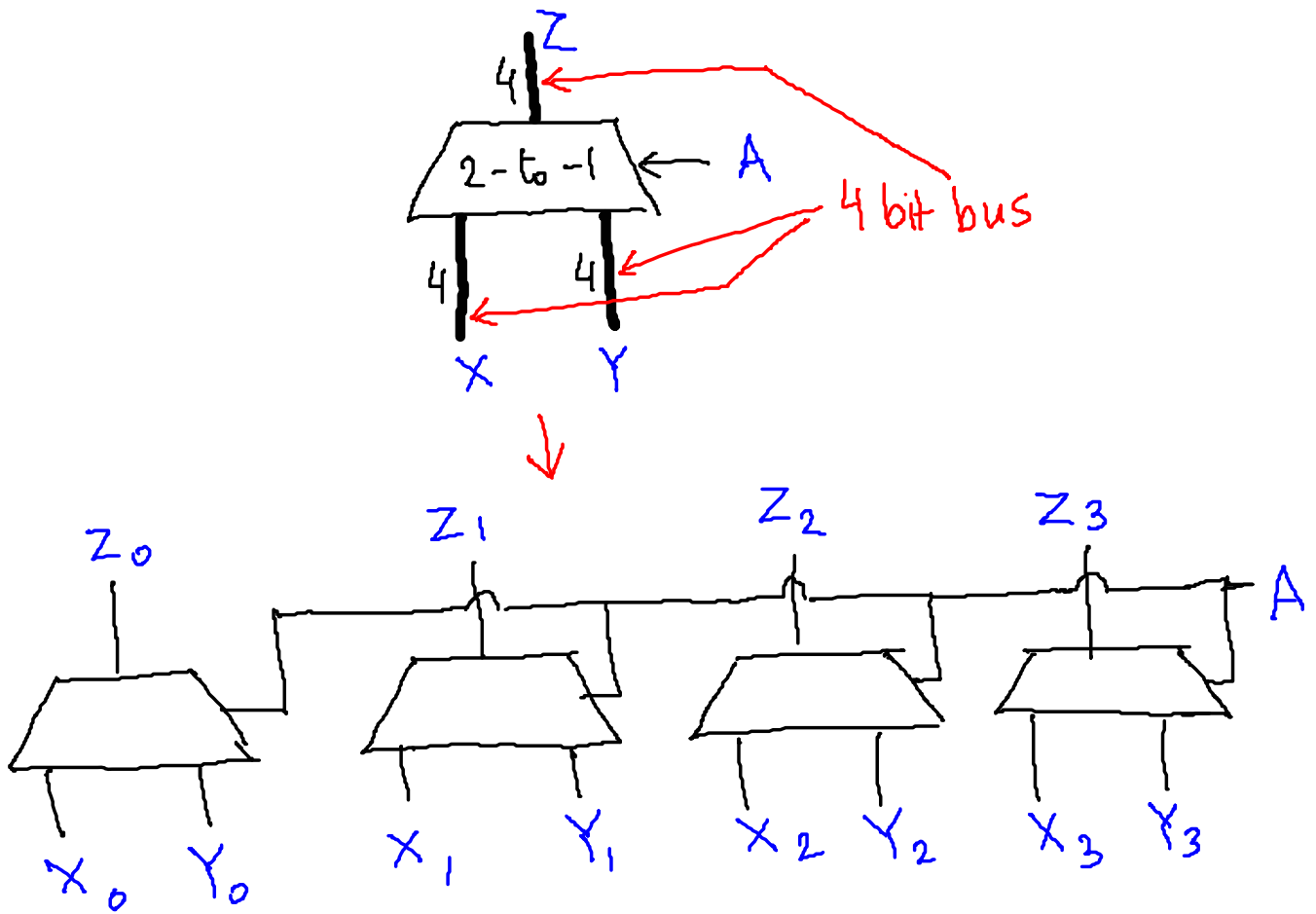


 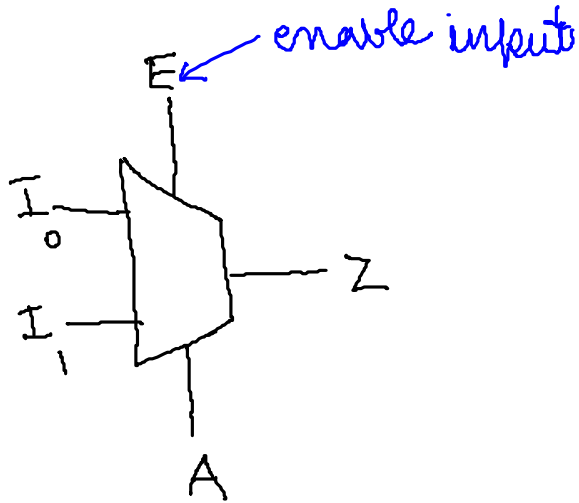


$E = 0$

$Z = 0$ independent of inputs (MUX disabled)

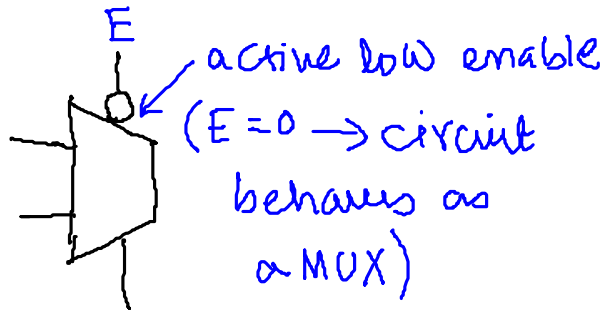 
$E = 1$ MUX behaves normally (MUX enabled)



9.3 Three State Buffers

 


Three state logic

 

$$B = 1 \Rightarrow C = A$$

$$B = 0 \Rightarrow C = \text{hiz infinite } Z$$
 
$$C \rightarrow \begin{cases} 0 \\ 1 \\ Z \end{cases}$$








B	A	C
0	0	Z
0	1	Z
1	0	0
1	1	1

B	A	C
0	0	Z
0	1	Z
1	0	1
1	1	0

B	A	C
0	0	
0	1	
1	0	
1	1	

B	A	C
0	0	1
0	1	0
Z	0	Z
Z	1	Z



Data selection

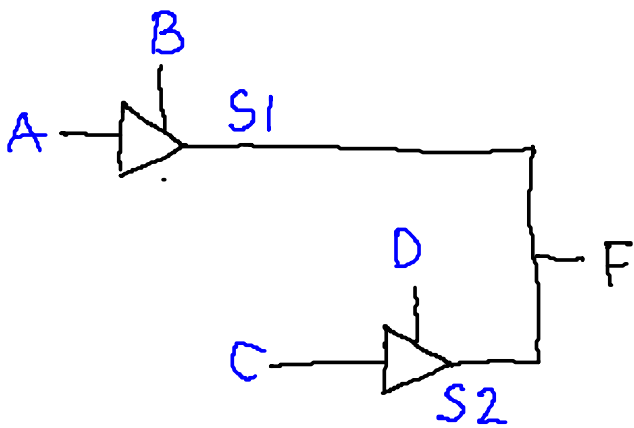    


S1	X	0	1	Z
X	X	X	X	X
0	X	0	X	0
1	X	X	1	1
Z	X	0	1	Z



X (unknown)

 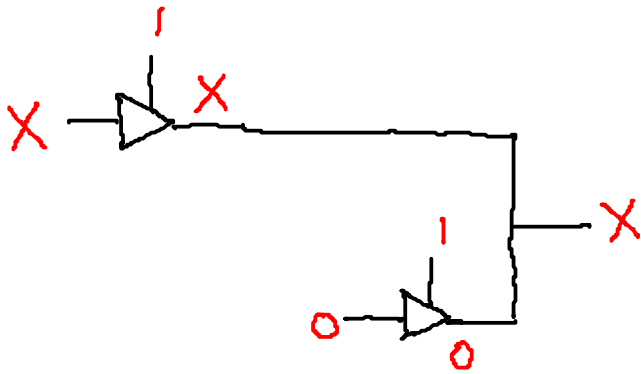

4 Bit adder with 4 sources

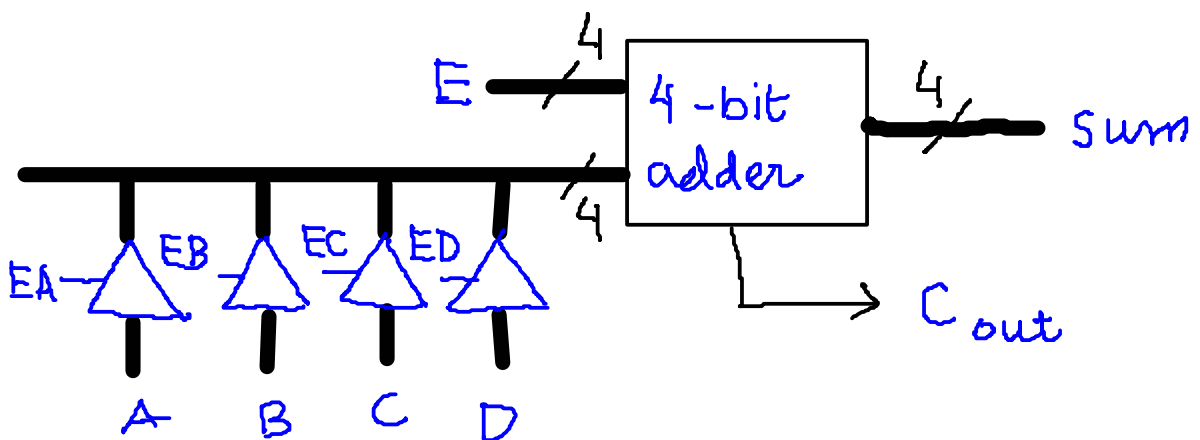

Bidirectional pins

