
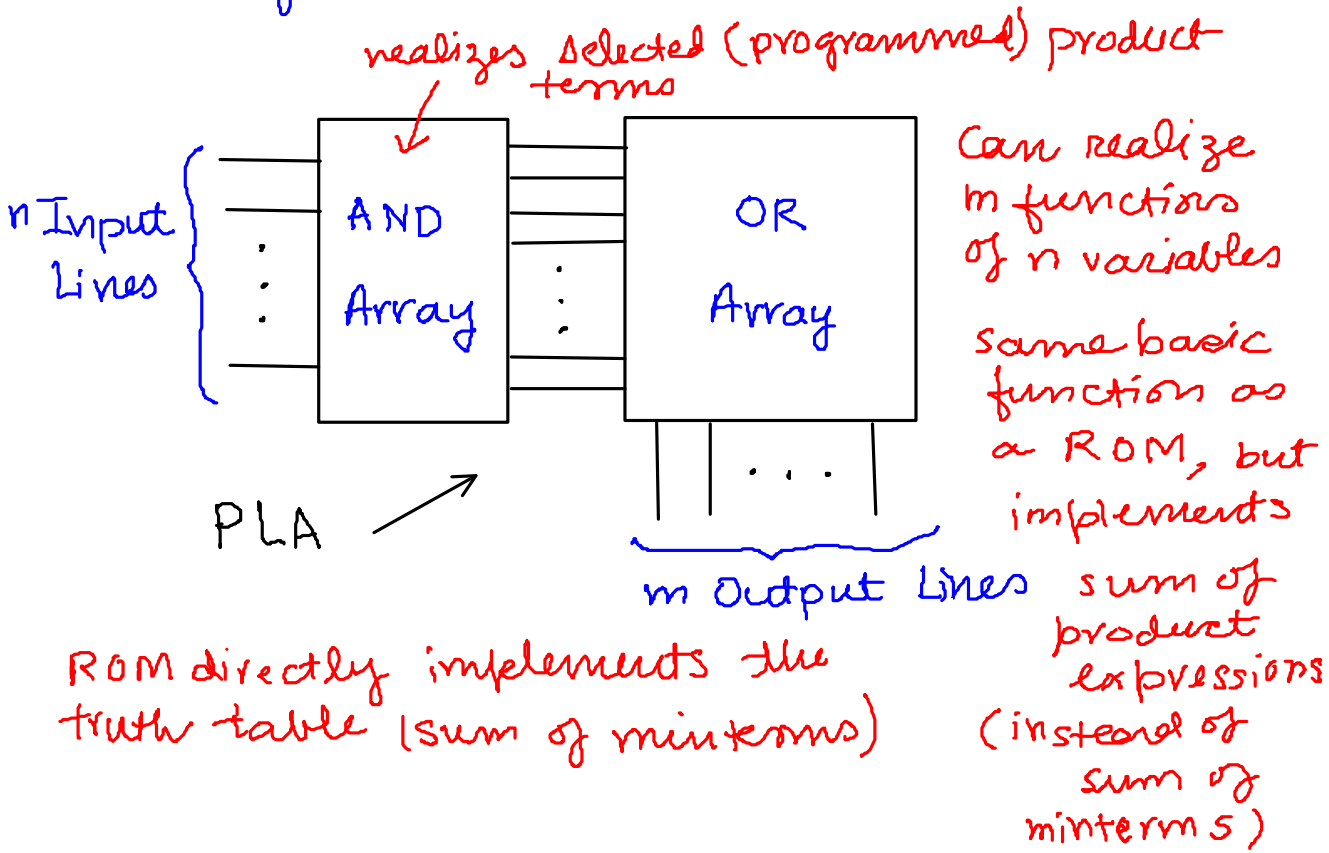


9.6 Programmable Logic Devices (PLD)

PLA (Programmable Logic Arrays)

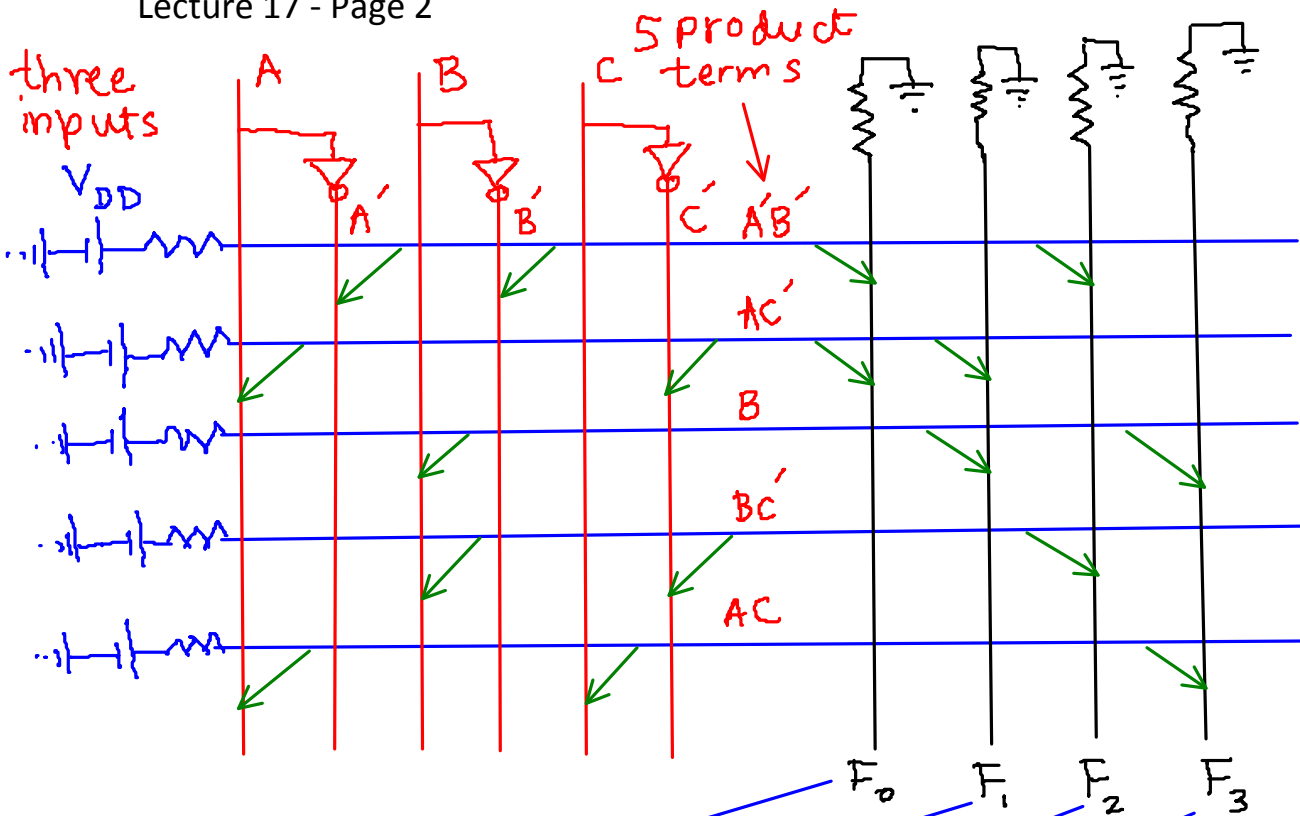



$$F_0 = A'B' + AC'$$

$$F_1 = B + AC'$$

$$F_2 = A'B' + BC'$$

$$F_3 = AC + B$$

4 outputs

PLA TABLE

Variable complemented

Variable not present

Product Term	Inputs A B C	F_0	F_1	F_2	F_3
$A'B'$	0 0 -	1	0	1	0
AC'	1 - 0	1	1	0	0
B	- 1 -	0	1	0	1
BC'	- 1 0	0	0	1	0
AC	1 - 1	0	0	0	1

$$F_0 = A'B' + AC'$$

$$F_1 = AC' + B$$

$$F_2 = A'B' + BC'$$

$$F_3 = B + AC$$

Variable not complemented


Example:

$$f_1 = a'b'd + abd + ab'c' + b'c$$

$$f_2 = c + a'b'd$$

$$f_3 = bc + ab'c' + abd$$


	a	b	c	d	f_1	f_2	f_3
$a'b'd$	0	1	-	1	1	1	0
abd	1	1	-	1	1	0	1
$ab'c'$	1	0	0	-	1	0	1
$b'c$	-	0	1	-	1	0	0
c	-	-	1	-	0	1	0
bc	-	1	1	-	0	0	1

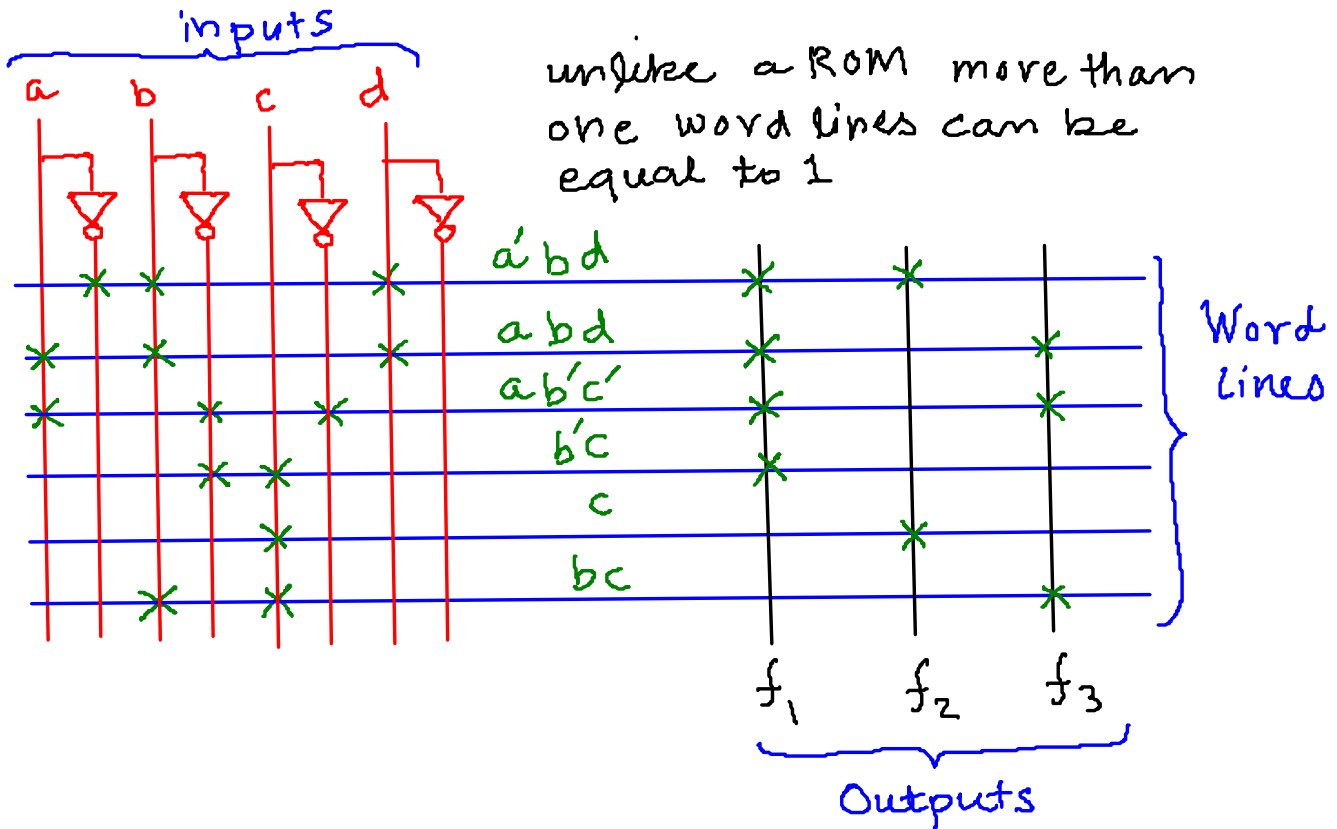


When the number of inputs is small a PROM may be more economical than a PLA.

To realize eight functions of 24 variables would require a PROM of $2^{24} \sim 16$ Million 8 bit words!

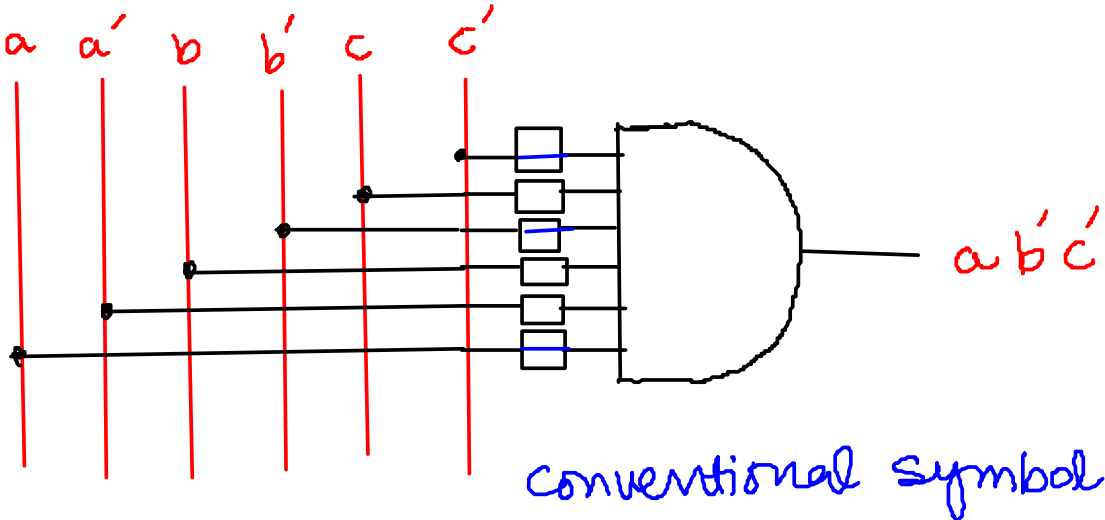The outputs of several PLAs can be ORed together to handle bigger functions




\equiv

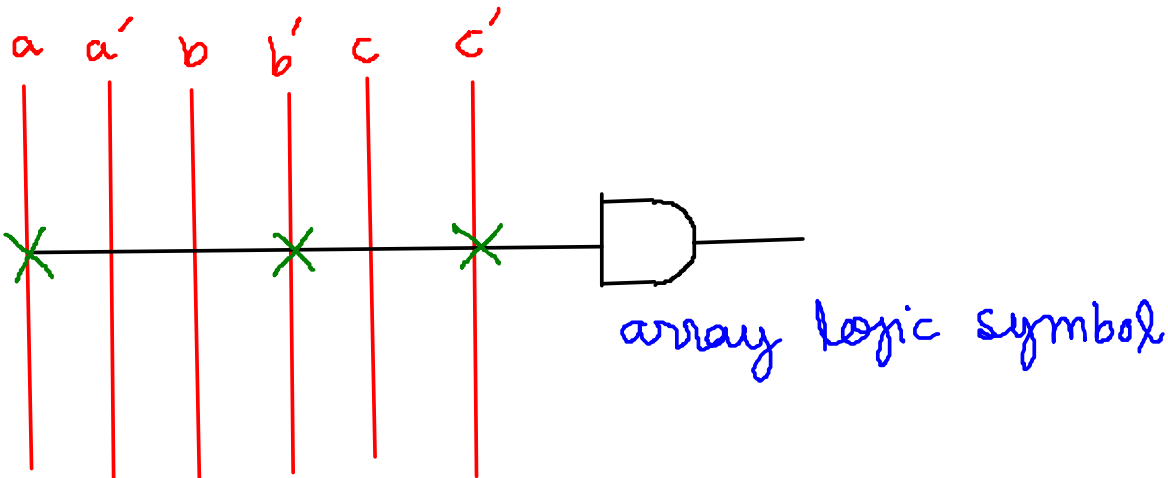

$$\text{Sum} = X'Y'C_{in} + X'YC_{in}' + XY'C_{in}' + XYC_{in}$$

$$C_{out} = XC_{in} + YC_{in} + XY$$

 

Unlike the PLA
the AND terms can
not be shared among
two or more gates.
* # of AND terms per OR gate
are fixed and limited