
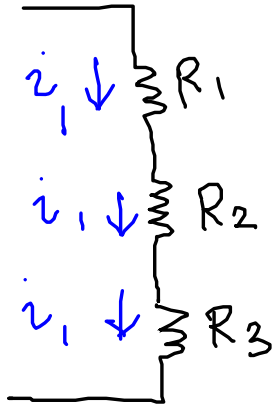


Resistances in series:

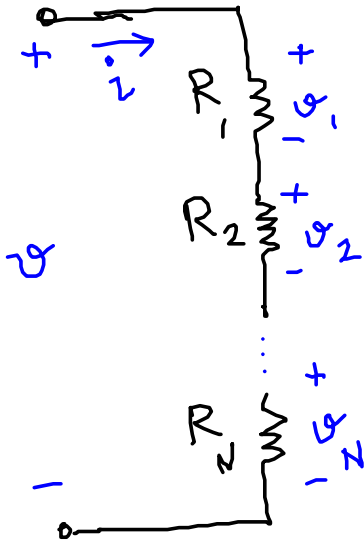

same current  
flows through  
all of the resistances  
in series


# Voltage division



$$v_1 = \frac{R_1}{R_1 + R_2 + \dots + R_N} v$$


$$v_2 = \frac{R_2}{R_1 + R_2 + \dots + R_N} v$$

⋮

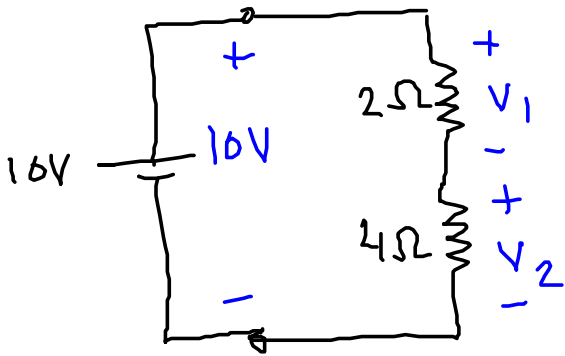


$$v_1 = \frac{2}{2+4} 10V = \frac{20}{6} V$$
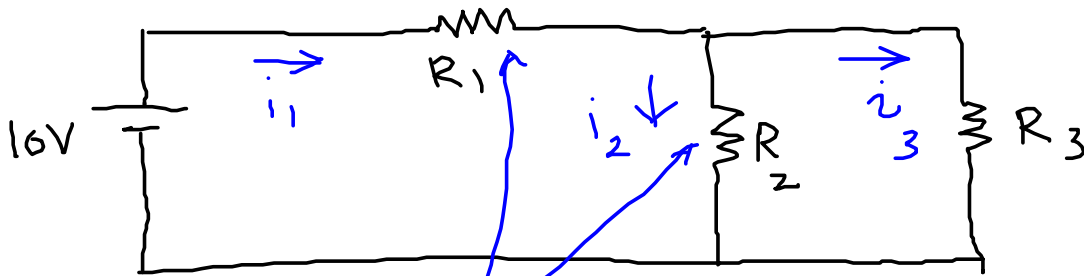
$$v_2 = \frac{4}{2+4} 10V = \frac{40}{6} V$$




$i_1 \neq i_2 \therefore$  not in series - can not use voltage division

# Parallel Resistors

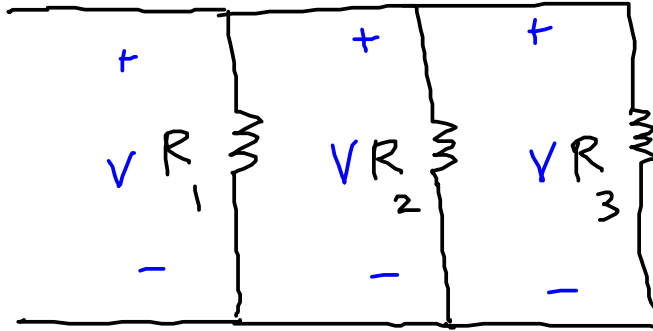


Same voltage across them

## Current Division Rule

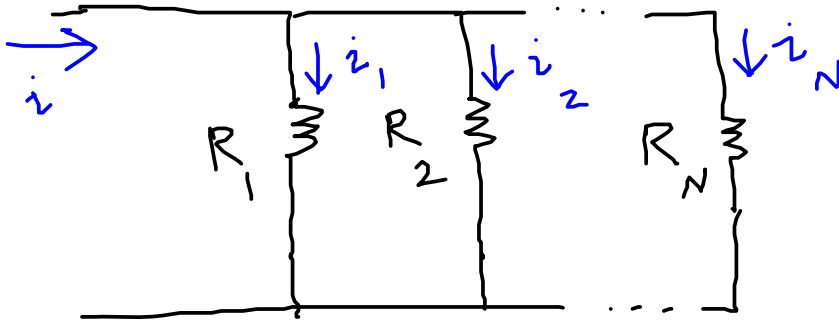


$$i_1 = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} i = \frac{G_1}{G_1 + G_2 + \dots + G_N} i$$
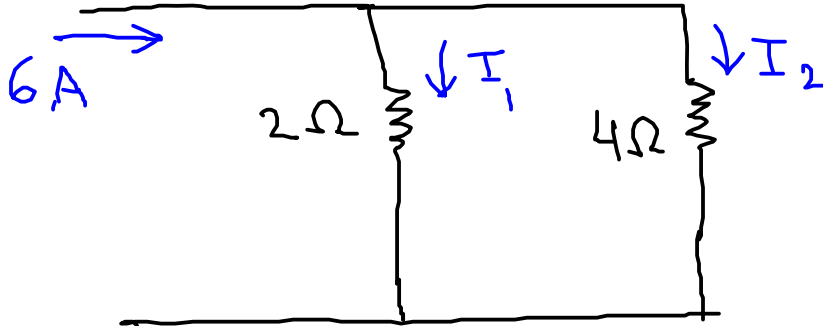
$$i_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}} i = \frac{G_2}{G_1 + G_2 + \dots + G_N} i$$




$$I_1 = \frac{\frac{1}{2}}{\frac{1}{2} + \frac{1}{4}} 6A = 4A$$
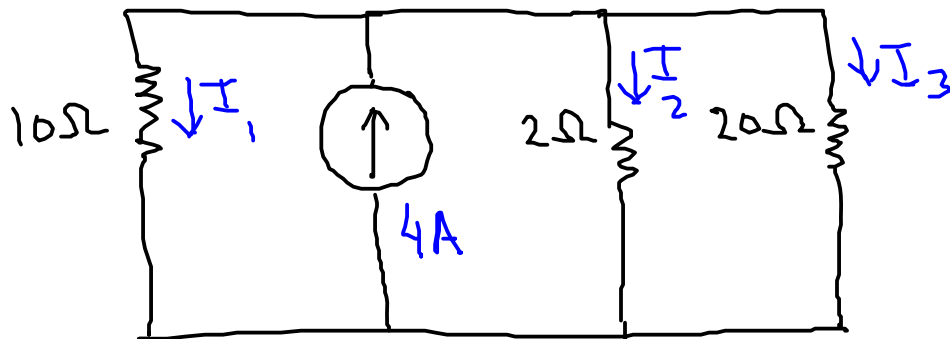
$$I_2 = \frac{\frac{1}{4}}{\frac{1}{2} + \frac{1}{4}} 6A = 2A$$



$$I_1 = \frac{\frac{1}{10}}{\frac{1}{10} + \frac{1}{2} + \frac{1}{20}} 4A = 0.6154A$$


# Equivalent Circuits

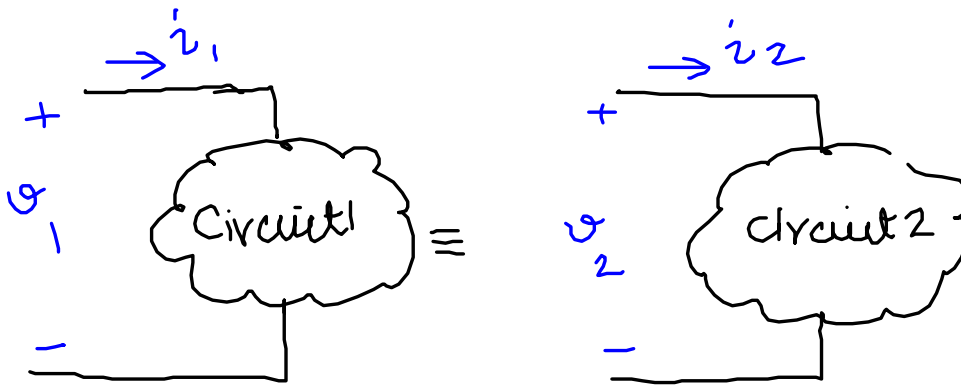


Circuit 1 & Circuit 2 are equivalent

$$if \ v_1 = v_2 \ \& \ i_1 = i_2$$


## Series resistance

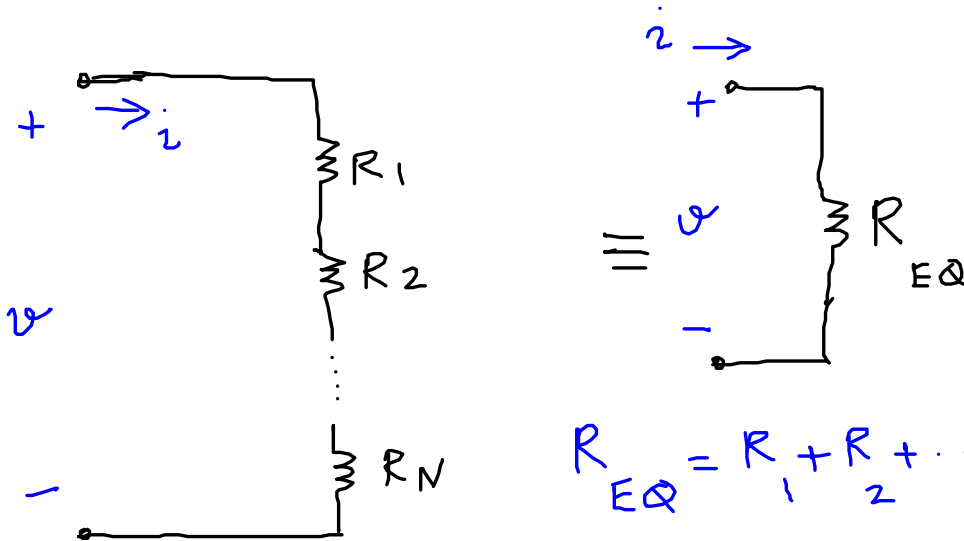

$$R_{EQ} = R_1 + R_2 + \dots + R_N$$




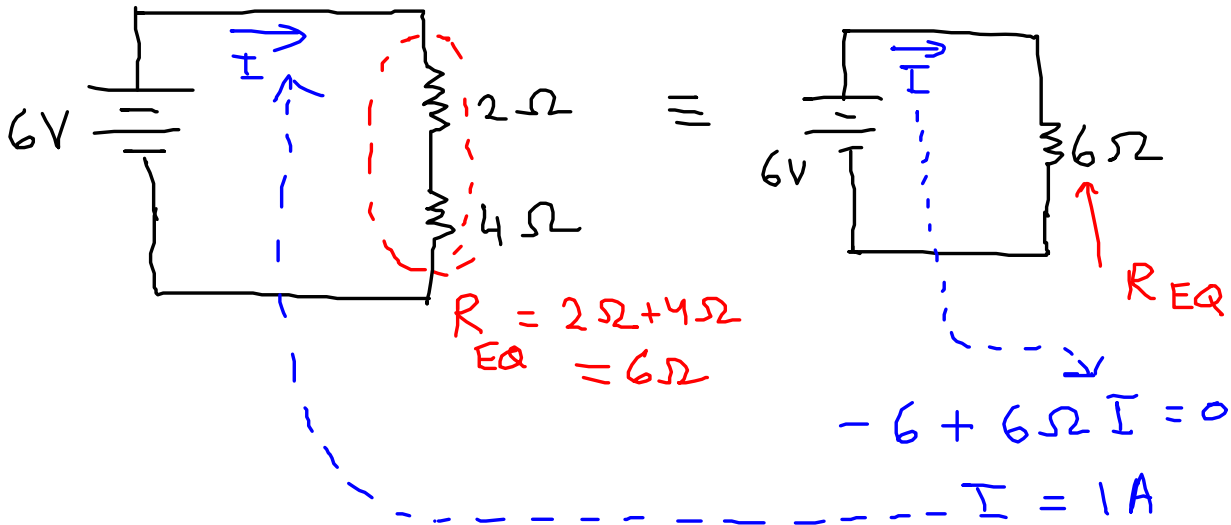


### Parallel Resistances

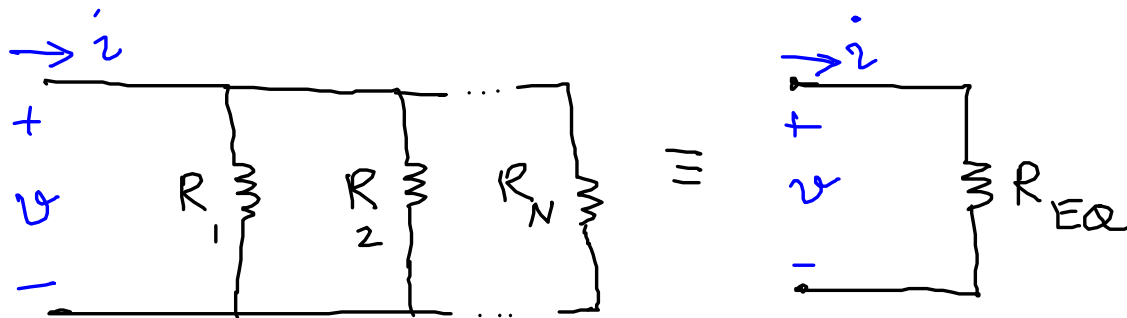

$$\frac{1}{R_{EQ}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N}$$


$$G_{EQ} = G_1 + G_2 + \dots + G_N$$

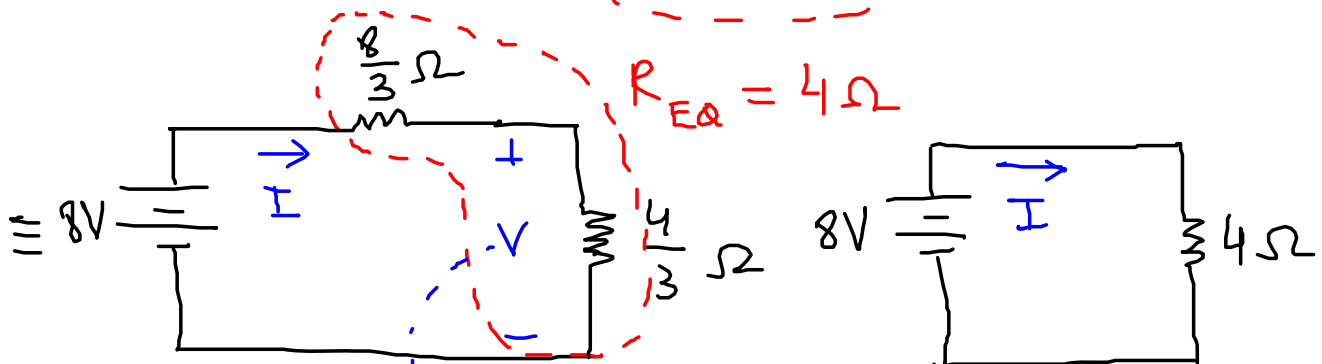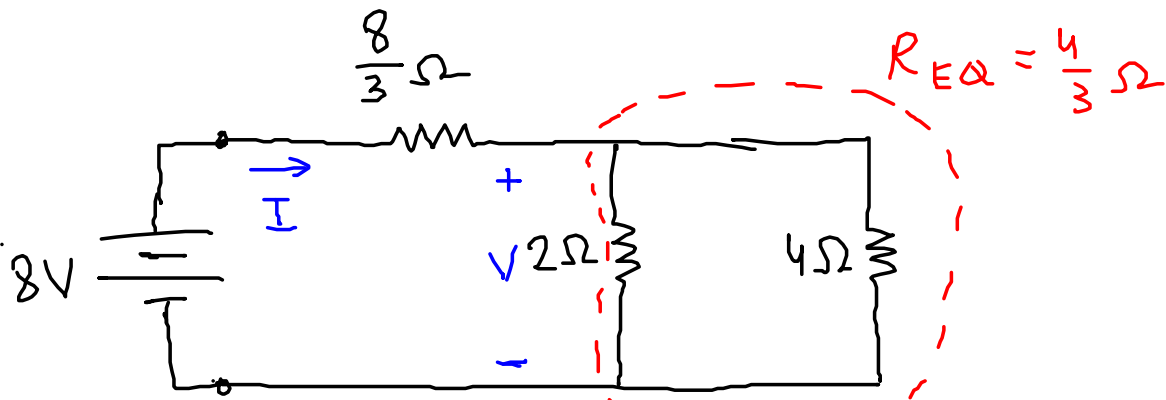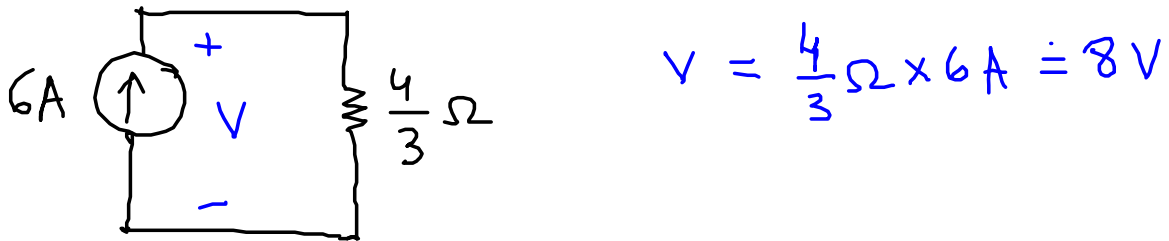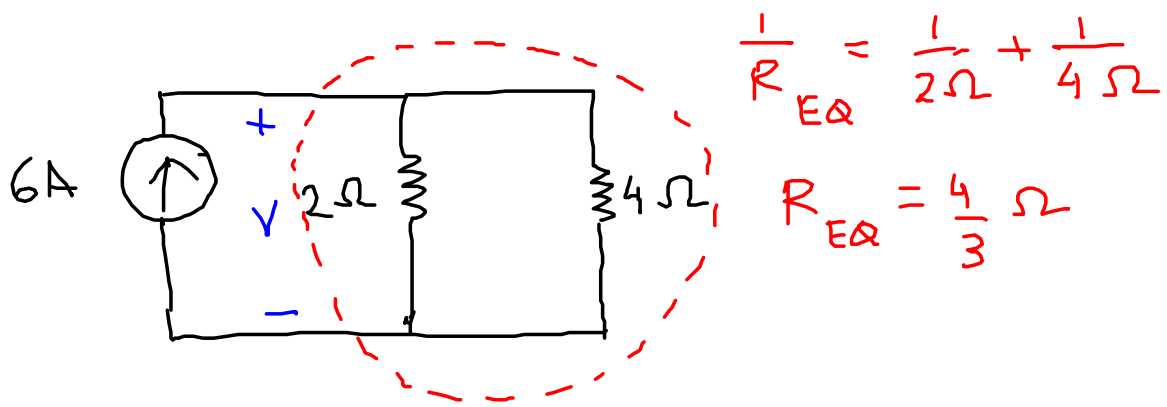


$$-8 + 4\Omega I = 0 \quad I = 2A$$

$$V = \frac{4}{3}\Omega \times I = \frac{4}{3}\Omega \times 2A = \frac{8}{3}V$$


Prob

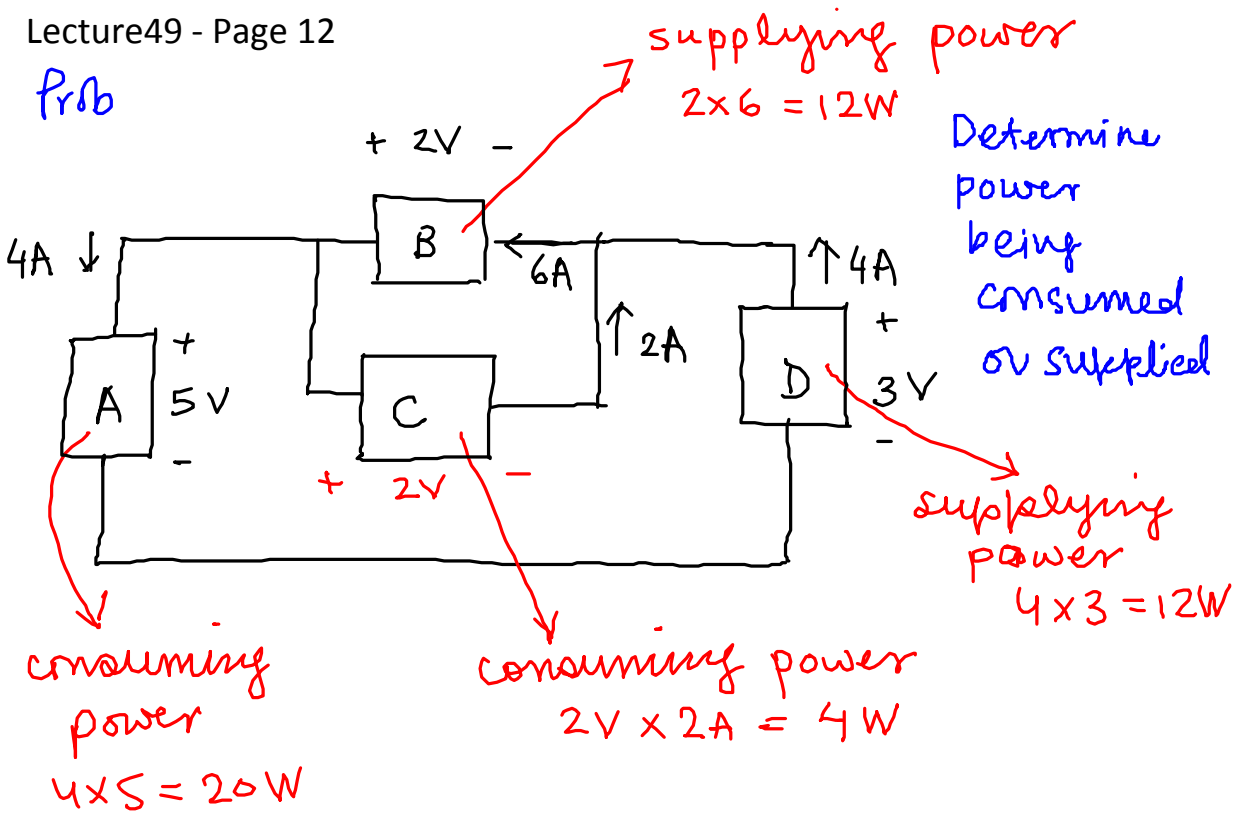

Prob

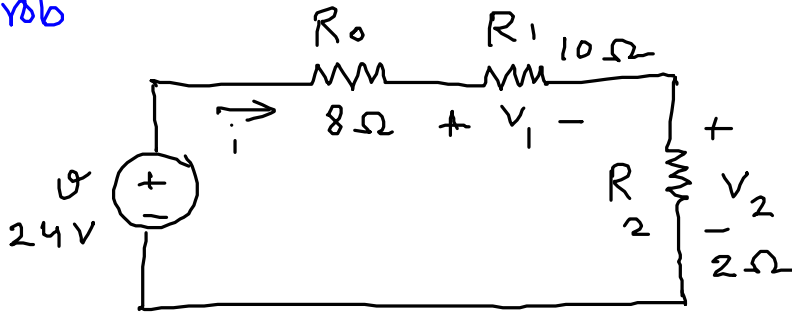

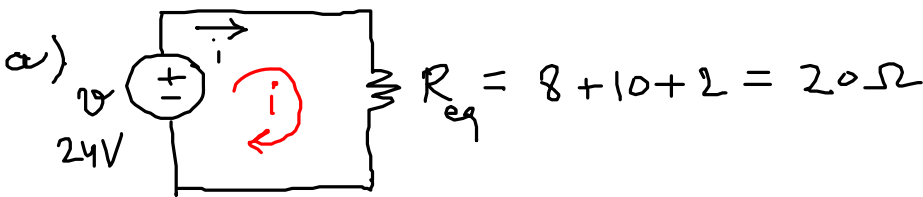$V_1?$   $V_2?$   
 Determine power supplied by the voltage source



b)  $\textcircled{1} -24V + i20\Omega = 0 \quad i = 1.2A$


c)  $24V \times 1.2A = 28.8W$



$$d) \quad V_1 = i \times R_1 = 1.2 \text{ A} \times 10 \Omega = 12 \text{ V}$$

$$V_2 = i \times R_2 = 1.2 \text{ A} \times 2 \Omega = 2.4 \text{ V}$$

Prb

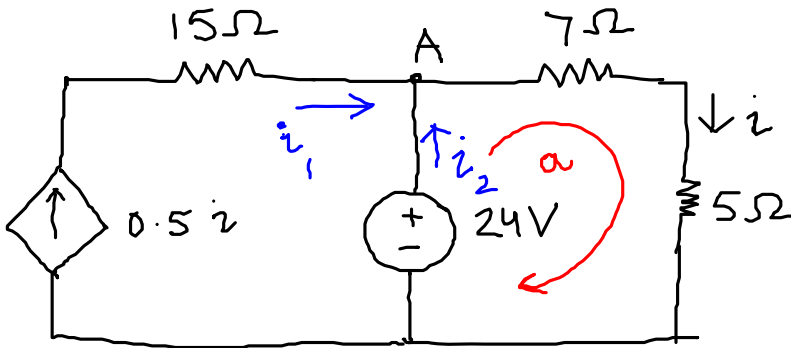

Determine  
power  
delivered  
by the  
independent  
source

$$\textcircled{a} \quad -24 \text{ V} + 7i + 5i = 0$$

$$i = \frac{24 \text{ V}}{12 \Omega} = 2 \text{ A}$$


$$i_1 = 0.5 i = 0.5 \times 2 = 1 \text{ A}$$

$$\text{KCL at A: } i_1 + i_2 - i = 0$$

$$i_2 = i - i_1 = 2 \text{ A} - 1 \text{ A} = 1 \text{ A}$$



$$\text{Power delivered by the ind. source} = 24 \text{ V} \times i_2 = 24 \text{ W}$$



Prob.

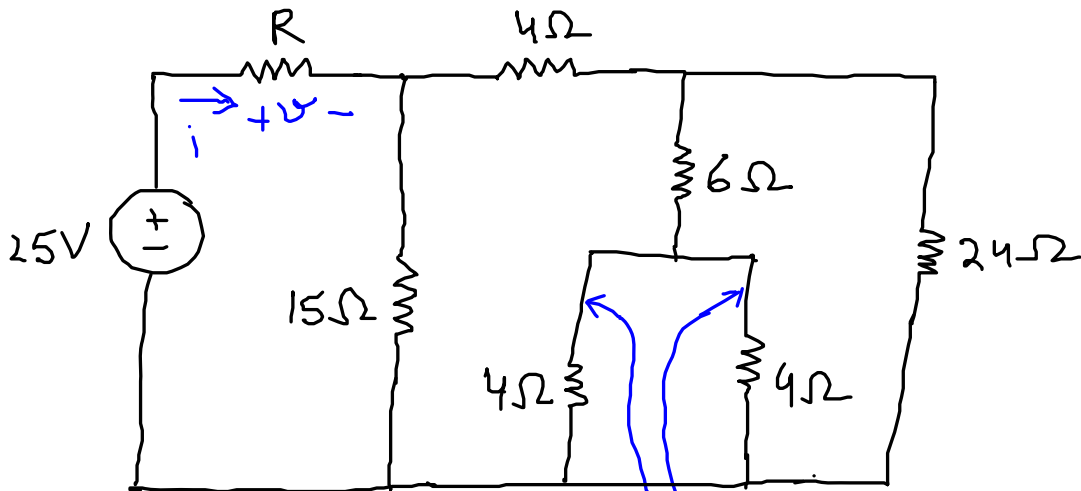

Given:  
 Power consumed  
 by the  $15\Omega$   
 resistance =  $15W$   
 Determine  $R$

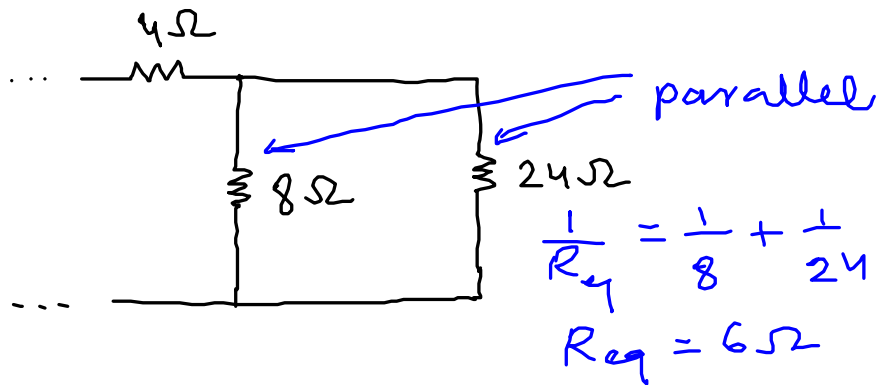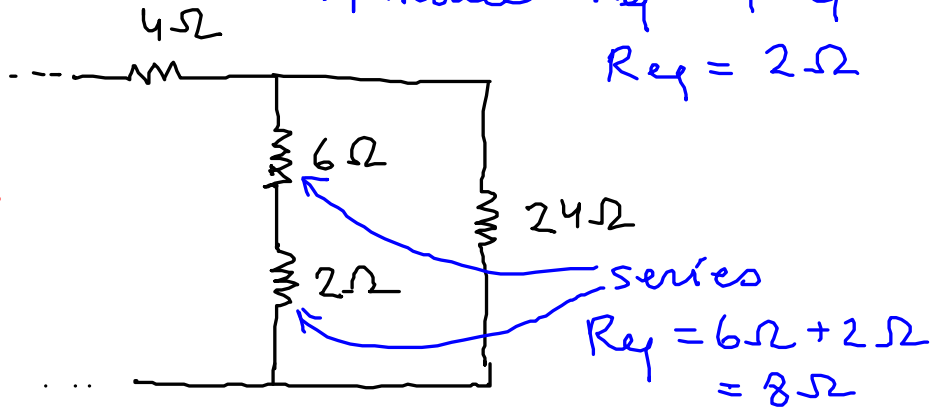Parallel  $\frac{1}{R_{eq}} = \frac{1}{4} + \frac{1}{4}$   
 $R_{eq} = 2\Omega$



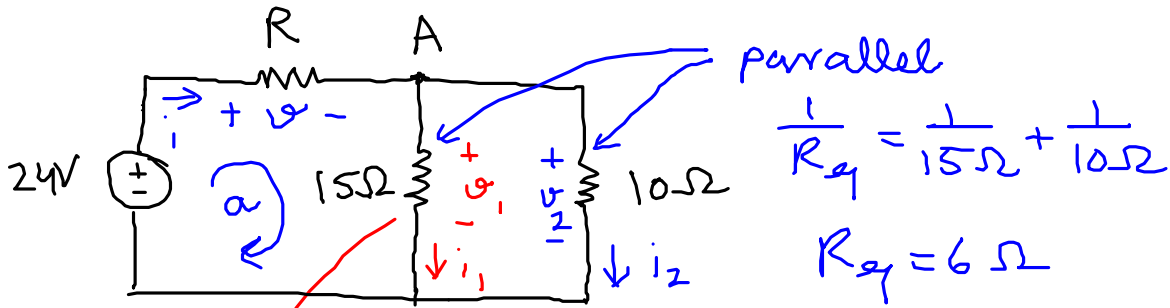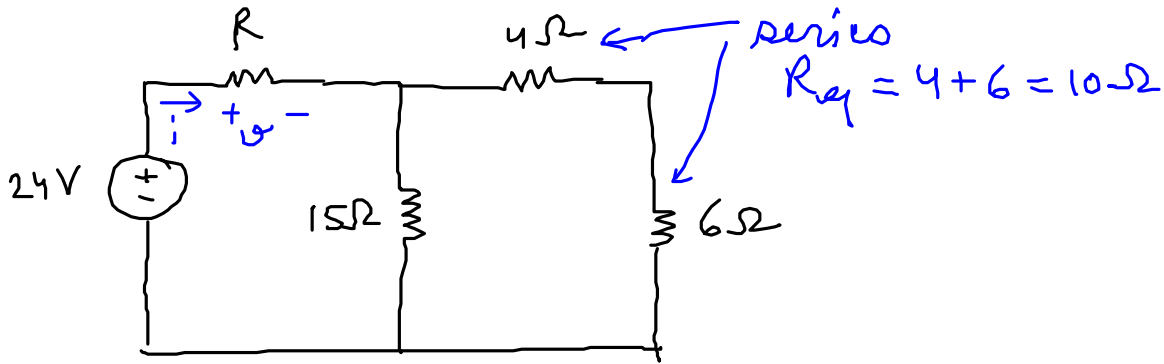

ohms Law

$$P = i_1 v_1 = \left(\frac{1}{15\Omega} v_1\right) v_1 = \frac{v_1^2}{15\Omega}$$

$$15W = \frac{v_1^2}{15\Omega}$$

$$v_1 = 15V$$

$$i_1 = \frac{1}{15\Omega} v_1 = 1A$$

$$v_2 = v_1 = 15V$$

$$i_2 = \frac{1}{10\Omega} v_2 = 1.5A$$


KCL at A:  $i - i_1 - i_2 = 0 \quad i = i_1 + i_2$

$$i = 1A + 1.5A = 2.5A$$

KVL a:  $-24 + v + 15 = 0 \quad v = 9V$

$$R = \frac{v}{i} = \frac{9V}{2.5A} = 3.6\Omega$$

Prob.

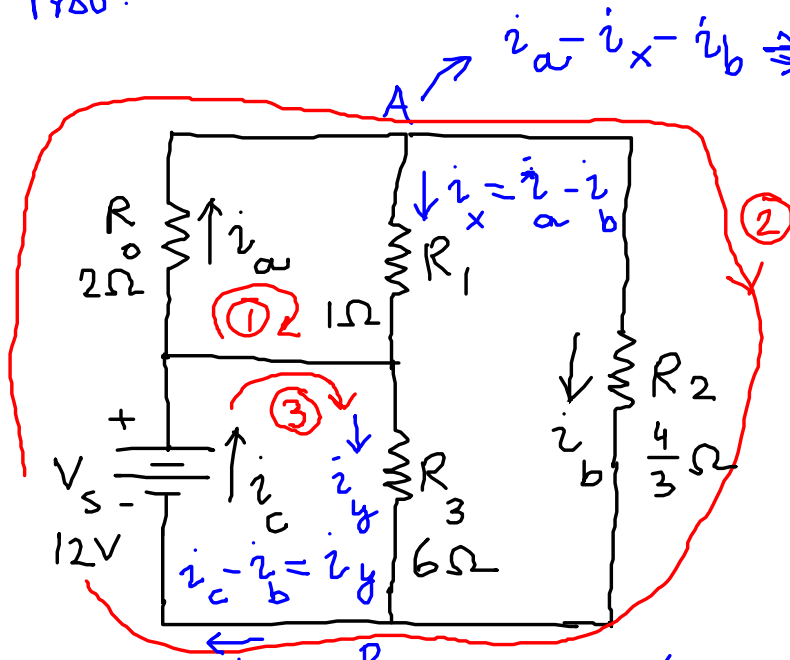

Determine  
 $i_x$  &  $i_y$

$$i_c - i_b = i_y \quad -i_c + i_y + i_b = 0 \quad i_y = i_c - i_b$$

Three unknowns:  $i_a$ ,  $i_b$  &  $i_c$

$$\text{KVL } \textcircled{1} : i_a 2\Omega + 1\Omega (i_a - i_b) = 0$$

$$i_b = 3i_a$$

$$\text{KVL } \textcircled{2} : -12V + 2i_a + \frac{4}{3}i_b = 0$$

$$-12V + 2i_a + 4i_a = 0$$

$$i_a = 2A$$

$$\rightarrow i_b = 3 \times 2 = 6A$$

$$\text{KVL } \textcircled{3}: -12V + 6i_y = 0$$

$$-12V + 6(i_c - \underset{\substack{\parallel \\ 6A}}{i_b}) = 0$$

$$-12V + 6i_c - 36V = 0$$


$$6i_c = 48V$$

$$i_c = 8A$$

$$i_x = i_a - i_b = 2A - 6A = -4A$$

$$i_y = i_c - i_b = 8A - 6A = 2A$$

Prb.

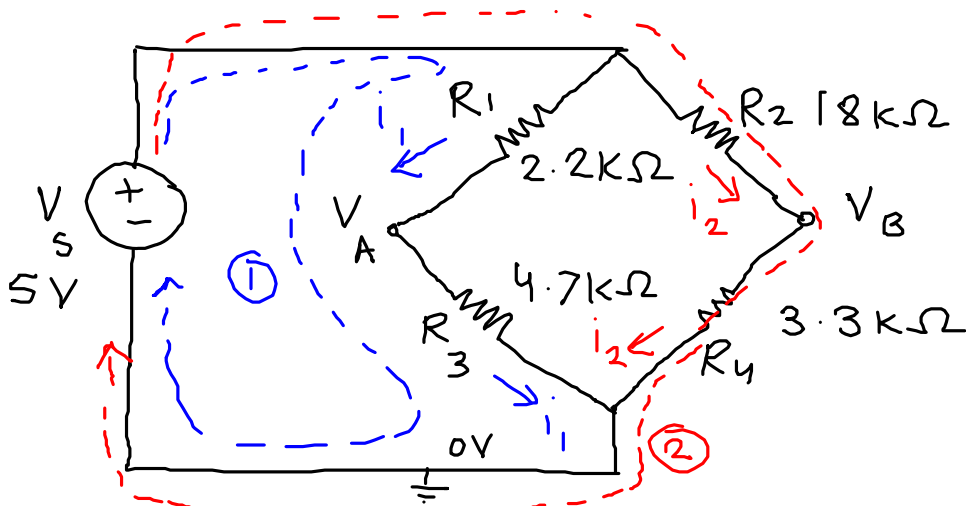Determine  $V_A - V_B$ 

$$\text{KVL } \textcircled{1}: -5 + 2.2k\Omega i_1 + 4.7k\Omega i_1 = 0$$

$$i_1 = \frac{5V}{6.9k\Omega} = \frac{5}{6.9} \text{ mA}$$

$$\text{KVL } \textcircled{2}: -5 + 18k\Omega i_2 + 3.3k\Omega i_2 = 0$$

$$i_2 = \frac{5V}{21.3k\Omega} = \frac{5}{21.3} \text{ mA}$$

$$V_A - 0 = R_3 i_1 = 4.7k\Omega \times \frac{5}{6.9} \text{ mA} = 3.4V$$

$$V_B - 0 = R_4 i_2 = 3.3k\Omega \times \frac{5}{21.3} \text{ mA} = 0.77V$$

$$V_A - V_B = 3.4V - 0.77V = 2.63V$$