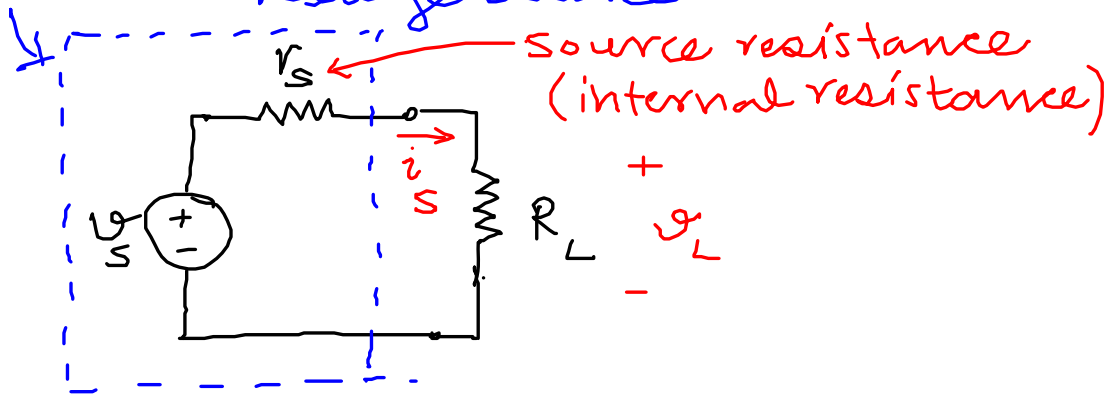


Practical Voltage & Current Sources

Non-ideal Voltage Source

Practical Voltage Source



Ideal voltage source $r_s = 0$

$$v_L = \frac{R_L}{r_s + R_L} v_s$$

$$v_L \sim v_s \quad \text{if } r_s \ll R_L$$


$$v_L \sim 0 \quad \text{if } r_s \gg R_L$$

maximum voltage source current

$$i_s = \frac{v_s}{r_s + R_L}$$

$$i_{s, \max} = \frac{v_s}{r_s} \quad R_L = 0 \text{ (short circuit)}$$

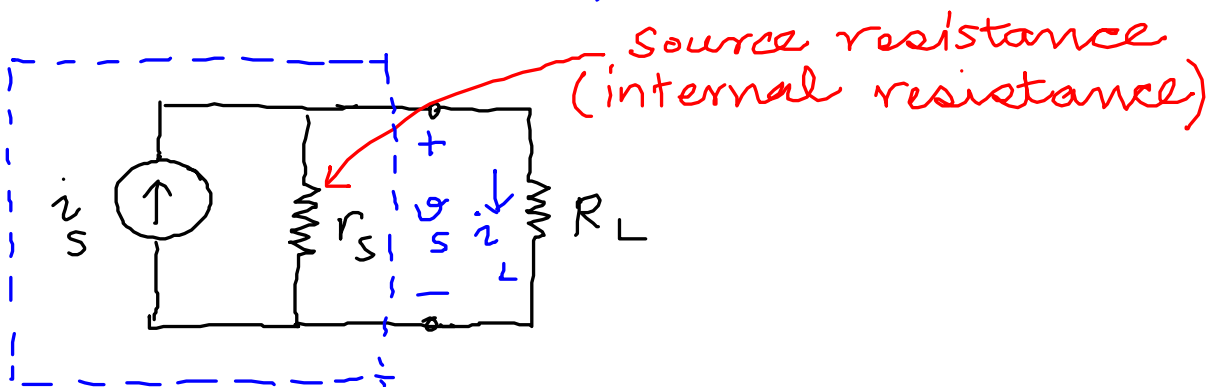Non-Ideal current source
Practical current source



ideal current source $r_s \rightarrow \infty$

$$i_L = \frac{\frac{1}{R_L}}{\frac{1}{r_s} + \frac{1}{R_L}} \quad i_s = \frac{r_s}{r_s + R_L} i_s$$


$$i_L \sim i_s \quad \text{if } r_s \gg R_L$$

$$i_L \sim 0 \quad \text{if } r_s \ll R_L$$


$$v_s = i_L R_L = \frac{r_s R_L}{r_s + R_L} i_s = \frac{i_s}{\frac{1}{r_s} + \frac{1}{R_L}}$$

$$v_{s, \max} = \frac{i_s}{\frac{1}{r_s}} = r_s i_s \quad \text{if } R_L \rightarrow \infty \text{ (open)}$$





Voltmeter

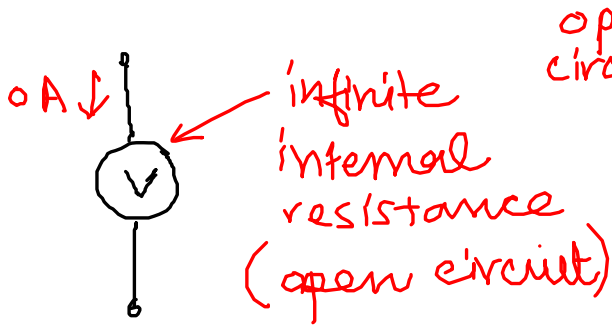

ideal Voltmeter

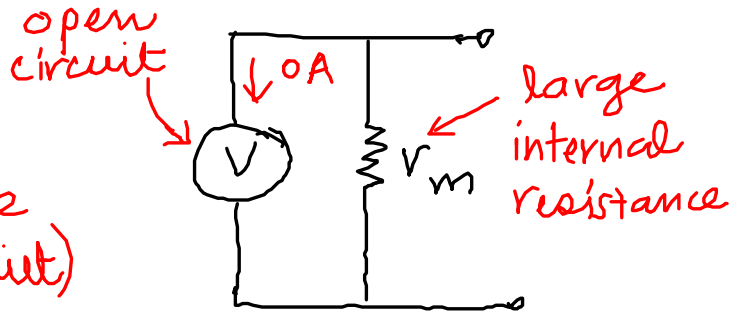


non-ideal (practical) Voltmeter

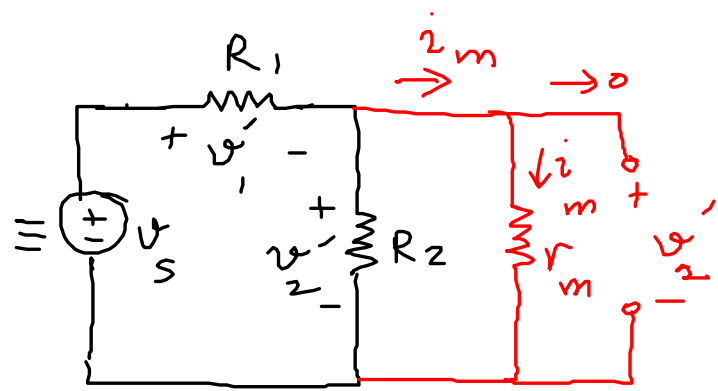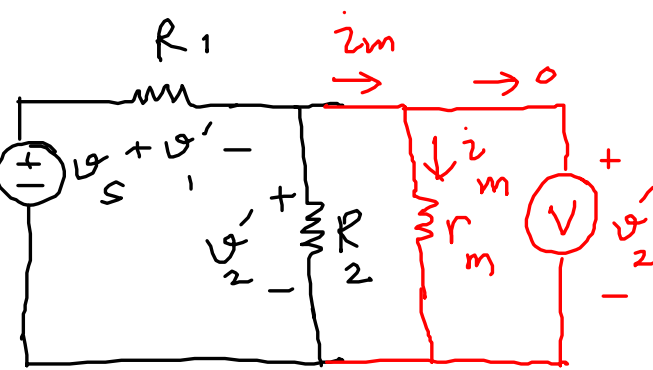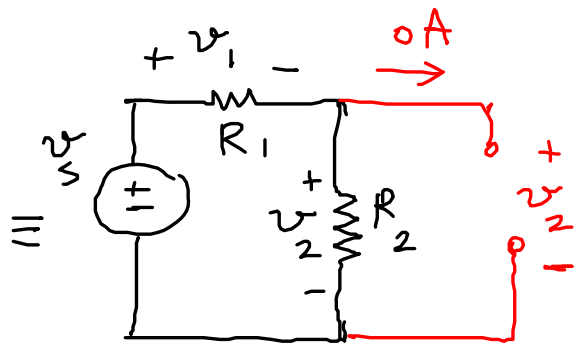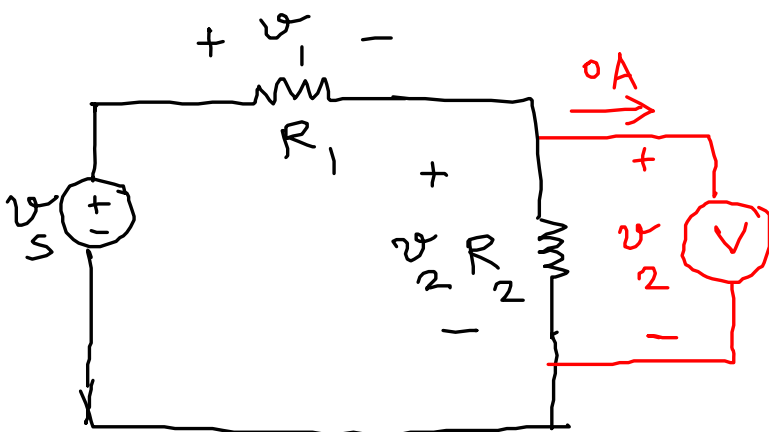


$$v'_1 \neq v_1 \quad v'_2 \neq v_2$$

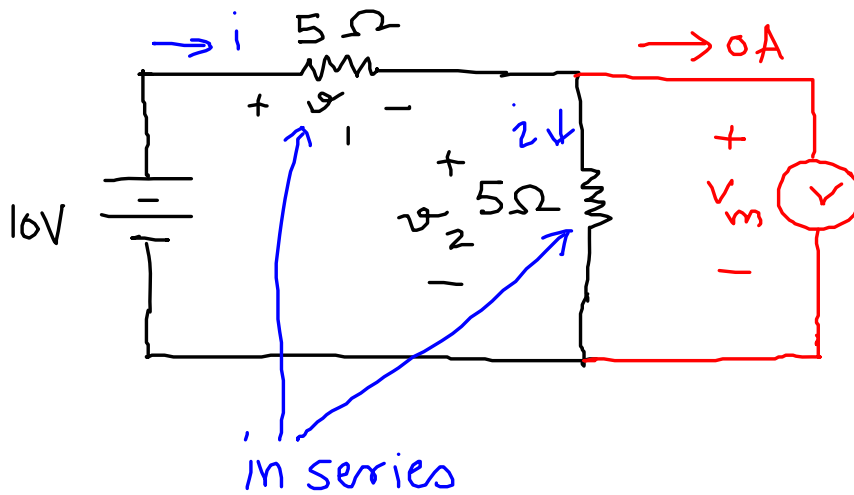non-ideal voltmeter affects the voltages being measured




$$v_1 = \frac{5}{5+5} 10 = 5V \quad v_2 = \frac{5}{5+5} 10 = 5V$$

$$V_m = v_2 = 5V$$

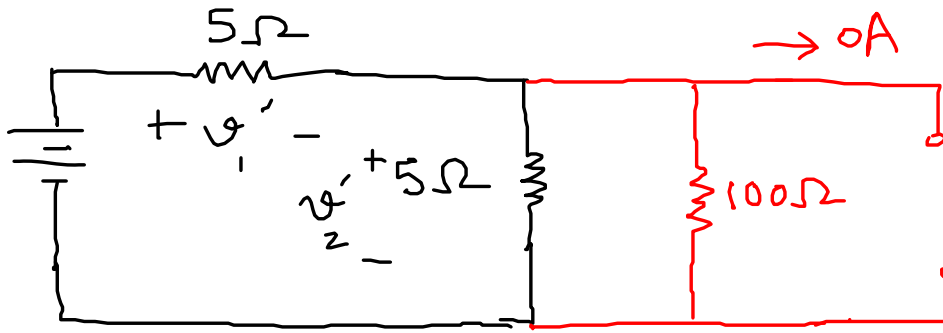






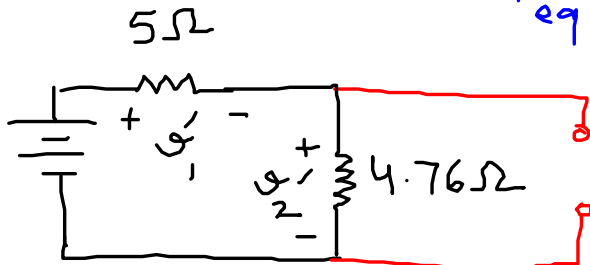
$$\frac{1}{R_{eq}} = \frac{1}{5} + \frac{1}{100} \quad R_{eq} = 4.76\Omega$$




$$v'_1 = \frac{5}{5+4.76} 10 = 5.12V$$


$$v'_2 = \frac{4.76}{5+4.76} 10 = 4.88V$$

Ammeter

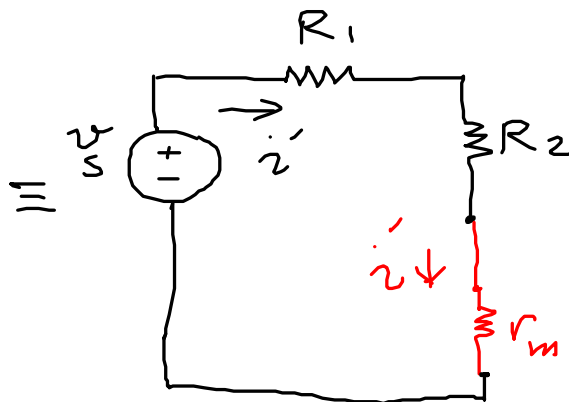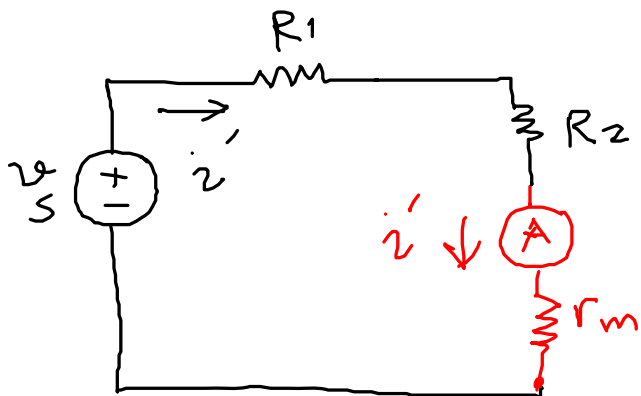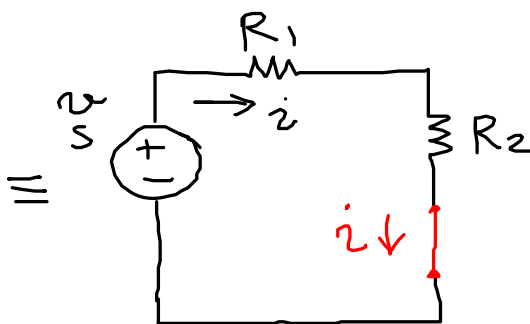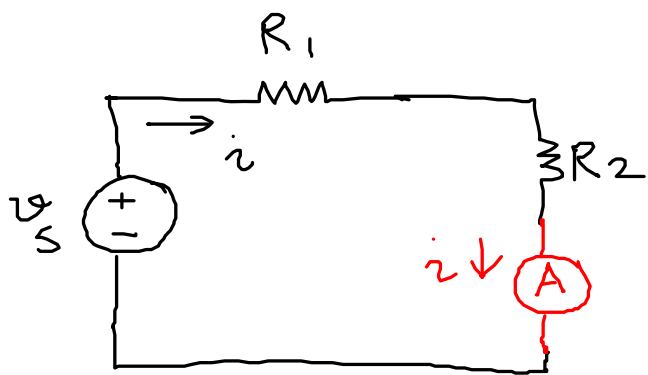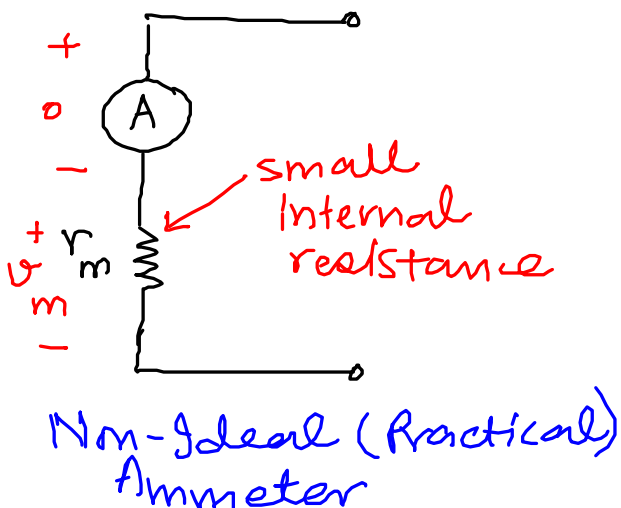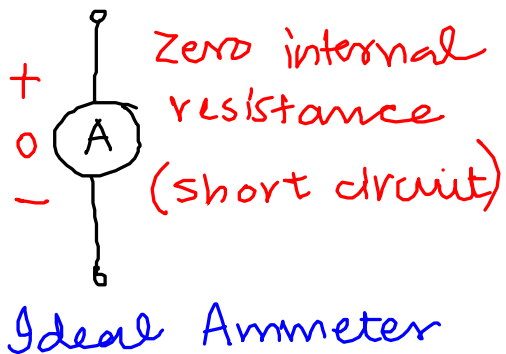

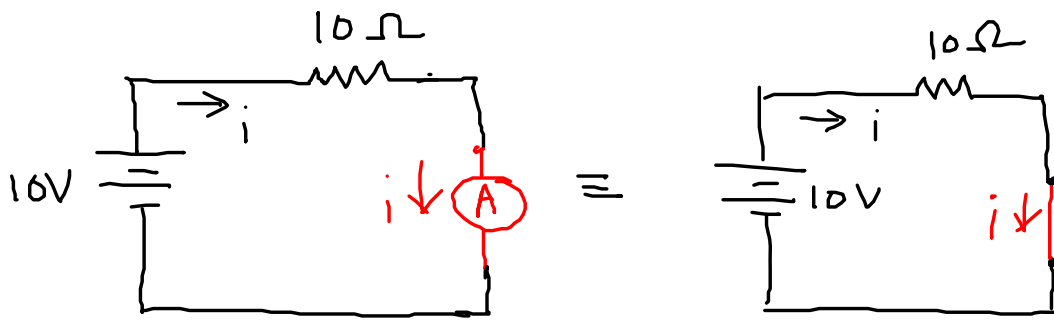


$$i = \frac{10V}{10\Omega} = 1A$$

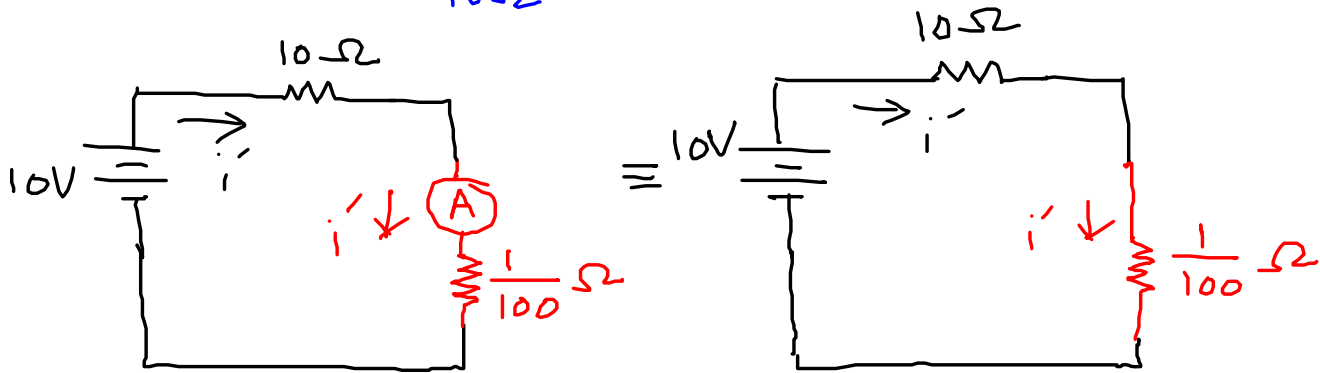


$$i' = \frac{10V}{10\Omega + 0.01\Omega} = 0.99A$$


Node Analysis

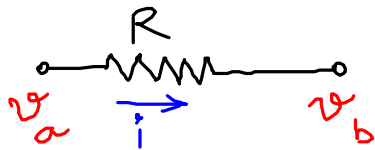

$$i = \frac{v_a - v_b}{R}$$

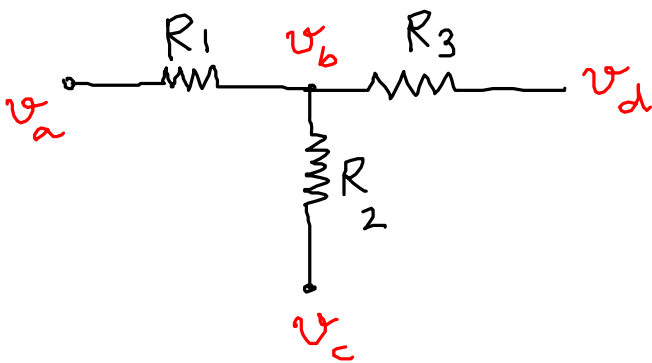

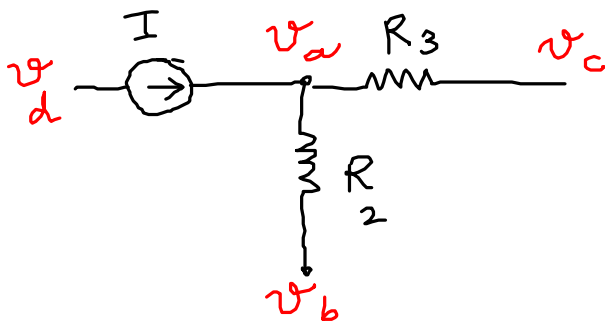
$$\text{KCL: } \frac{v_a - v_b}{R_1} + \frac{v_c - v_b}{R_2} + \frac{v_d - v_b}{R_3} = 0$$




v_d does not appear in this equation
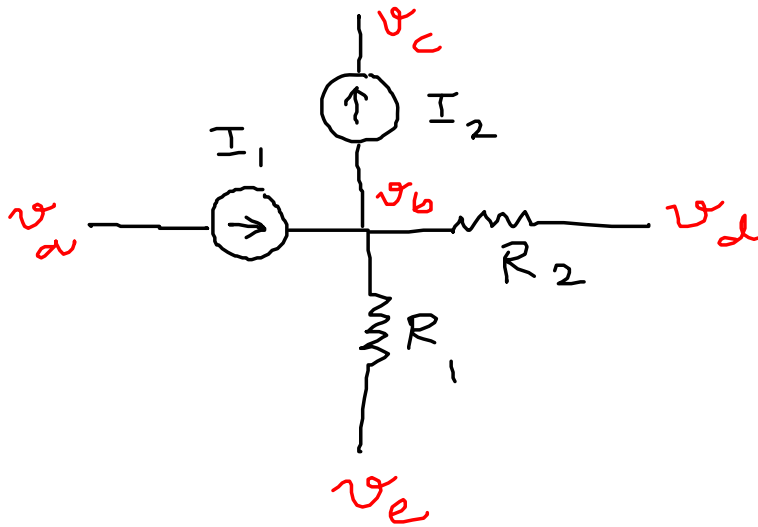
$$\text{KCL: } I + \frac{v_b - v_a}{R_2} + \frac{v_c - v_a}{R_3} = 0$$


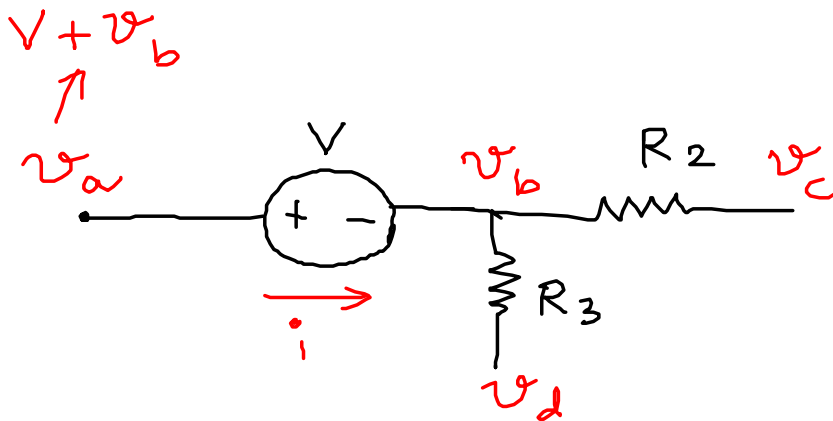
$$\text{KCL: } I_1 - I_2 + \frac{v_e - v_b}{R_1} + \frac{v_d - v_b}{R_2} = 0$$



$$\text{KCL: } i + \frac{v_d - v_b}{R_3} + \frac{v_c - v_b}{R_2} = 0$$