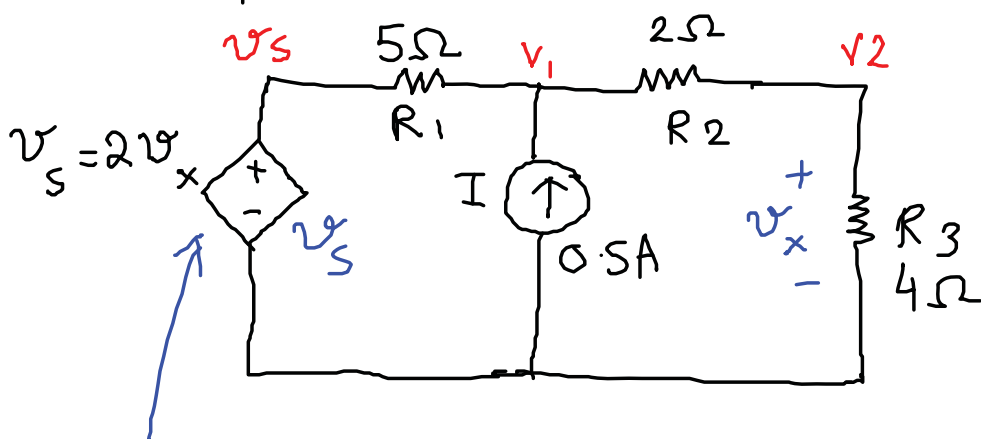


Node & Mesh Analysis with Dependent sources



Treat this as a normal voltage source

$$\frac{v_s - v_1}{5\Omega} + 0.5A + \frac{v_2 - v_1}{2\Omega} = 0$$

$$\frac{v_1 - v_2}{2\Omega} + \frac{0 - v_2}{4\Omega} = 0$$


$$v_s = 2v_x = 2(v_2 - 0) = 2v_2$$

express v_x in terms of unknowns

$$\frac{2v_2 - v_1}{5\Omega} + 0.5A + \frac{v_2 - v_1}{2\Omega} = 0$$

$$\frac{v_1 - v_2}{2\Omega} + \frac{0 - v_2}{4\Omega} = 0$$

Two equations in two unknowns

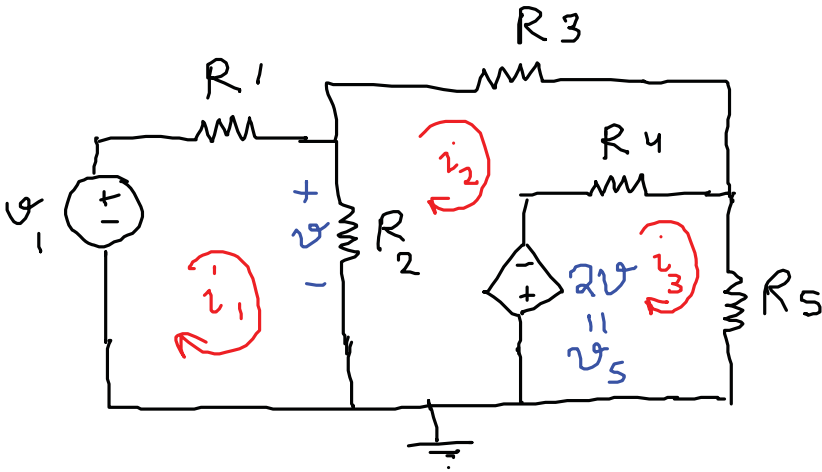

$$-v_1 + R_1 i_1 + R_2 (i_1 - i_2) = 0$$

$$R_3 i_2 + R_4 (i_2 - i_3) - v_5 - R_2 (i_2 - i_1) = 0$$

$$R_4 (i_3 - i_2) + R_5 i_3 + v_5 = 0$$


$$v_5 = 2v$$

express in terms of unknowns

$$v = R(i_1 - i_2)$$

$$v_5 = 2R(i_1 - i_2)$$

Three equations in three unknowns

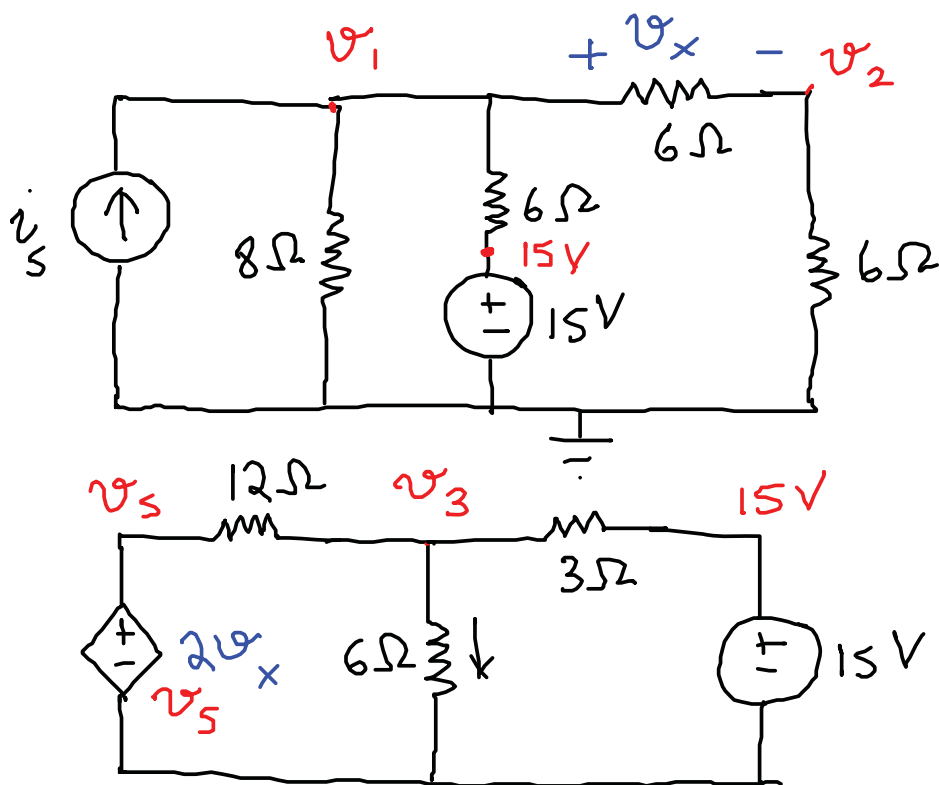


$$v_1: i_s + \frac{0 - v_1}{8\Omega} + \frac{15V - v_1}{6\Omega} + \frac{v_2 - v_1}{6\Omega} = 0$$

$$v_2: \frac{v_1 - v_2}{6\Omega} + \frac{0 - v_2}{6\Omega} = 0$$

$$v_3: \frac{v_5 - v_3}{12} + \frac{0 - v_3}{6\Omega} + \frac{15 - v_3}{3\Omega} = 0$$

$$v_5 = 2v_x = 2(v_1 - v_2)$$

Three equations in 3 unknowns

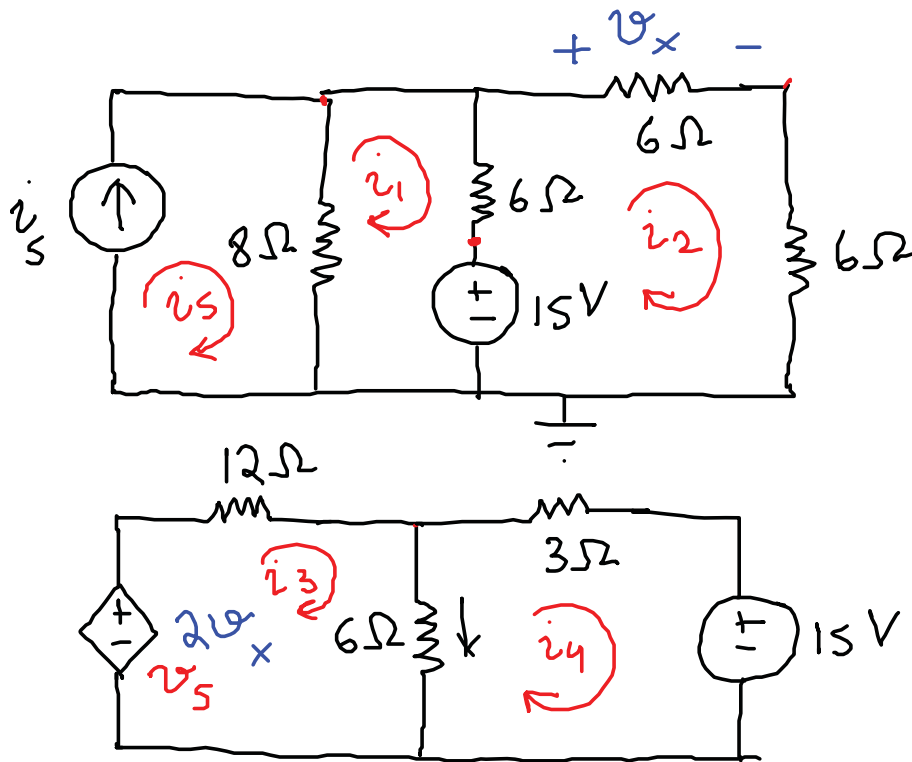

$$i_1: 15V + 8\Omega(i_1 - i_s) + 6\Omega(i_1 - i_2) = 0$$

$$i_2: -15V + 6\Omega(i_2 - i_1) + 6\Omega i_2 + 6\Omega i_2 = 0$$

$$i_3: -v_s + 12\Omega i_3 + 6\Omega(i_3 - i_4) = 0$$

$$i_4: 15V + 6\Omega(i_4 - i_3) + 3\Omega i_4 = 0$$


$$v_s = 2v_x = 2 \times 6\Omega i_2 = 12i_2$$

$$v_s = 12i_2$$


4 equations in 4 unknowns

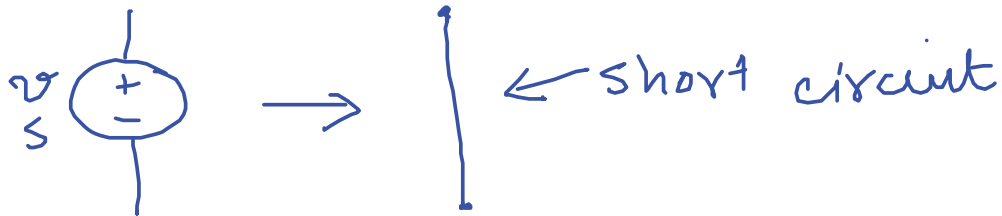3.5 Principle of Superposition

How to kill an independent voltage source :



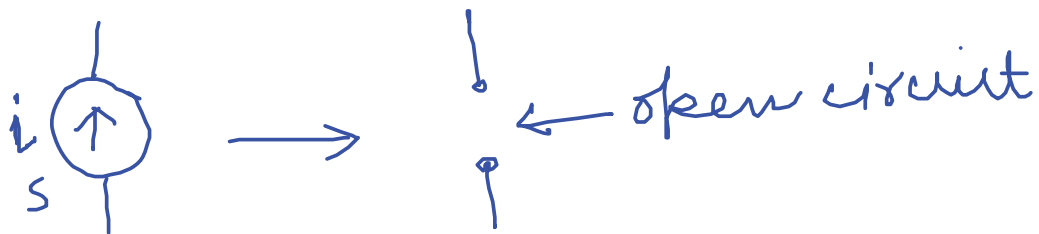How to kill an independent current source



visit an independent source



kill all independent sources
except for the visited source





solve the problem and determine
the voltages and currents




visit the next independent source

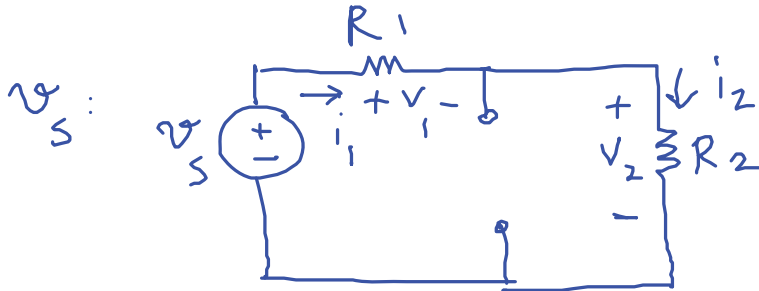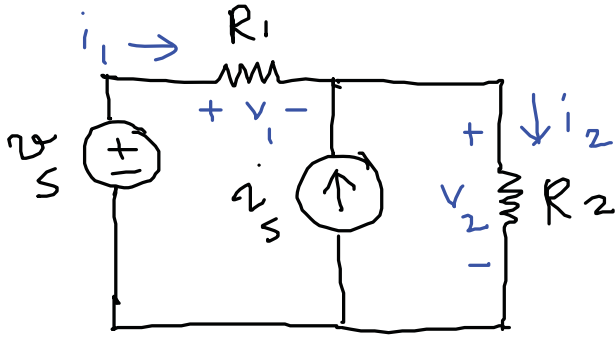add the voltages and currents
from each visited independent
source




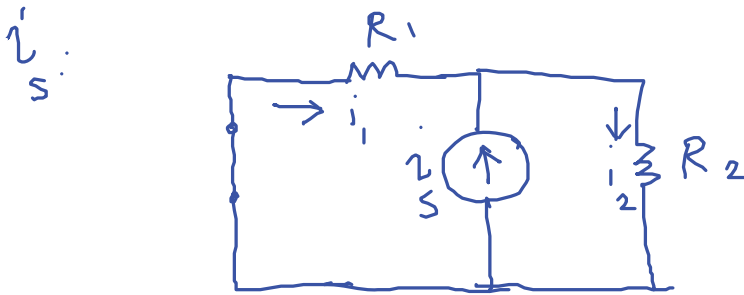
$$i_1 = i_2 = \frac{v_s}{R_1 + R_2} \quad v_1 = \frac{R_1}{R_1 + R_2} v_s \quad v_2 = \frac{R_2}{R_1 + R_2} v_s$$



$$i_1 = -\frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} i_s = -\frac{R_2}{R_1 + R_2} i_s, \quad v_1 = -\frac{R_1 R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} i_s = \frac{R_1}{R_1 + R_2} i_s, \quad v_2 = \frac{R_1 R_2}{R_1 + R_2} i_s$$

Use superposition to get the correct total answer

$$v_1 = \frac{R_1}{R_1 + R_2} v_s - \frac{R_1 R_2}{R_1 + R_2} i_s$$

$$v_2 = \frac{R_2}{R_1 + R_2} v_s + \frac{R_1 R_2}{R_1 + R_2} i_s$$

$$i_1 = \frac{v_s}{R_1 + R_2} - \frac{R_2}{R_1 + R_2} i_s$$

$$i_2 = \frac{v_s}{R_1 + R_2} + \frac{R_1}{R_1 + R_2} i_s$$

