
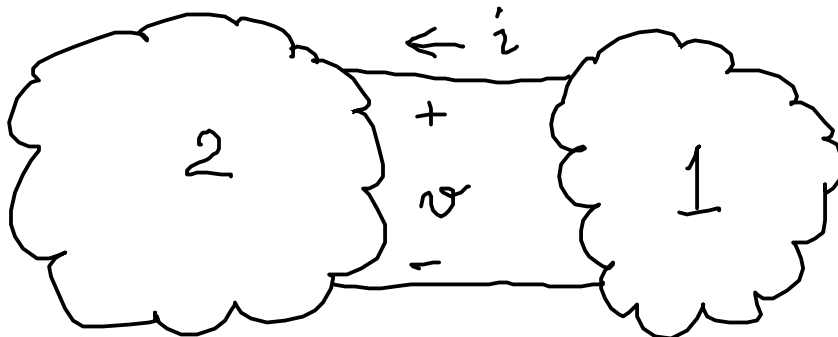


Equivalent Circuits

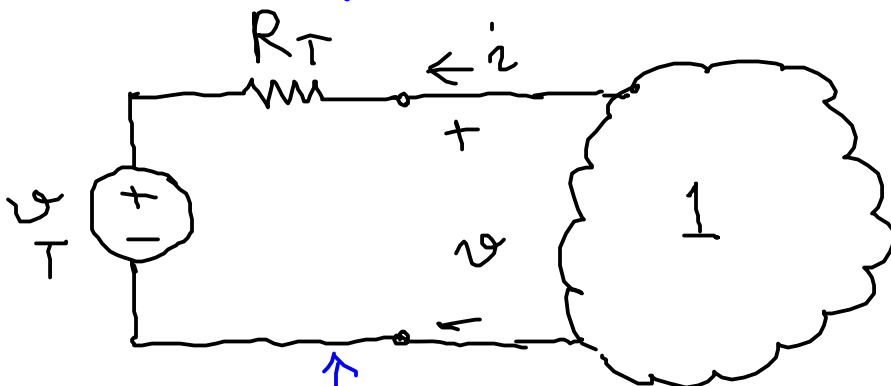


|||





↑
Thevenin's Equivalent

|||

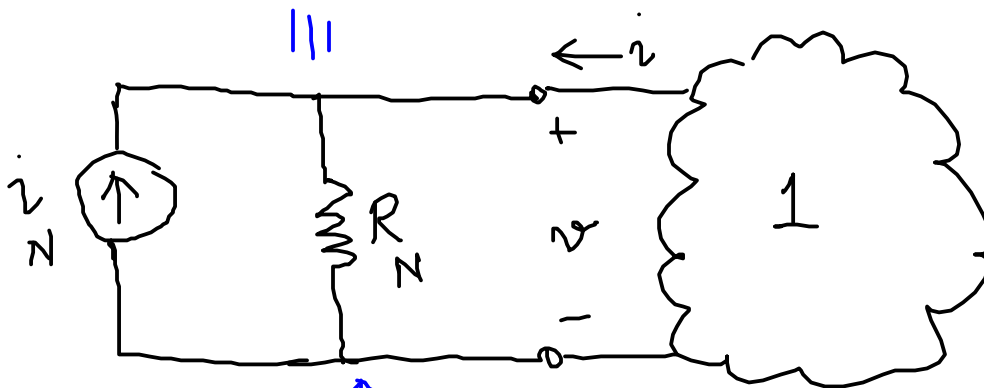

↑
Norton's Equivalent


Determining v_T , i_N , R_T , R_N

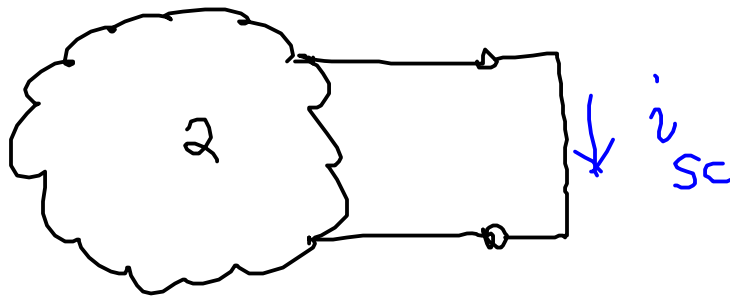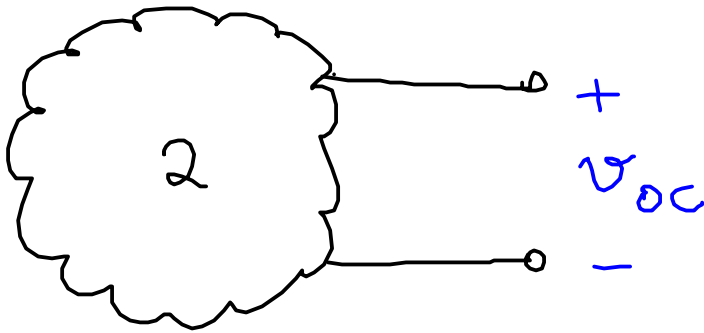


$$v_T = v_{oc}$$

$$i_N = i_{sc}$$


$$R_T = R_N = \frac{v_{oc}}{i_{sc}}$$

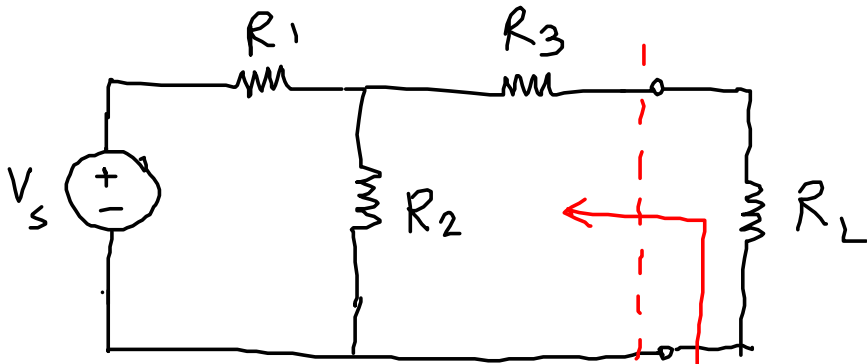

T & N equivalent

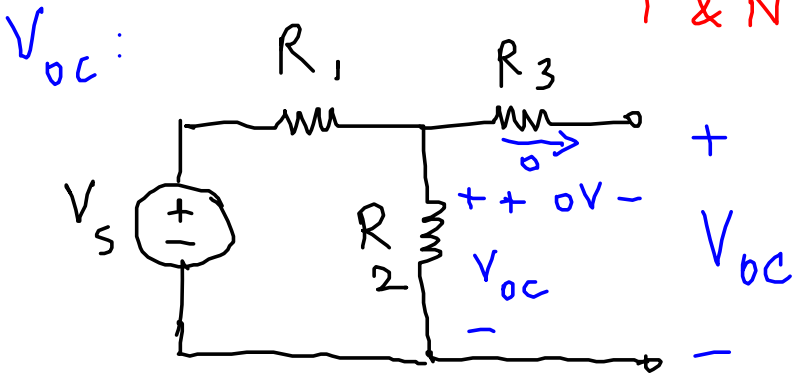


$$V_{oc} = \frac{R_2}{R_1 + R_2} V_s$$

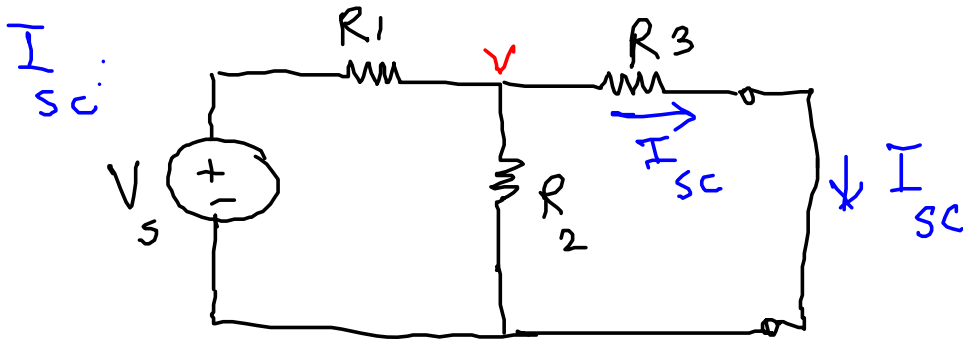


$$\frac{V_s - V}{R_1} + \frac{0 - V}{R_2} + \frac{0 - V}{R_3} = 0 \quad \text{find } V$$

$$I_{sc} = \frac{V}{R_3}$$
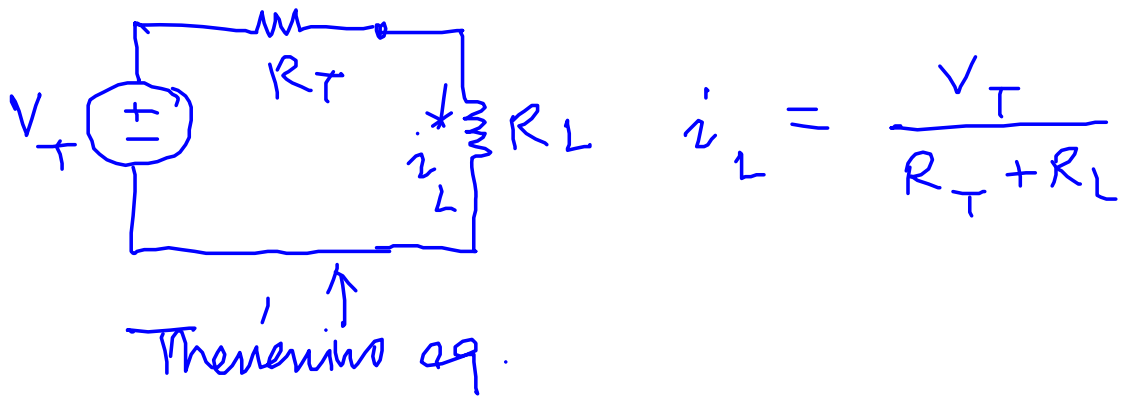
$$V_T = V_{oc}, \quad I_N = I_{sc}, \quad R_N = R_T = \frac{V_{oc}}{I_{sc}}$$




$$i_L = \frac{V_T}{R_T + R_L}$$

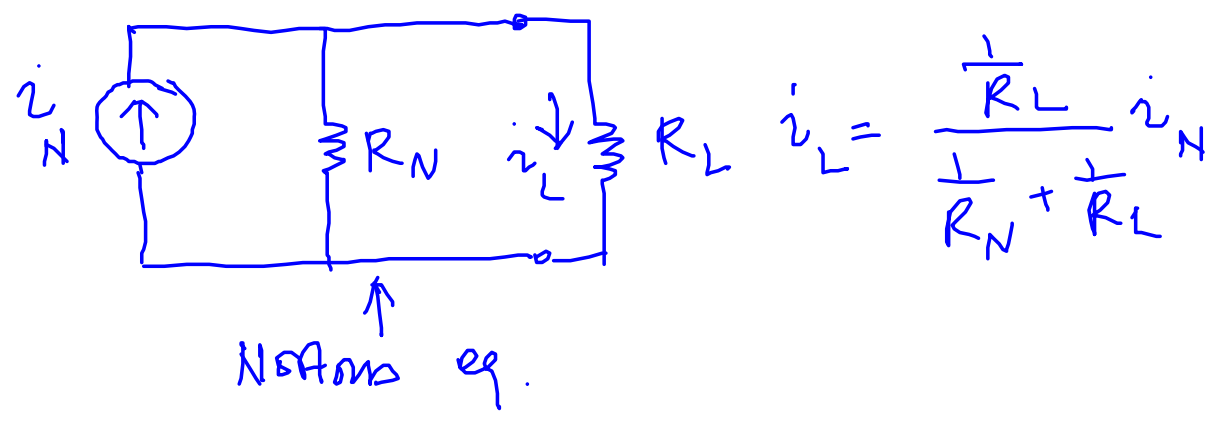


$$i_L = \frac{\frac{1}{R_L} i_N}{\frac{1}{R_N} + \frac{1}{R_L}}$$

Problem

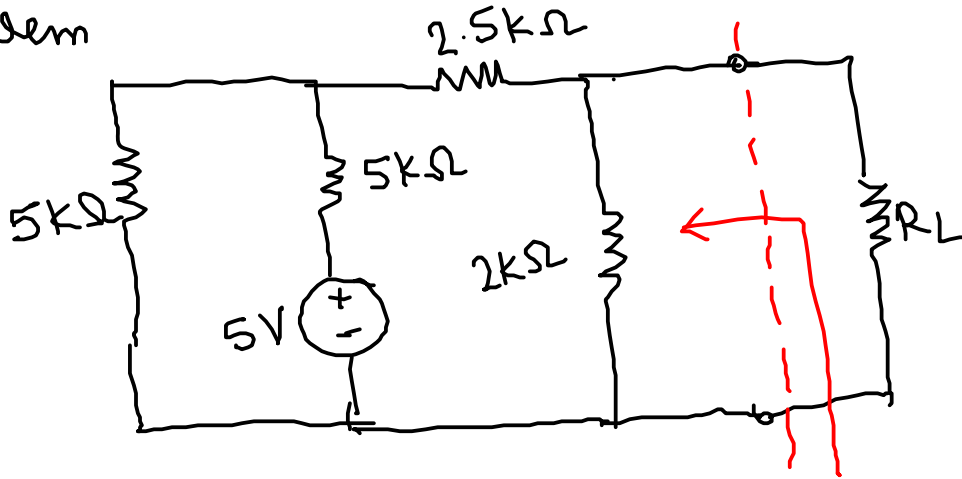


T & N eq.

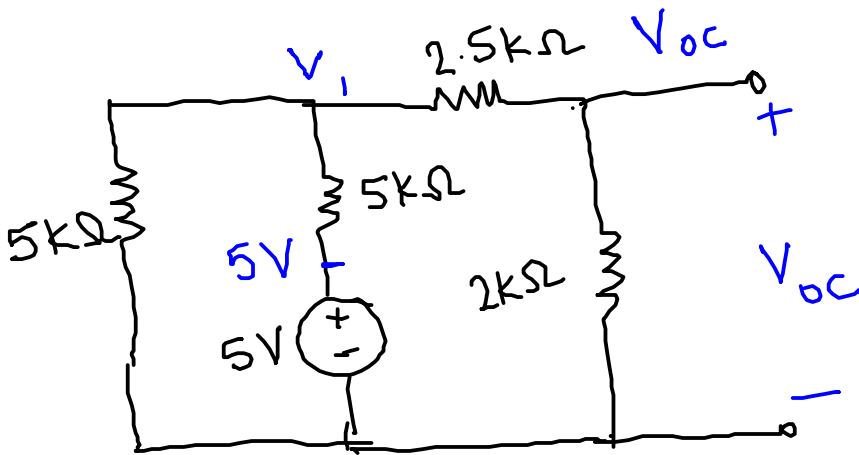

$$0 - \frac{V_1}{5k\Omega} + \frac{5V - V_1}{5k\Omega} + \frac{V_{oc} - V_1}{2.5k\Omega} = 0$$

$$\frac{V_1 - V_{oc}}{2.5k\Omega} + \frac{0 - V_{oc}}{2k\Omega} = 0$$

find V_1 & V_{oc}

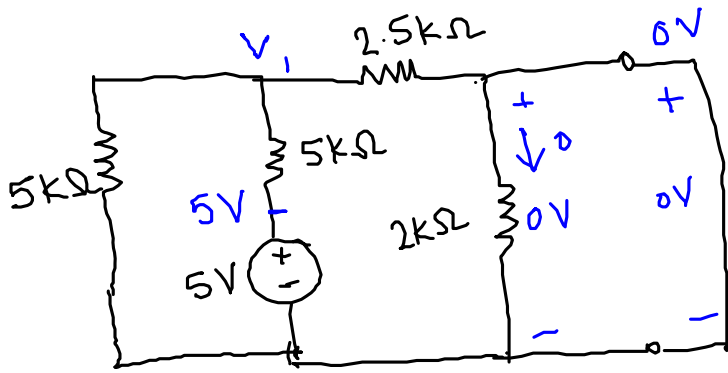


$$I_{sc} = \frac{V_1 - 0}{2.5k\Omega}$$

$$\frac{0 - V_1}{5k} + \frac{5 - V_1}{5k} + \frac{0 - V_1}{2.5k} = 0$$


find V_1

$$I_{sc} = \frac{V_1}{2.5k\Omega}$$

Problem

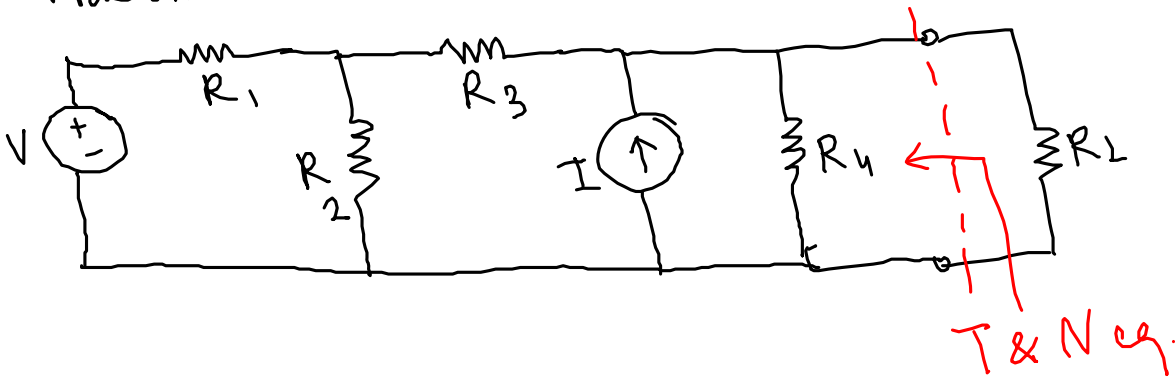


T & N eq.

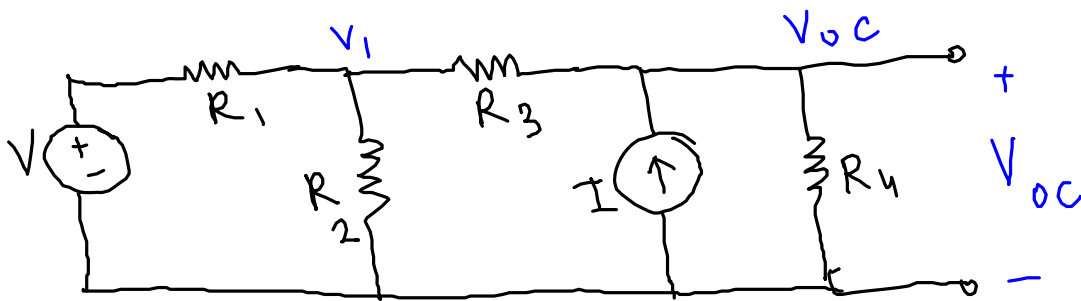

$$\frac{V - V_1}{R_1} + 0 - \frac{V_1}{R_2} + \frac{V_{oc} - V_1}{R_3} = 0$$
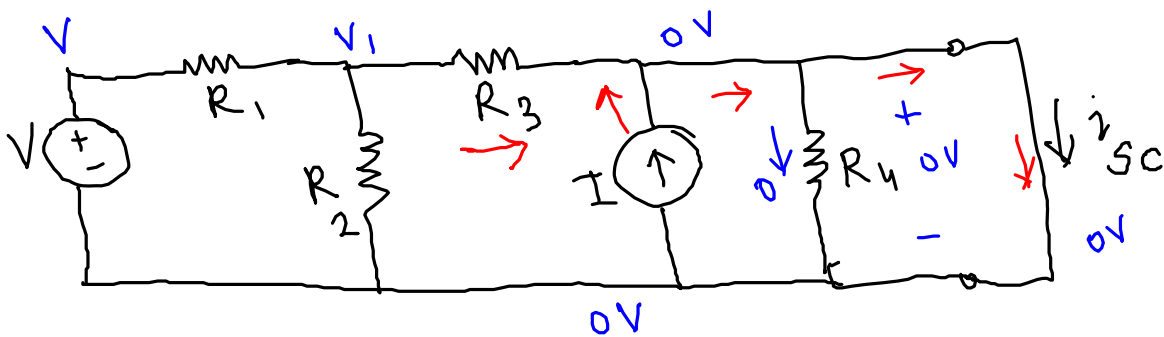
$$\frac{V_1 - V_{oc}}{R_3} + I + 0 - \frac{V_{oc}}{R_4} = 0 \quad \text{find } V_1 \text{ \& } V_{oc}$$





$$\frac{V - V_1}{R_1} + 0 - \frac{V_1}{R_3} + \frac{0 - V_1}{R_2} = 0 \quad \text{find } V_1$$


$$i_{sc} = \frac{V_1 - 0V}{R_3} + I$$

Problem

T & N eq.

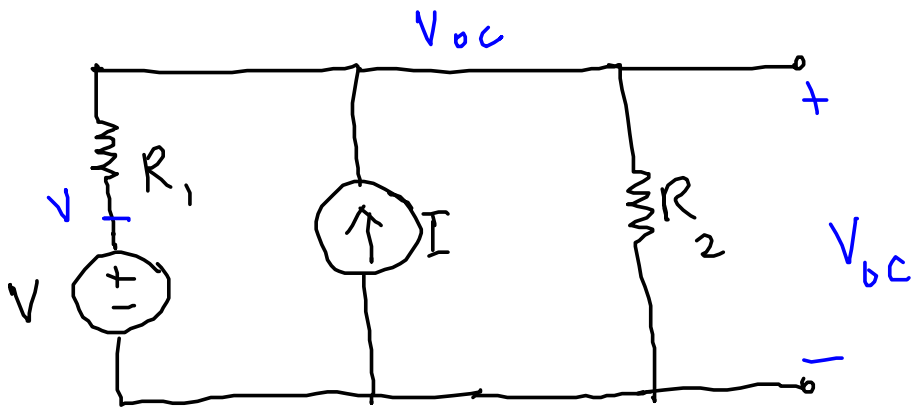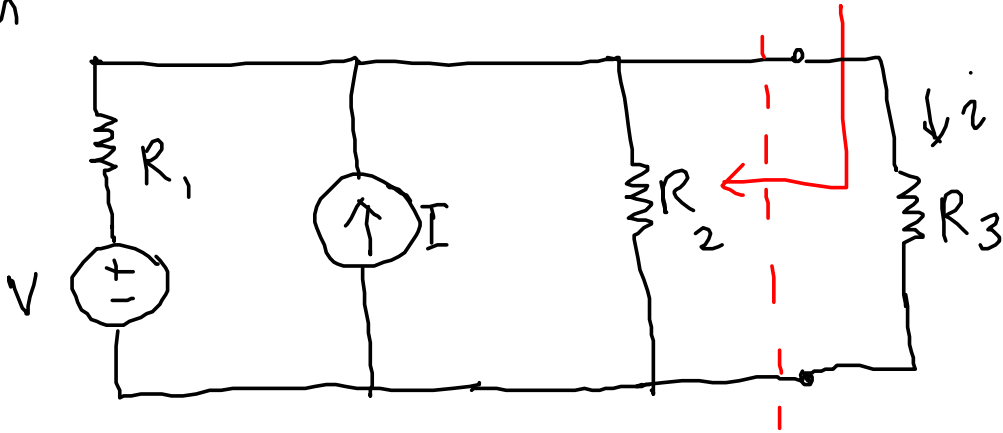


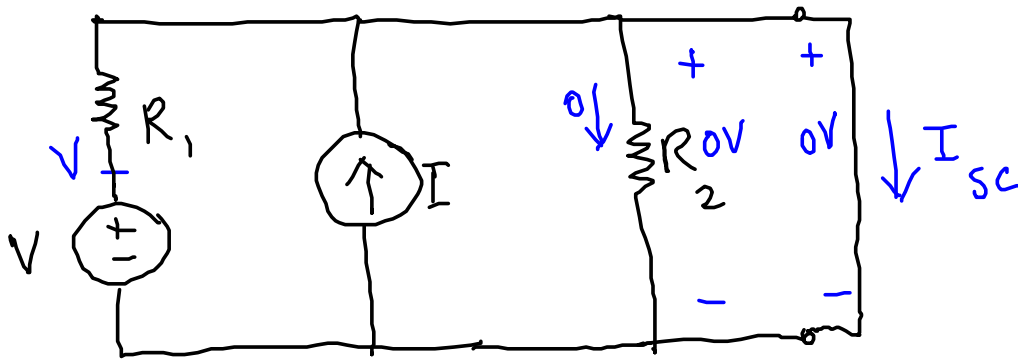
$$\frac{V - V_{oc}}{R_1} + I + \frac{0 - V_{oc}}{R_2} = 0 \quad \text{find } V_{oc}$$



$$I_{sc} = \frac{V - 0}{R_1} + I$$


Problem

T & N eq.

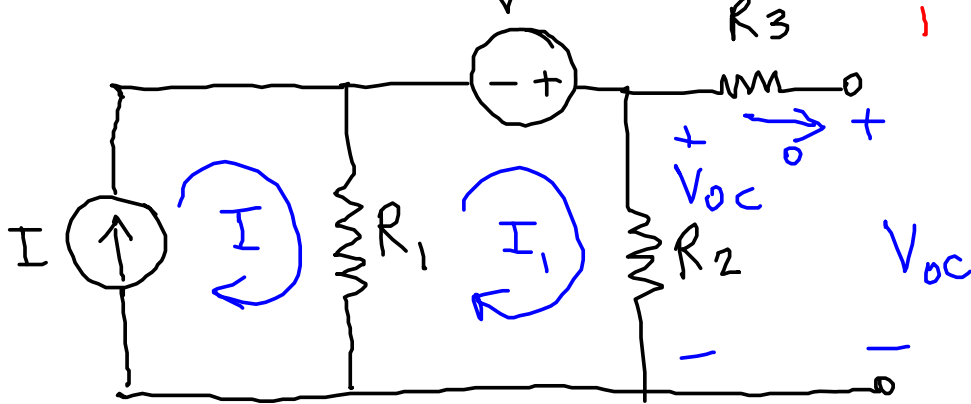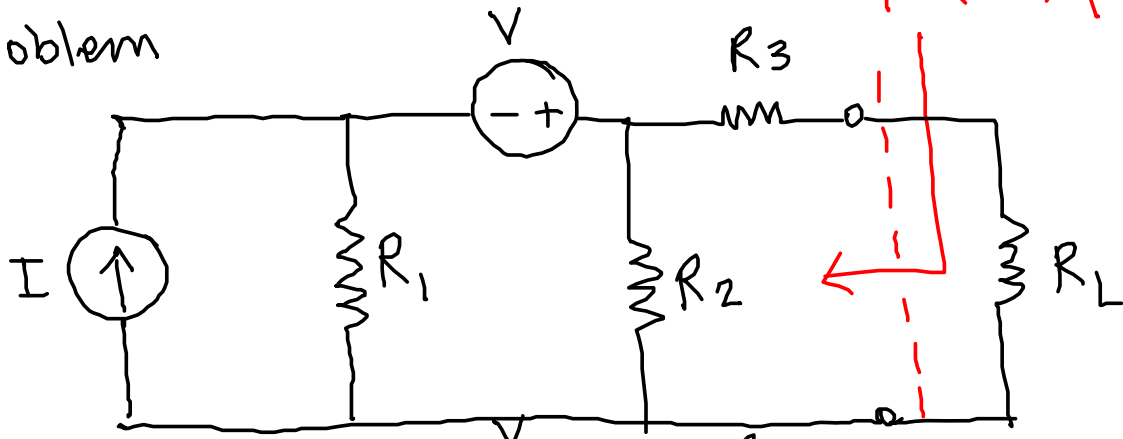

$$R_1(I_1 - I) - V + R_2 I_1 = 0 \quad \text{find } I_1$$



$$V_{oc} = R_2 I_1$$

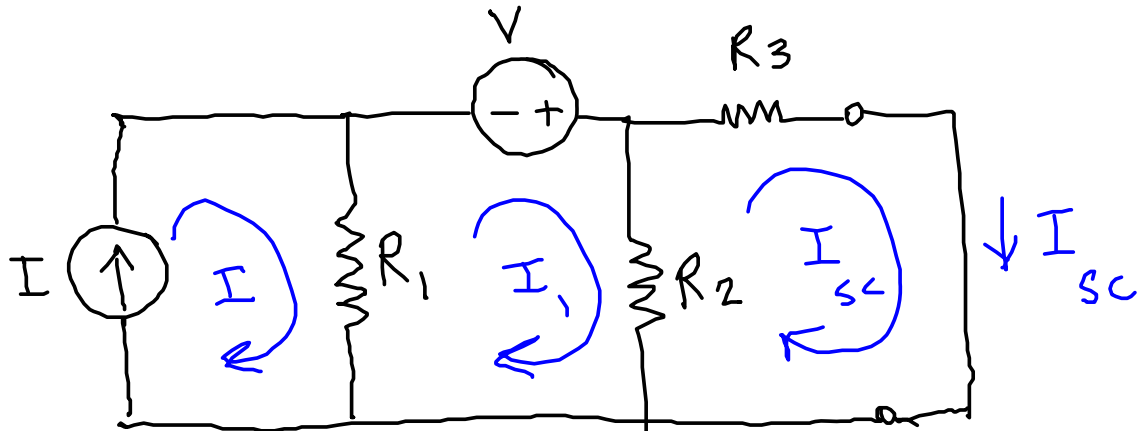

$$R_1(I_1 - I) - V + R_2(I_1 - I_{sc}) = 0$$


$$R_3 I_{sc} + R_2(I_{sc} - I_1) = 0 \quad \text{find } I_{sc}$$

Problem

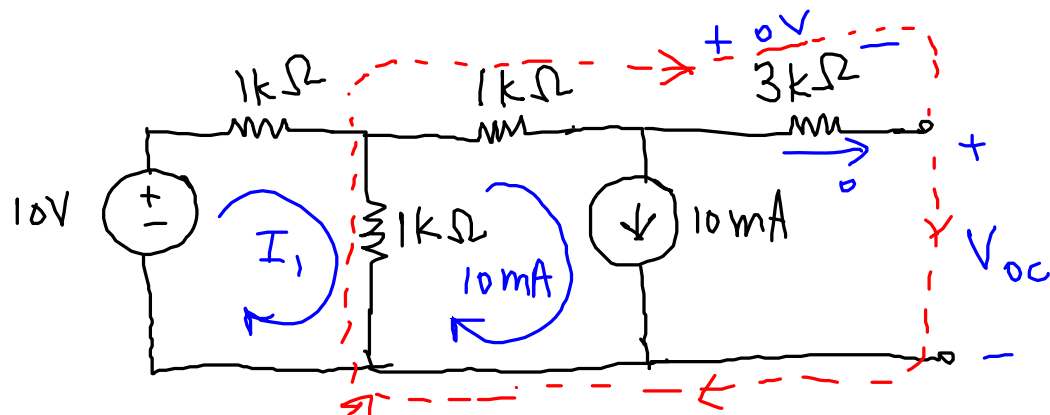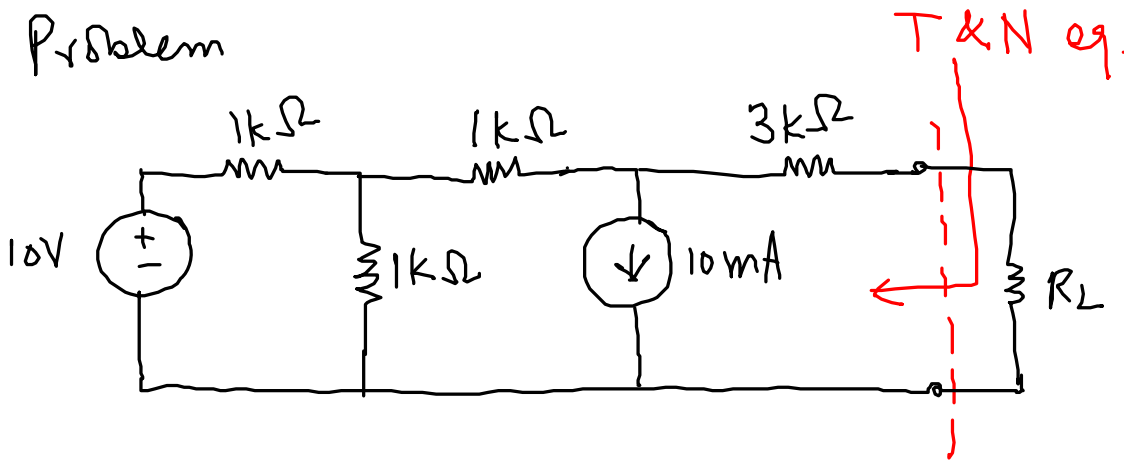

$$-10V + 1k\Omega I_1 + 1k\Omega (I_1 - 10mA) = 0 \quad \text{find } I_1$$
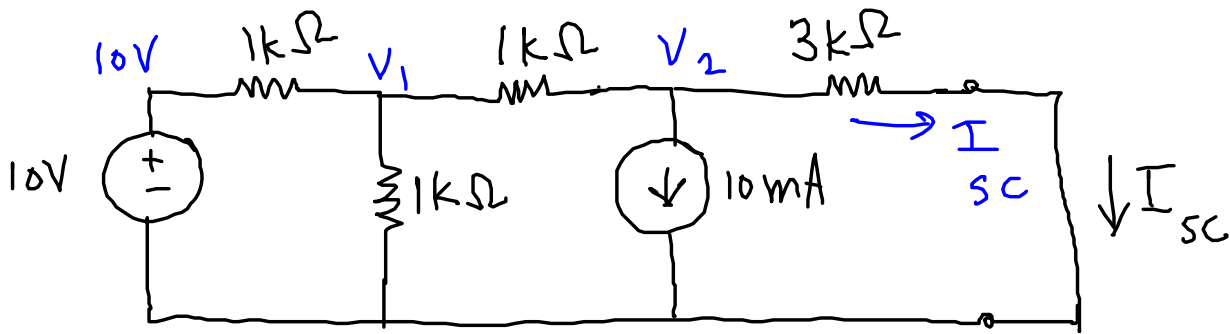
$$V_{oc} + 1k\Omega (10mA - I_1) + 1k\Omega (10mA) = 0 \quad \text{find } V_{oc}$$



$$\frac{10V - V_1}{1k\Omega} + \frac{0 - V_1}{1k\Omega} + \frac{V_2 - V_1}{1k\Omega} = 0$$

$$\frac{V_1 - V_2}{1k\Omega} - 10mA + \frac{0 - V_2}{3k\Omega} = 0 \quad \text{find } V_1 \text{ \& } V_2$$

$$I_{sc} = \frac{V_2 - 0}{3k\Omega}$$