
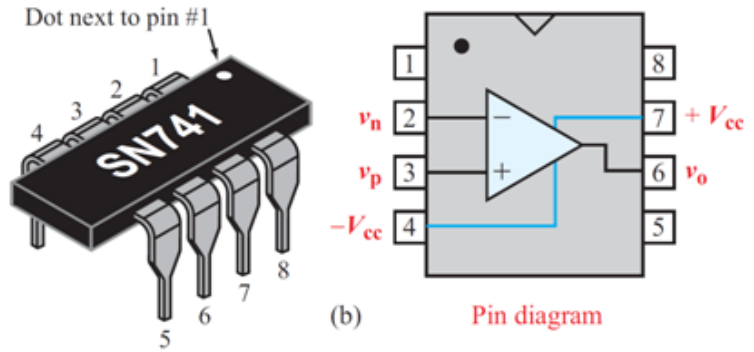


Operational Amplifier “Op Amp”

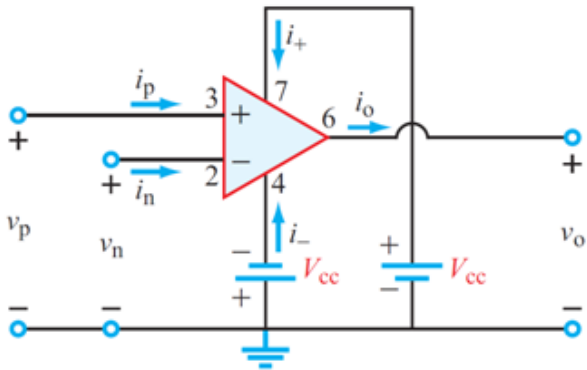
- Two input terminals, positive (non-inverting) and negative (inverting)
- One output
- Power supply $+V_{cc}$ and $-V_{cc}$



Op Amp showing power supply




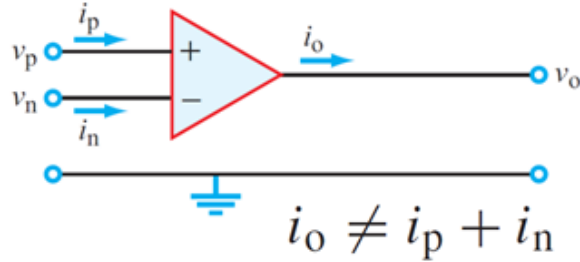Op Amp with power supply not shown (which is how we usually display op amp circuits)




Inside The Op-Amp (741)

Schematic Diagram

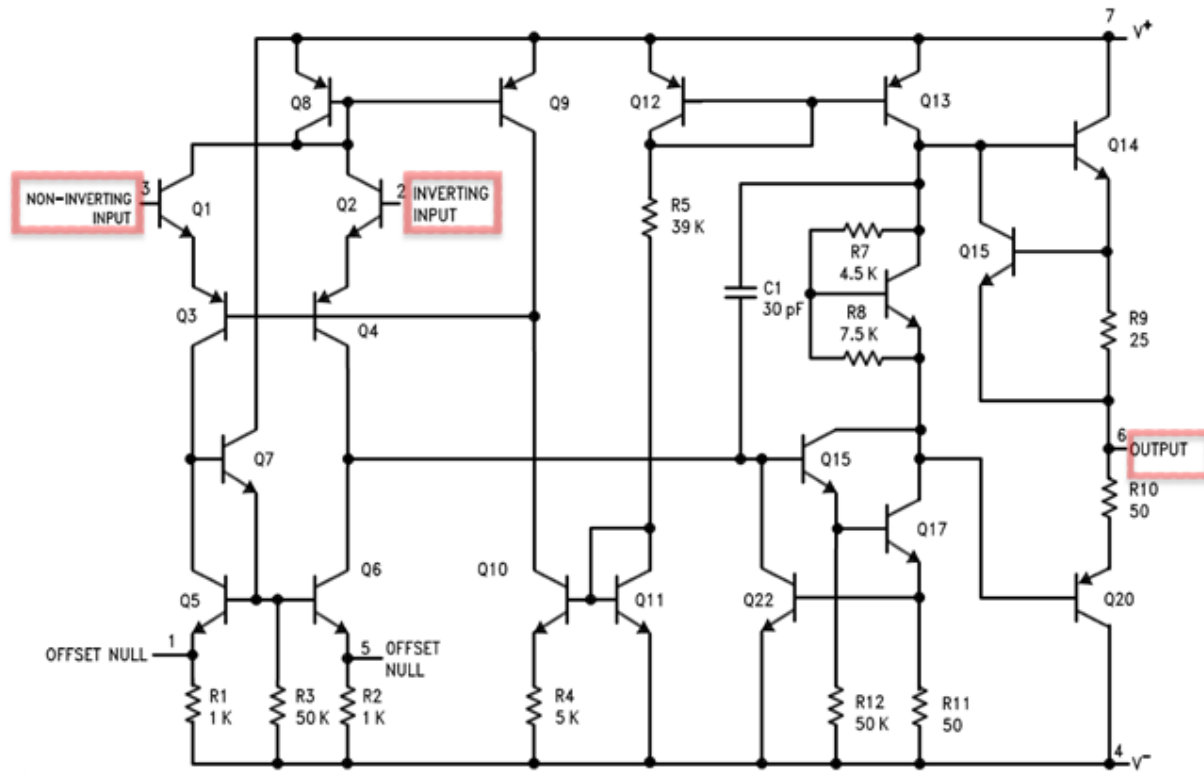


Gain


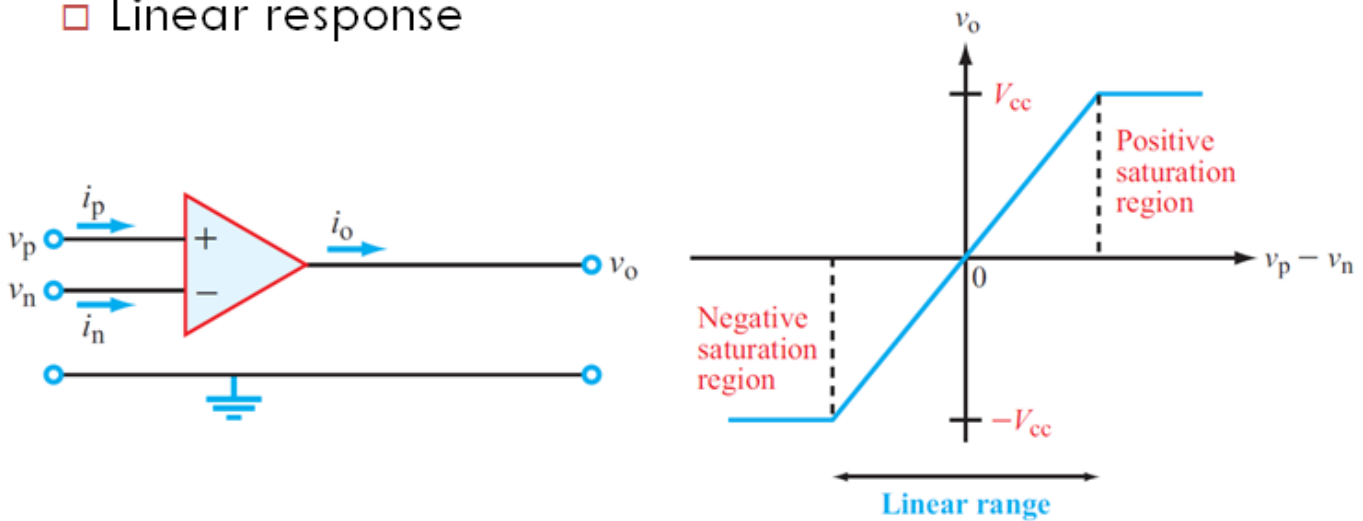
- Key important aspect of op amp: **high voltage gain**
- Output $v_o = A(v_p - v_n)$ **op-amp gain** (or **open-loop gain**) – different from **circuit gain G**
- Linear response



Equivalent Circuit

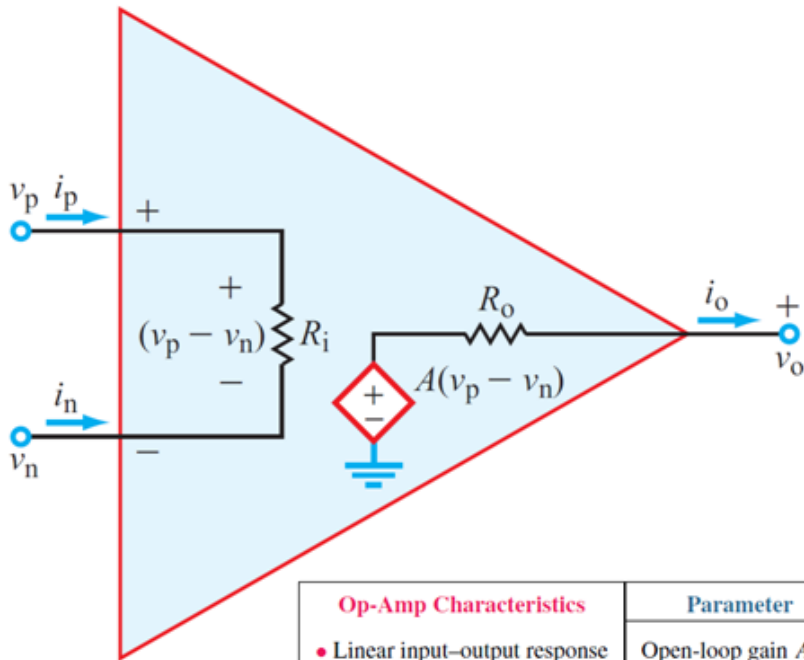

Op-Amp Characteristics	Parameter	Typical Range	Ideal Op Amp
• Linear input–output response	Open-loop gain A	10^4 to 10^8 (V/V)	∞
• High input resistance	Input resistance R_i	10^6 to 10^{13} Ω	∞ Ω
• Low output resistance	Output resistance R_o	1 to 100 Ω	0 Ω
• Very high gain	Supply voltage V_{cc}	5 to 24 V	As specified by manufacturer

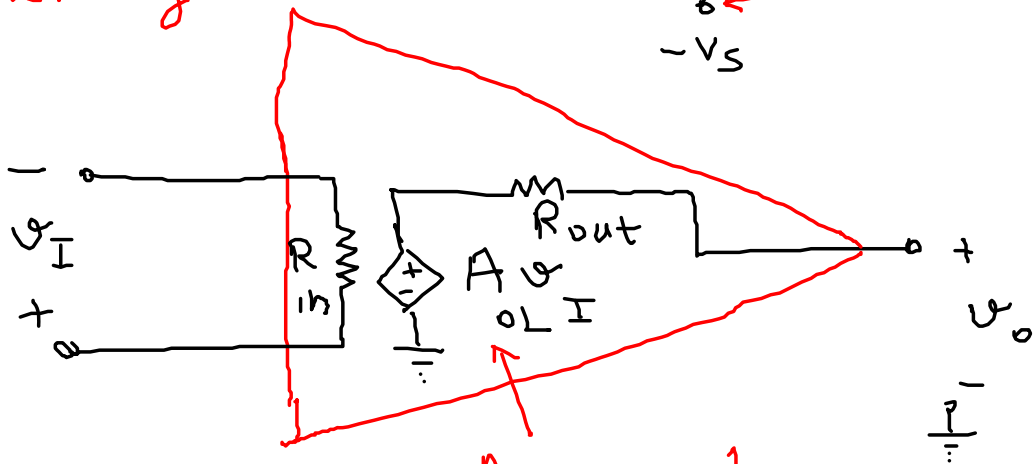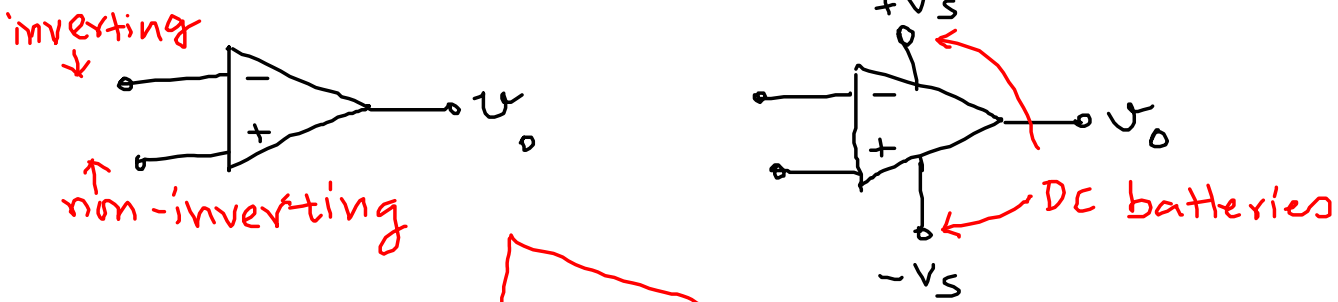


A_{OL} : open Loop gain

ideal op-amp

$$R_{in} \rightarrow \infty$$

$$R_{out} \rightarrow 0$$

$$A_{OL} \rightarrow \infty$$

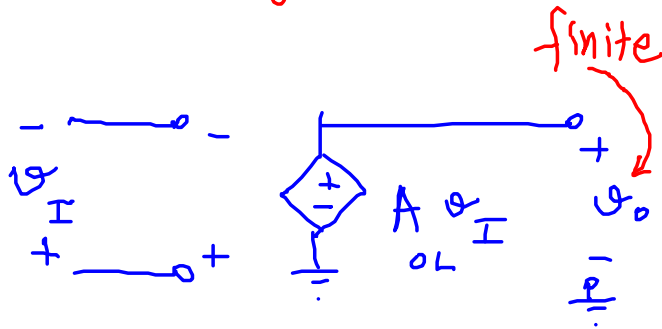


$$v_o = A_{OL} v_I$$


$$\text{finite} = \infty \cdot v_I$$

$$v_I \rightarrow 0$$

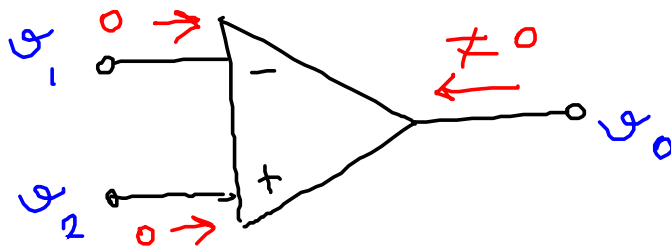\therefore if $v_o = \text{finite}$
then $v_I = 0$ (virtual short)




$v_1 = v_2$ (virtual short)

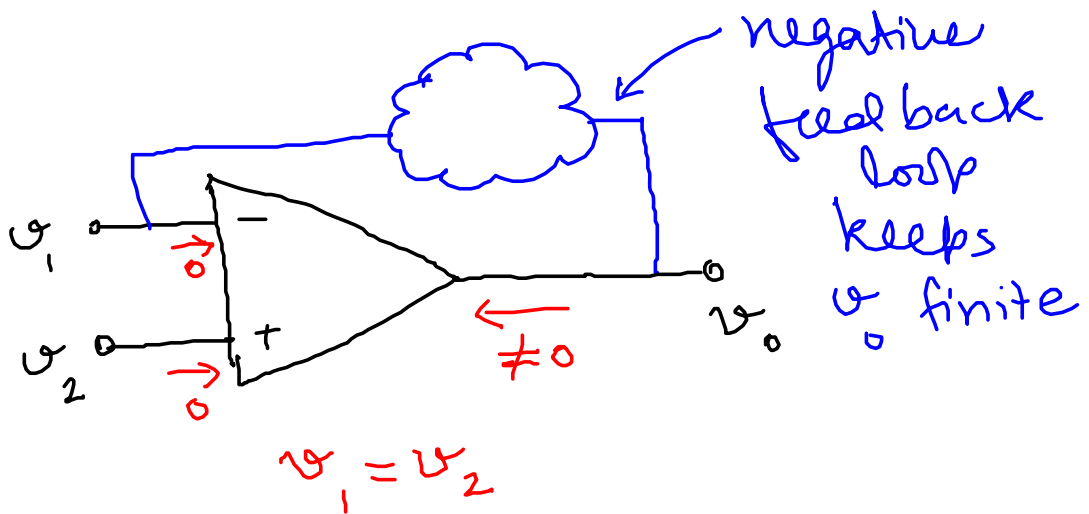

$v_1 = v_2$

The inverting Amp :

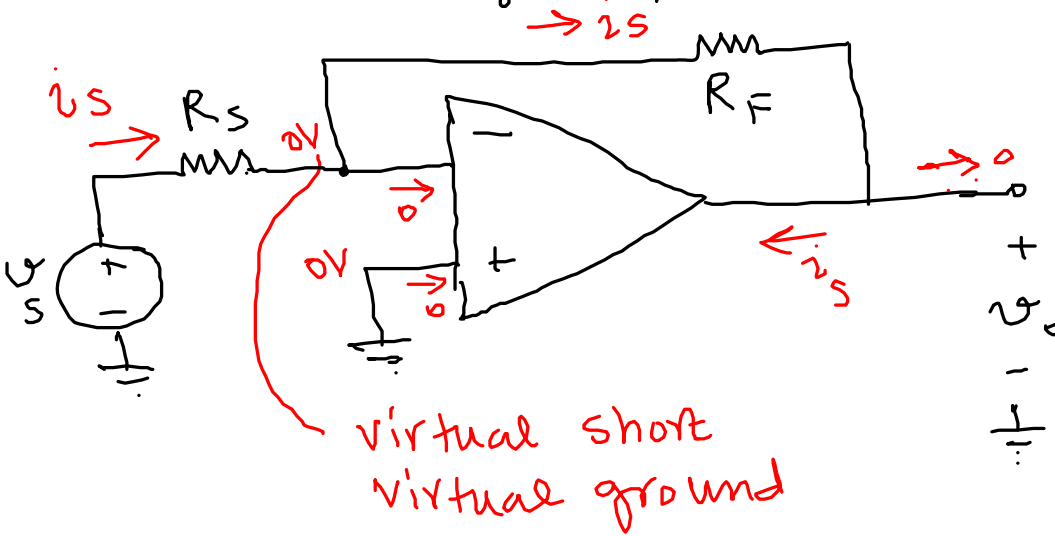


closed loop gain $\frac{v_o}{v_s} = ?$

$$\frac{v_s - 0V}{R_s} = \frac{0V - v_o}{R_f}$$

$$\frac{v_o}{v_s} = -\frac{R_f}{R_s}$$
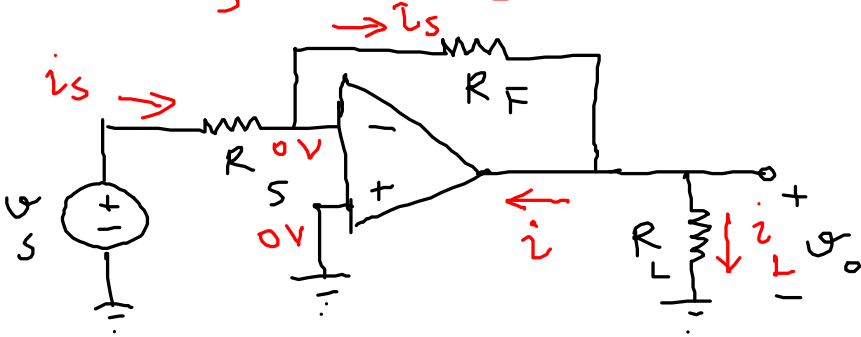
$$i_s = \frac{v_s - 0}{R_s} = \frac{v_s}{R_s}$$




$$\frac{v_s - 0V}{R_s} = \frac{0V - v_o}{R_f} \Rightarrow \frac{v_o}{v_s} = -\frac{R_f}{R_s}$$

$$i_s = \frac{v_s - 0}{R_s} = \frac{v_s}{R_s}$$

$$i_L = \frac{v_o}{R_L} = -\frac{1}{R_L} \frac{R_f}{R_s} v_s$$

Summing Amp

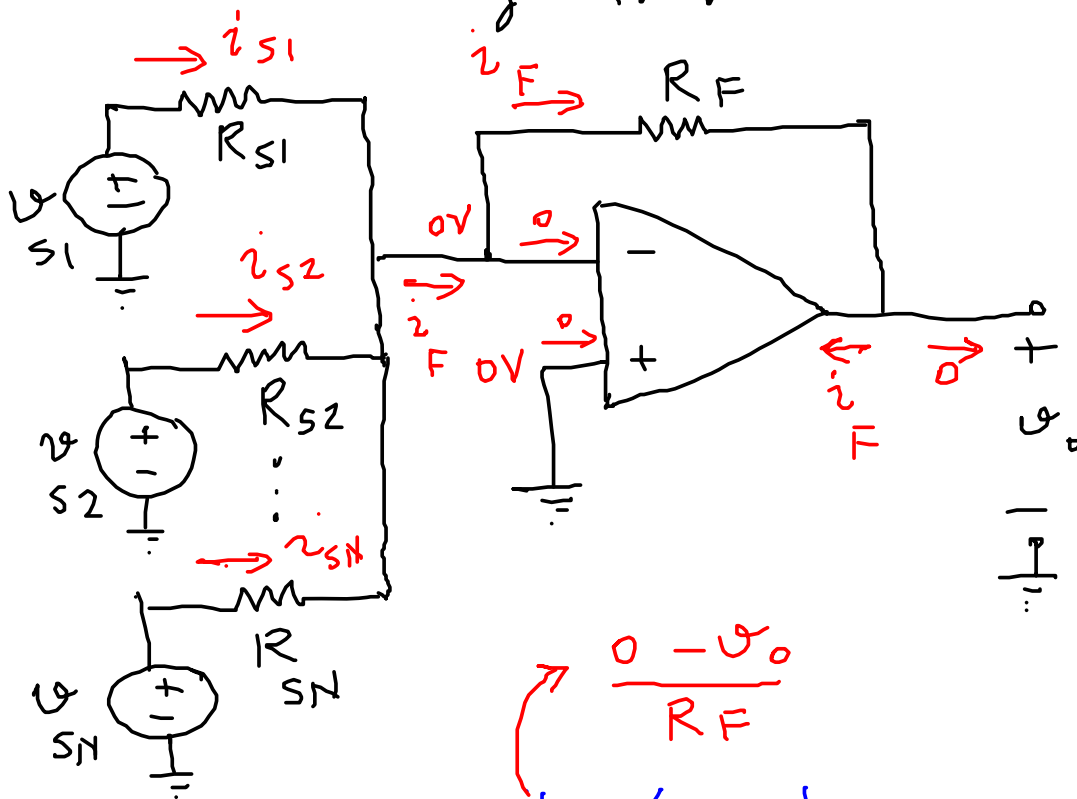


$$i_F = i_{S1} + i_{S2} + \dots + i_{SN}$$

$$\frac{0 - v_o}{R_F} = \frac{v_{S1} - 0}{R_{S1}} + \frac{v_{S2} - 0}{R_{S2}} + \dots + \frac{v_{SN} - 0}{R_{SN}}$$

$$-\frac{v_o}{R_F} = \frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \dots + \frac{v_{SN}}{R_{SN}}$$

$$v_o = -R_F \left[\frac{v_{S1}}{R_{S1}} + \frac{v_{S2}}{R_{S2}} + \dots + \frac{v_{SN}}{R_{SN}} \right]$$

The non-inverting amp

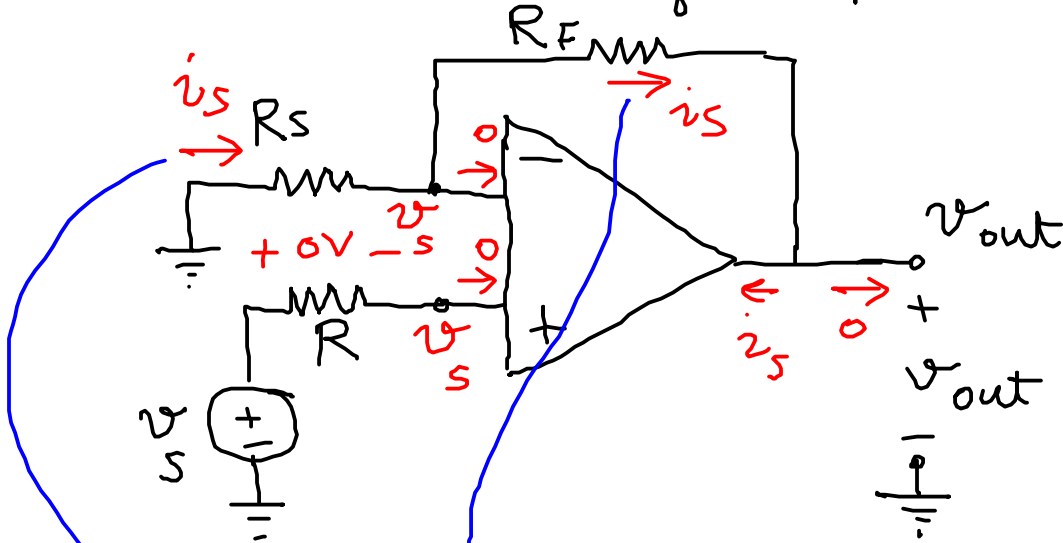


$$\frac{0 - v_s}{R_S} = \frac{v_s - v_{out}}{R_F}$$

$$\frac{v_{out}}{v_s} = 1 + \frac{R_F}{R_S}$$

Voltage Follower


$$R_S \rightarrow \infty, R_F = 0$$

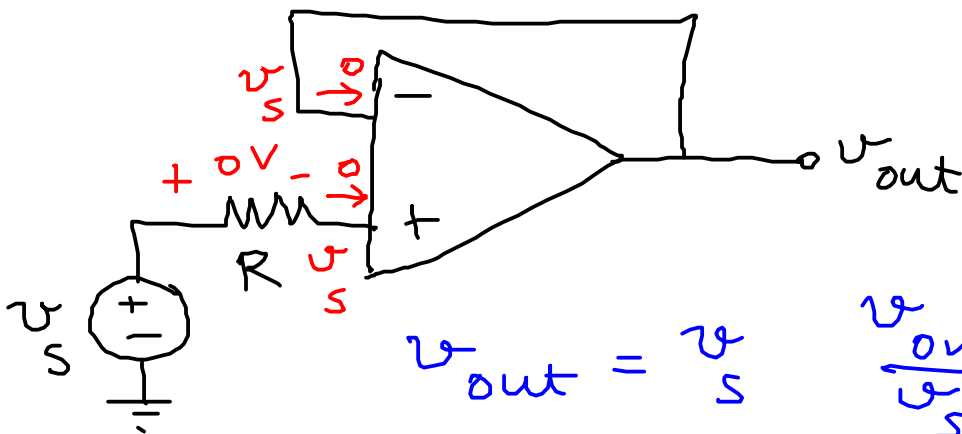


$$v_{out} = v_s$$

$$\frac{v_{out}}{v_s} = 1$$


note: $v_{out} = v_s$ independent of R_L

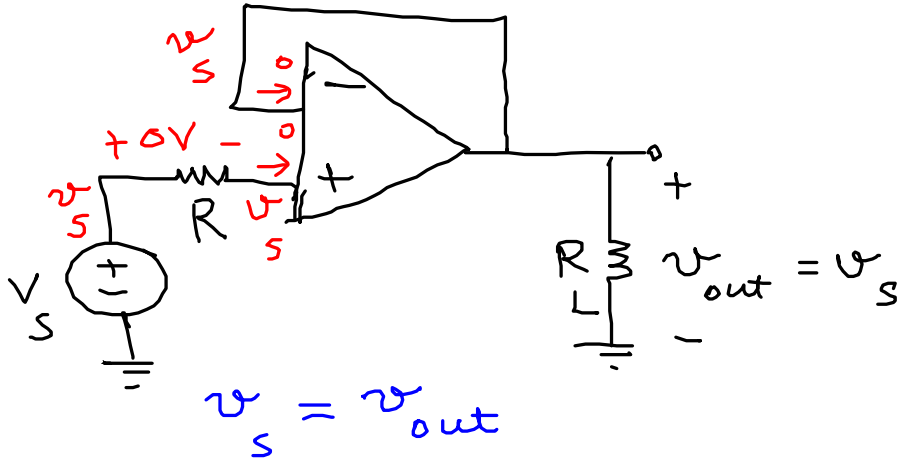


unlike here

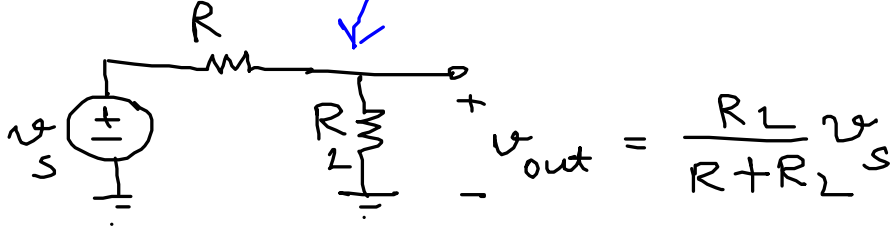

Differential Amp

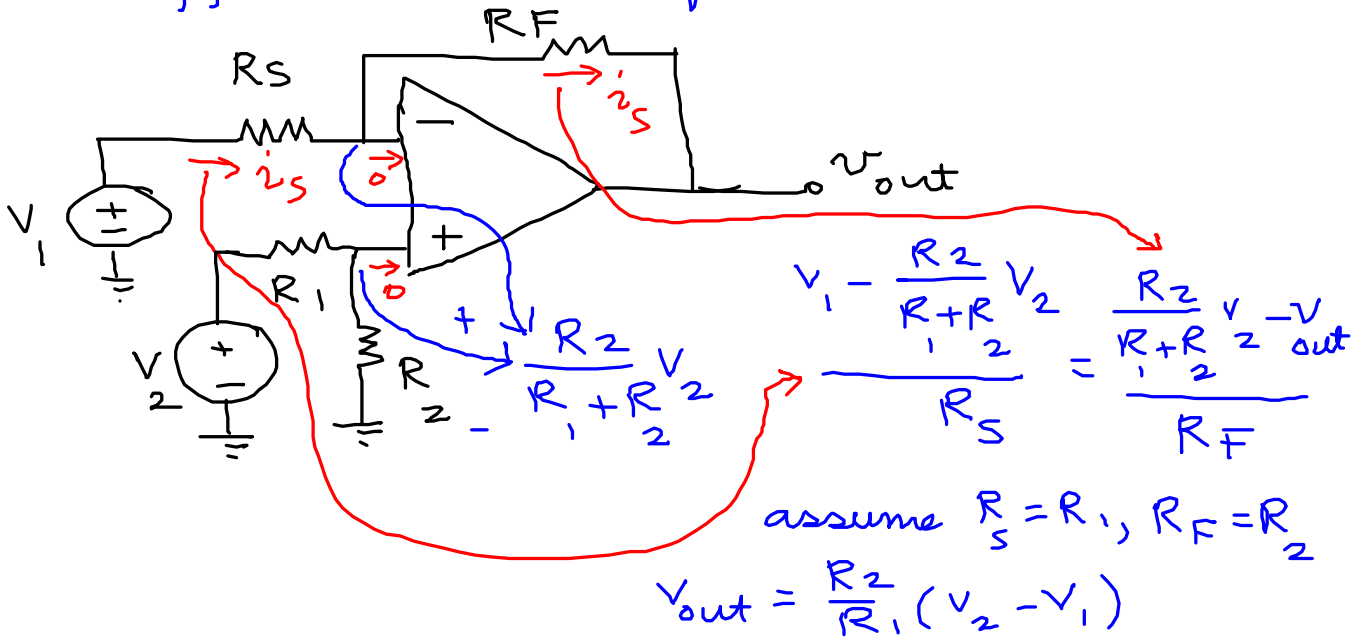

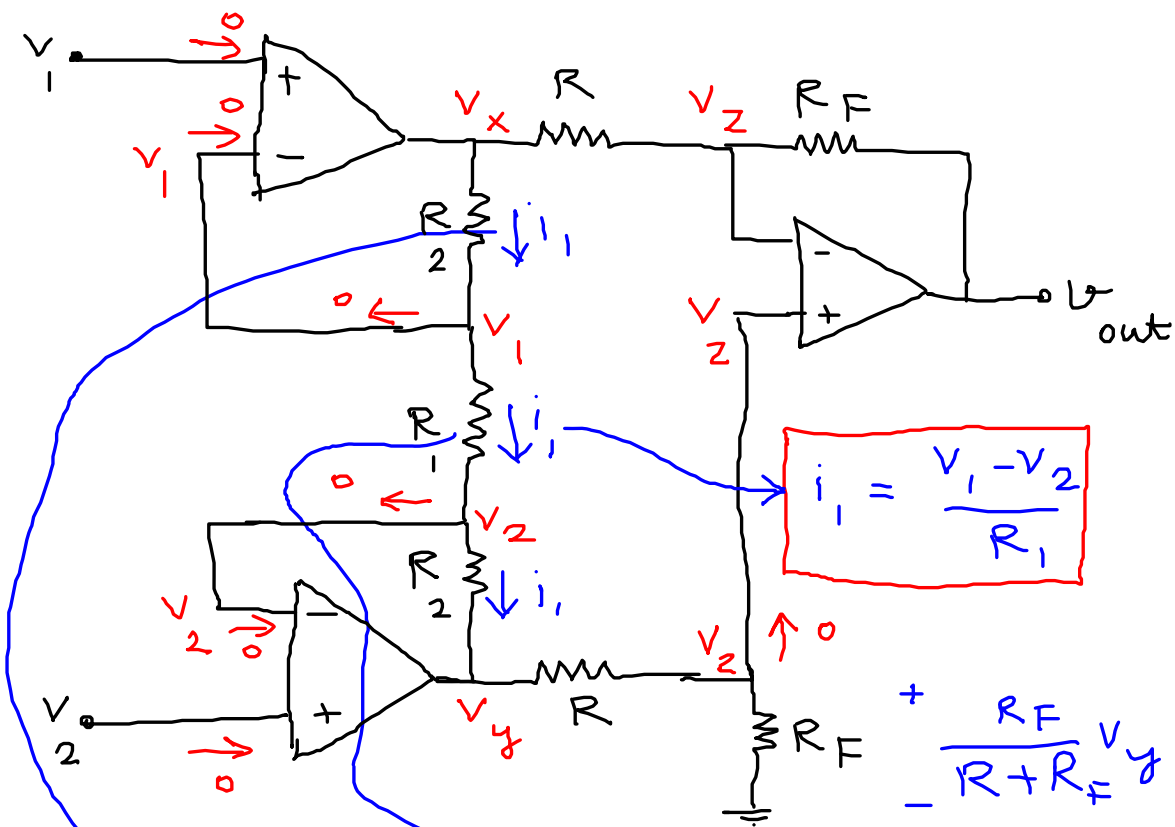

$$\frac{V_x - V_1}{R_2} = \frac{V_1 - V_2}{R_1}$$

$$\frac{V_1 - V_2}{R_1} = \frac{V_2 - V_y}{R_2}$$


$$V_x = \left(1 + \frac{R_2}{R_1}\right)V_1 - \frac{R_2}{R_1}V_2$$

$$V_y = \left(1 + \frac{R_2}{R_1}\right)V_2 - \frac{R_2}{R_1}V_1$$

$$V_z = \frac{R_F}{R + R_F}V_y$$

$$\frac{V_{out} - V_z}{R_F} = \frac{V_z - V_x}{R}$$

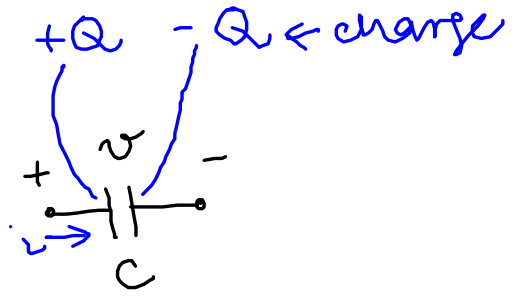
$$V_{out} = \frac{R_F}{R} \left(1 + \frac{2R_2}{R_1}\right) (V_2 - V_1)$$



$$i = C \frac{dv}{dt}$$

$$C = \frac{Q}{v}$$

Ideal Integrator


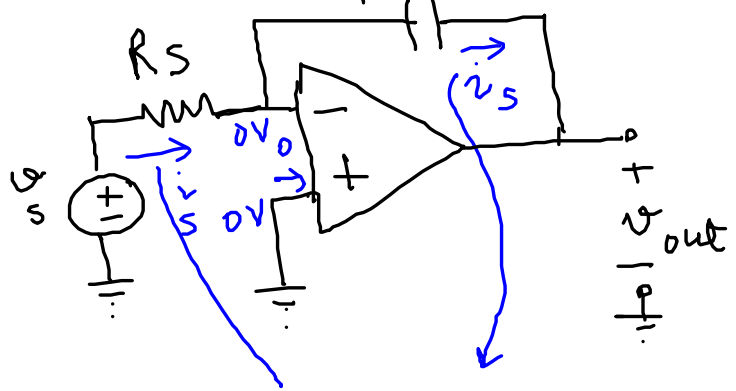


$$\frac{v_s - 0}{R_s} = C_F \frac{d}{dt} [0 - v_{out}(t)]$$


$$v_s(t) = -R_s C_F \frac{dv_{out}(t)}{dt}$$

$$\int_{-\infty}^t v_s(t') dt' = -R_s C_F \int_{-\infty}^t \frac{dv_{out}(t')}{dt'} dt'$$
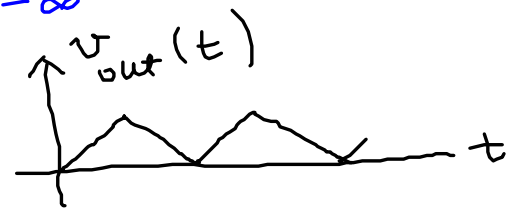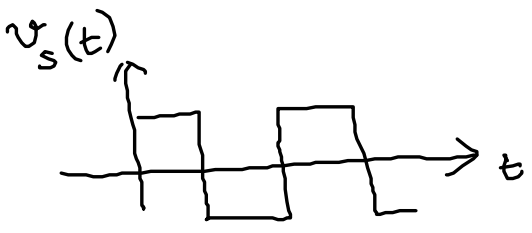
$$v_{out}(t) = -\frac{1}{R_s C_F} \int_{-\infty}^t v_s(t') dt'$$



Ideal Differentiator

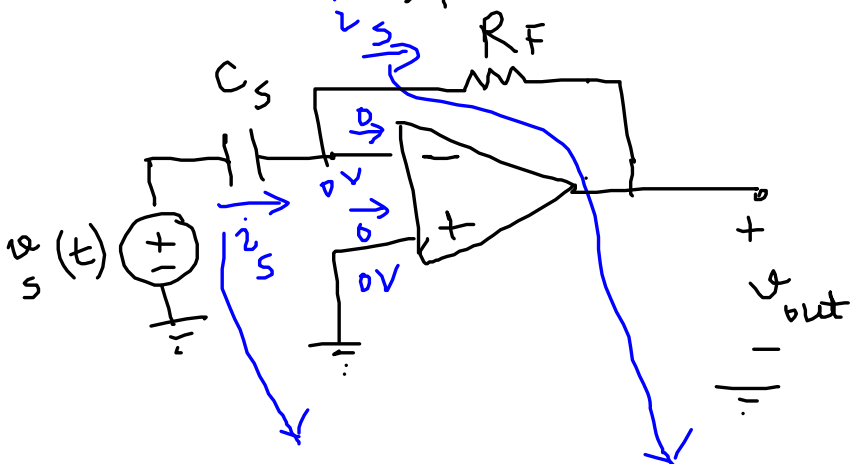

$$C \frac{d}{dt} [v_s(t) - 0] = \frac{0 - v_{out}}{R_F}$$

$$v_{out}(t) = -R_F C \frac{d}{dt} v_s(t)$$

