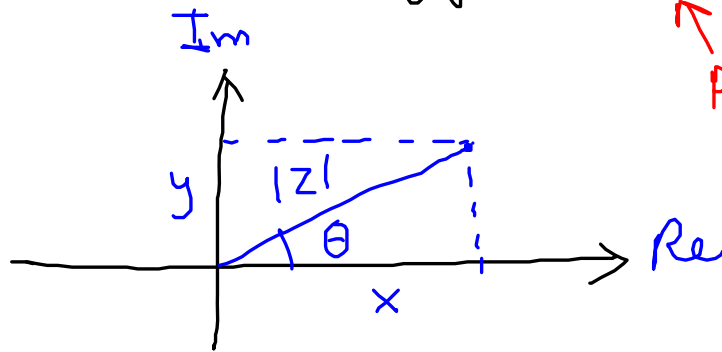


$$z = x + jy = |z| e^{j\theta} = |z| \angle \theta$$



rectangular to polar

$$|z| = \sqrt{x^2 + y^2}$$


$$\theta = \begin{cases} \tan^{-1}\left(\frac{y}{x}\right) & \text{if } (x > 0 \ \& \ y > 0) \text{ or } (x > 0 \ \& \ y \leq 0) \\ \tan^{-1}\left(\frac{y}{x}\right) - \pi & \text{if } (x < 0 \ \& \ y < 0) \\ \tan^{-1}\left(\frac{y}{x}\right) + \pi & \text{if } (x < 0 \ \& \ y \geq 0) \end{cases}$$

polar to rectangular

$$x = |z| \cos \theta$$

$$y = |z| \sin \theta$$


Convert to phasor land

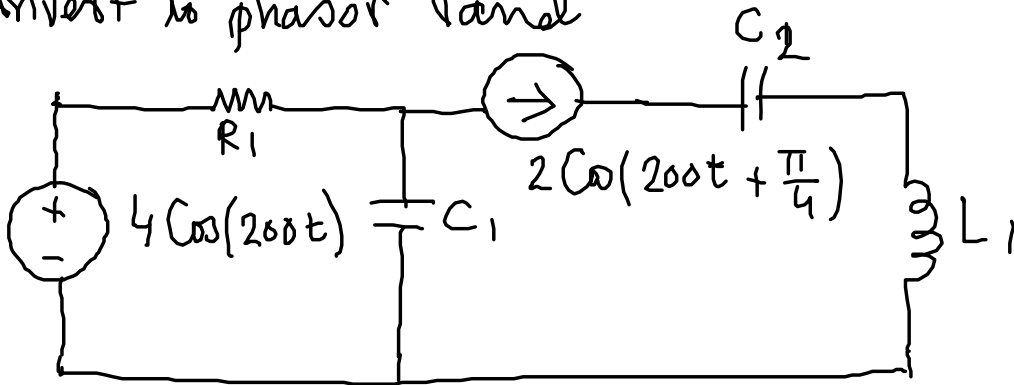


⇓

$$4 \cos(200t) \rightarrow 4 \angle 0$$
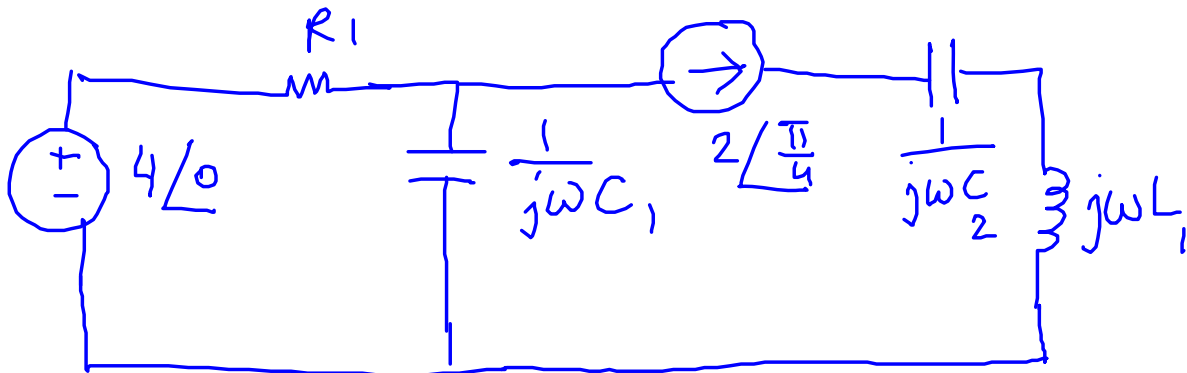
$$2 \cos(200t + \frac{\pi}{4}) \rightarrow 2 \angle \frac{\pi}{4} \quad \omega = 200$$



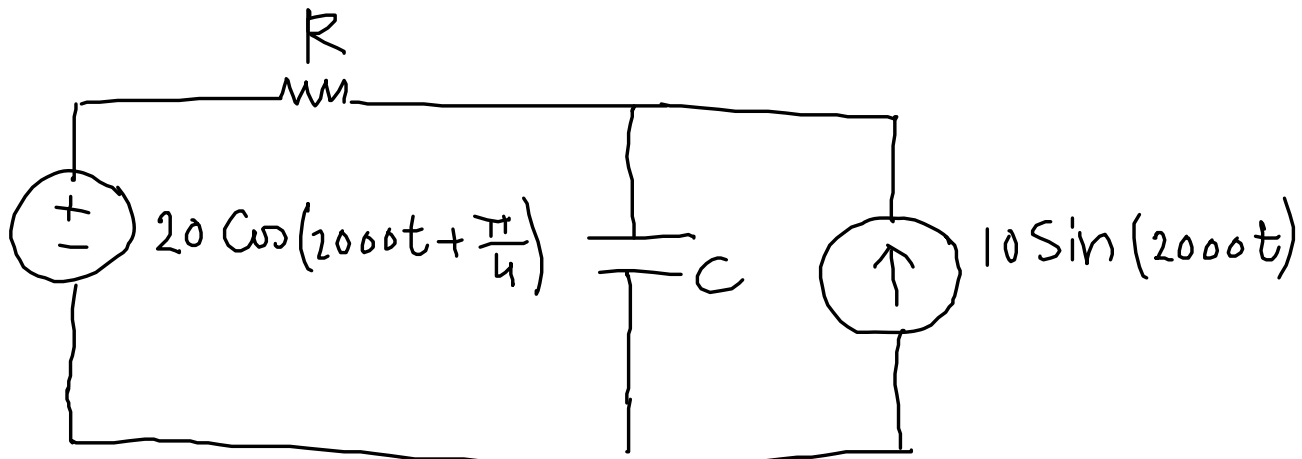Convert to frequency domain (phasor land)




$$\omega = 2000 \text{ rad/sec}$$


$$20 \cos(2000t + \frac{\pi}{4}) \rightarrow 20 \angle \frac{\pi}{4}$$

$$10 \sin(2000t) = 10 \cos(2000t - \frac{\pi}{2}) \rightarrow 10 \angle -\frac{\pi}{2}$$


$$-\frac{\pi}{2} = \frac{3\pi}{2}$$

$$10 \angle \frac{3\pi}{2}$$

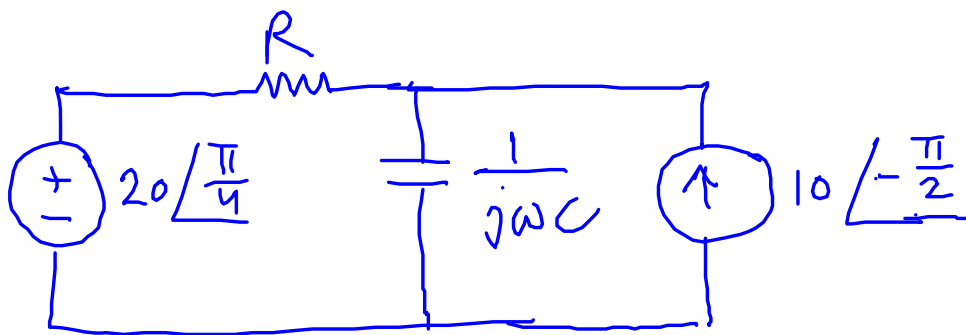

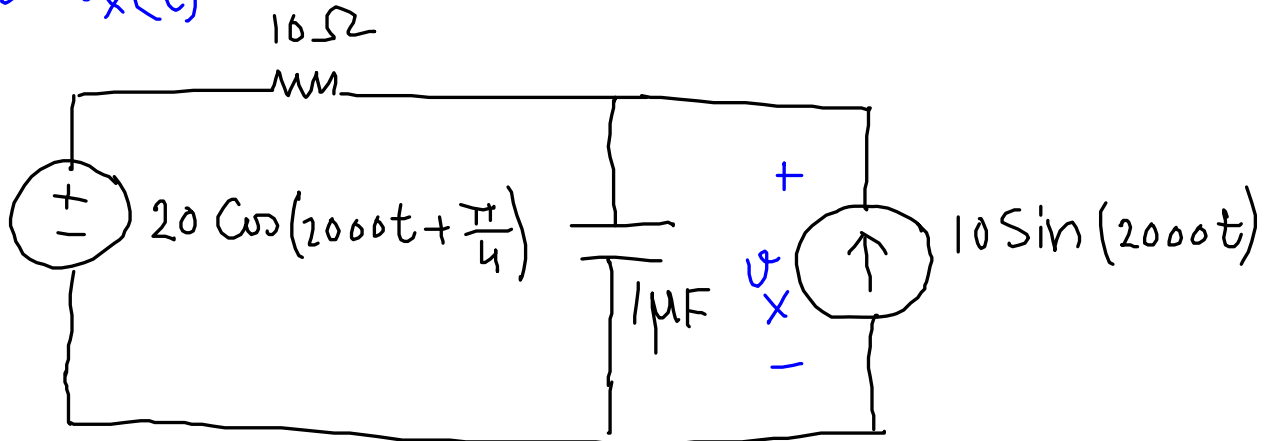Find $v_x(t)$ 

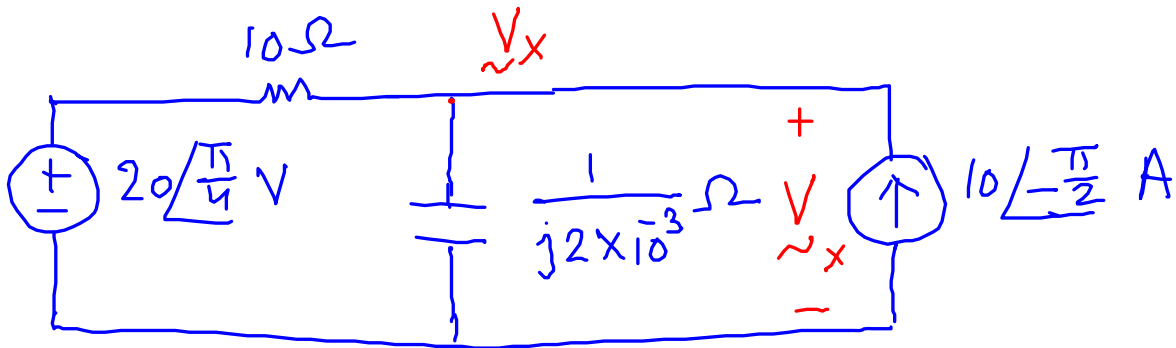$\omega = 2000$ rad/s \Downarrow phasor land



node analysis

$$\frac{20 \angle \frac{\pi}{4} - v_x}{10 \Omega} + \frac{0 - v_x}{\frac{1}{j2 \times 10^{-3}} \Omega} + 10 \angle -\frac{\pi}{2} = 0$$

$$2 \angle \frac{\pi}{4} - 0.1 v_x - j2 \times 10^{-3} v_x + 10 \angle -\frac{\pi}{2} = 0$$

$$v_x (0.1 + j2 \times 10^{-3}) = 2 \angle \frac{\pi}{4} + 10 \angle -\frac{\pi}{2}$$

$$\underline{V}_X(0.1 + j2 \times 10^{-3}) = 2 \angle \frac{\pi}{4} + 10 \angle -\frac{\pi}{2}$$

$$\underline{V}_X = \frac{2 \angle \frac{\pi}{4} + 10 \angle -\frac{\pi}{2}}{0.1 + j2 \times 10^{-3}}$$

$$= \frac{2 \left(\cos \frac{\pi}{4} + j \sin \frac{\pi}{4} \right) + 10 \left(\cos \frac{\pi}{2} + j \sin \left(-\frac{\pi}{2} \right) \right)}{0.1 + j2 \times 10^{-3}}$$

$$\begin{aligned} &\downarrow \\ &\sin \left(-\frac{\pi}{2} \right) \\ &= -\sin \frac{\pi}{2} \\ &= -1 \end{aligned}$$

$$= \frac{2(0.707 + j0.707) + 10(0 - j)}{0.1 + j2 \times 10^{-3}}$$

$$= \frac{1.414 + j1.414 - 10j}{0.1 + j2 \times 10^{-3}}$$

$$= \frac{1.414 - j8.586}{0.1 + j2 \times 10^{-3}}$$

$$= \frac{1.414 - j8.586}{0.1 + j2 \times 10^{-3}}$$

$$= \frac{\sqrt{(1.414)^2 + (8.586)^2} \tan^{-1}\left(\frac{-8.586}{1.414}\right)}{\sqrt{(0.1)^2 + (2 \times 10^{-3})^2} \tan^{-1}\left(\frac{2 \times 10^{-3}}{0.1}\right)}$$

$$= \frac{\sqrt{75.7} \angle -1.4}{\sqrt{0.010004} \angle 0.0199} = \frac{\sqrt{75.7} \angle -1.4 - 0.02}{\sqrt{0.01}}$$


$$\underline{V}_x = 87 \angle -1.42 \text{ V} = 87 \angle -81.36^\circ \text{ V}$$

$$\underline{V}_x = 87 e^{-j1.42} \text{ V}$$

↓ real domain


$$v_x(t) = \text{Re} \left[e^{j2000t} 87 e^{-j1.42} \right] \text{ V}$$
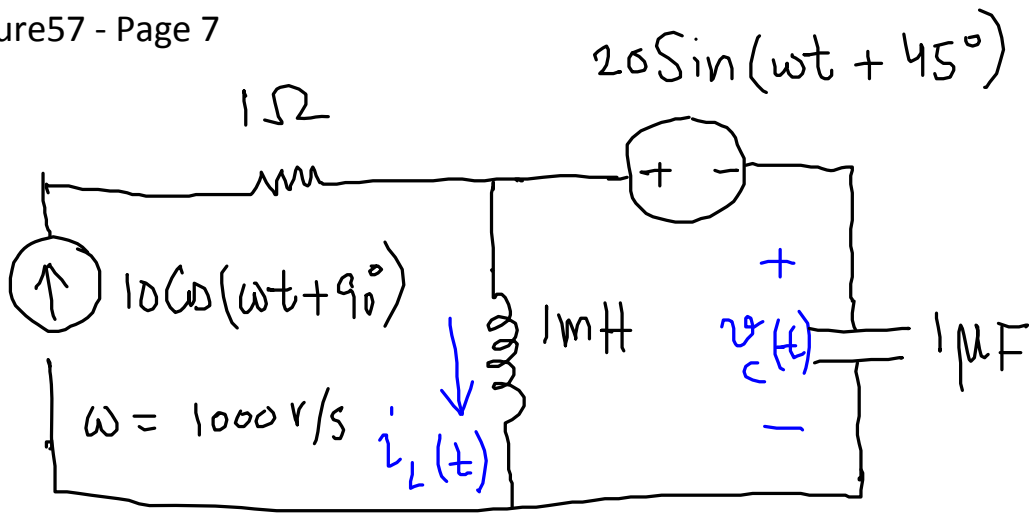
$$v_x(t) = 87 \cos(2000t - 81.36^\circ) \text{ V}$$



determine $i_L(t)$ & $v_C(t)$

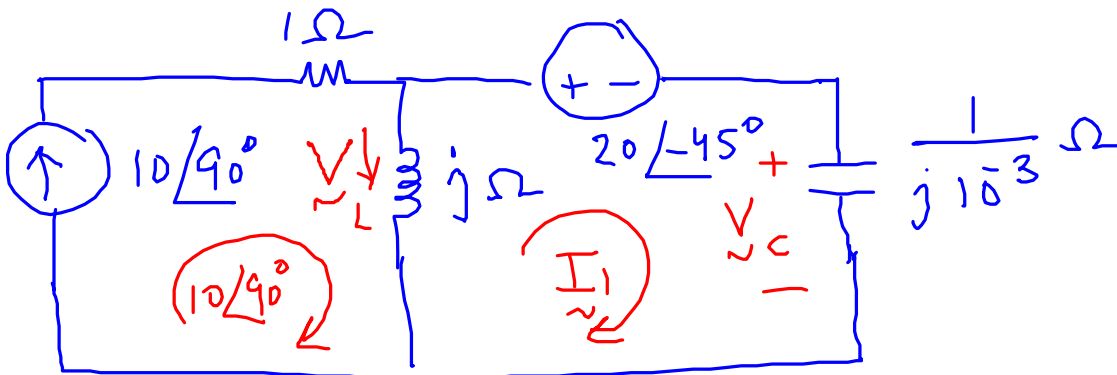phasor level $\sin(\omega t + 45) = \cos(\omega t - 45)$ $\frac{45^\circ - 90^\circ}{1}$



Note!
this should have been $j10\angle 90^\circ$

$$j\Omega(I_1 - 10\angle 90^\circ) + 20\angle -45^\circ + \frac{1}{j10^3}I_1 = 0$$

$$I_1(j - j10^3) = 10\angle 90^\circ - 20\angle -45^\circ$$

Note!
this should have been -999

$$j0.999 I_1 = 10[\cos 90 + j\sin 90] - 20[\cos(-45) + j\sin(-45)]$$

$$\begin{aligned}
 j0.999 \underline{\underline{I}}_1 &= 10 [\cos 90 + j \sin 90] \\
 &\quad - 20 [\cos(-45) + j \sin(-45)] \\
 &= 10 [0 + j] - 20 [0.707 - j 0.707] \\
 &= 10j - 14.14 + j 14.14
 \end{aligned}$$

$$j0.999 \underline{\underline{I}}_1 = -14.14 + j 24.14 \quad x < 0 \quad y > 0$$

$$\underline{\underline{I}}_1 = \frac{\sqrt{(14.14)^2 + (24.14)^2} / \tan^{-1}\left(-\frac{24.14}{14.14}\right) + 180^\circ}{0.999 \angle 90^\circ}$$

$$\frac{27.97 \angle -\tan^{-1}(1.707) + 180^\circ}{0.999 \angle 90^\circ}$$

$$\frac{27.97 \angle -59.64^\circ + 180^\circ}{0.999 \angle 90^\circ}$$

$$\frac{27.97 \angle 120.36^\circ}{0.999 \angle 90^\circ} = 27.99 \angle 120.36^\circ - 90^\circ$$

$$\underline{\underline{I}}_1 = 28 \angle 30.36^\circ$$

$$\begin{aligned}
 \underline{V}_L &= j\Omega (10 \angle 90^\circ - \underline{I}) \\
 &= j\Omega (10 \angle 90^\circ - 28 \angle 30.36^\circ) \\
 &= 1 \angle 90^\circ \left[10(\cos 90^\circ + j \sin 90^\circ) \right. \\
 &\quad \left. - 28(\cos(30.36^\circ) + j \sin(30.36^\circ)) \right]
 \end{aligned}$$

$$\begin{aligned}
 &= 1 \angle 90^\circ [10j - 28(\cos(30.36^\circ) + j \sin(30.36^\circ))] \\
 &= 1 \angle 90^\circ [10j - 28(0.863 + j0.505)] \\
 &= 1 \angle 90^\circ [10j - 24.16 - j14.14] \text{ A} \\
 &= 1 \angle 90^\circ [-24.16 + j4.14] \text{ A} \quad \begin{matrix} x < 0 \\ y > 0 \end{matrix}
 \end{aligned}$$

$$= 1 \angle 90^\circ \left[\sqrt{(24.16)^2 + (4.14)^2} \angle \tan^{-1} \frac{4.14}{24.16} + 180^\circ \right]$$

$$= (1 \angle 90^\circ) (24.51 \angle -9.72^\circ + 180^\circ)$$

$$= (1 \angle 90^\circ) (24.51 \angle 170.28^\circ)$$

$$\underline{V}_L = 24.51 \angle 90^\circ + 170.28^\circ = 24.51 \angle 260.28^\circ$$

$$\underline{V}_L = 24.51 \angle 260.28^\circ \text{ V}$$

$$\underline{V}_C = \underline{I} \frac{1}{j10^{-3}} = \frac{28 \angle 30.36^\circ}{10^{-3} \angle 90^\circ}$$

$$\underline{V}_C = 28 \times 10^3 \angle 30.36^\circ - 90.64^\circ$$

$$\underline{V}_C = 28 \times 10^3 \angle -59.64^\circ \quad \text{V}$$

↓ real time domain

$$\underline{V}_L = 24.51 \angle 260.28^\circ$$

↓

$$v_L(t) = 24.51 \cos(1000t + 260.28^\circ)$$

$$v_C(t) = 28 \times 10^3 \cos(1000t - 59.64^\circ) \text{ V}$$