

Problem



$$\omega = 3000 \text{ rad/sec}$$

$$j\omega L = j 3 \times 10^3 \times 190 \times 10^{-3} \Omega$$

$$= j570 \Omega$$


$$\frac{1}{j\omega C} = \frac{1}{j \cdot 3 \times 10^3 \times 55 \times 10^{-9} \text{ F}}$$
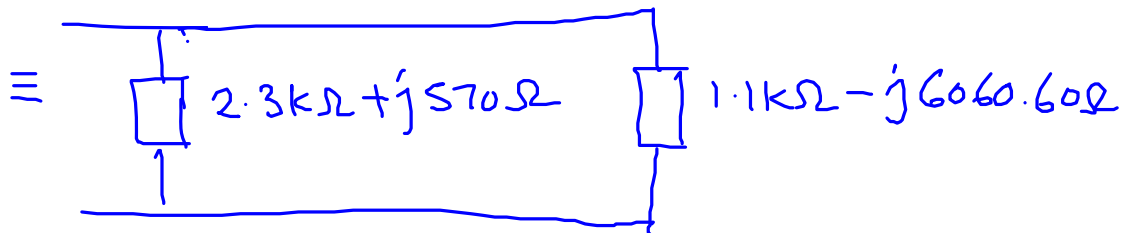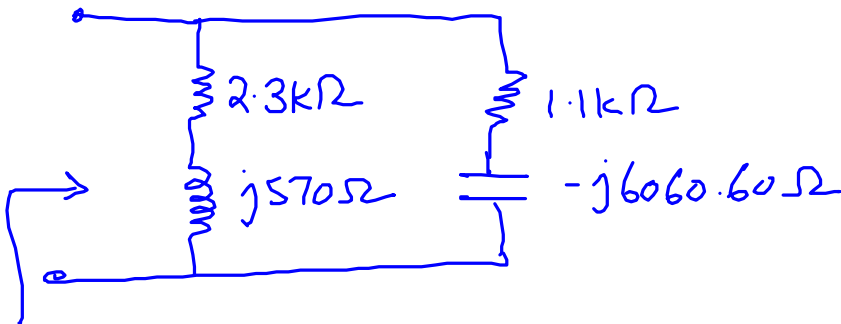
$$= \frac{-j}{165 \times 10^{-6}} \Omega = -j6060.60 \Omega$$



$$\frac{1}{Z_{eq}} = \frac{1}{2.3k\Omega + j570\Omega} + \frac{1}{1.1k\Omega - j6060.60\Omega}$$


Problem

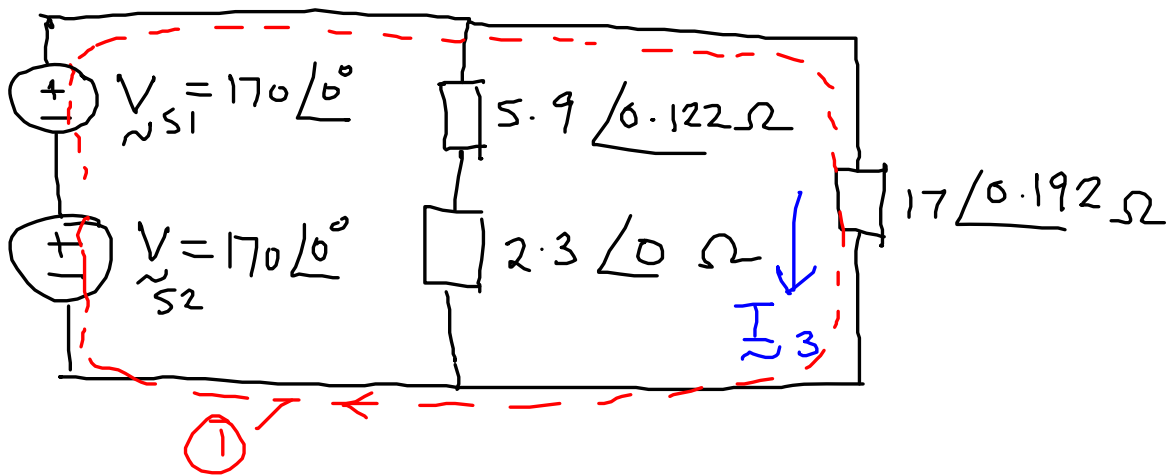

Loop ①:
$$\underline{I}_3 \cdot 17 \angle 0.192 - 170 \angle 0 - 170 \angle 0 = 0$$

$$\underline{I}_3 = \frac{340 \angle 0}{17 \angle 0.192}$$

Problem

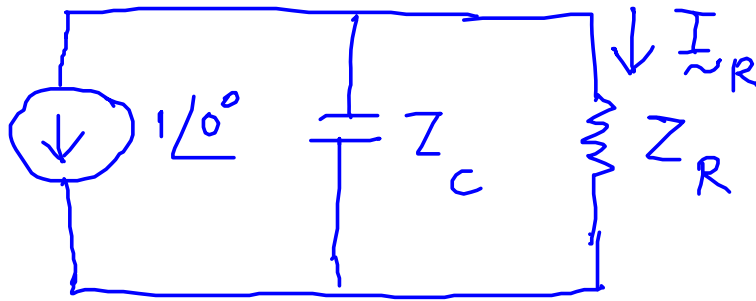

$$Z_C = \frac{1}{j(200\pi) 100 \times 10^{-6}} \Omega$$

\uparrow
 ω


$$Z_R = 100 \Omega$$

current division

$$\frac{I}{I_R} = \frac{\frac{1}{Z_R}}{\frac{1}{Z_C} + \frac{1}{Z_R}} (-1\angle 0^\circ)$$

Problem

In phasor land.

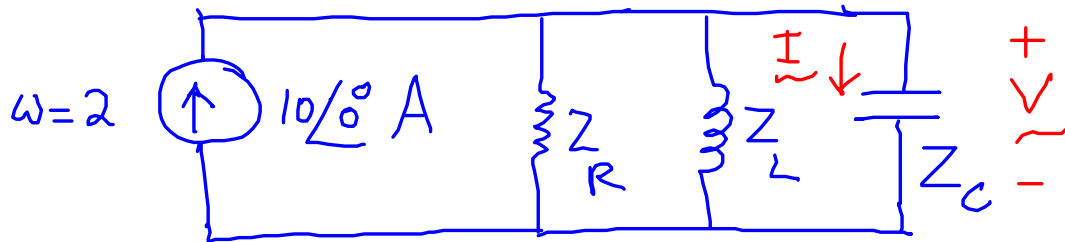

$$Z_R = 3 \Omega \quad Z_L = j \underset{\substack{\uparrow \\ \omega}}{(2)} \underset{\substack{\uparrow \\ L}}{3} \quad Z_C = \frac{-j}{\underset{\substack{\uparrow \\ \omega}}{(2)} \underset{\substack{\uparrow \\ C}}{(\frac{1}{3})}}$$

current division:


$$\tilde{I} = \frac{\frac{1}{Z_C}}{\frac{1}{Z_R} + \frac{1}{Z_L} + \frac{1}{Z_C}} 10 \angle 0^\circ$$

$$\tilde{V} = Z_C \tilde{I}$$

↓ real domain

$$v(t) = \text{Re} \left[\tilde{V} e^{j \omega t} \right]$$

Problem

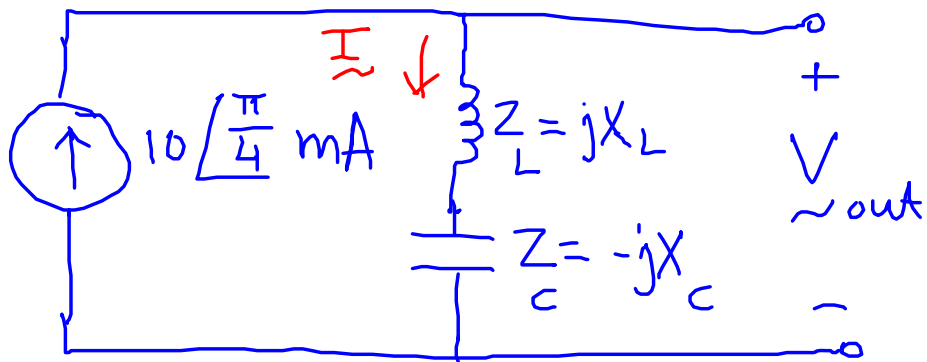


$$\tilde{I} = 10 \angle \frac{\pi}{4}$$

$$\begin{aligned} \tilde{V}_{out} &= \tilde{I} (Z_L + Z_C) \\ &= 10 \angle \frac{\pi}{4} \times 10^{-3} \text{ A} (j1\text{k}\Omega - j10\text{k}\Omega) \\ &= 10^{-2} \angle \frac{\pi}{4} (-9j \times 10^3) \quad -j = \angle -\frac{\pi}{2} \end{aligned}$$


$$= 10 \angle \frac{\pi}{4} 9 \angle -\frac{\pi}{2} \text{ V}$$

$$\tilde{V}_{out} = 90 \angle -\frac{\pi}{4} \text{ V}$$

Problem

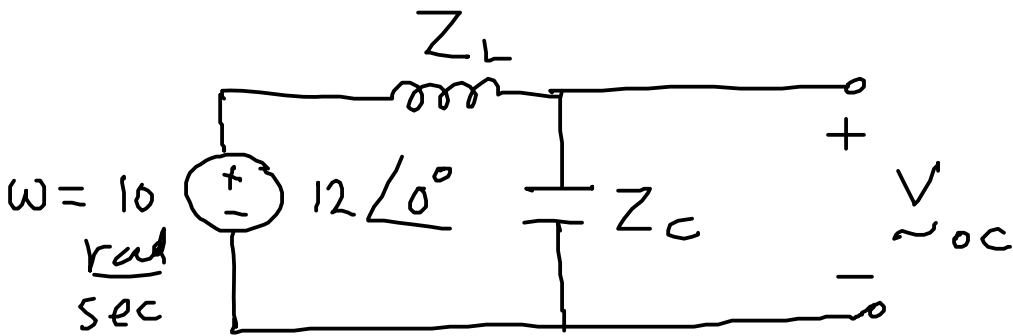

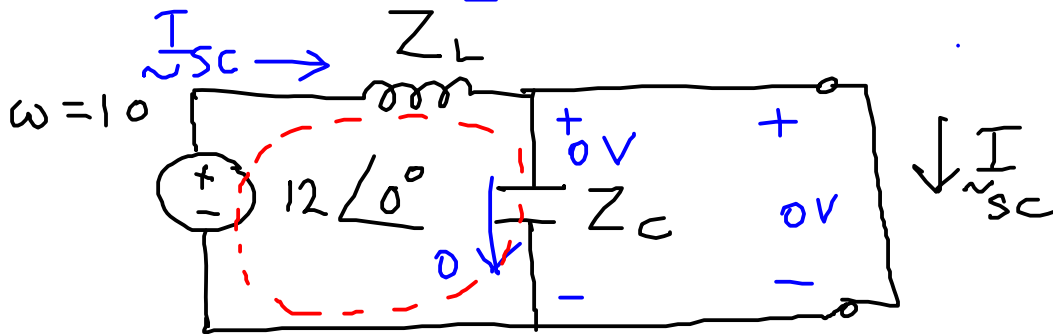
$$\underline{V}_{oc} = \frac{Z_C}{Z_L + Z_C} 12 \angle 0^\circ$$



$$-12 \angle 0^\circ \text{ V} + Z_L \underline{I}_{sc} + 0 = 0$$

$$\underline{I}_{sc} = \frac{12 \angle 0^\circ \text{ V}}{j\omega L}$$


0.114
10 rad/sec

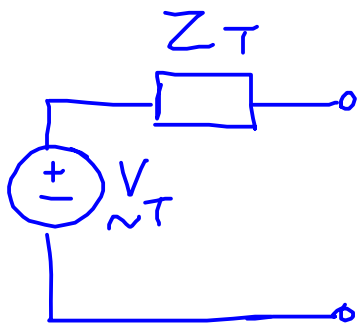

$$\underline{V}_T = \underline{V}_{oc}$$

$$Z_T = \underline{V}_{oc} / \underline{I}_{sc}$$

Problem

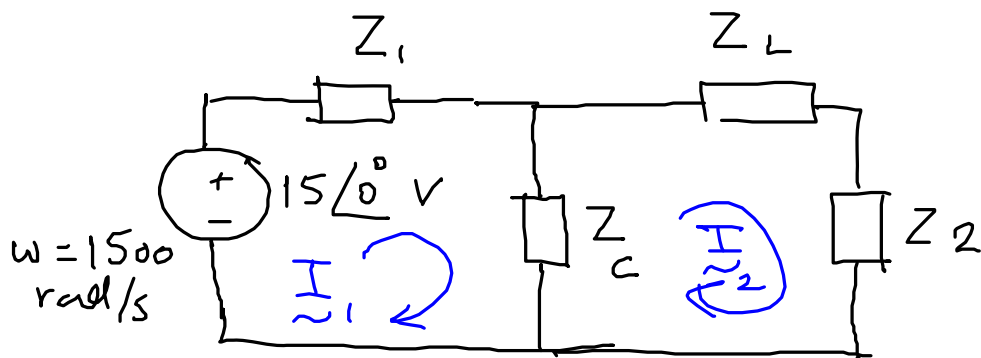

$$Z_1 = 75\Omega \quad Z_2 = 100\Omega \quad Z_c = \frac{1}{j(1500)(10^{-6})} \Omega$$

$$Z_L = j(1500)0.5 \text{ H}$$

$$\textcircled{1} \quad -15\angle 0^\circ + Z_1 I_1 + Z_c (I_1 - I_2) = 0$$


$$\textcircled{2} \quad Z_c (I_2 - I_1) + Z_L I_2 + Z_2 I_2 = 0$$

determine I_1 & I_2

$$i_1(t) = \text{Re} [I_1 e^{j\omega t}]$$

$$i_2(t) = \text{Re} [I_2 e^{j\omega t}]$$

Problem

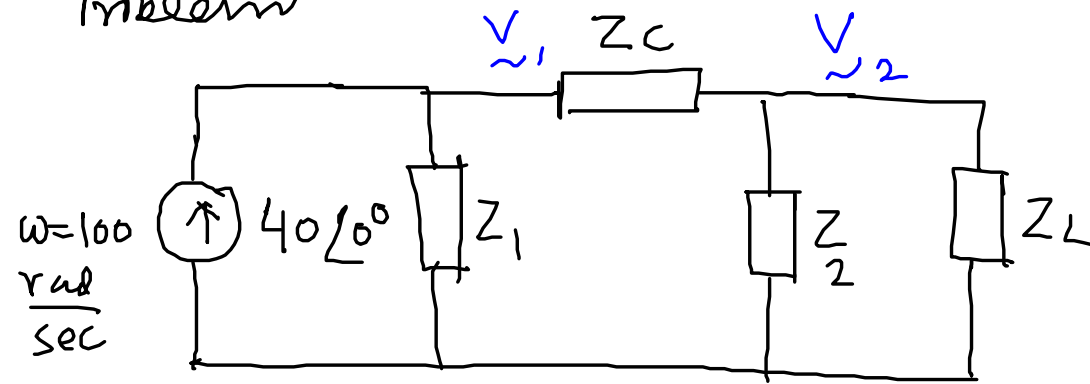

$$Z_1 = 40 \Omega \quad Z_2 = 10 \Omega \quad Z_L = j(100)0.2 \Omega$$

\uparrow
 ω

$$Z_C = \frac{-j}{(100)500 \times 10^{-6}} \Omega$$

\uparrow
 ω

$$1 \quad 40 \angle 0^\circ + 0 \frac{-V_1}{Z_1} + \frac{V_2 - V_1}{Z_C} = 0$$


$$2 \quad \frac{V_1 - V_2}{Z_C} + 0 \frac{-V_2}{Z_2} + 0 \frac{-V_2}{Z_L} = 0$$

determine V_1 & V_2

$$v_1(t) = \text{Re} [V_1 e^{j\omega t}]$$

$$v_2(t) = \text{Re} [V_2 e^{j\omega t}]$$

Problem

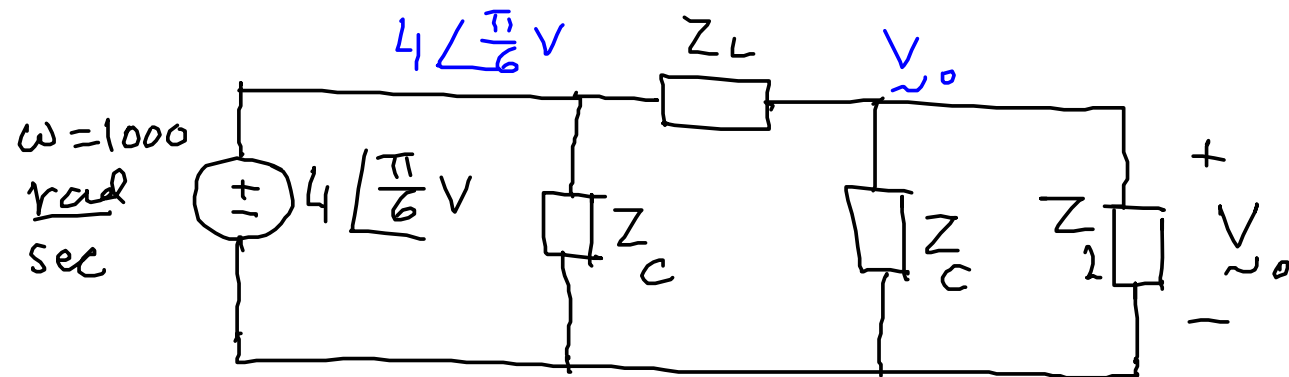

$$Z_L = j(1000)60 \times 10^{-3} \Omega$$

$$Z_2 = 120 \Omega$$

$$Z_C = \frac{-j}{(1000)12.5 \times 10^{-6}} \Omega$$

node analysis

$$\frac{4 \angle \frac{\pi}{6} \text{ V} - \underline{V}_o}{Z_L} + \frac{0 - \underline{V}_o}{Z_C} + \frac{0 - \underline{V}_o}{Z_2} = 0$$

Determine \underline{V}_o

$\nearrow 1000 \text{ rad/sec}$

$$v_o(t) = \text{Re} [\underline{V}_o e^{j\omega t}]$$