

Transfer Function

Transfer function of a circuit or system describes the **output response** to an **input excitation** as a function of the angular frequency ω .

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_{\text{out}}(\omega)}{\mathbf{V}_{\text{in}}(\omega)} \quad \text{Voltage Gain}$$

$$\mathbf{H}(\omega) = M(\omega) e^{j\phi(\omega)},$$

where by definition,

$$M(\omega) = |\mathbf{H}(\omega)|, \quad \phi(\omega) = \tan^{-1} \left\{ \frac{\Im[\mathbf{H}(\omega)]}{\Re[\mathbf{H}(\omega)]} \right\}$$

Magnitude

Phase


Other Transfer Functions

Current gain: $\mathbf{H}_I(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)},$


Transfer impedance: $\mathbf{H}_Z(\omega) = \frac{\mathbf{V}_{\text{out}}(\omega)}{\mathbf{I}_{\text{in}}(\omega)},$

Transfer admittance: $\mathbf{H}_Y(\omega) = \frac{\mathbf{I}_{\text{out}}(\omega)}{\mathbf{V}_{\text{in}}(\omega)}.$


Filters

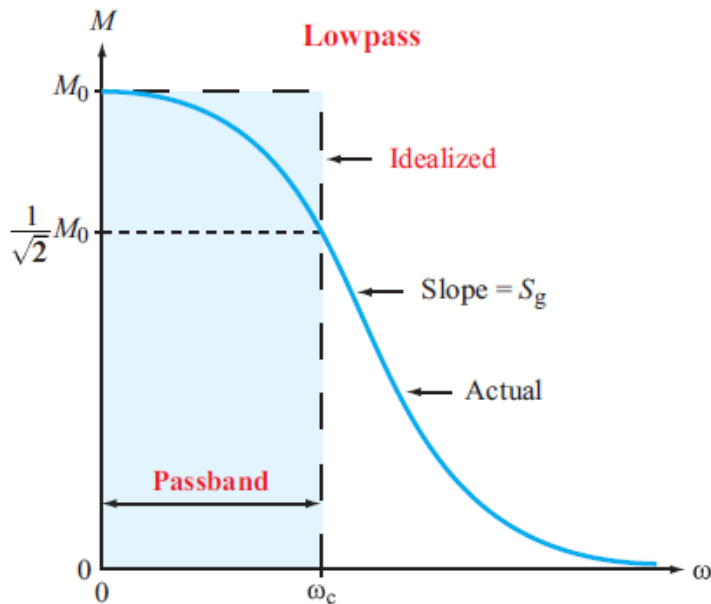


(a) Lowpass filter

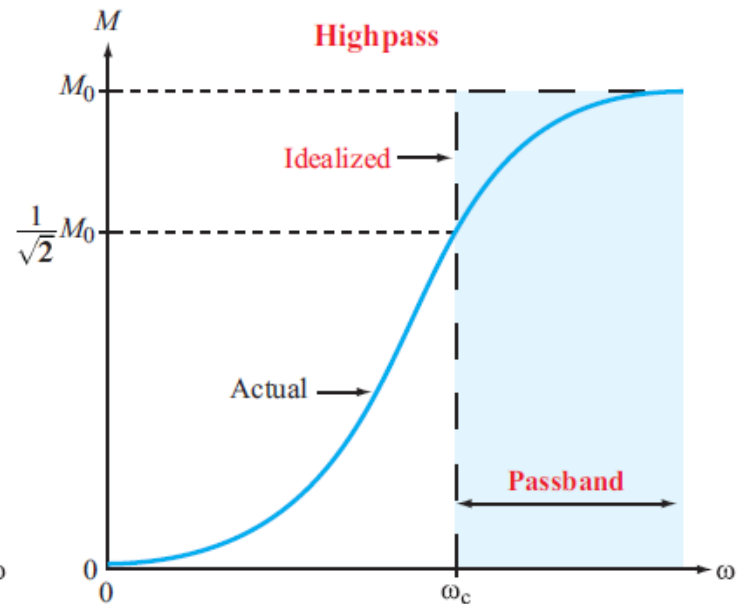

(b) Highpass filter

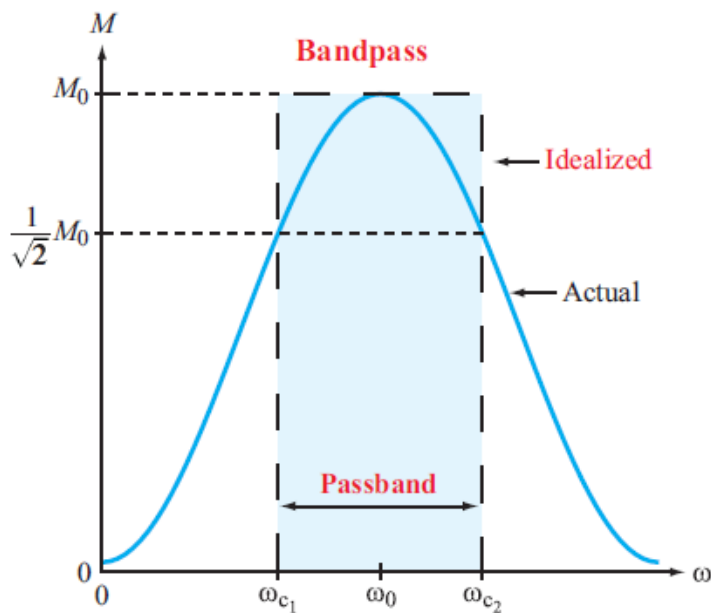


(c) Bandpass filter

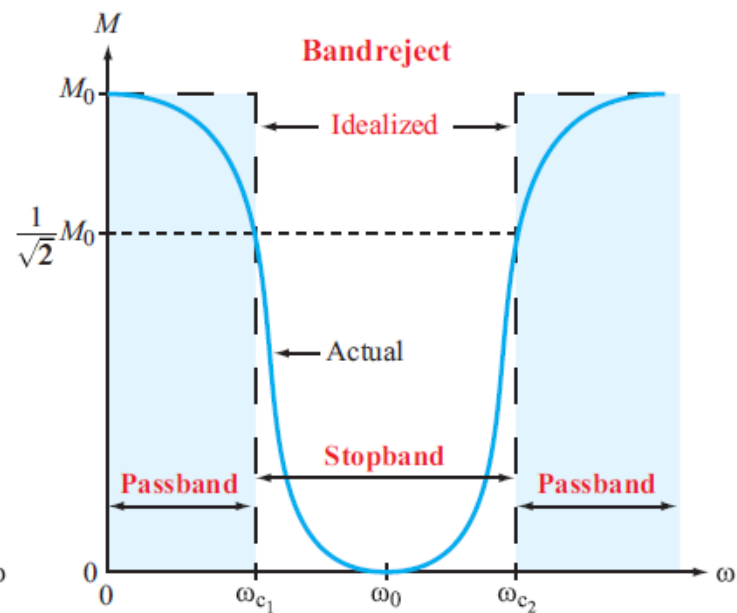

(d) Bandreject filter

Low Pass Filter

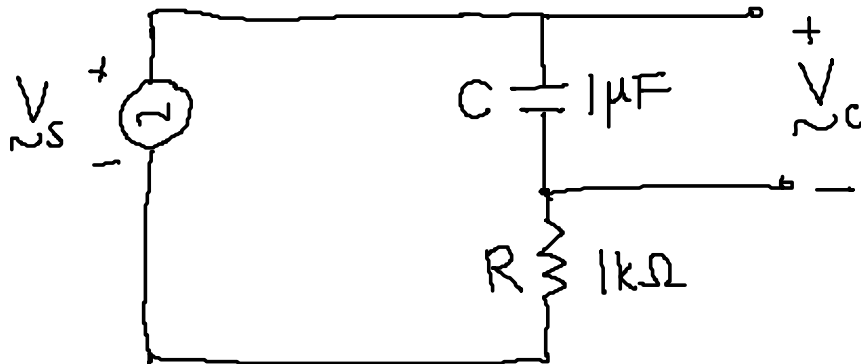

$$V_c = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} V_s$$

$$H_c(\omega) = \frac{V_c}{V_s} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$M_c(\omega) = |H_c(\omega)| = \frac{1}{|1 + j\omega RC|} = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$


```

R = 10^3;
C = 10^-6;
w_max = 5*10^3;
w = [0:w_max/100:w_max];
H_mag = 1./sqrt(1 + (w*R*C).^2);
plot(w, H_mag);

```

MATLAB

Low Pass Filter

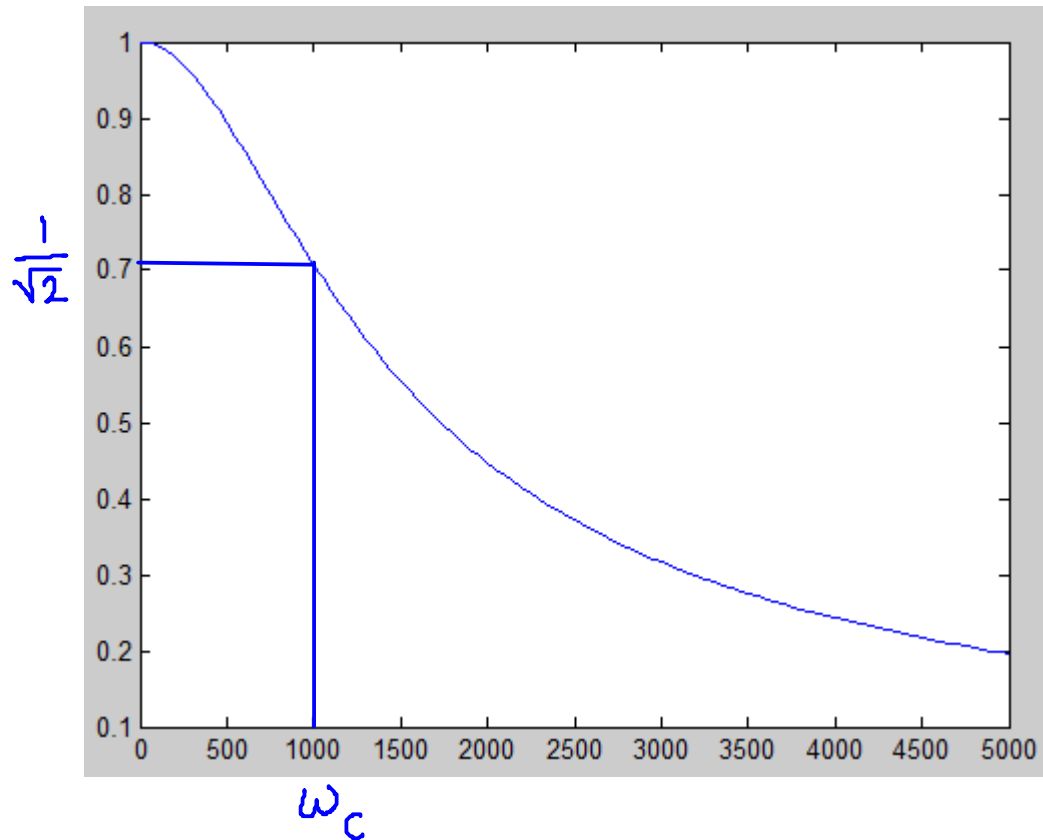


$$M_c(\omega_c) = \frac{1}{\sqrt{2}}$$

$$\frac{1}{\sqrt{1 + \omega_c^2 R^2 C^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{1}{1 + \omega_c^2 R^2 C^2} = \frac{1}{2}$$

$$\omega_c = \frac{1}{RC} = 1000 \text{ rad/s}$$

High Pass Filter

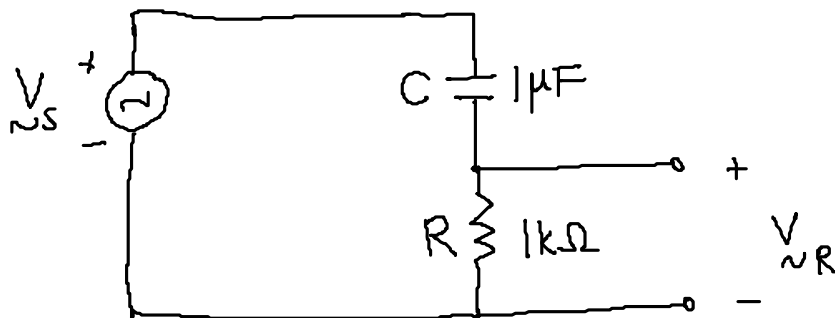

$$V_{\sim R} = \frac{R}{R + \frac{1}{j\omega C}} V_{\sim S}$$

$$H_R(\omega) = \frac{V_{\sim R}}{V_{\sim S}} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$

$$M_R(\omega) = |H_R(\omega)| = \frac{|j\omega RC|}{|1 + j\omega RC|} = \frac{\omega RC}{\sqrt{1 + \omega^2 R^2 C^2}}$$


```

R = 10^3;
C = 10^-6;
w_max = 5*10^3;
w = [0:w_max/100:w_max];
H_mag = (w*C*R)/sqrt(1 + (w*R*C).^2);
plot(w, H_mag);

```

MATLAB

High Pass Filter

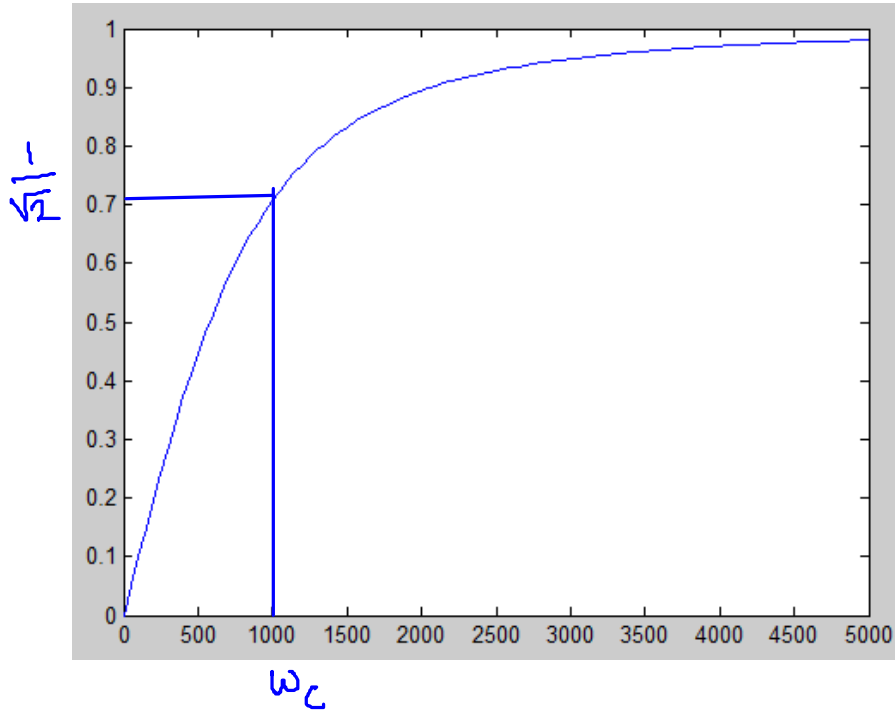


$$M_R(\omega_c) = \frac{1}{\sqrt{2}} \quad \frac{\omega_c CR}{\sqrt{1 + \omega_c^2 C^2 R^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_c^2 C^2 R^2}{1 + \omega_c^2 C^2 R^2} = \frac{1}{2}$$

$$\omega_c = \frac{1}{CR} = 1000 \text{ rad/s}$$

dB Scale

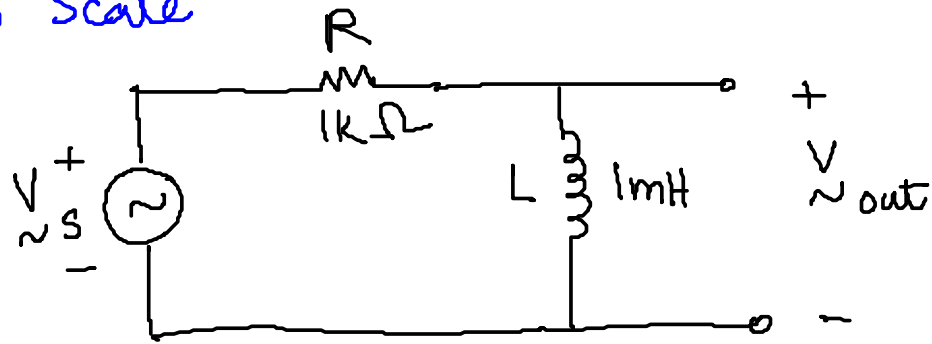

$$V_{out} = \frac{j\omega L}{R + j\omega L} V_s$$

$$H(\omega) = \frac{V_{out}}{V_s} = \frac{j\omega L}{R + j\omega L}$$

$$M(\omega) = |H(\omega)| = \frac{|j\omega L|}{|R + j\omega L|} = \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}}$$


```

R = 10^3;
L = 10^-3;
w_max = 5*10^6;
w = [0:w_max/100:w_max];
H_mag = (w*L)./sqrt(R^2 + (w*L).^2);
plot(w, H_mag);

```

MATLAB

High Pass Filter

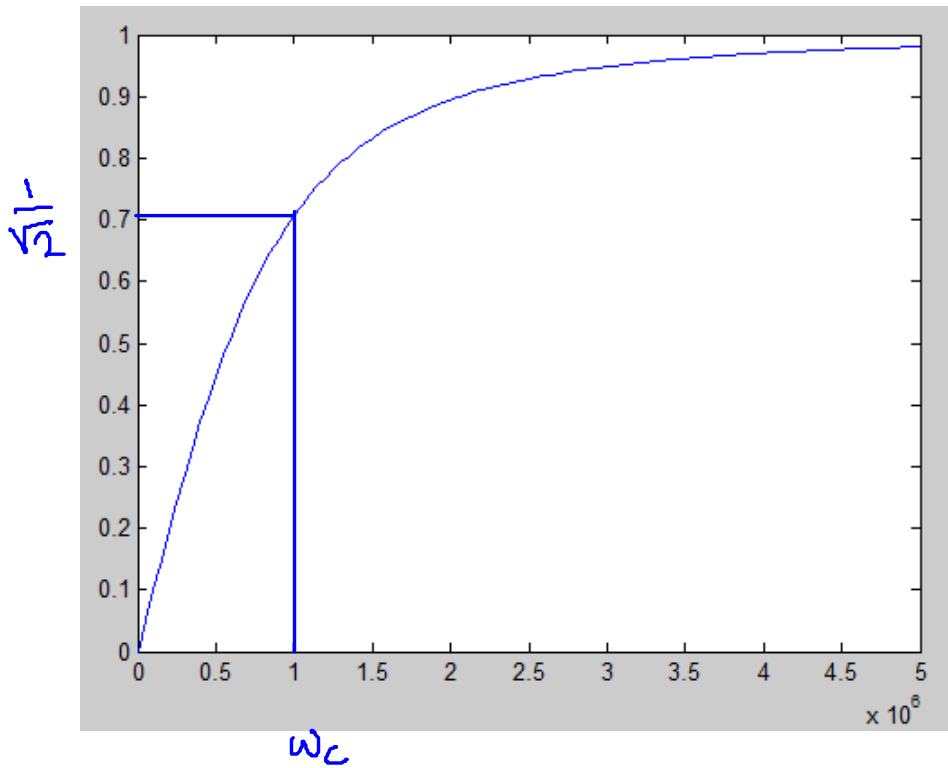

$$M(\omega_c) = \frac{1}{\sqrt{2}} \quad \frac{\omega_c L}{\sqrt{R^2 + \omega_c^2 L^2}} = \frac{1}{\sqrt{2}}$$

$$\frac{\omega_c^2 L^2}{R^2 + \omega_c^2 L^2} = \frac{1}{2} \quad \omega_c = \frac{R}{L} = 10^6 \text{ rad/s}$$


Bode Plot (dB scale)

$20 \log M(\omega)$ vs. $\log(\omega)$

```
w_log = log10(w);
H_mag_dB = 20*log10(H_mag);
plot(w_log, H_mag_dB);
```

MATLAB

Magnitude Bode Plot

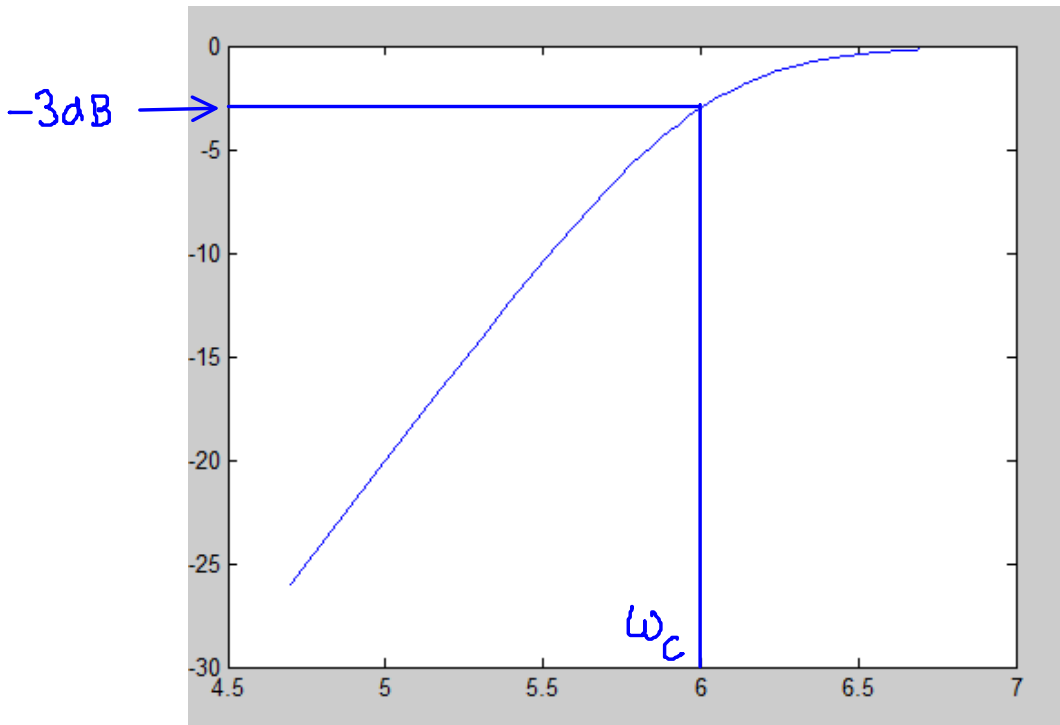

ω

10^5

10^6


10^7 rad/s

$\log \omega = 5$
 $\omega = 10^5$

$\log \omega = 6$
 $\omega = 10^6$

$\log \omega = 7$
 $\omega = 10^7$

$\omega_c = 10^6$ rad/s

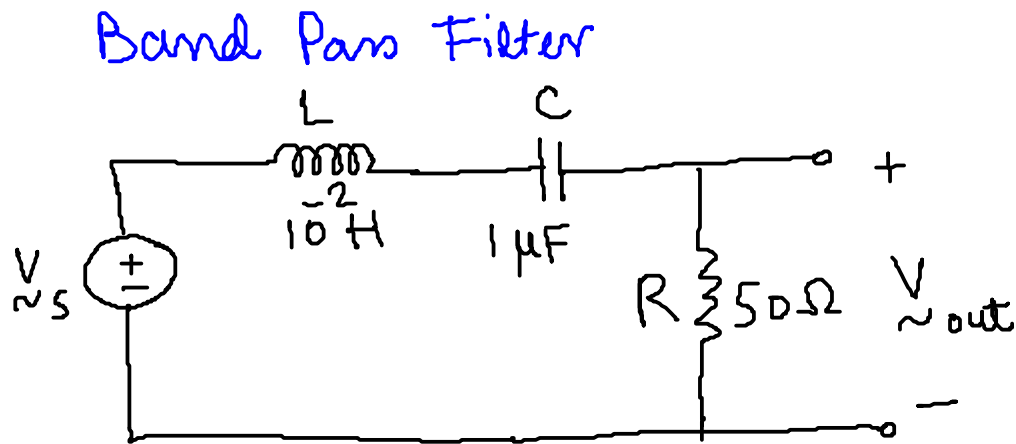

$$\tilde{V}_{out} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}} \tilde{V}_{out}$$

$$H(\omega) = \frac{\tilde{V}_{out}}{\tilde{V}_s} = \frac{R}{R + j\omega L + \frac{1}{j\omega C}}$$

$$H(\omega) = \frac{j\omega RC}{(1 - \omega^2 LC) + j\omega RC}$$


$$M(\omega) = |H(\omega)| = \frac{|j\omega RC|}{|(1 - \omega^2 LC) + j\omega RC|}$$

$$M(\omega) = \frac{\omega RC}{\sqrt{(1 - \omega^2 LC)^2 + \omega^2 R^2 C^2}}$$

Lecture 59

```

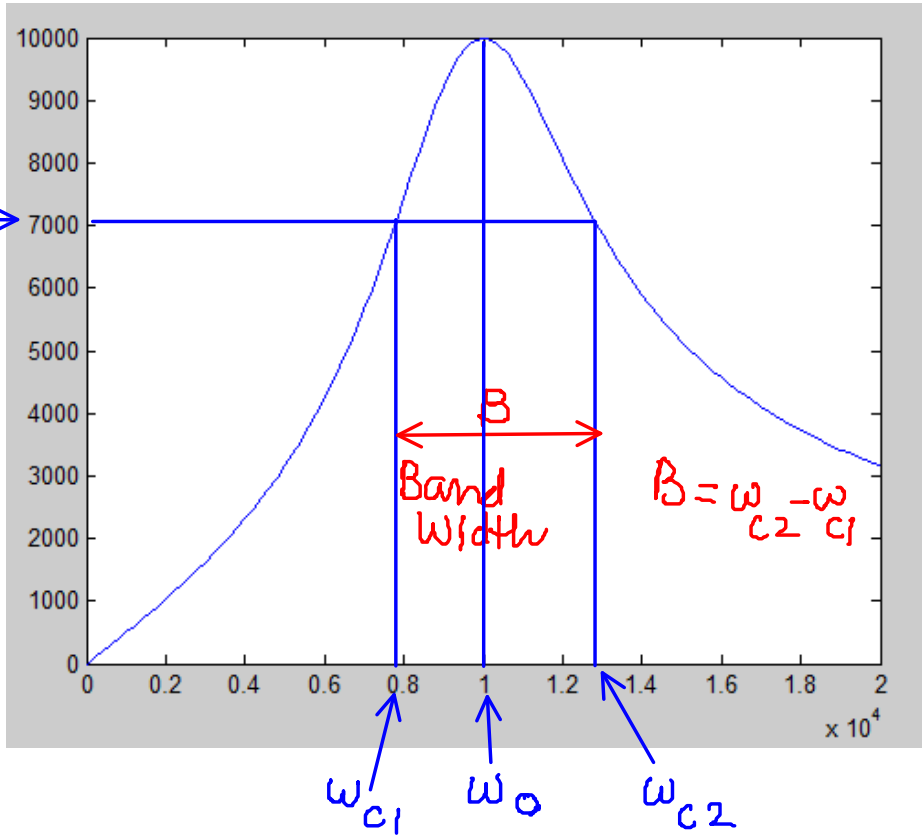R = 50;
L = 10^-2;
C = 10^-6;
w_max = 2*10^4;
w = [0:w_max/100:w_max];
H_mag = (w*R*L)./sqrt( (1 - w.^2*L*C).^2 + (w*R*C).^2);
plot(w, H_mag);
    
```




$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}},$$

$$\omega_0 = \frac{1}{\sqrt{LC}}.$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}.$$


$$B = \omega_{c2} - \omega_{c1} = \frac{R}{L}.$$

Active Filters

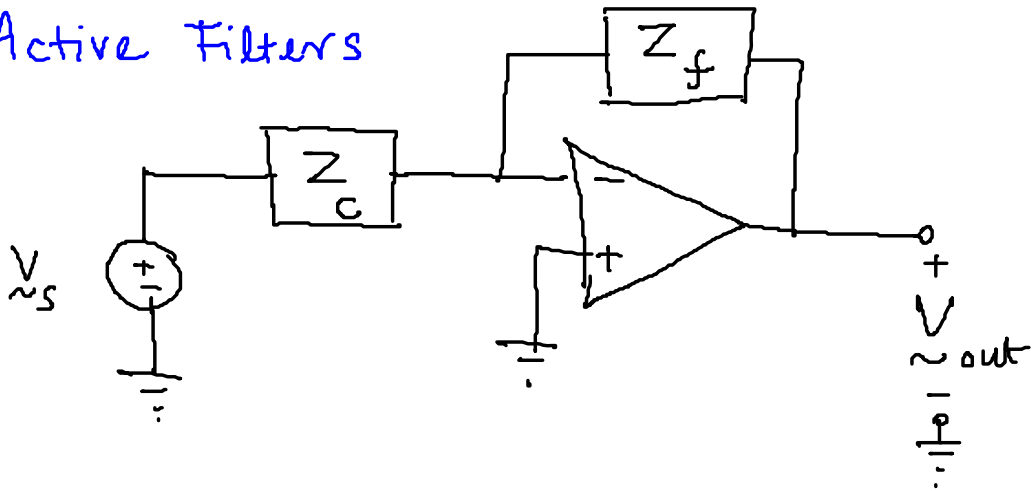

$$H(\omega) = \frac{V_{out}}{V_s} = - \frac{Z_f}{Z_c}$$

Active Low Pass

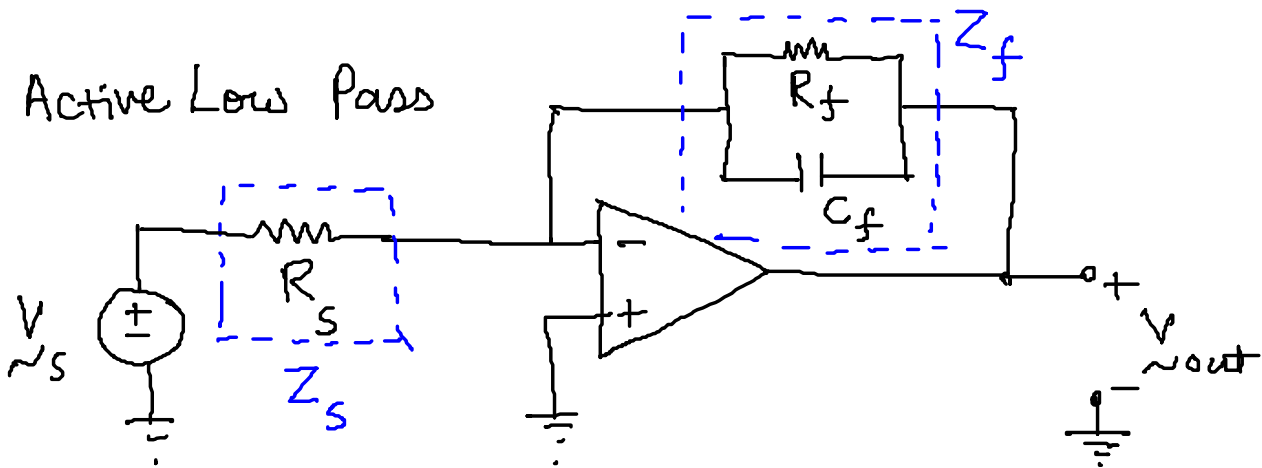

$$Z_f = R_f \parallel \frac{1}{j\omega C_f}$$


$$\frac{1}{Z_f} = \frac{1}{R_f} + \frac{1}{\frac{1}{j\omega C_f}}$$

$$Z_f = \frac{R_f}{1 + j\omega R_f C_f}$$

$$H(\omega) = \frac{V_{out}}{V_s} = - \frac{Z_f}{Z_s} = - \frac{\frac{R_f}{1 + j\omega R_f C_f}}{R_s}$$

$$H(\omega) = - \frac{R_f}{R_s} \frac{1}{1 + j\omega R_f C_f}$$

$$M(\omega) = |H(\omega)| = \frac{R_f}{R_s} \frac{1}{\sqrt{1 + \omega^2 R_f^2 C_f^2}} = \frac{1}{\sqrt{2}} \frac{R_f}{R_s}$$

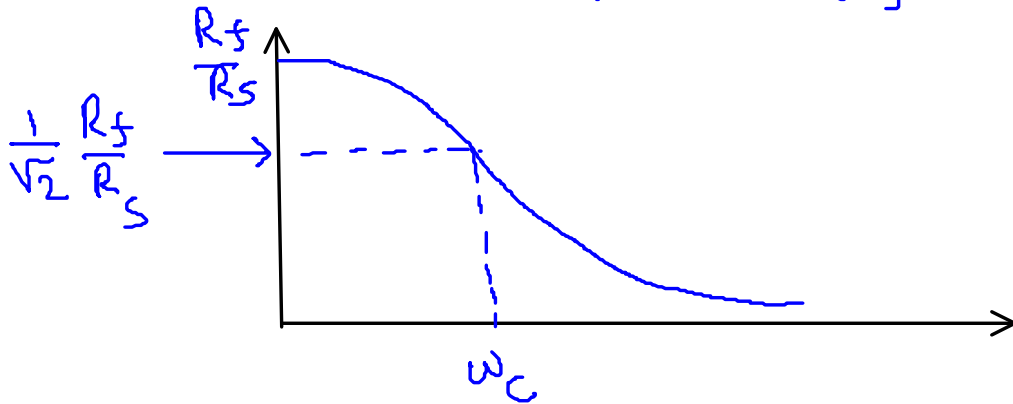


$$\omega_c = \frac{1}{R_f C_f}$$

$$H(\omega) = - \frac{R_f}{R_s} \frac{1}{1 + j \left(\frac{\omega}{\omega_c} \right)}$$

LP
Filter

High Pass Active Filter

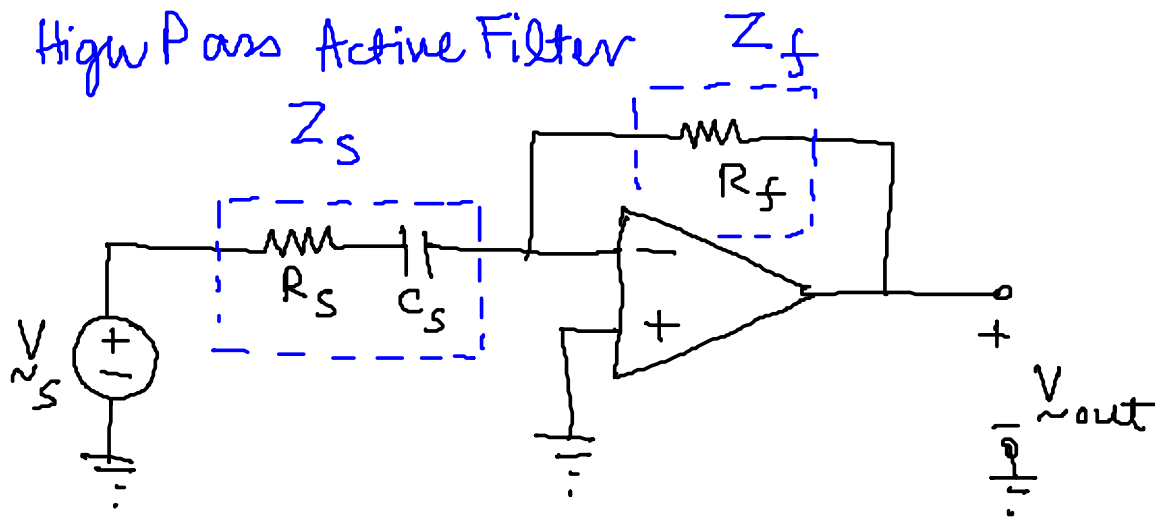

$$Z_s = R_s + \frac{1}{j\omega C_s}$$


$$Z_f = R_f$$

$$H(\omega) = \frac{V_{out}}{V_s} = - \frac{Z_f}{Z_s} = - \frac{R_f}{R_s + \frac{1}{j\omega C_s}}$$

$$H(\omega) = - \frac{R_f}{R_s} \frac{j\omega C_s R_s}{1 + j\omega C_s R_s}$$

$$|M(\omega)| = \frac{R_f}{R_s} \frac{\omega C_s R_s}{\sqrt{1 + \omega^2 C_s^2 R_s^2}}$$

Lecture 59

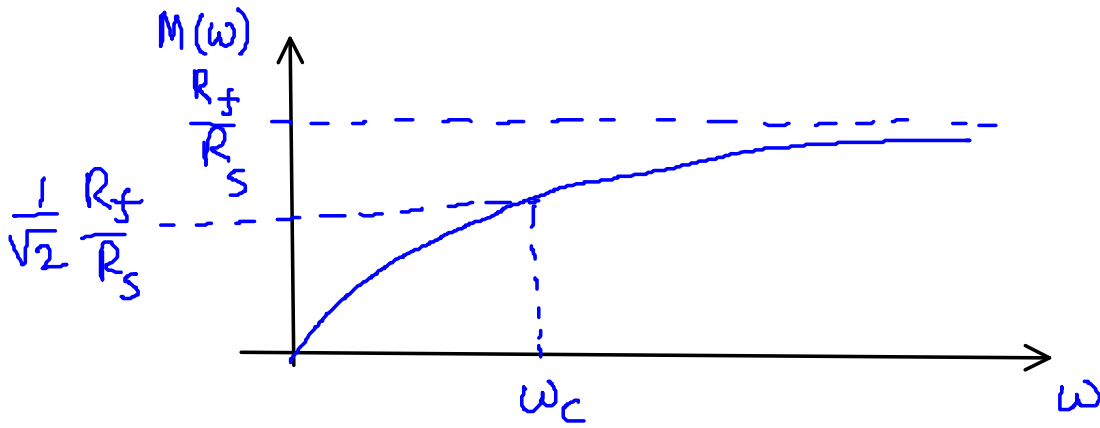

$$M(\omega_c) = \frac{1}{\sqrt{2}}$$


$$\frac{R_f}{R_s} \frac{\omega C_s R_s}{\sqrt{1 + \omega^2 C_s^2 R_s^2}} = \frac{1}{\sqrt{2}} \frac{R_f}{R_s} \quad \omega_c = \frac{1}{C_s R_s}$$

$$H(\omega) = - \frac{R_f}{R_s} \frac{j\omega C_s R_s}{1 + j\omega C_s R_s}$$


$$H(\omega) = - \frac{R_f}{R_s} \frac{j \frac{\omega}{\omega_c}}{1 + j \frac{\omega}{\omega_c}}$$

HP
Filter

Cascading Active Filters

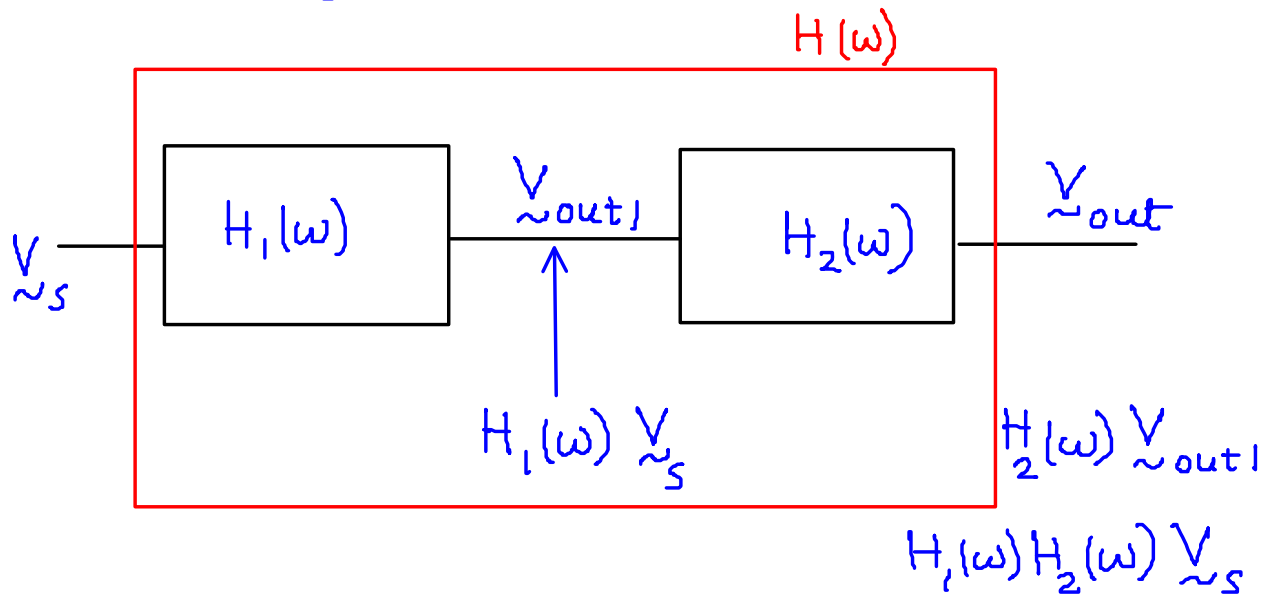


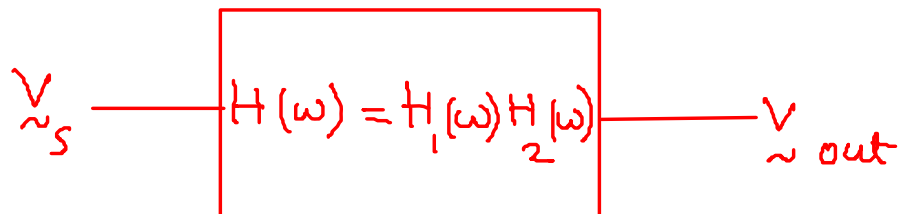
$$V_{out} = H_1(\omega) H_2(\omega) V_s$$




$$|H(\omega)| = |H_1(\omega)| |H_2(\omega)|$$

$$M(\omega) = M_1(\omega) M_2(\omega)$$

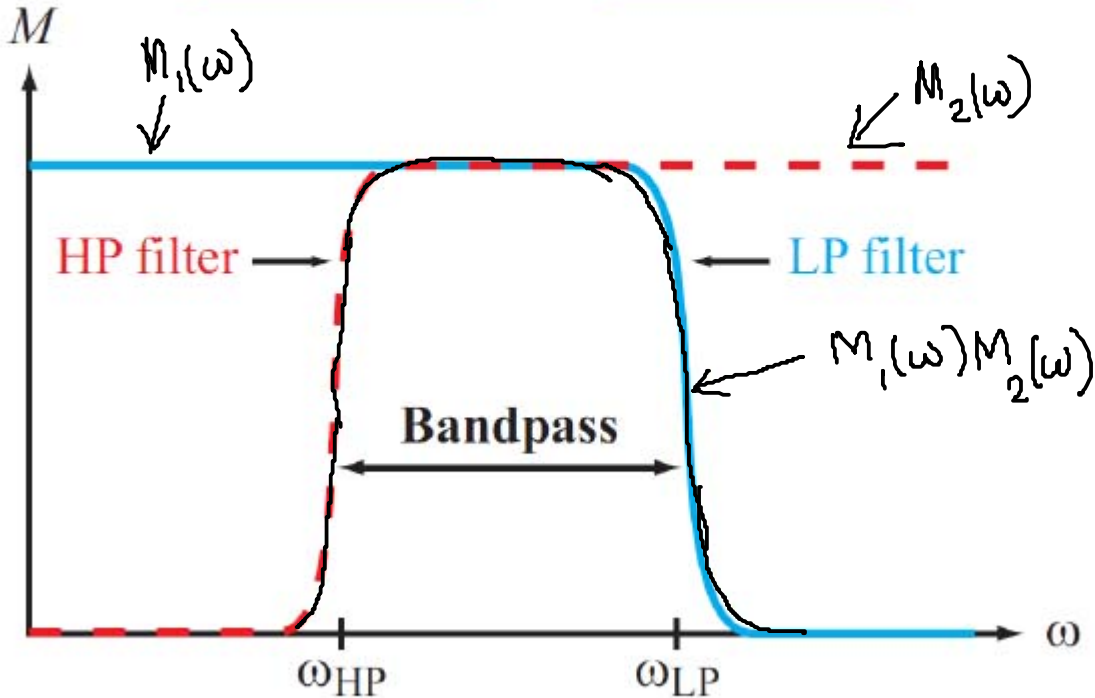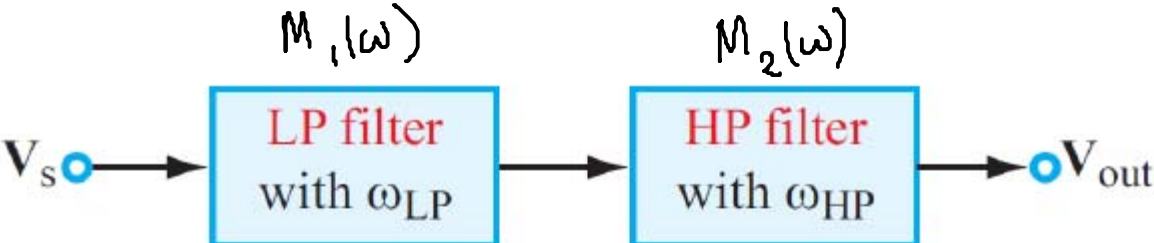
$$20 \log M(\omega) = 20 \log M_1(\omega) + 20 \log M_2(\omega)$$



(a) Bandpass filter


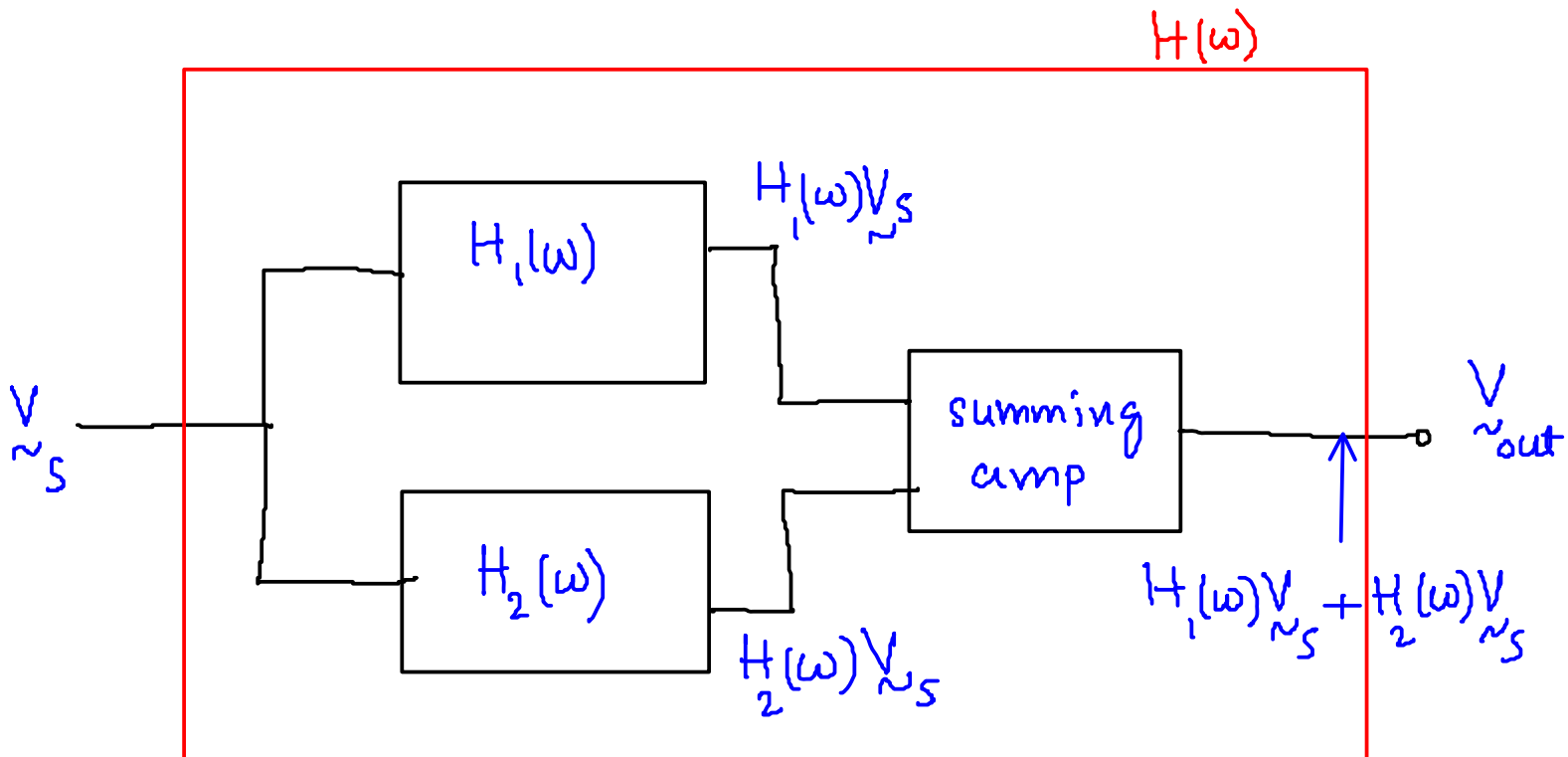

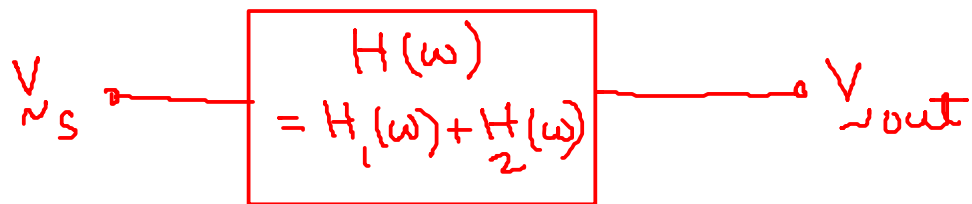
$$V_{out} = [H_1(\omega) + H_2(\omega)] V_s$$




$$H(\omega) = \frac{V_{out}}{V_s} = H_1(\omega) + H_2(\omega)$$

$$|H(\omega)| = |H_1(\omega) + H_2(\omega)|$$

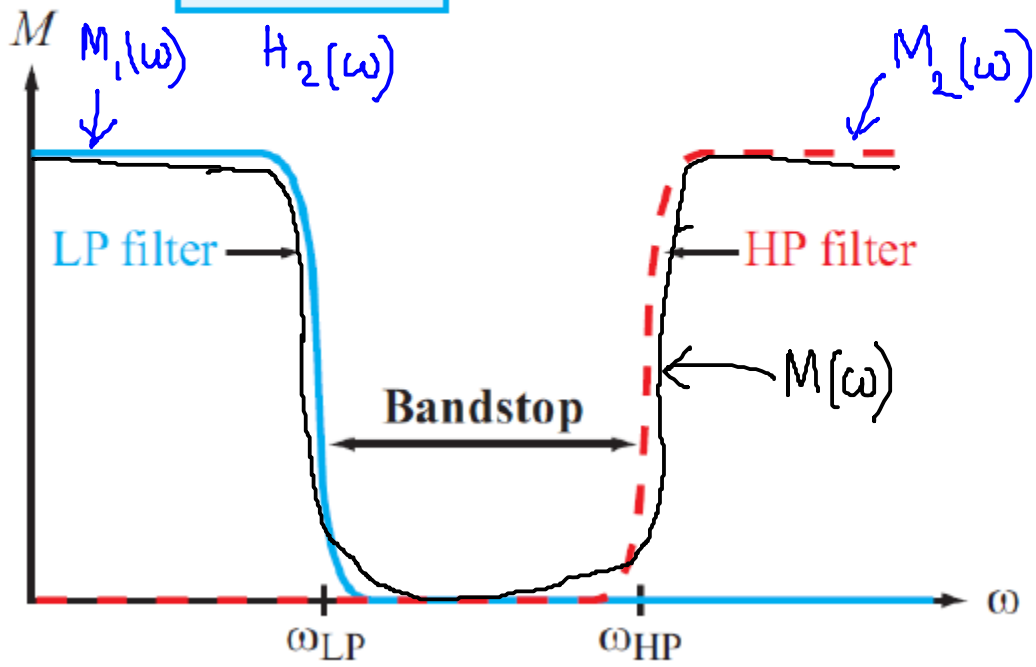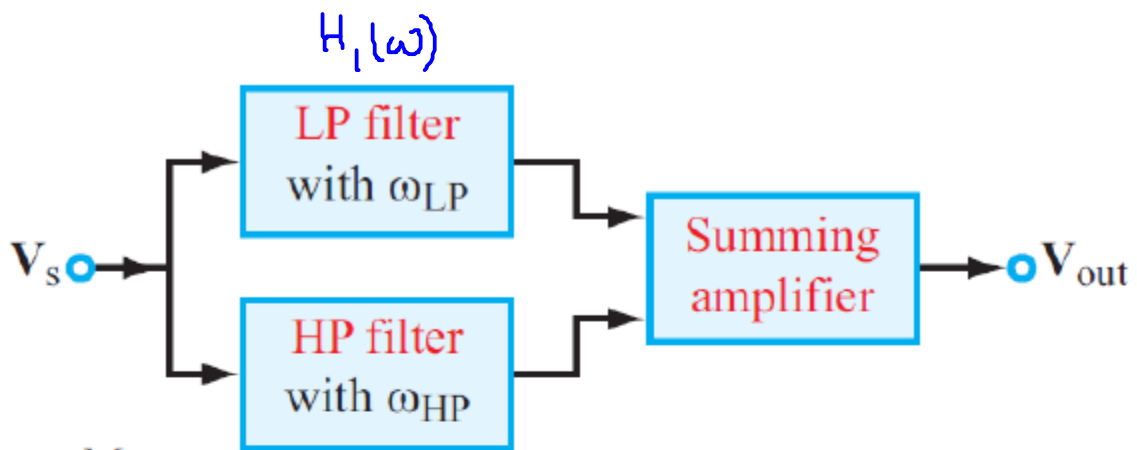

(b) Bandreject filter

Example 9-11

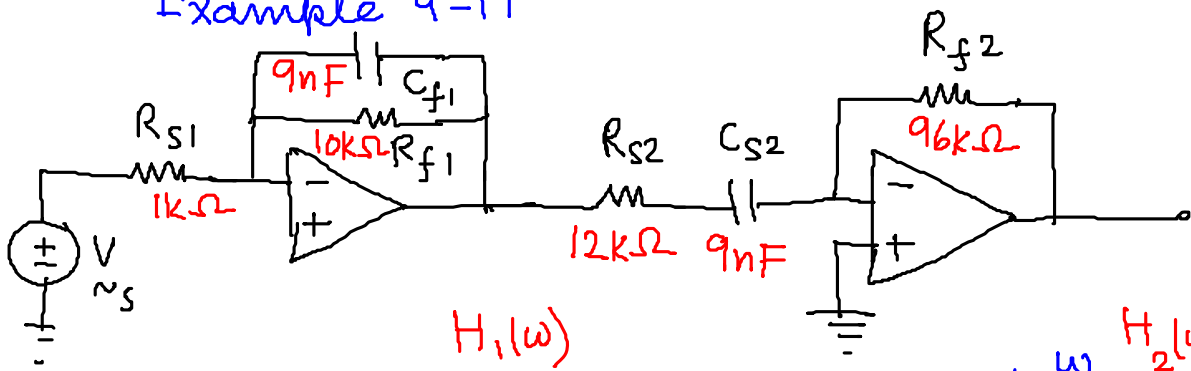

$H_1(\omega)$

$H_2(\omega)$

$$R_{s1} \left(\frac{R_{f1}}{1 + j \frac{\omega}{\omega_{CLP}}} \right)$$

$$- \left(\frac{R_{f2}}{R_{s2}} \right) \frac{j \frac{\omega}{\omega_{CHP}}}{1 + j \frac{\omega}{\omega_{CHP}}}$$

$$\frac{1}{R_{s1} C_{f1}} = 11.11 \text{ krad/s}$$

$$\frac{1}{R_{s2} C_{s2}} = 9.26 \text{ krad/s}$$

$$H(\omega) = \frac{R_{f1} R_{f2}}{R_{s1} R_{s2}} \frac{1}{1 + j \frac{\omega}{\omega_{CLP}}} \frac{j \frac{\omega}{\omega_{CHP}}}{1 + j \frac{\omega}{\omega_{CHP}}}$$

Lecture 59

```
Rs1 = 10^3;  
Rf1 = 10*10^3;  
Rs2 = 12*10^3;  
Rf2 = 96*10^3;  
Cf1 = 9*10^-9;  
Cs2 = 9*10^-9;  
wcLP = 1/(Rf1*Cf1);  
wcHP = 1/(Rs2*Cs2);
```


MATLAB

```
w_max = 4*10^4;  
w = [0:w_max/5000:w_max];
```

```
H_mag1 = (Rf1/Rs1)*1./(1 + (w/wcLP).^2);  
H_mag2 = (Rf2/Rs2)*(w/wcHP)./(1 + (w/wcHP).^2);
```

```
H_mag = H_mag1 .* H_mag2;  
plot(w, H_mag);
```

$M(\omega)$

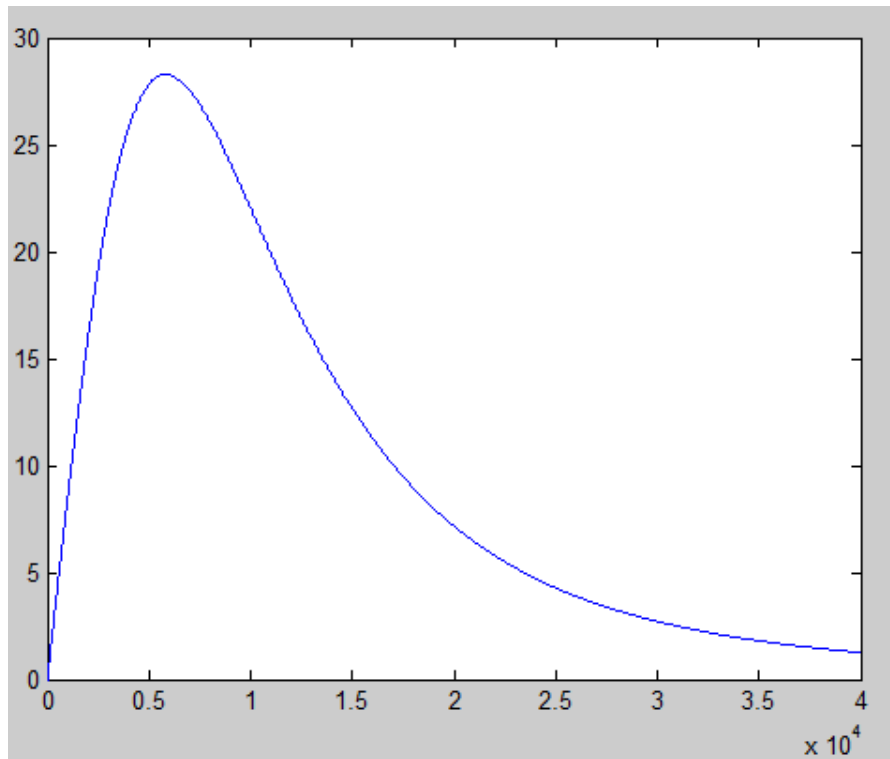

Magnitude
plot