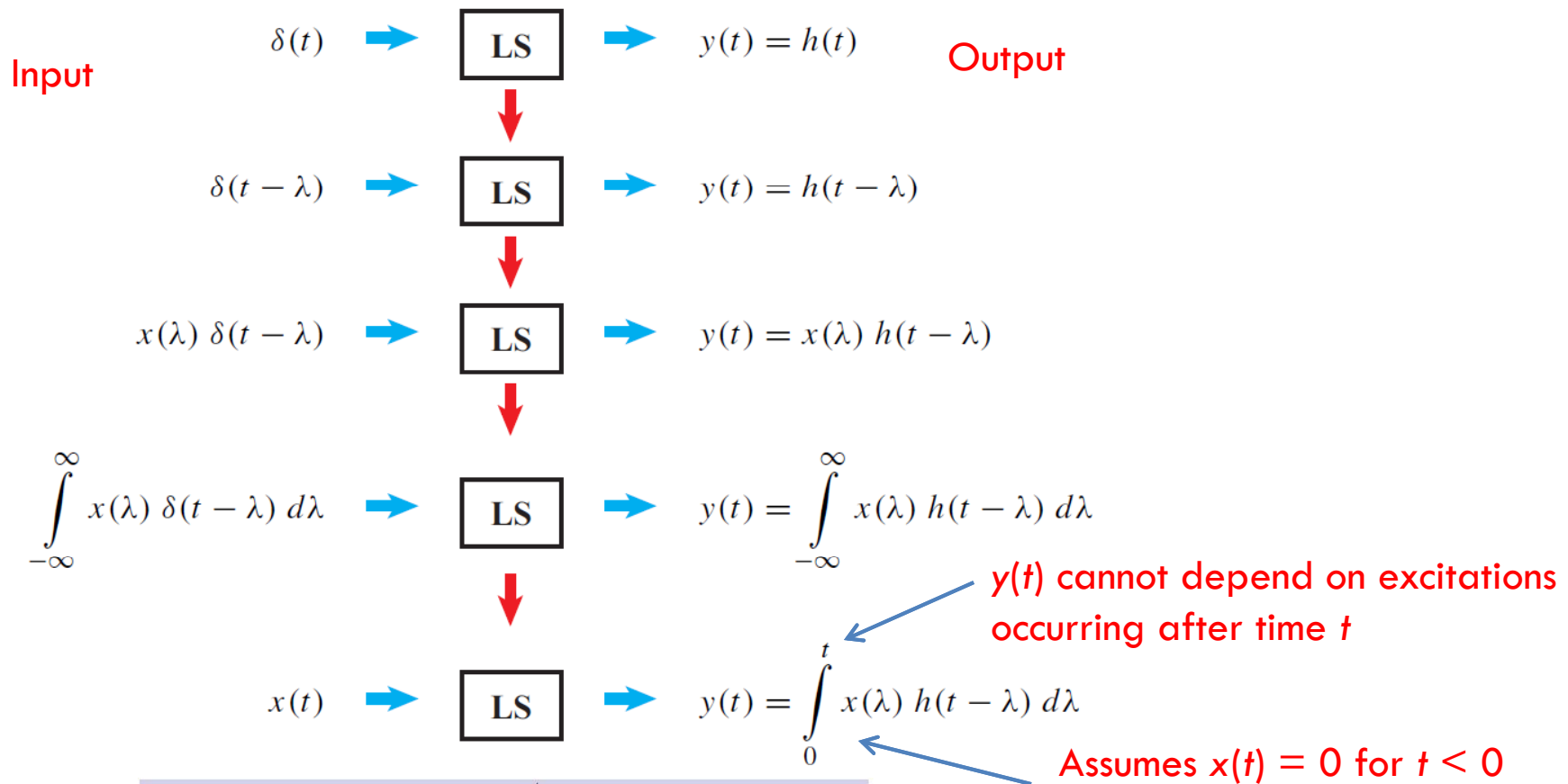


Convolution Integral

Impulse Response $h(t)$: output of linear system when input is a delta function

Linear Time-Invariant Circuit



$$y(t) = x(t) * h(t) = \int_0^t x(\lambda) h(t - \lambda) d\lambda.$$

Definition of convolution

Transfer Function

In the **s-domain**, the circuit is characterized by a **transfer function** $\mathbf{H(s)}$, defined as the ratio of the **output** $\mathbf{Y(s)}$ to the **input** $\mathbf{X(s)}$, assuming that all initial conditions relating to currents and voltages in the circuit are zero at $t = 0^-$.

$$\mathbf{H(s)} = \frac{\mathbf{Y(s)}}{\mathbf{X(s)}}$$

$$\mathbf{H(s)} = \mathbf{Y(s)}, \quad (\text{when } x(t) = \delta(t)).$$

Convolution Integral


- Can be used to determine output response entirely in the time domain
- Can be useful when input is a sequence of experimental data or not a function with a definable Laplace transform
- Convolution can be performed by shifting $h(t)$ or $x(t)$:

$$y(t) = x(t) * h(t) = \int_0^t x(\lambda) h(t - \lambda) d\lambda.$$

$h(t)$ shifted

$$y(t) = x(t) * h(t) = \int_0^t x(t - \lambda) h(\lambda) d\lambda.$$

$x(t)$ shifted

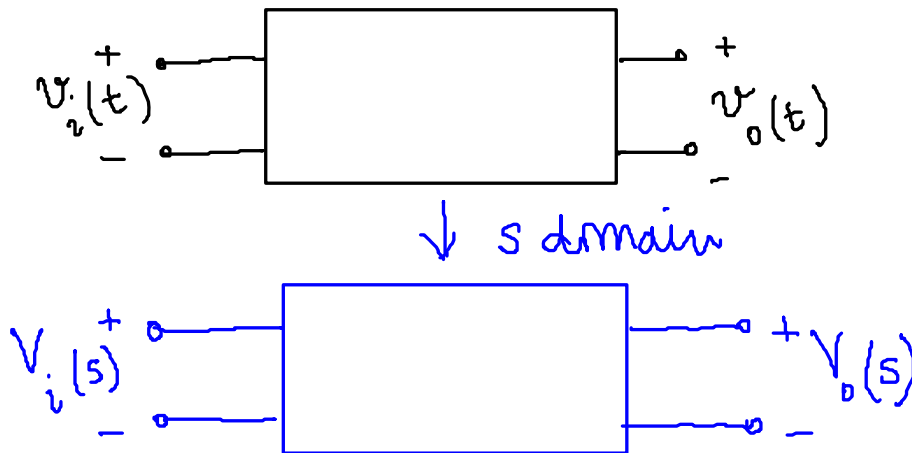

$$\frac{V_o(s)}{V_i(s)} = H(s) \quad [\text{ignore initial conditions}]$$



Transfer function in s-domain
System function

↓ Frequency domain

$$H(j\omega) = H(s) \Big|_{s=j\omega}$$

Magnitude Response $|H(j\omega)|$
Phase Response $\angle H(j\omega)$

RC filter

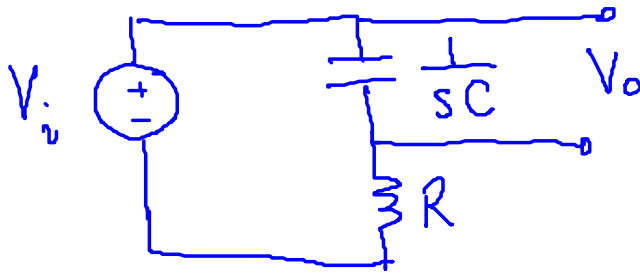
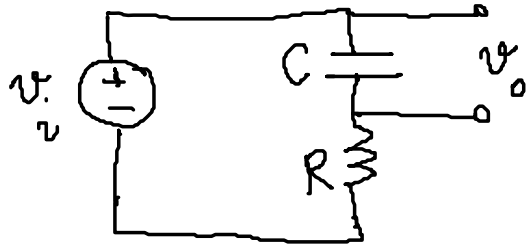


$$V_o = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i \quad \frac{V_o}{V_i} = \frac{1}{1 + sCR}$$

$$H(s) = \frac{1}{1 + sCR} \quad \text{Transfer function}$$

Freq. response
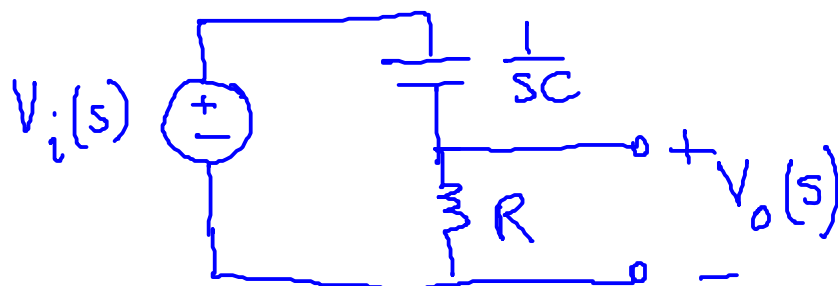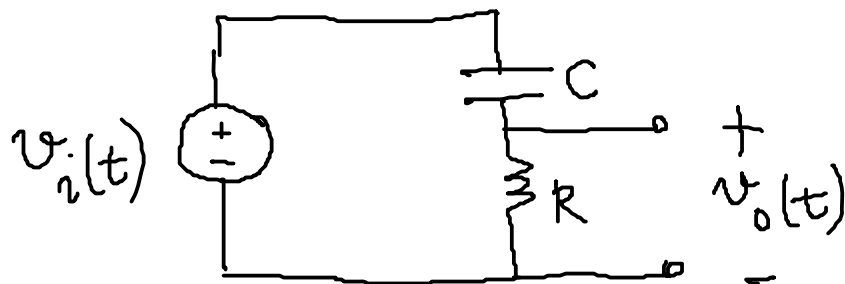
$$H(j\omega) = \frac{1}{1 + j\omega CR}$$




$$V_o = \frac{R}{1 + \frac{1}{sC}} V_i = \frac{sCR}{1 + sCR} V_i$$

$$H(s) = \frac{sCR}{1 + sCR}$$

Frequency Response
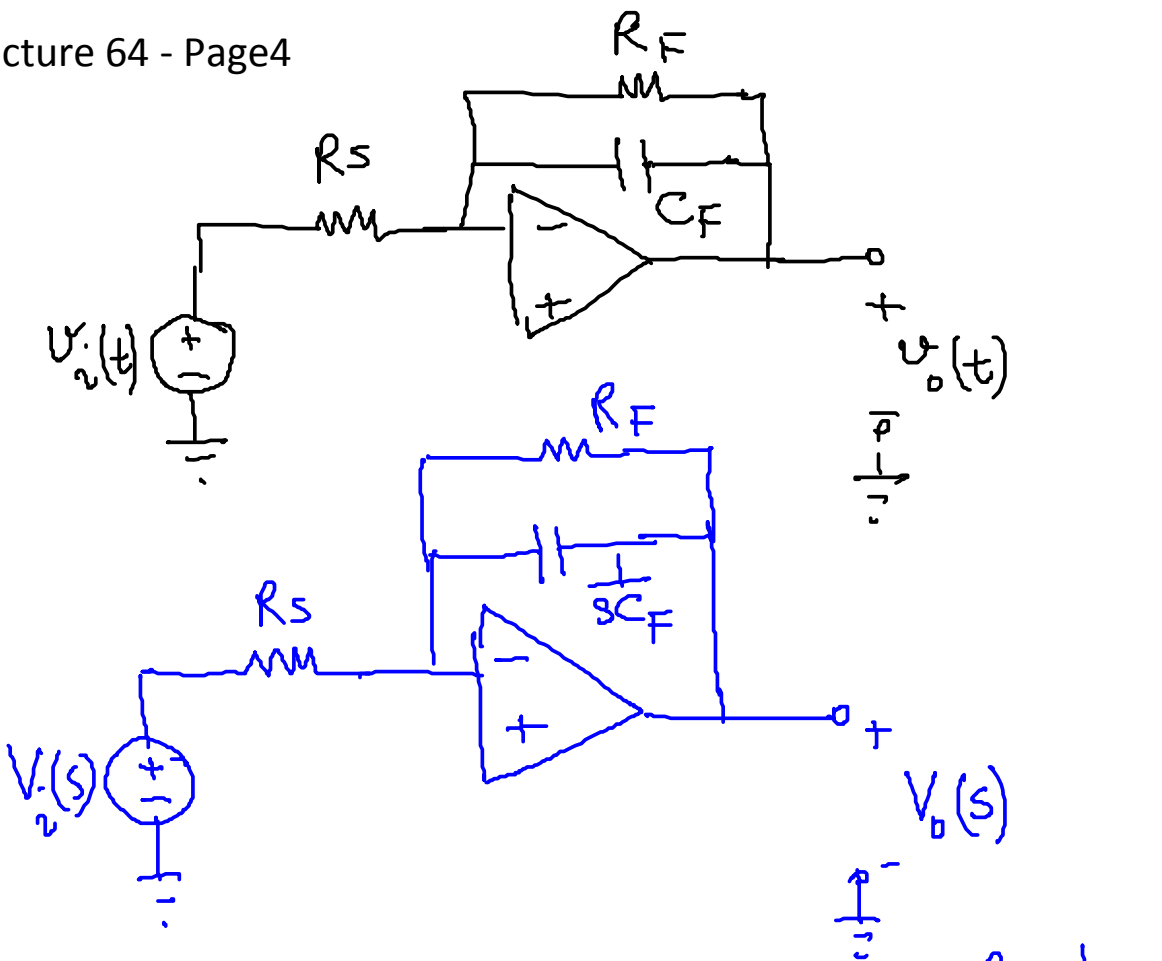
$$H(j\omega) = \frac{j\omega CR}{1 + j\omega CR}$$





$$Z_F = R_F \parallel \frac{1}{sC_F} = \frac{R_F \frac{1}{sC_F}}{R_F + \frac{1}{sC_F}}$$

$$Z_F = \frac{R_F}{1 + sC_F R_F}$$

$$\frac{V_o}{V_i} = - \frac{Z_F}{R_S} = - \frac{1}{R_S} \frac{R_F}{1 + sC_F R_F}$$

$$H(s) = - \frac{R_F}{R_S} \frac{1}{1 + sC_F R_F}$$
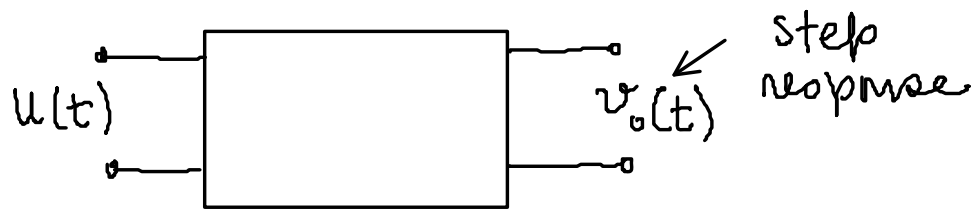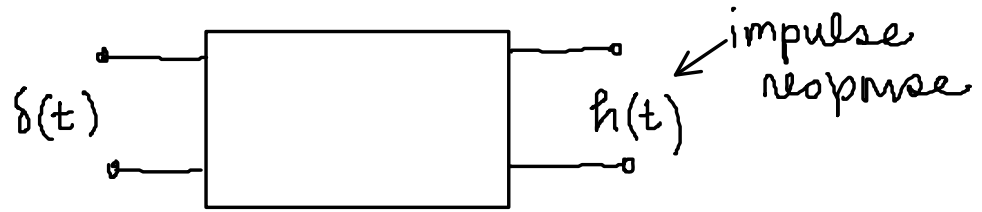
$$H(j\omega) = - \frac{R_F}{R_S} \frac{1}{1 + j\omega C_F R_F}$$



MATLAB

```
>> n = [2 5 1];  
>> d = [1 2 3];  
>> tf(n,d)
```

transfer function

Transfer function:

$$2s^2 + 5s + 1$$

$$s^2 + 2s + 3$$

```
>> tf([2 5 1], [1 2 3])
```

Transfer function:

$$2s^2 + 5s + 1$$

$$s^2 + 2s + 3$$

```
>>  
>> pole(tf(n,d))
```

poles

ans =

$$-1.0000 + 1.4142i$$

$$-1.0000 - 1.4142i$$

```
>> zero(tf(n,d))
```

zeros

ans =

$$-2.2808$$

$$-0.2192$$

Lecture 64 - Page 7

>> t = tf(n,d) ← transfer function

Transfer function:

$$2s^2 + 5s + 1$$

$$s^2 + 2s + 3$$

>> pole(t) ← poles

ans =

$$-1.0000 + 1.4142i$$

$$-1.0000 - 1.4142i$$

>> zero(t) ← zeros

ans =


$$-2.2808$$

$$-0.2192$$

>>

>> pzmap(t) ← pole zero map

>> grid

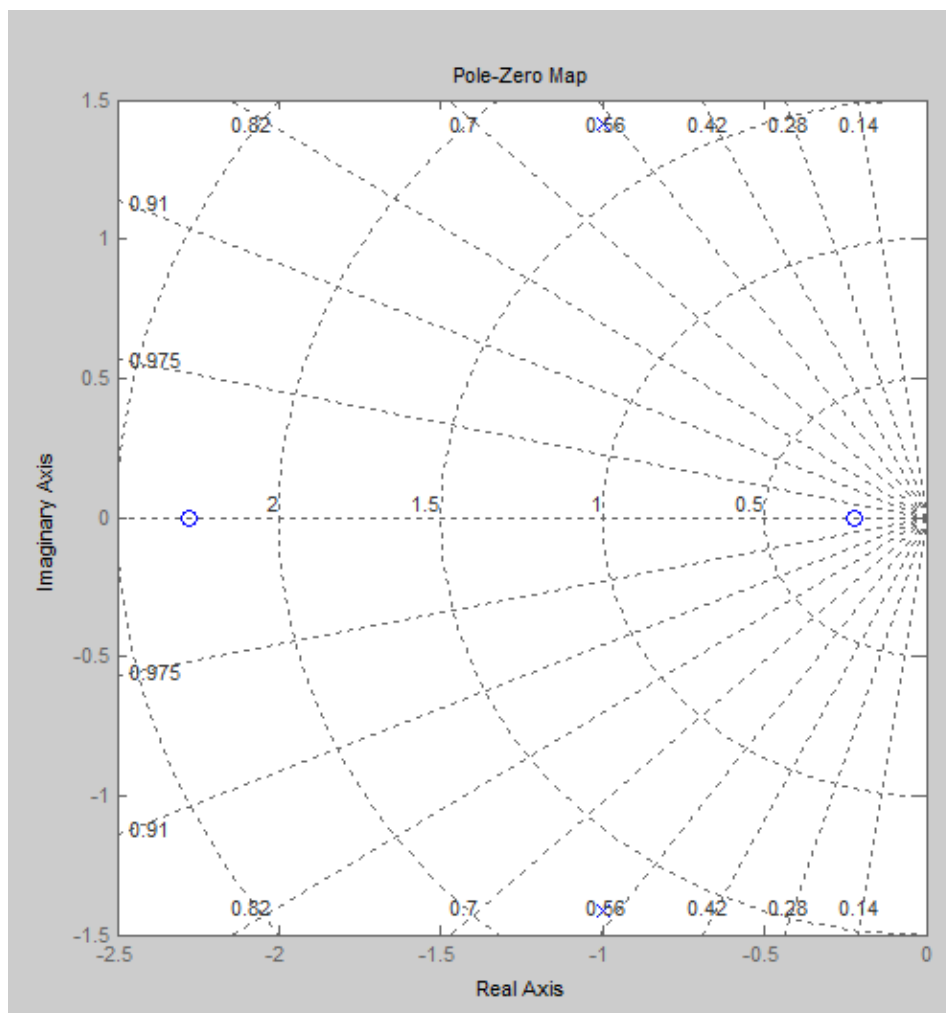

Lecture 64 - Page 8

```
>> num = [1 1]
```

```
num =
```

```
1 1
```

```
>> den = [1 2 2]
```

```
den =
```

```
1 2 2
```

```
>> H = tf(num, den)
```

← transfer function


Transfer function:

$s + 1$


 $s^2 + 2s + 2$

```
>> pzmap(H)
```


← pole zero map

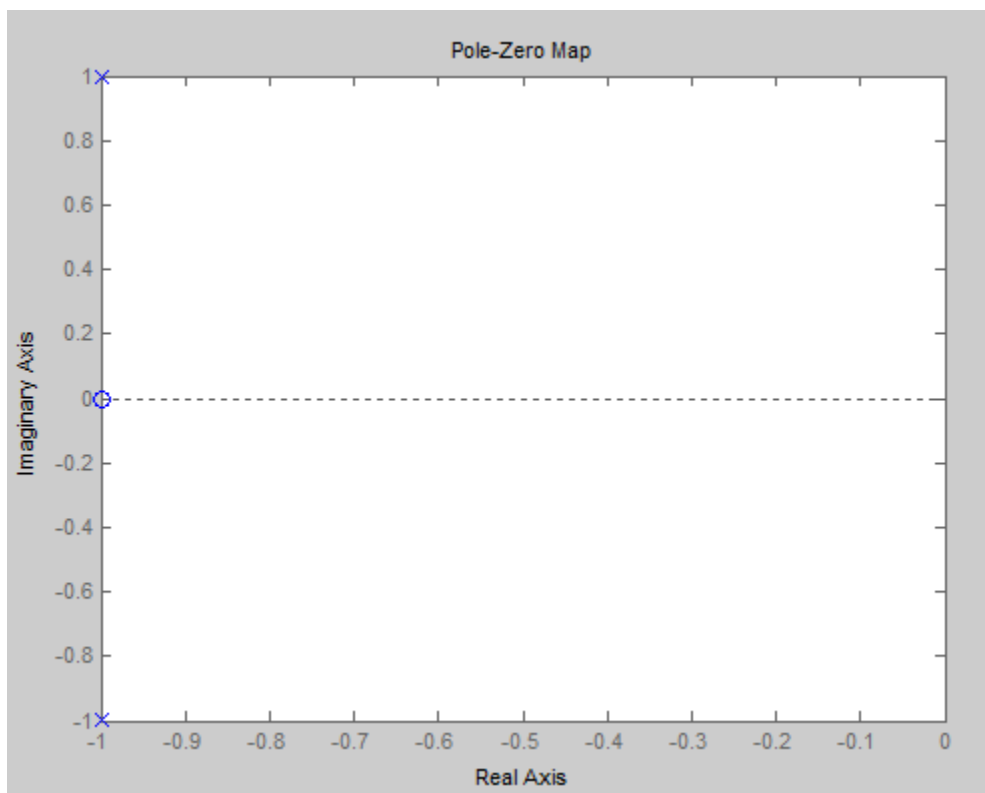

impulse(H) ← *Impulse Response*

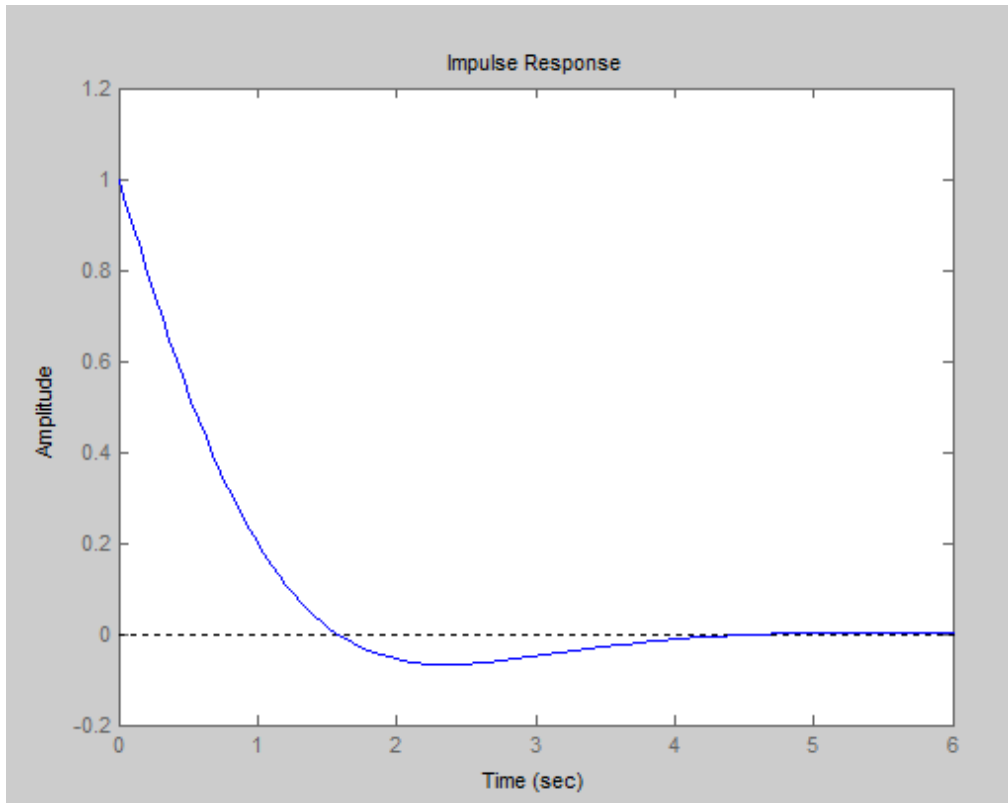

step(H) ← *step response*

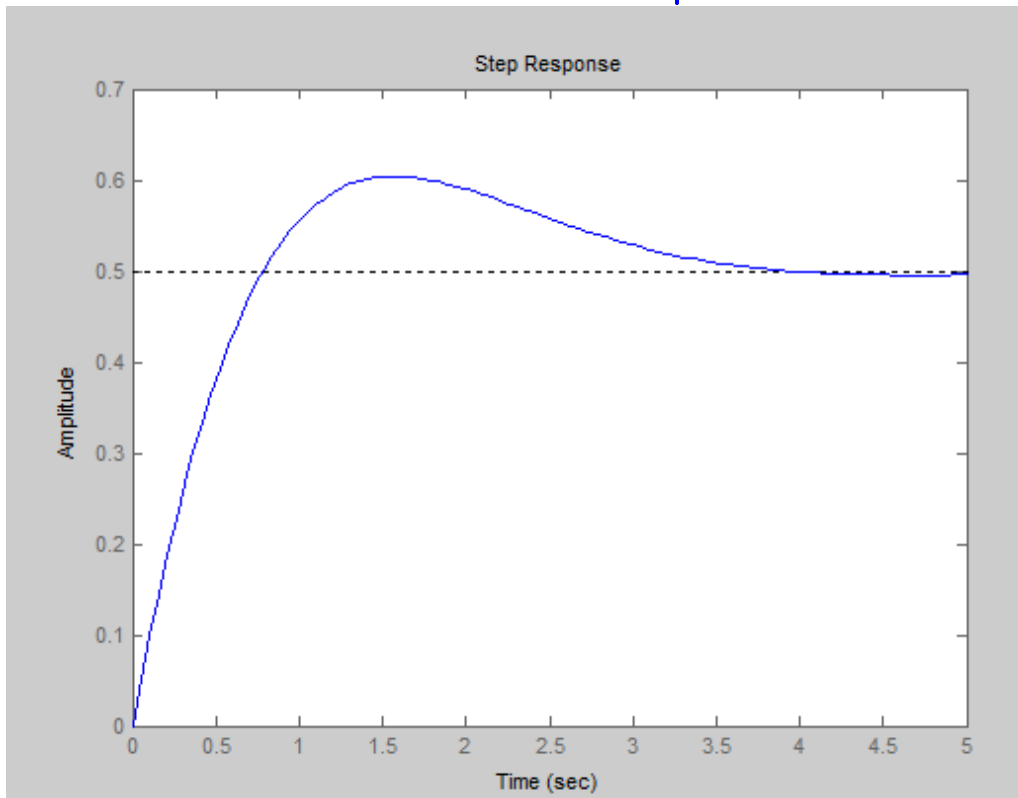

Bode(H) ← Bode Plot

