
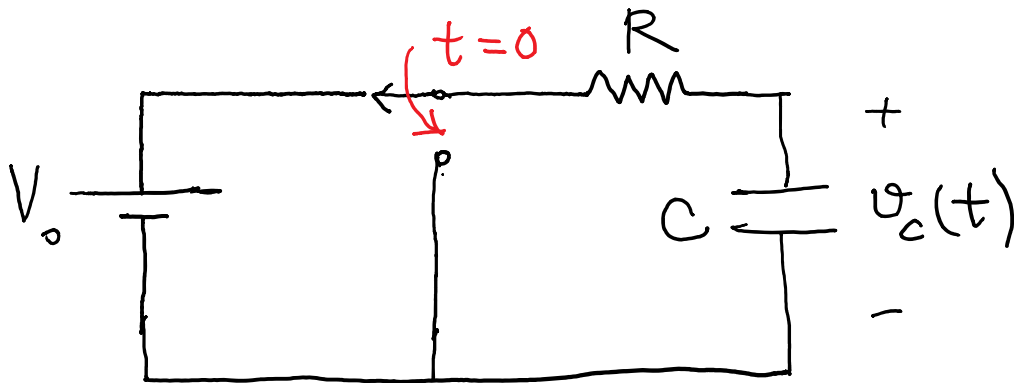


RC & RL First Order Circuits

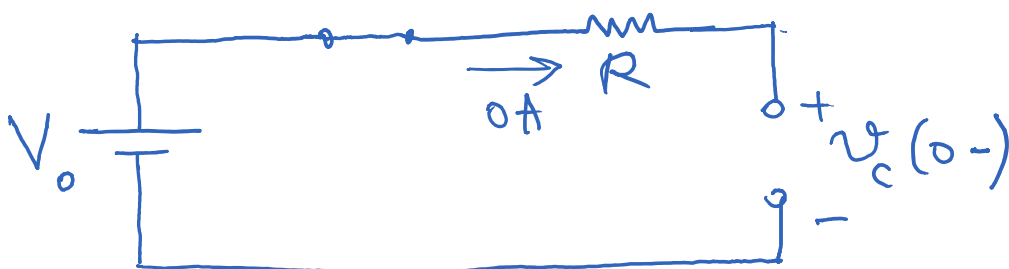


$t = 0^-$ dc-conditions



$$v_c(0^-) = V_0$$

$t > 0$

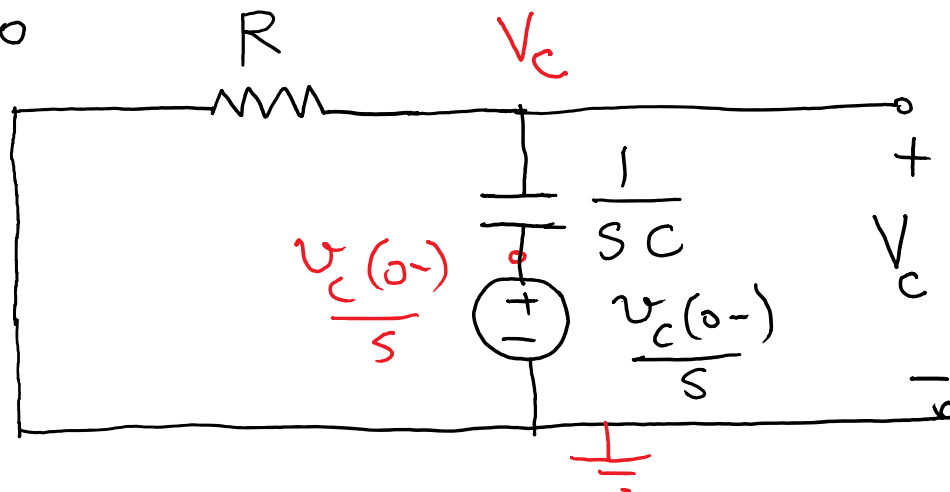

Node Analysis:

$$\frac{0 - V_c}{R} + \frac{\frac{v_c(0^-)}{s} - V_c}{\frac{1}{sC}} = 0$$

$$V_c \left[\frac{1}{CR} + s \right] = v_c(0-)$$

$$V_c = \frac{v_c(0-)}{\frac{1}{CR} + s}$$

$$v_c(0-) = V_0$$

$$v_c(t) = V_0 e^{-\frac{t}{CR}} u(t)$$


$t > 0$

$\tau = CR$
(time constant (seconds))


$$v_c(t) = V_0 e^{-\frac{t}{\tau}} u(t)$$


$t > 0$

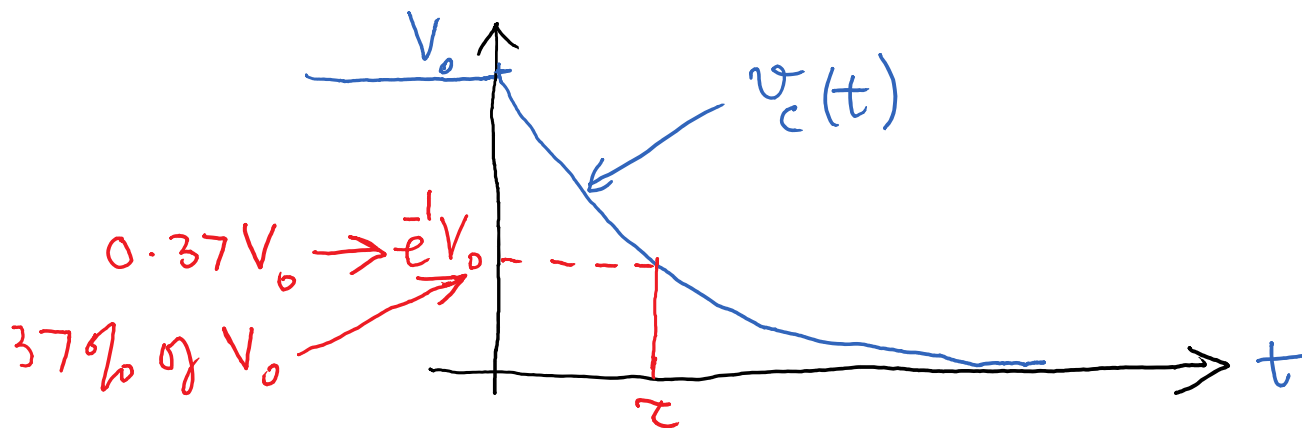time constant: Measure of how fast or how slow a circuit responds to a change




t	$v_c(t)$
τ	$.37V_0$
2τ	$.14V_0$
$\vdots$	
5τ	$0.01V_0 \leftarrow 1\% \text{ of } V_0$

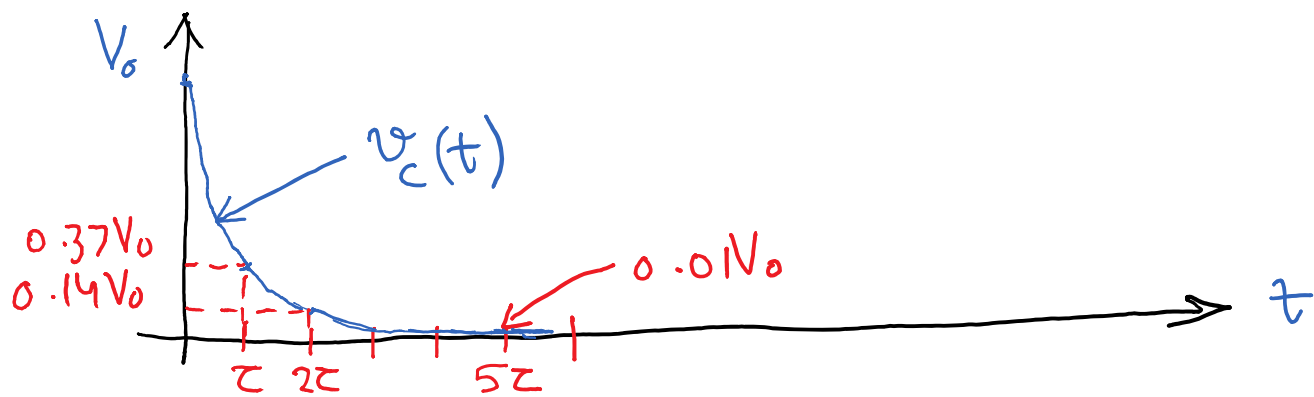


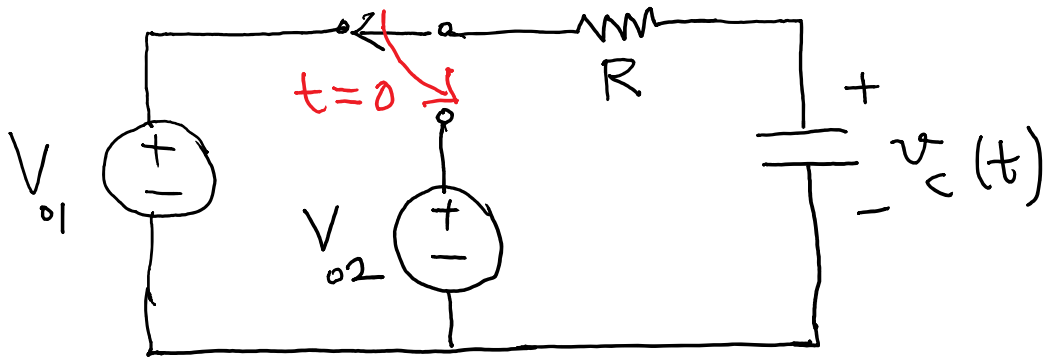


$t = 0^-$ ac-conditions

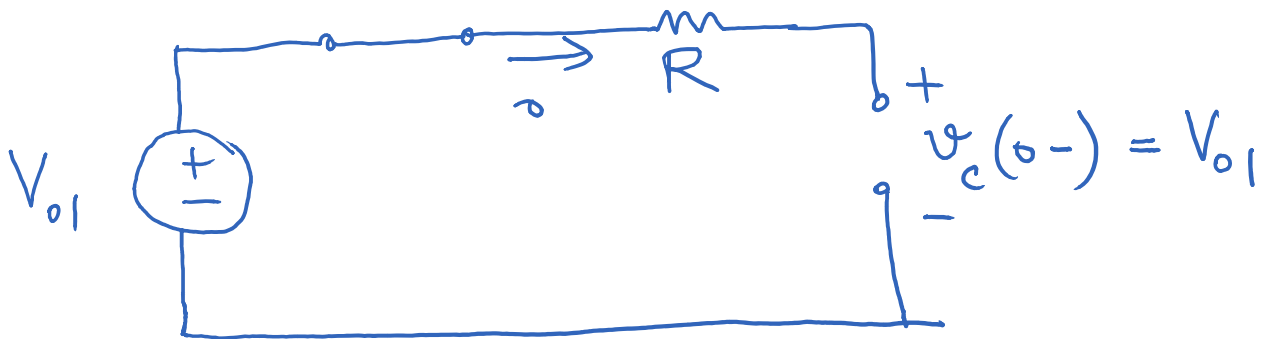


$t > 0$

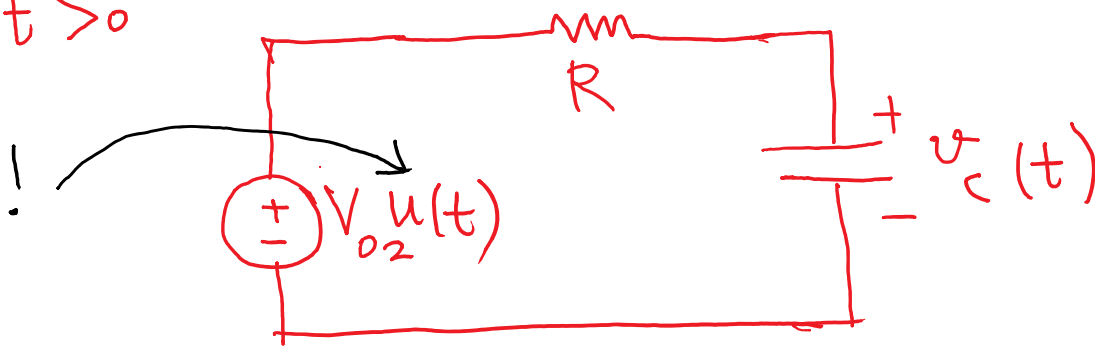

$t \rightarrow \infty$ dc-conditions

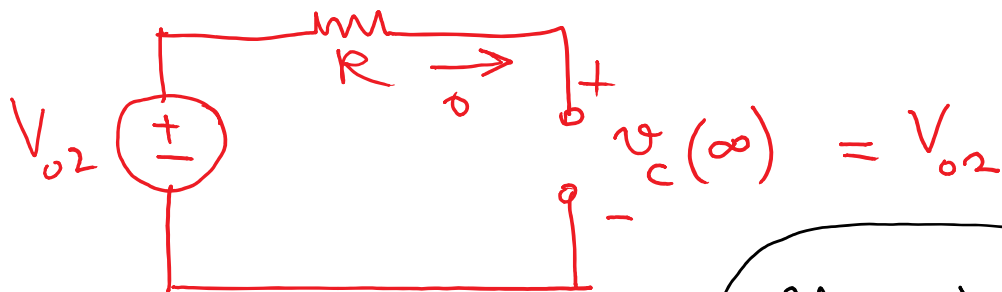

$$v_c(\infty) = V_{o2}$$

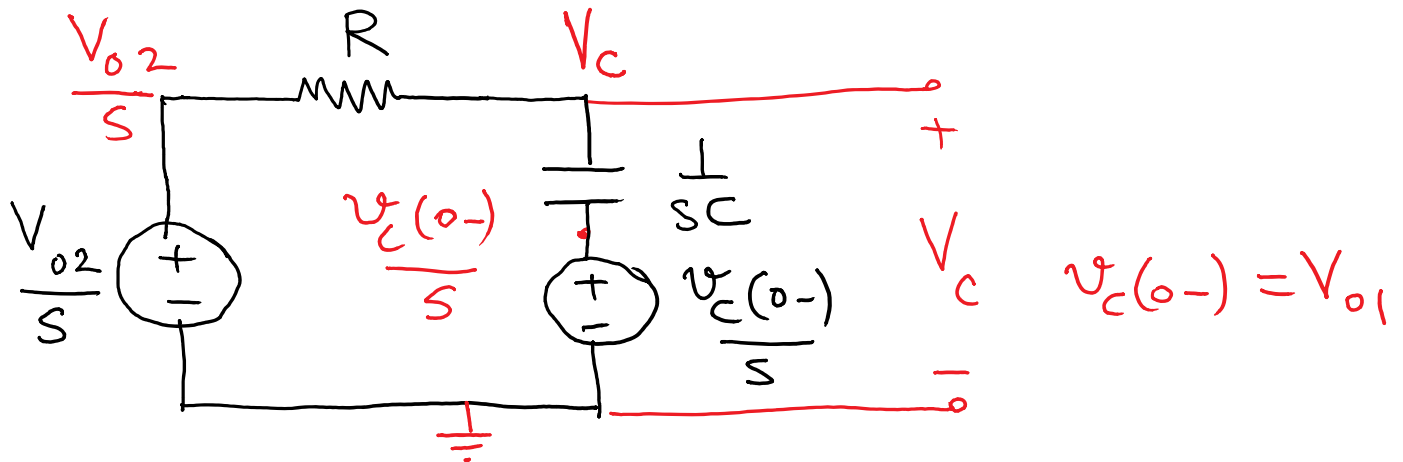

Node Analysis:

$$\frac{\frac{V_{o2}}{s} - V_c}{R} + \frac{\frac{v_c(0-)}{s} - V_c}{\frac{1}{sC}} = 0$$

$$V_c \left(\frac{1}{RC} + s \right) = \frac{1}{RC} \frac{V_{o2}}{s} + V_{o1}$$

$$V_c = \frac{1}{RC} \frac{V_{o2}}{s \left(s + \frac{1}{RC} \right)} + \frac{V_{o1}}{s + \frac{1}{RC}}$$

$$\frac{1}{s \left(s + \frac{1}{RC} \right)} = \frac{A}{s} + \frac{B}{s + \frac{1}{RC}} \quad A = \left. \frac{1}{s + \frac{1}{RC}} \right|_{s=0} = RC$$

$$B = \left. \frac{1}{s} \right|_{s=-\frac{1}{RC}} = -RC$$


$$\frac{1}{s \left(s + \frac{1}{RC} \right)} = \frac{RC}{s} - \frac{RC}{s + \frac{1}{RC}}$$


$$V_c = \frac{V_{o2}}{s} - \frac{V_{o2}}{s + \frac{1}{RC}} + \frac{V_{o1}}{s + \frac{1}{RC}}$$

$$v_c(t) = V_{o2}u(t) - V_{o2}e^{-\frac{t}{RC}}u(t) + V_{o1}e^{-\frac{t}{RC}}u(t)$$


$$v_c(t) = \left[(V_{o1} - V_{o2})e^{-\frac{t}{\tau}} + V_{o2} \right] u(t)$$

$\tau = RC$ time constant (sec.)

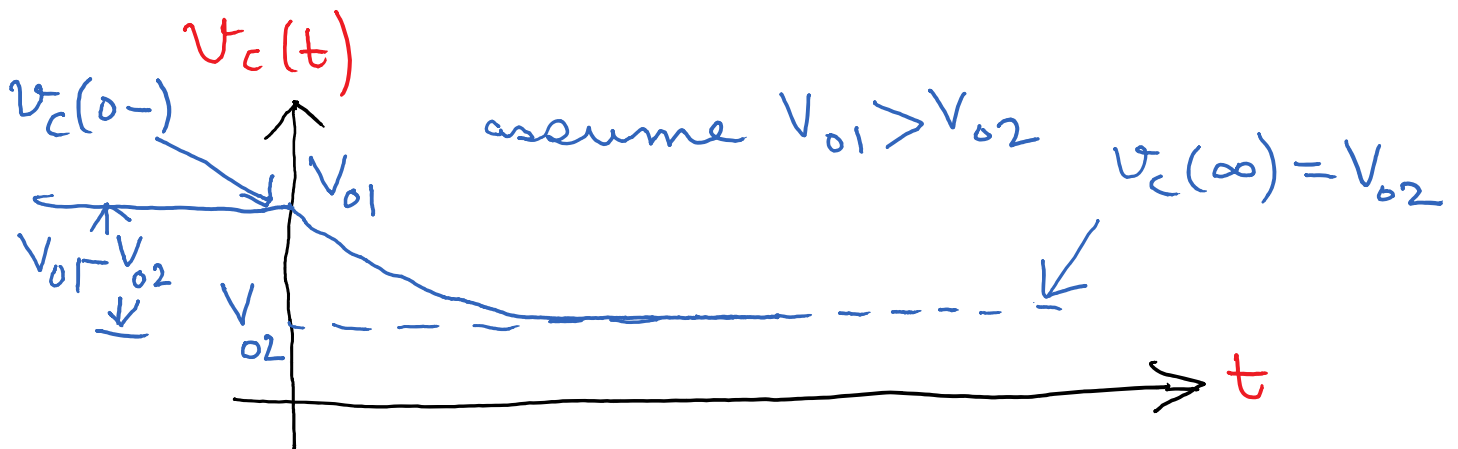

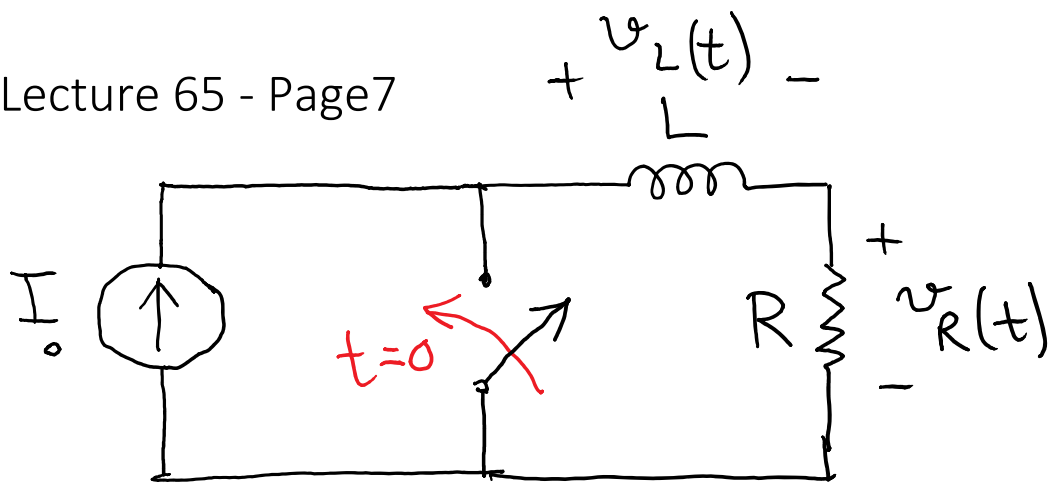


$t = 0^-$ dc-conditions

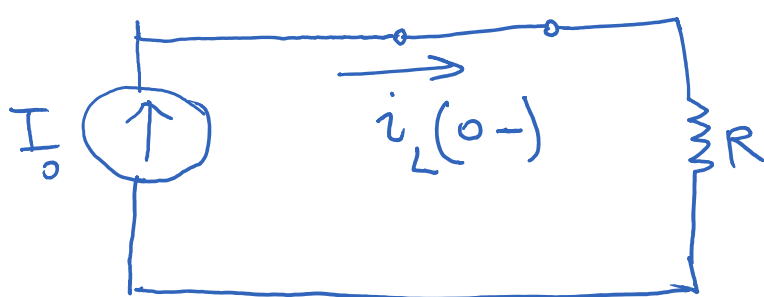


$$i_L(0^-) = I_0$$

$t > 0$

$t \rightarrow \infty$ dc-conditions

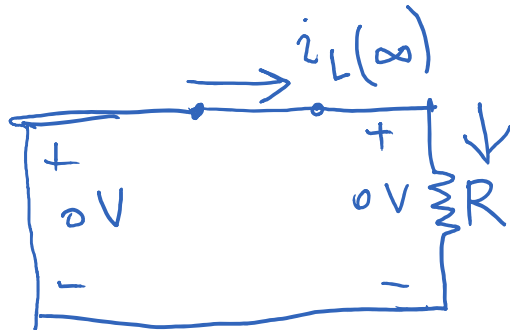

$$i_L(\infty) = 0$$

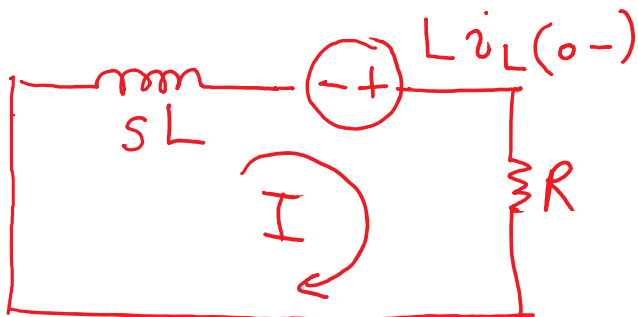

Mesh Analysis: $sLI - L i_L(0^-) + RI = 0$

$$I(sL + R) = L \dot{v}_L(0^-) \quad \dot{v}_L(0^-) = I_0$$

$$I = \frac{L I_0}{sL + R} = \frac{I_0}{s + \frac{R}{L}}$$

$$V_L = sLI - L \dot{v}_L(0^-)$$

$$V_L = \frac{sL}{s + \frac{R}{L}} I_0 - L I_0$$

$$= L I_0 \left(\frac{s}{s + \frac{R}{L}} - 1 \right)$$


$$s + \frac{R}{L} \overline{\begin{array}{r} s \\ -s + \frac{R}{L} \\ \hline -\frac{R}{L} \end{array}} \quad \frac{s}{s + \frac{R}{L}} = 1 - \frac{\frac{R}{L}}{s + \frac{R}{L}}$$

$$V_L = L I_0 \left(1 - \frac{\frac{R}{L}}{s + \frac{R}{L}} - 1 \right)$$


$$V_L = -I_0 R \frac{1}{s + \frac{R}{L}}$$

$$v_L(t) = -I_0 R e^{-\frac{R}{L}t} u(t) = -I_0 R e^{-\frac{t}{\tau}} u(t)$$

$\tau = \frac{L}{R}$ time constant

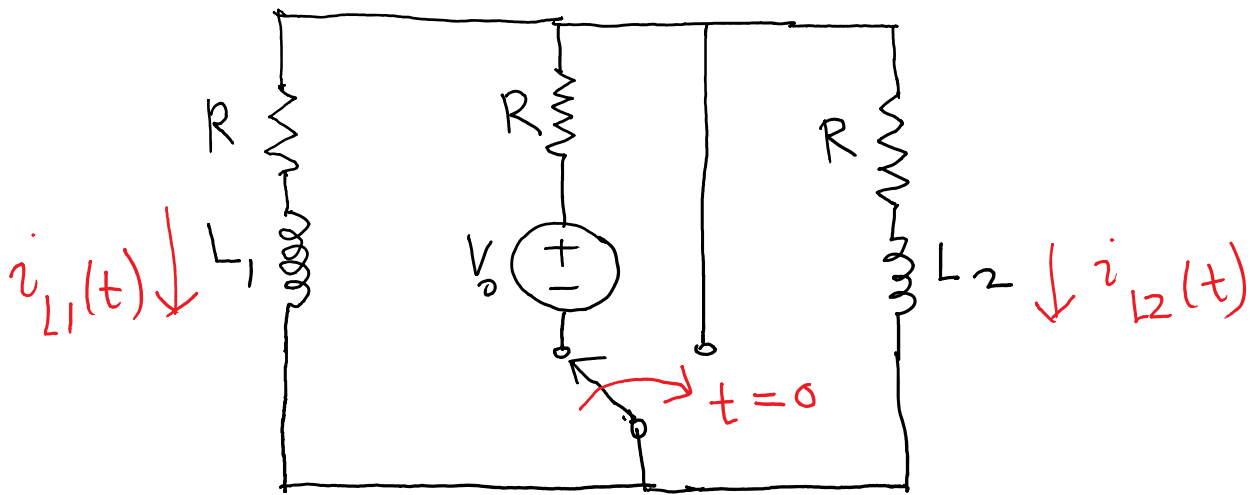

$t = 0^-$ dc conditions

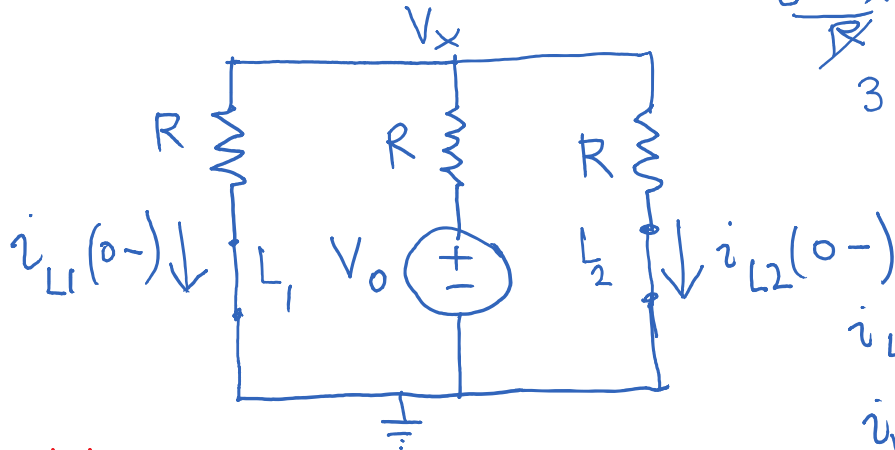

$$\frac{0 - V_x}{R} + \frac{V_0 - V_x}{R} + \frac{0 - V_x}{R} = 0$$

$$3V_x = V_0$$


$$V_x = \frac{V_0}{3}$$

$$i_{L1}(0^-) = \frac{V_x}{R} = \frac{1}{3} \frac{V_0}{R}$$

$$i_{L2}(0^-) = \frac{V_x}{R} = \frac{1}{3} \frac{V_0}{R}$$


$t > 0$

$t \rightarrow \infty$ dc-conditions

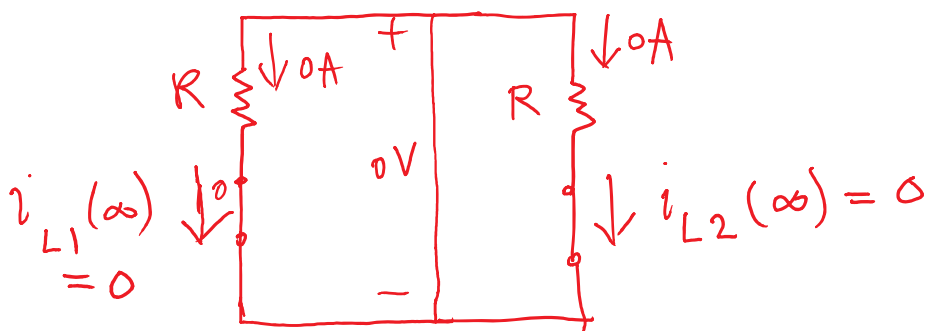

$$i_{L1}(\infty) = 0$$

$$i_{L2}(\infty) = 0$$

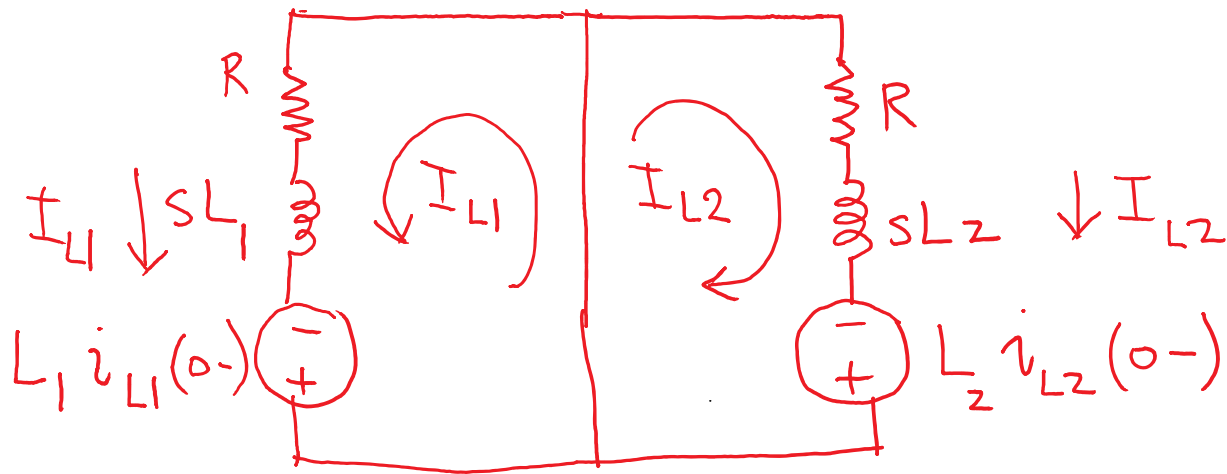

$$RI_{L2} + sL_2 I_{L2} - L_2 \dot{i}_{L2}(0-) = 0$$

$$\dot{i}_{L2}(0-) = \frac{1}{3} \frac{V_0}{R}$$

$$(R + sL_2) I_{L2} = \frac{1}{3} L_2 \frac{V_0}{R}$$

$$I_{L2} = \frac{1}{3} \frac{V_0}{R} \frac{1}{s + \frac{R}{L_2}}$$

$$i_{L2}(t) = \frac{1}{3} \frac{V_0}{R} e^{-\frac{R}{L_2} t} u(t) = \frac{1}{3} \frac{V_0}{R} e^{-\frac{t}{\tau_2}} u(t)$$


$$\tau_2 = \frac{L_2}{R}$$

similarly

$$i_{L1}(t) = \frac{1}{3} \frac{V_0}{R} e^{-\frac{t}{\tau_1}} u(t) \quad \tau_1 = \frac{L_1}{R}$$

In general for a stable
first order LTI system

single real pole $-s$

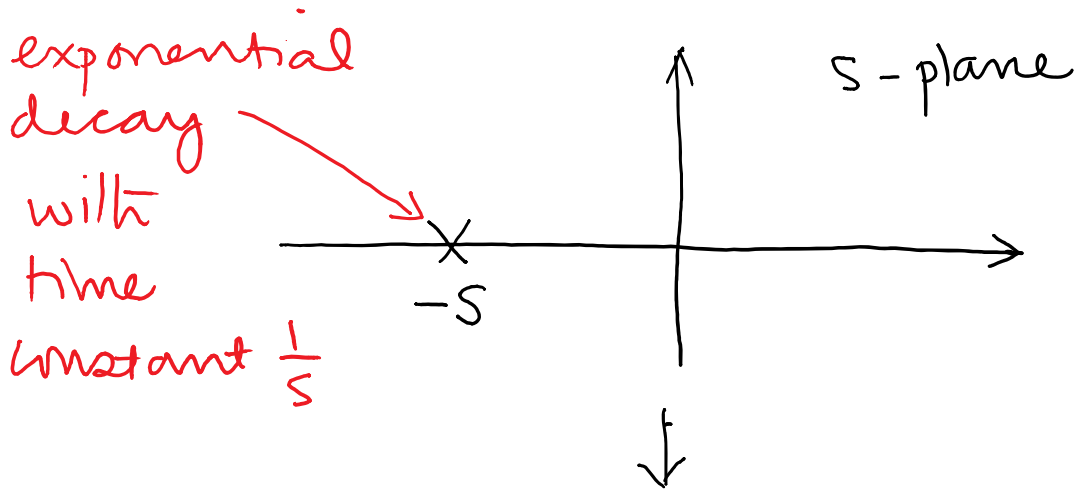

exponential decay
 $e^{-st} u(t)$

with time constant

$$\tau = \frac{1}{s}$$