
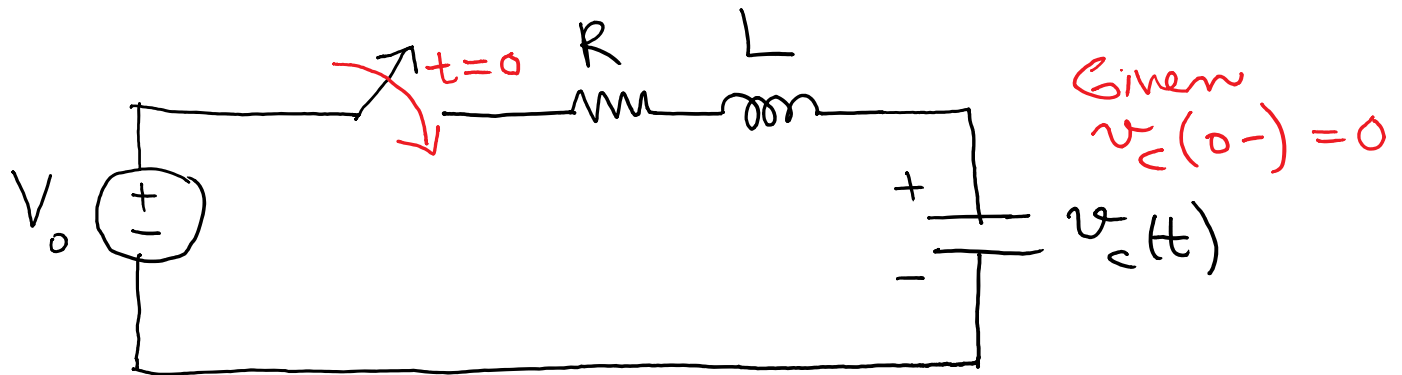


RLC Second Order Circuits


Series RLC circuit

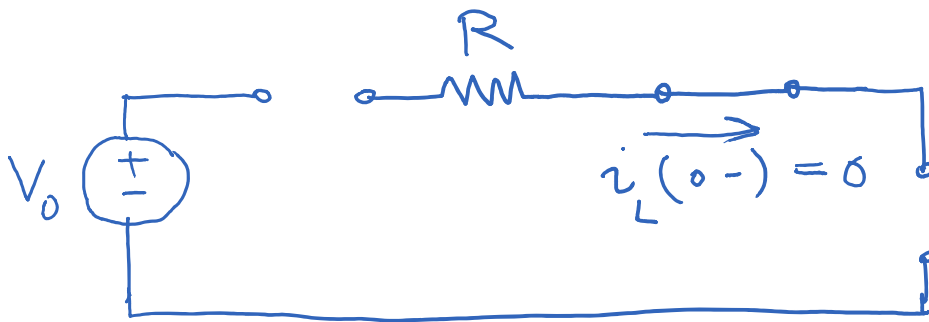


$t = 0^-$ dc-conditions




$t \rightarrow \infty$ dc-conditions.

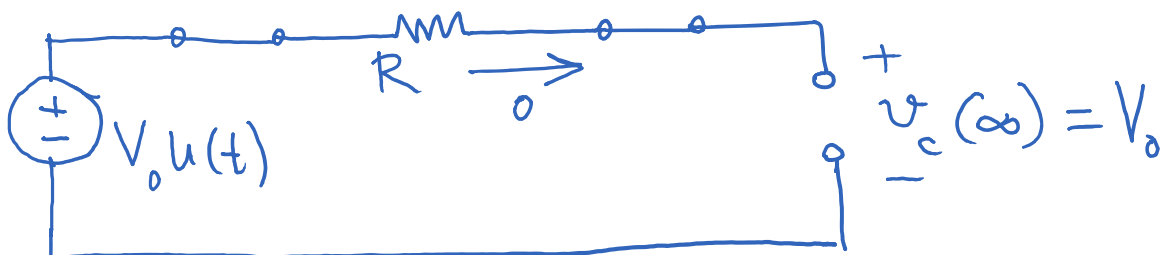

$t > 0$

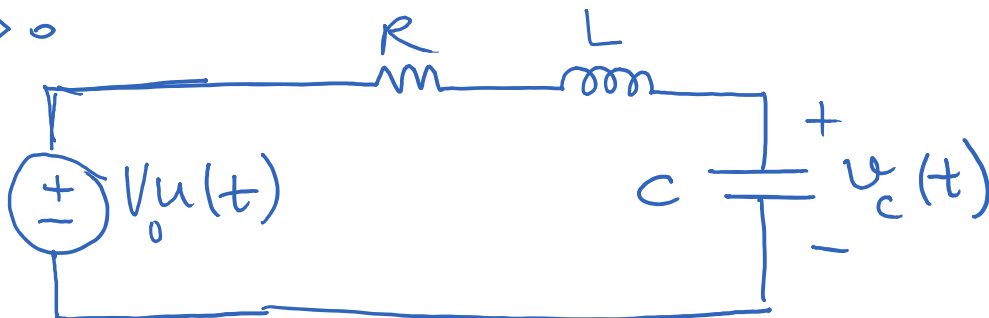

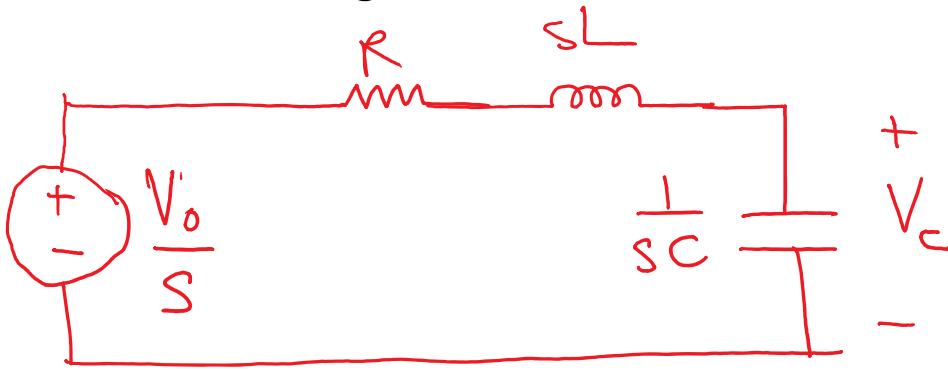

$$V_c = \frac{\frac{1}{sC}}{R + sL + \frac{1}{sC}} \frac{V_o}{s}$$

$$V_c = \frac{1}{LC} \frac{1}{s^2 + s \left(\frac{R}{L} \right) + \left(\frac{1}{LC} \right)} \frac{V_o}{s}$$

The term $\frac{1}{s^2 + s \left(\frac{R}{L} \right) + \left(\frac{1}{LC} \right)}$ is circled in blue and labeled "Transfer function $H(s)$ ". The term $\frac{V_o}{s}$ is labeled "input". A blue arrow points from the $\frac{1}{LC}$ term to ω_o^2 . Another blue arrow points from the $\frac{R}{L}$ term to 2α .

define $\alpha = \frac{R}{2L}$ $\omega_o = \frac{1}{\sqrt{LC}}$

$$H(s) = \frac{\omega_o^2}{s^2 + 2\alpha s + \omega_o^2}$$

α : Damping Coefficient

ω_o : Resonant frequency

$$H(s) = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2}$$



poles

$$s_{1,2} = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2}$$

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$j\text{Im}s$

s -plane

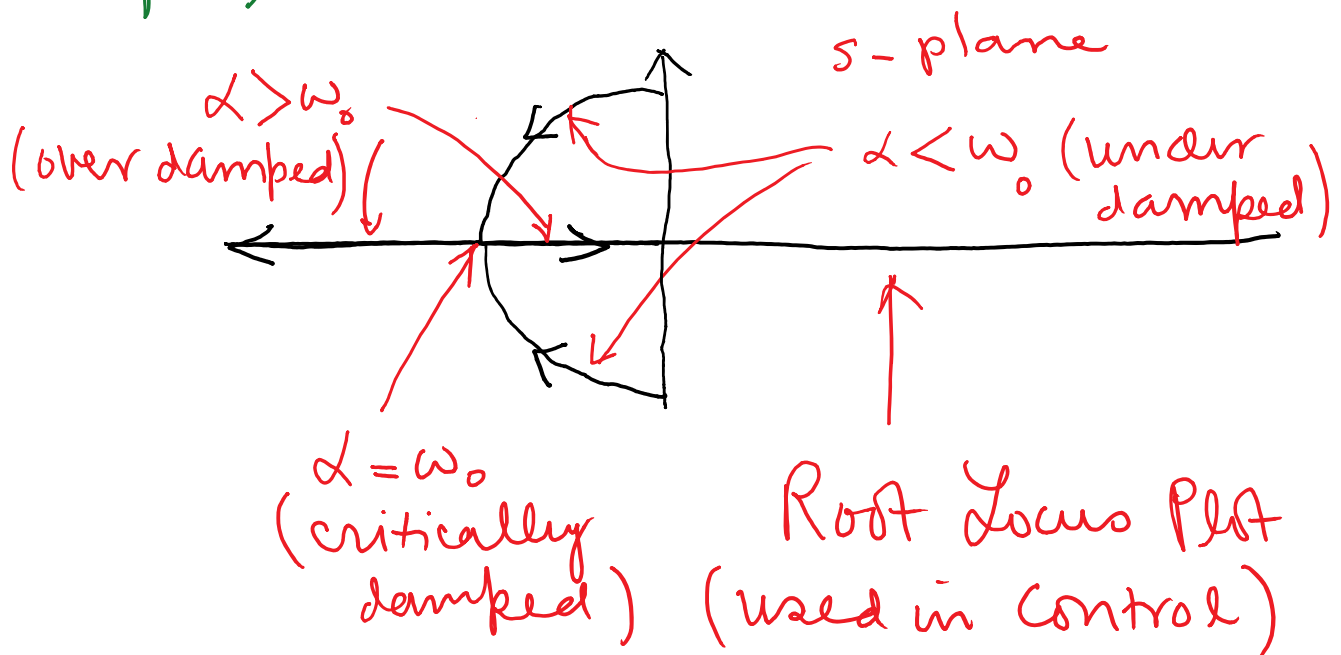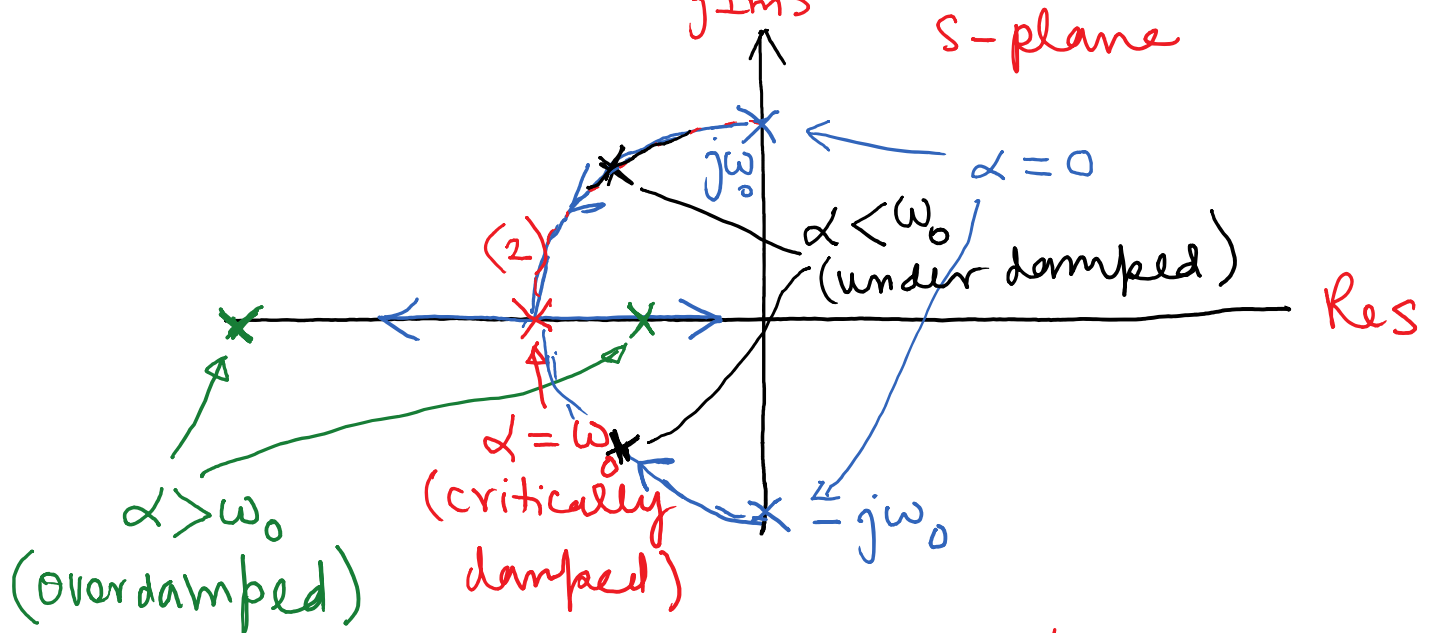


$$V_c = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2} \frac{V_0}{s}$$

poles: $s=0$, $s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$

$$V_c = V_0 \omega_0^2 \left[\frac{A}{s} + \frac{B}{s + \alpha + \sqrt{\alpha^2 - \omega_0^2}} + \frac{C}{s + \alpha - \sqrt{\alpha^2 - \omega_0^2}} \right]$$

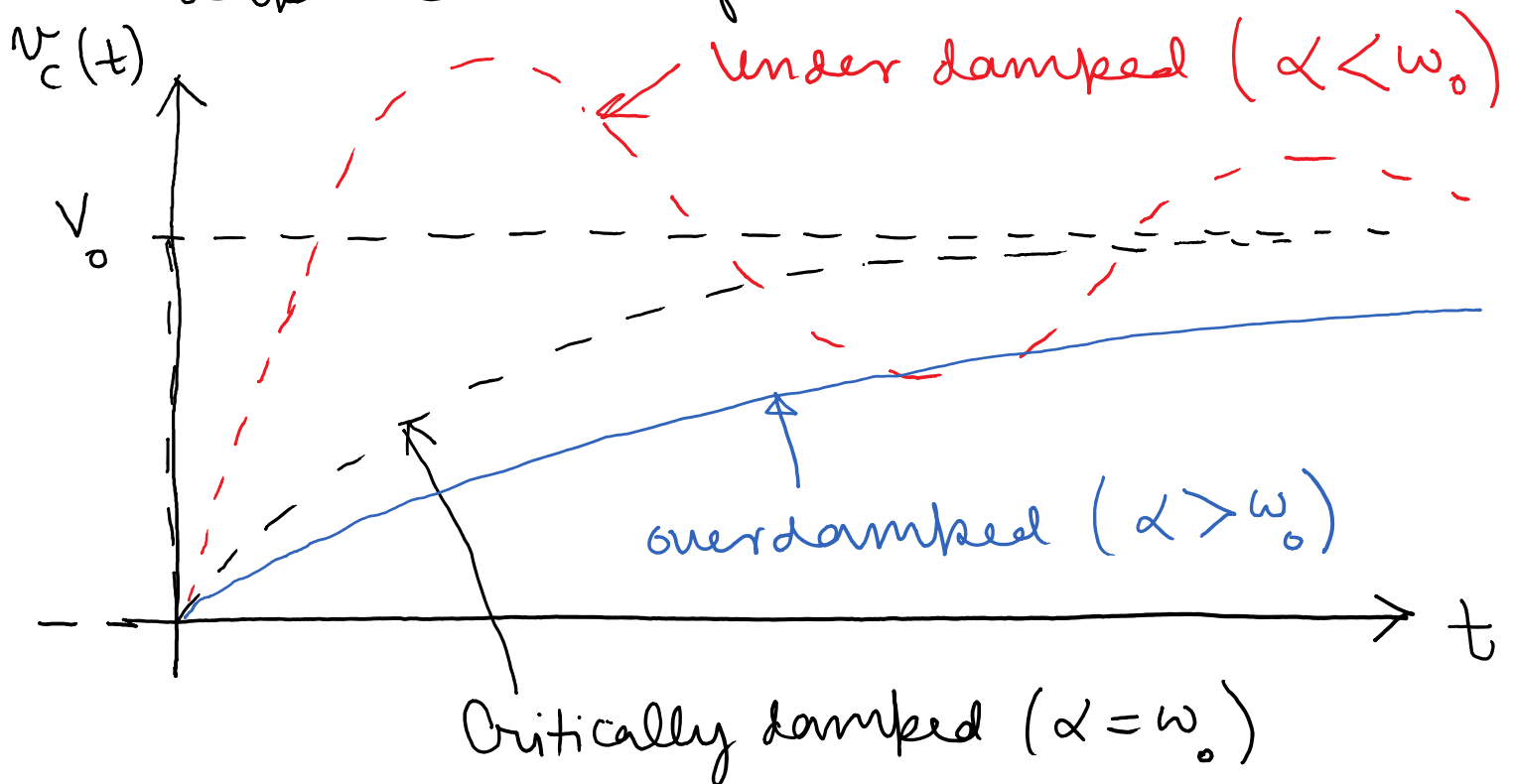solve for A, B & C then take inverse Laplace transform



```
>> w0=100;  
>> alpha=w0/2;  
>> num=[0, 0, w0*w0];  
>> den=[1, 2*alpha, w0*w0];  
>> H=tf(num, den)
```


MATLAB example
 $\alpha = \frac{\omega_0}{2}$
(under damped)

H =

$$\frac{10000}{s^2 + 100 s + 10000}$$

Continuous-time transfer function.

```
>> step(H)  
>>
```

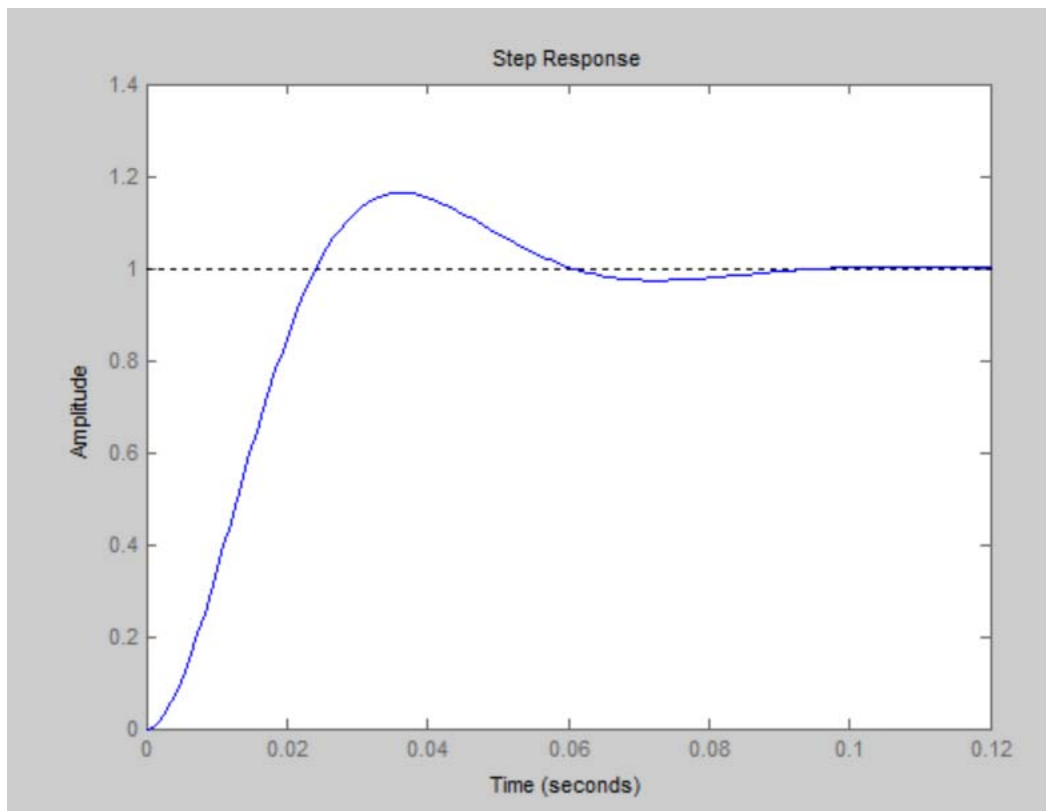

```
>> w0=100;  
>> alpha=w0;  
>> num=[0, 0, w0*w0];  
>> den=[1, 2*alpha, w0*w0];  
>> H=tf(num, den)
```


MATLAB Example
 $\alpha = \omega_0$
(critically damped)

H =

$$\frac{10000}{s^2 + 200s + 10000}$$

Continuous-time transfer function.

```
>> step(H)  
>>
```

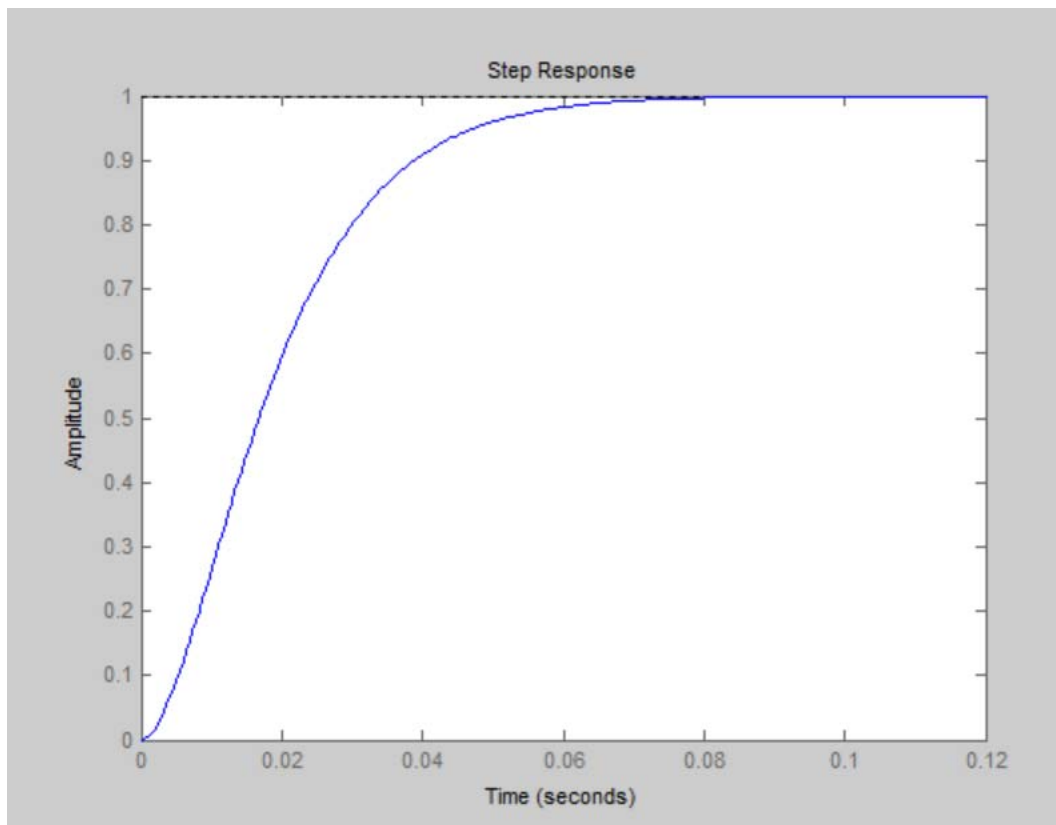

```
>> w0=100;  
>> alpha=2*w0;  
>> num=[0, 0, w0*w0];  
>> den=[1, 2*alpha, w0*w0];  
>> H=tf(num, den)
```


MATLAB Example
over damped
 $\alpha = 2\omega_0$

H =

$$\frac{10000}{s^2 + 400s + 10000}$$

Continuous-time transfer function.

```
>> step(H)  
>>
```

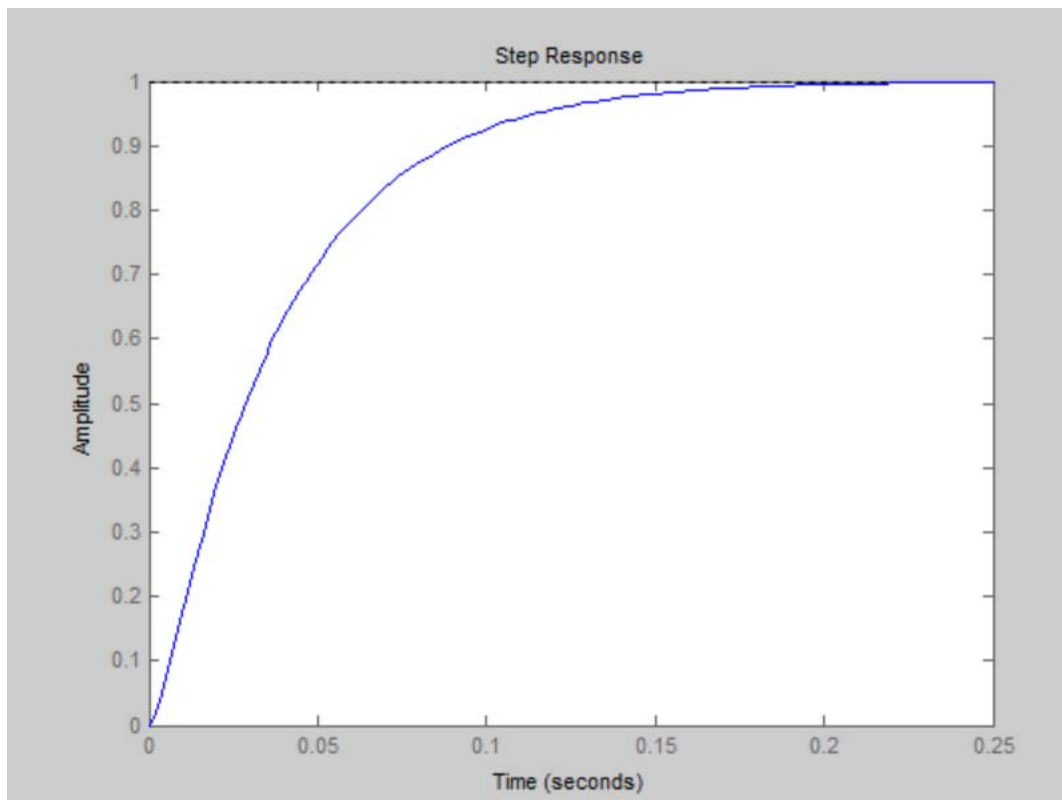

poles of transfer function

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

over damped. ($\alpha > \omega_0$)


two distinct real poles

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

exponential
decay
with time
constant $\frac{1}{|s_1|}$

exponential
decay
with time
constant $\frac{1}{|s_2|}$

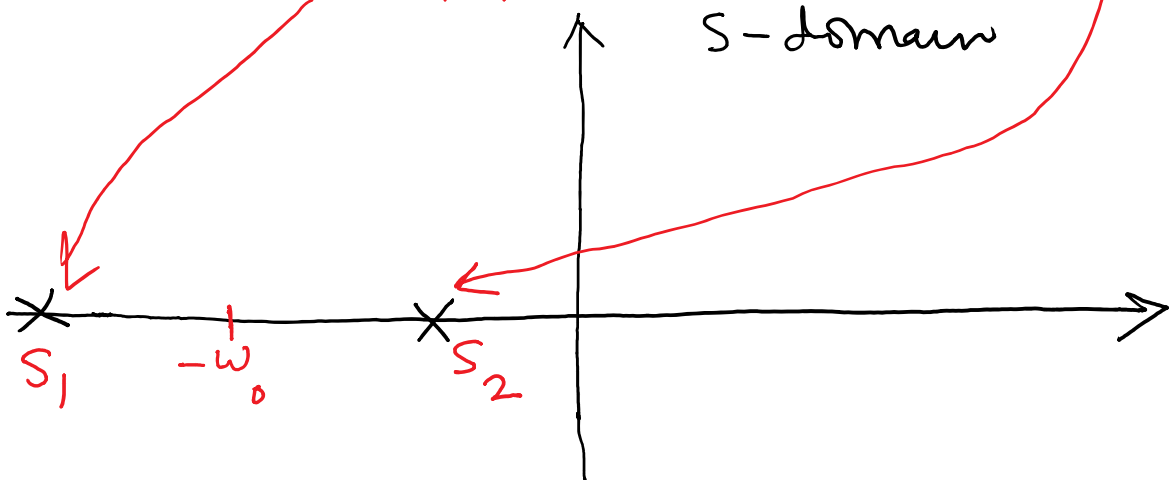

Underdamped ($\alpha < \omega_0$)

poles of transfer function


$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2} \quad \text{real}$$

over damped. ($\alpha > \omega_0$)


two distinct complex conjugate poles

$$s_1 = -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \quad s_2 = -\alpha - j\sqrt{\omega_0^2 - \alpha^2}$$

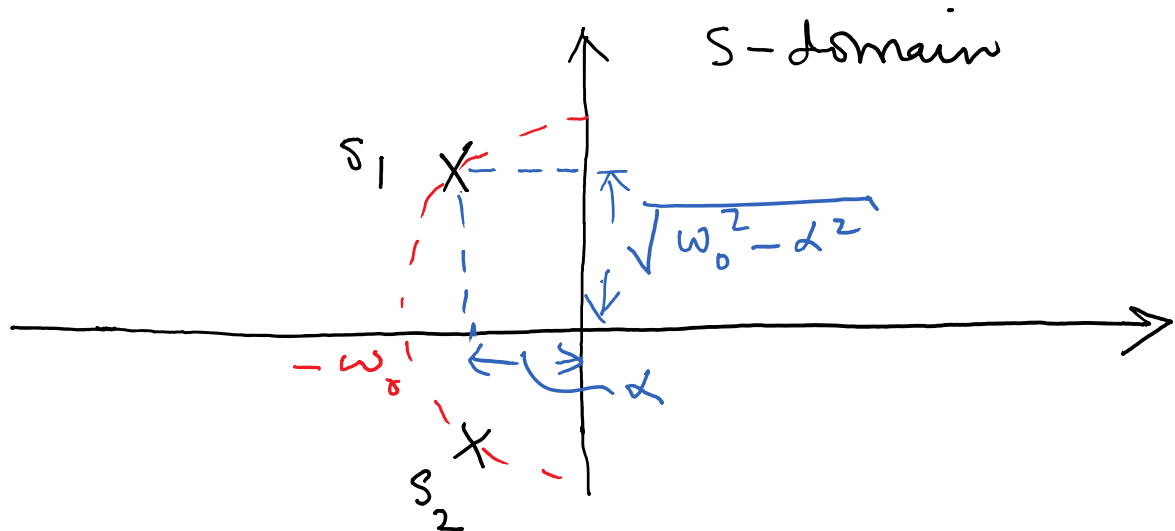
Sinusoidal frequency $\sqrt{\omega_0^2 - \alpha^2}$ with
exponential decay $e^{-\alpha t}$ with time
constant $\frac{1}{\alpha}$




Parallel RLC Circuit


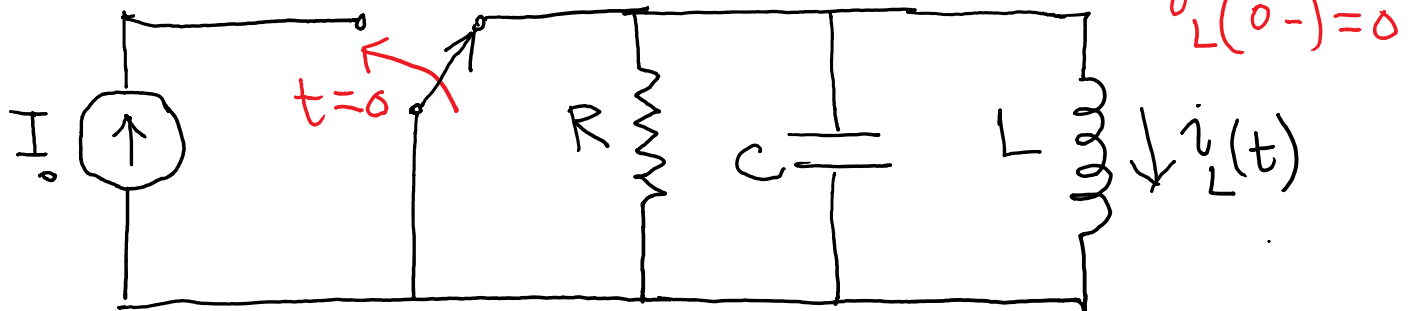


$t = 0^-$ dc-conditions

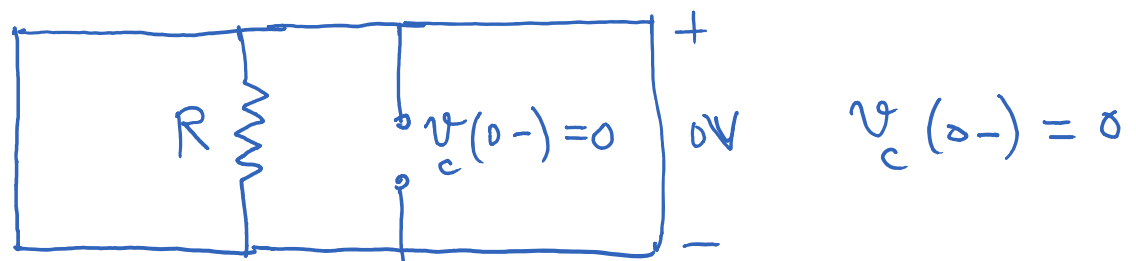

$t \rightarrow \infty$ dc-conditions

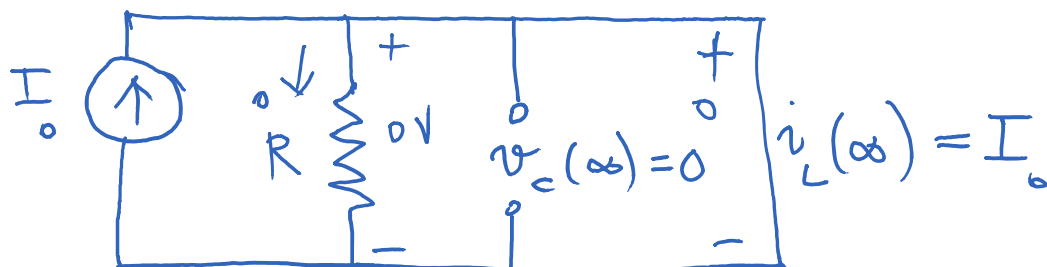

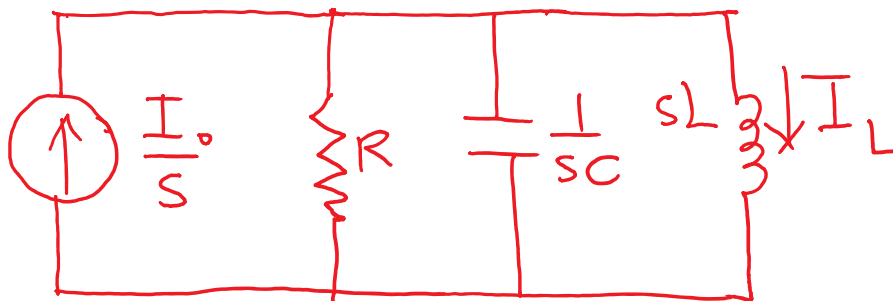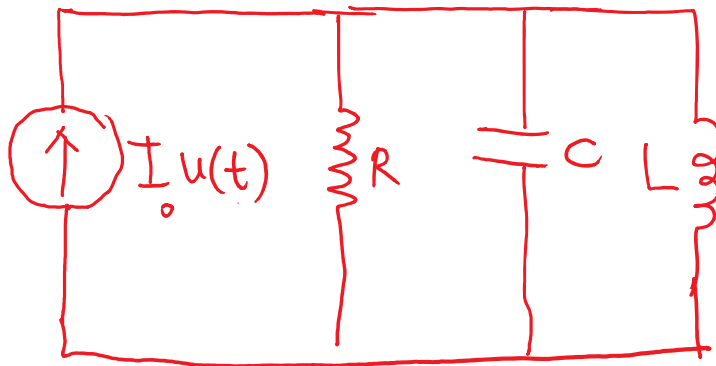$t > 0$ 

$$I_L = \frac{\frac{1}{sL}}{\frac{1}{R} + sC + \frac{1}{sL}} \frac{I_0}{s} \quad \text{current division}$$


$$= \frac{1}{CL} \frac{1}{s^2 + s \frac{1}{RL} + \frac{1}{CL}} \frac{I_0}{s}$$

define $\alpha = \frac{1}{2RL} \quad \omega_0 = \frac{1}{\sqrt{CL}}$

$$I_L = \frac{\omega_0^2}{s^2 + 2\alpha s + \omega_0^2} \frac{I_0}{s}$$

second order system

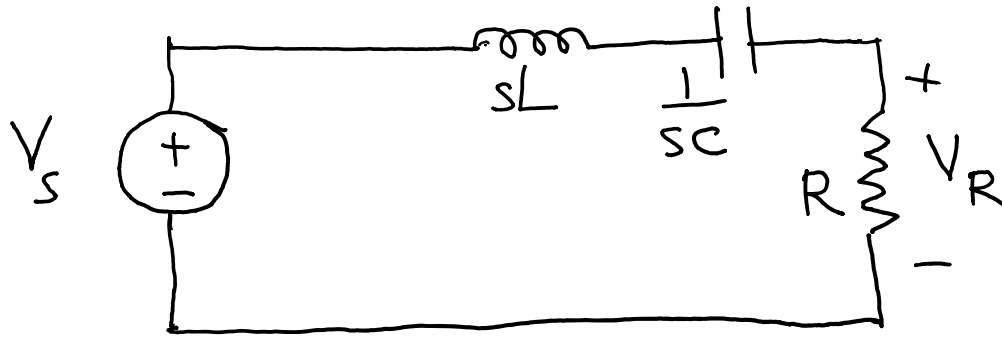Frequency Response of RLC Second order Circuits



zero initial conditions

$$V_R = \frac{R}{sL + \frac{1}{sC} + R} V_s$$

$$H(s) = \frac{V_R}{V_s} = \frac{R}{sL + \frac{1}{sC} + R}$$

$$H(s) = \frac{R}{L} \frac{s}{s^2 + s \frac{R}{L} + \frac{1}{LC}}$$

$$\alpha = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Damping coefficient

Resonant frequency

$$H(s) = \frac{2\alpha s}{s^2 + 2\alpha s + \omega_0^2}$$


to frequency domain

$$H(j\omega) = \frac{2\alpha j\omega}{-\omega^2 + 2\alpha j\omega + \omega_0^2}$$


$$= \frac{j2\alpha\omega}{(\omega_0^2 - \omega^2) + j2\alpha\omega}$$

$$M(\omega) = |H(j\omega)| = \frac{2\alpha\omega}{\sqrt{(\omega_0^2 - \omega^2)^2 + 4\alpha^2\omega^2}}$$

Magnitude
Frequency Response

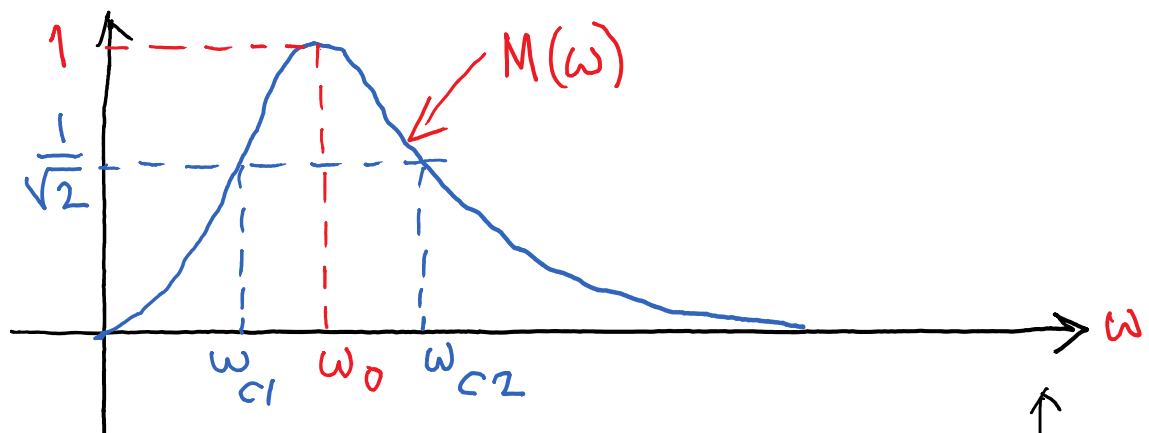

$$BW = \omega_{c2} - \omega_{c1}$$

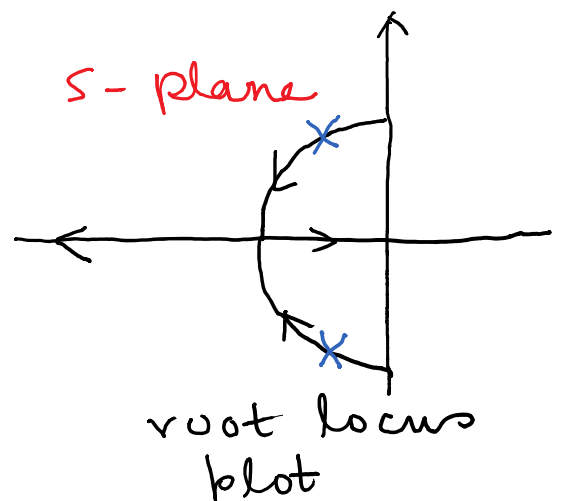

$$BW = \omega_{c2} - \omega_{c1}$$

$$\frac{1}{\sqrt{2}} = \frac{2\alpha\omega_c}{\sqrt{(\omega_o^2 - \omega_c^2) + 4\alpha^2\omega_c^2}}$$

$$\frac{1}{2} = \frac{4\alpha^2\omega_c^2}{(\omega_o^2 - \omega_c^2) + 4\alpha^2\omega_c^2}$$

$$(\omega_o^2 - \omega_c^2) + 4\alpha^2\omega_c^2 = 8\alpha^2\omega_c^2$$

$$(\omega_o^2 - \omega_c^2) = 4\alpha^2\omega_c^2$$


$$\omega_{c1} = -\alpha + \sqrt{\alpha^2 + \omega_o^2}$$

$$\omega_{c2} = \alpha + \sqrt{\alpha^2 + \omega_o^2}$$


$$BW = 2\alpha$$

$$\begin{aligned}\omega_{c1}\omega_{c2} &= (\sqrt{\alpha^2 + \omega_o^2})^2 - \alpha^2 \\ &= \alpha^2 + \omega_o^2 - \alpha^2 = \omega_o^2\end{aligned}$$
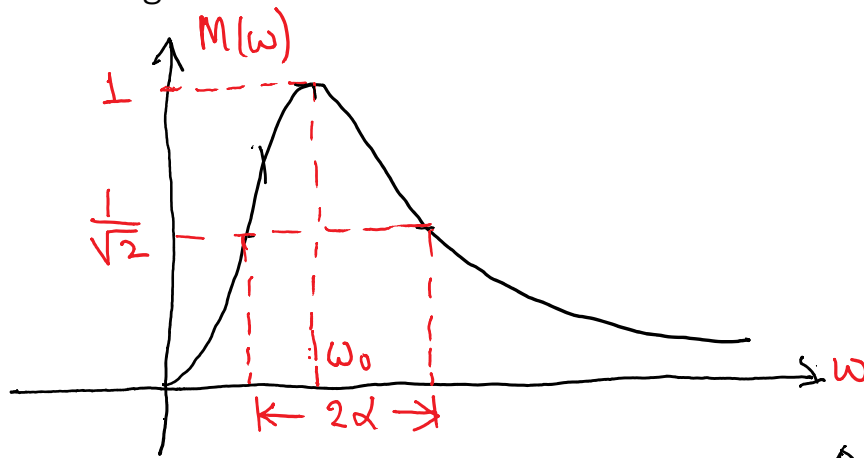
$$\omega_o = \sqrt{\omega_{c1}\omega_{c2}} \leftarrow \text{geometric mean}$$



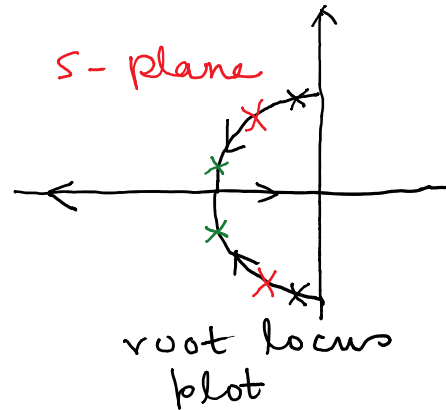
$$Q = \frac{\omega_0}{BW} = \frac{\omega_0}{2\alpha}$$



Quality Factor

M [dB] (Degree of selectivity)

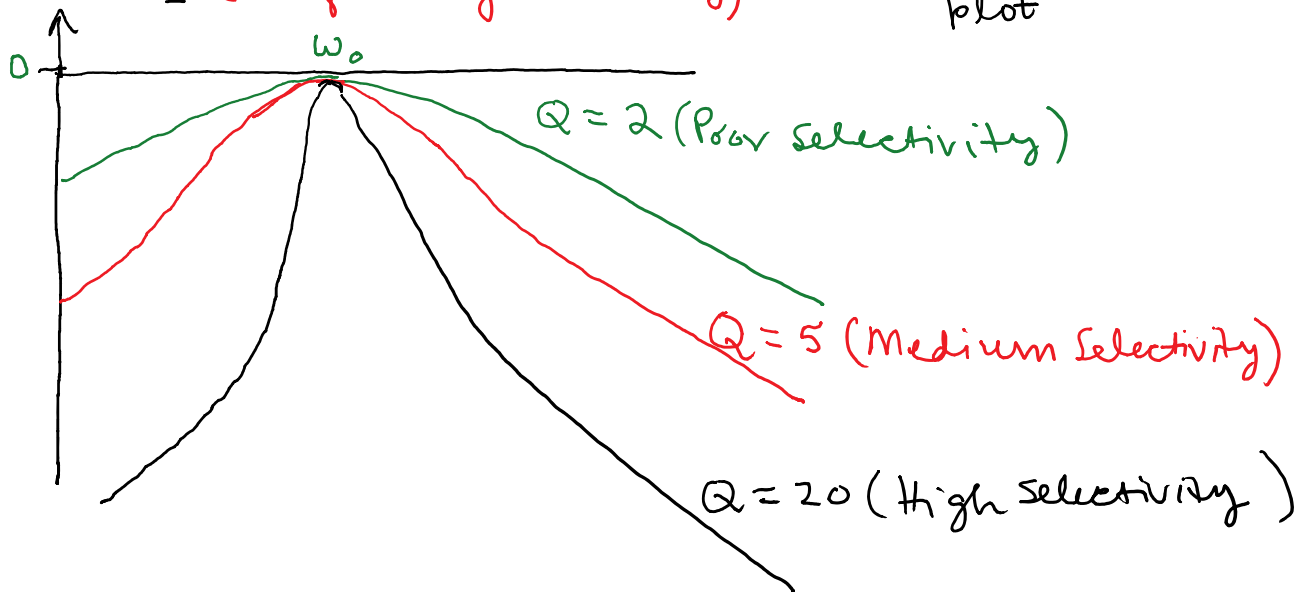

Bode Plot of M

```
>> w0=400;
>> alpha=10;
>> num = [0, 2*alpha, 0];
>> den = [1, 2*alpha, w0*w0];
>> H = tf(num, den)
```

H =

$$\frac{20 s}{s^2 + 20 s + 160000}$$

Continuous-time transfer function.

```
>> bode(H)
```

MATLAB example

$$Q = 20$$


$$\frac{w_0}{2\alpha} = 20$$

$$\alpha = \frac{w_0}{40}$$

choose

$$w_0 = 400$$

$$\alpha = \frac{400}{40} = 10$$

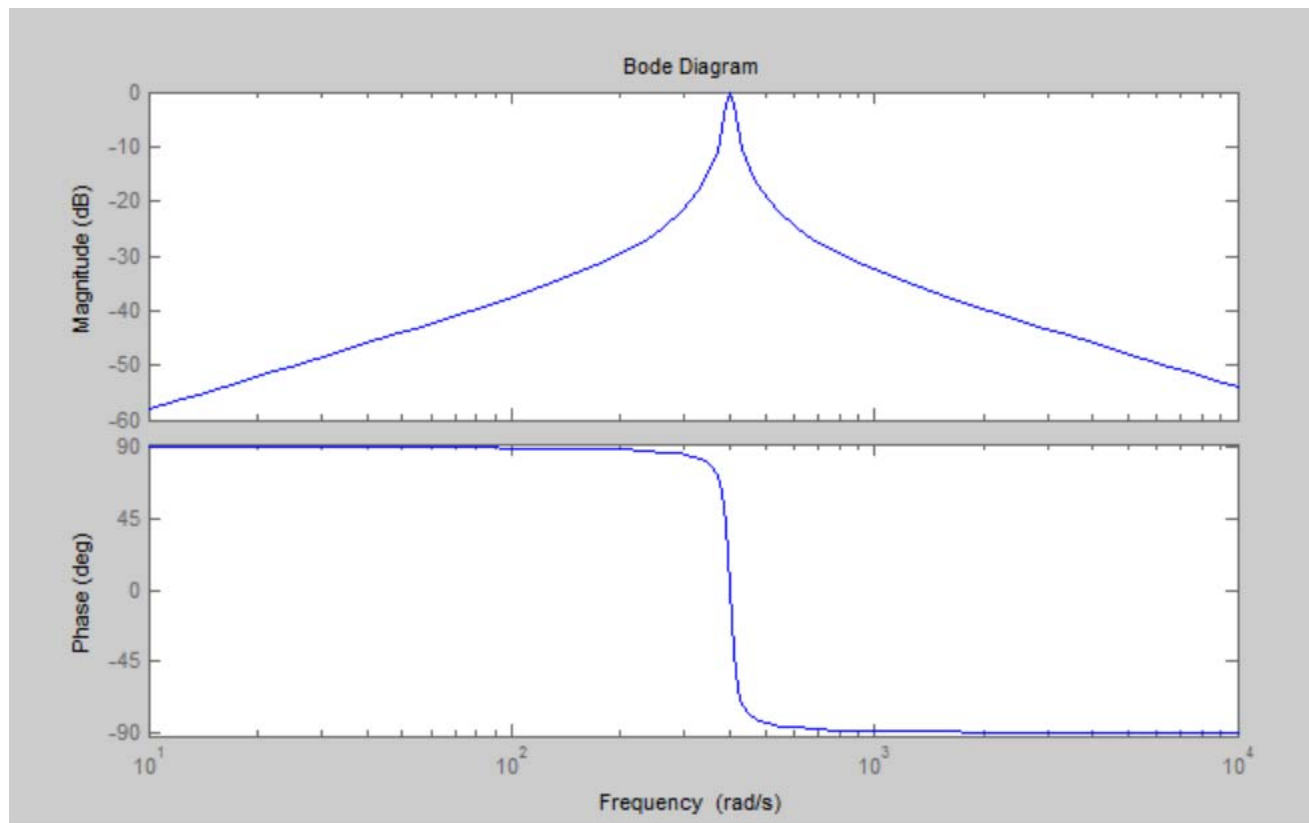

```
>> w0=400;
>> alpha=800;
>> num = [0, 2*alpha, 0];
>> den = [1, 2*alpha, w0*w0];
>> H = tf(num, den)
```

H =

$$\frac{1600 s}{s^2 + 1600 s + 160000}$$

MATLAB example

$$Q = 0.25$$

$$\frac{\omega_0}{2\alpha} = 0.25$$

$$\alpha = \frac{\omega_0}{2 \times 0.25} = 2\omega_0$$

choose

$$\omega_0 = 400$$

$$\alpha = 800$$

Continuous-time transfer function.

```
>> bode(H)
```

```
>>
```

